
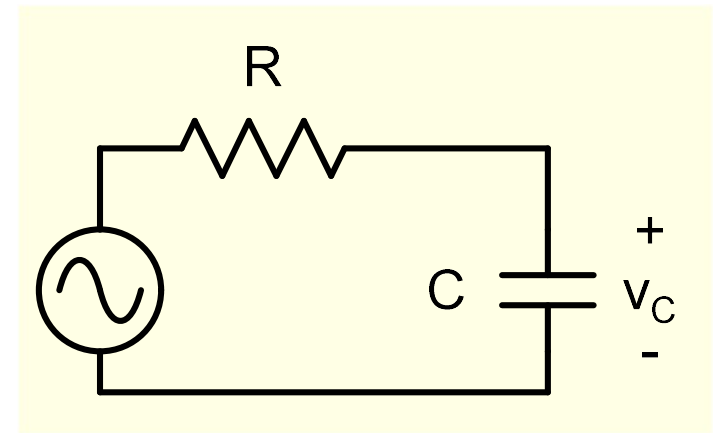


ESC201T : Introduction to Electronics

Lecture 14: Sinusoidal **Steady State** Analysis using Phasors




B. Mazhari
Dept. of EE, IIT Kanpur



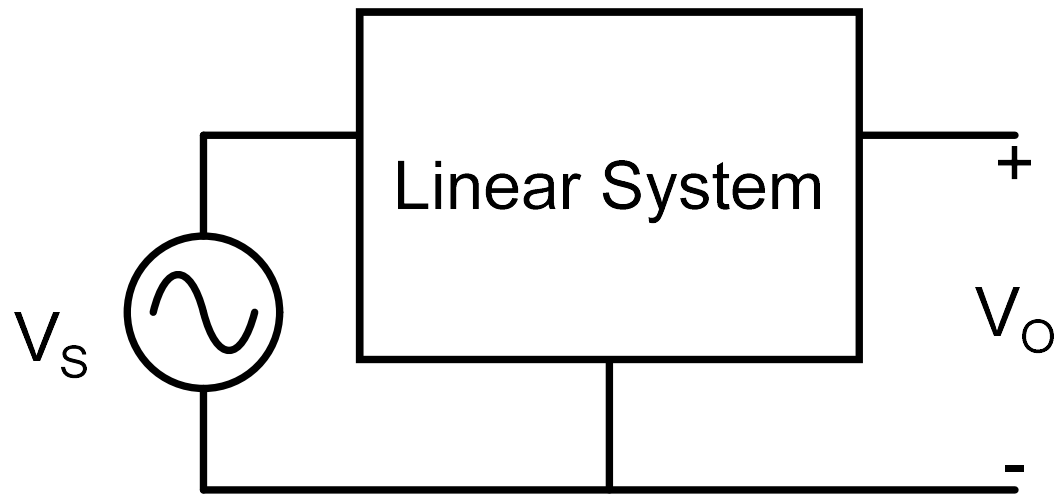


$$V_S = 1 \times \cos(\omega t)$$

$$V_O = A_O(\omega) \times \cos(\omega t + \theta(\omega))$$

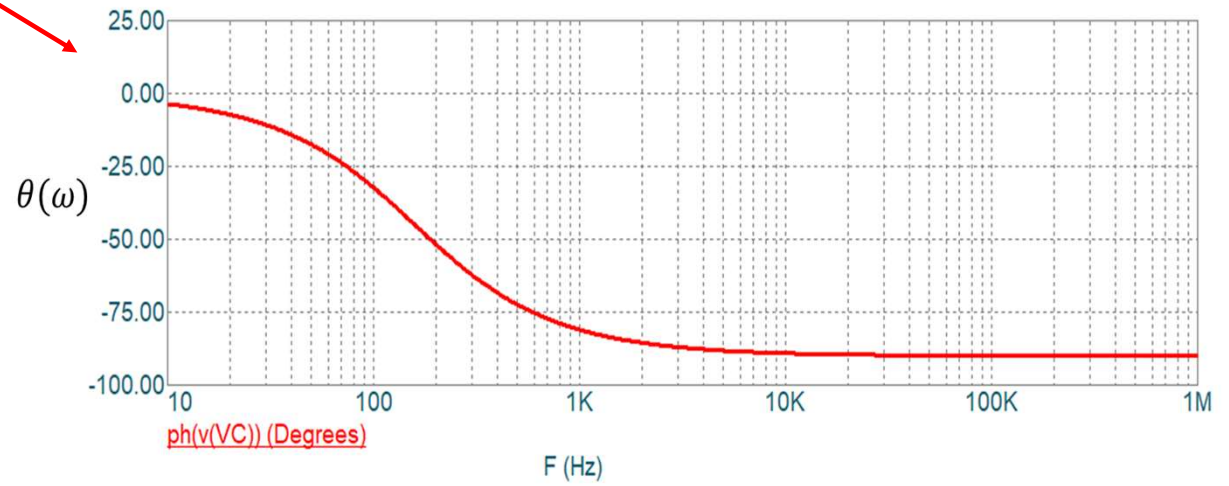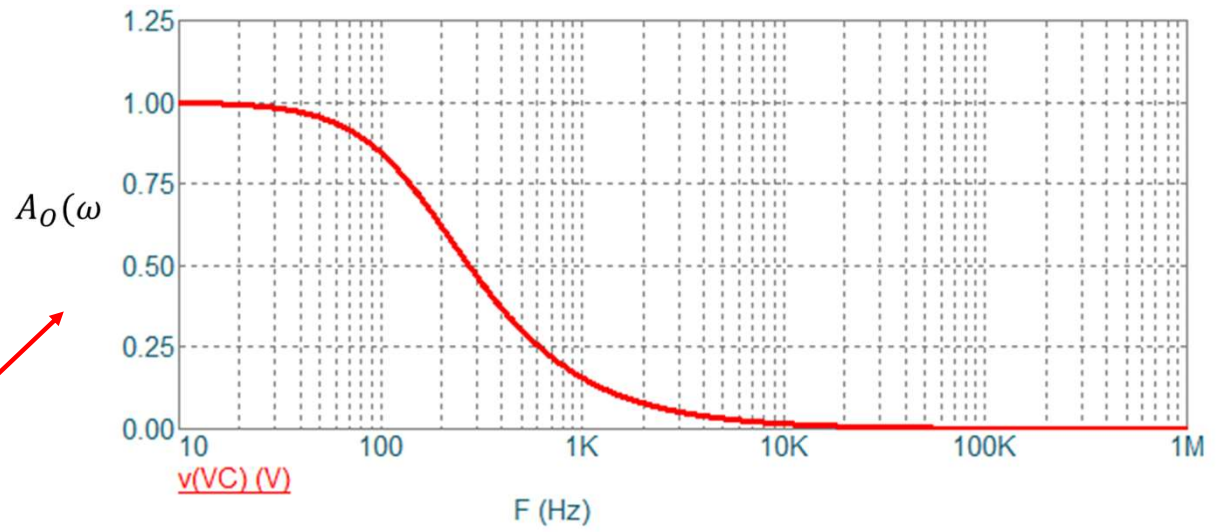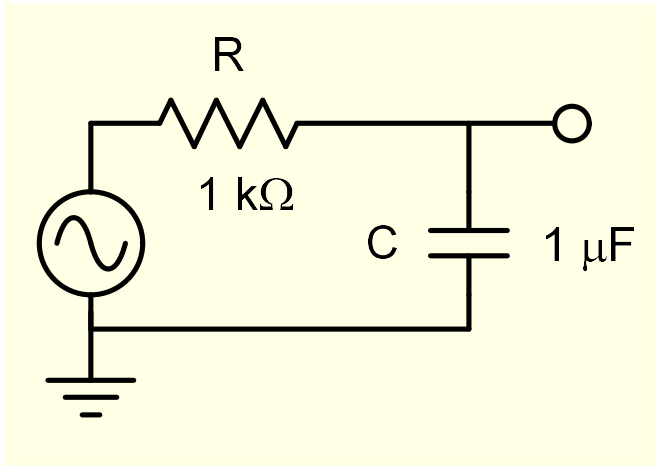$A_O(\omega)$ and $\theta(\omega)$ determine the complete characteristics of the system




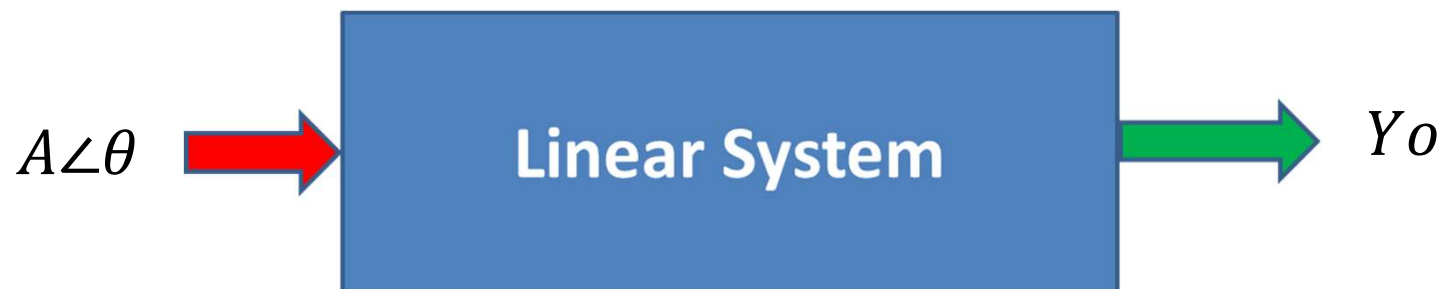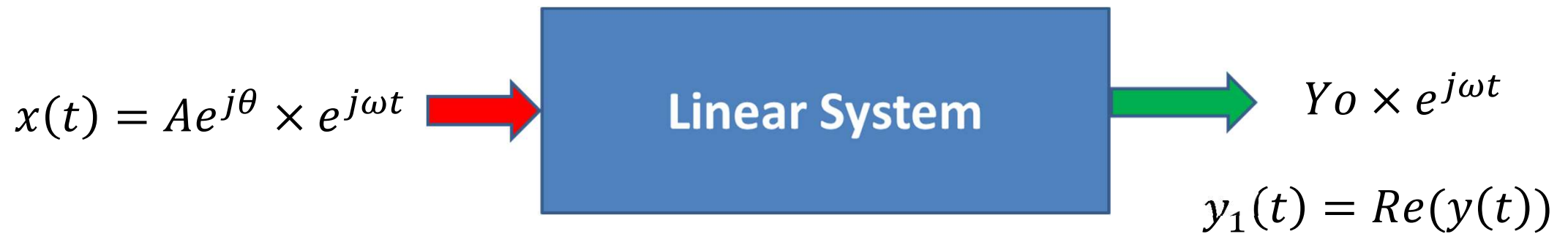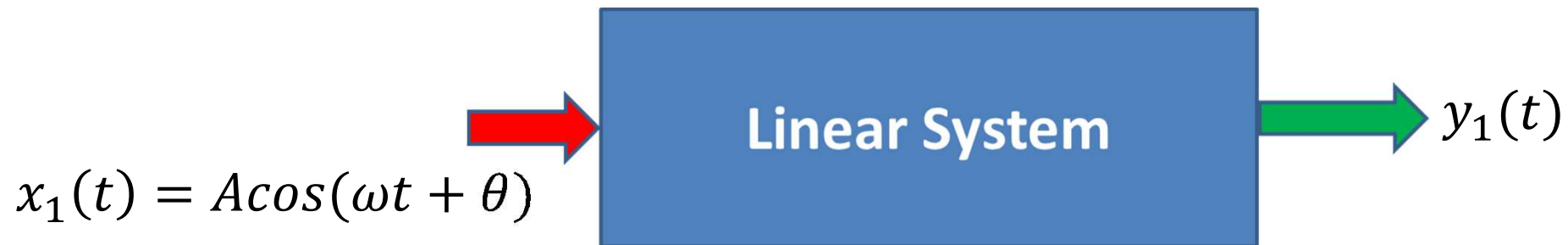

Complex Impedances



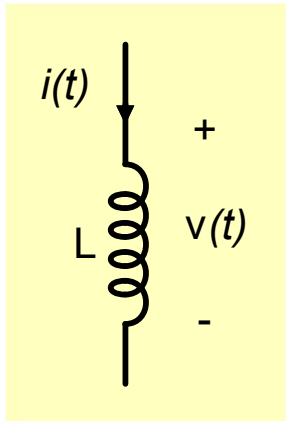For the purpose of sinusoidal steady state analysis, circuit elements such as inductors and capacitors can be represented as **Complex Impedances**



$$I_L = I_m \times e^{j(\omega t + \theta)} \rightarrow I_m \angle \theta$$

$$v_L = L \times \frac{dI_L}{dt} = j\omega L \times I_m \times e^{j(\omega t + \theta)} \quad \rightarrow V_L = j\omega L \times I_m \angle \theta$$
$$V_L = \omega L \angle 90^\circ \times I_m \angle \theta$$


Current through the inductor lags the voltage by 90°

$$V_L = j\omega L \times I_L$$

$$V_L = Z_L \times I_L \quad Z_L = j\omega L$$

This is like ohms law relationship between phasor voltage and current

Capacitor

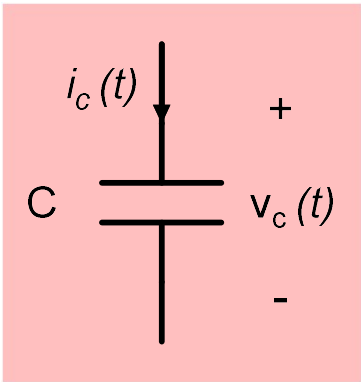

$$i_c = C \frac{dv_c}{dt}$$

$$v_c(t) = V_M \times e^{j(\omega t + \theta)}$$

$$V_C = V_M \angle \theta$$

$$i_c(t) = j\omega C V_M \times e^{j(\omega t + \theta)}$$

$$I_C = j\omega C V_M \angle \theta$$

$$I_C = j\omega C V_M \angle \theta + 90^\circ$$

In a capacitor, current leads voltage by 90°

$$I_C = j\omega C \times V_M \angle \theta$$

$$V_C = I_C \times Z_C$$

$$Z_C = \frac{1}{j\omega C} = -j \frac{1}{\omega C}$$

Resistor

$$v_R(t) = V_M \cos(\omega t + \theta)$$


$$i_R(t) = \frac{V_M}{R} \cos(\omega t + \theta)$$

$$V_R = V_M \angle \theta$$

$$I_R = \frac{V_M}{R} \angle \theta$$

$$I_R = \frac{V_R}{R}$$

Example-1

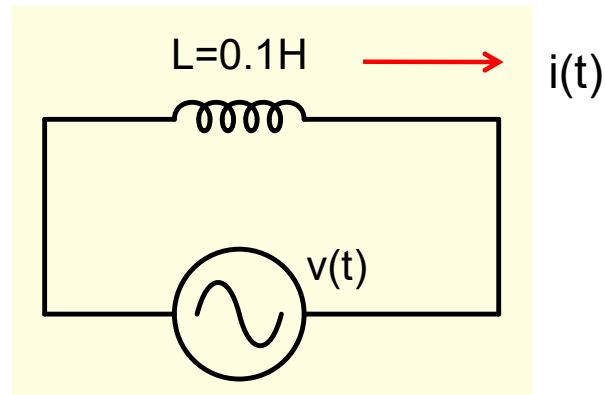

$$v(t) = 2 \cos(200t + 45)$$


$$\omega = 200$$

$$V_L = 2 \angle 45$$



$$V_L = I_L \times j\omega L \Rightarrow I_L = \frac{V_L}{j\omega L}$$

$$I_L = \frac{2 \angle 45}{j20} = \frac{2 \angle 45}{20 \angle 90} = 0.1 \angle -45$$

$$i(t) = 0.1 \cos(200t - 45)$$

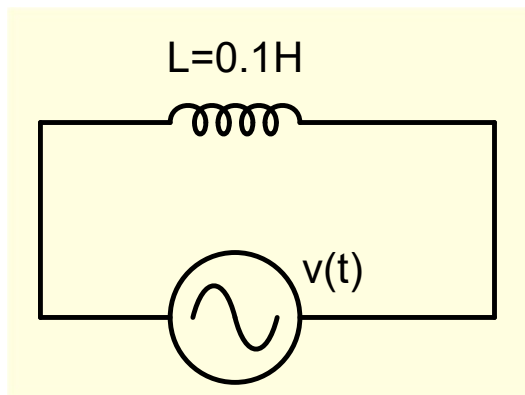


$$Z_L = j\omega L$$

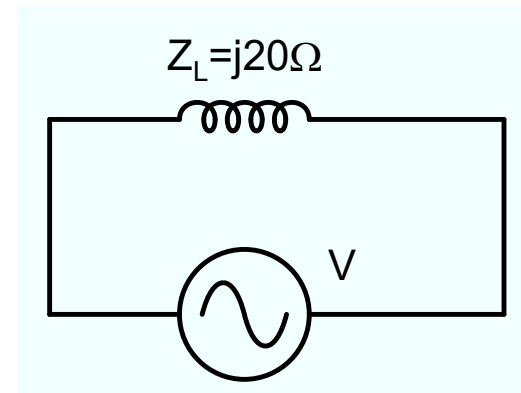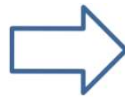

$$I_L = \frac{V_L}{j20}$$

Carry out analysis with phasors keeping in mind that we can always transform phasor to the sinusoidal voltage or current as the case maybe.



Example-2

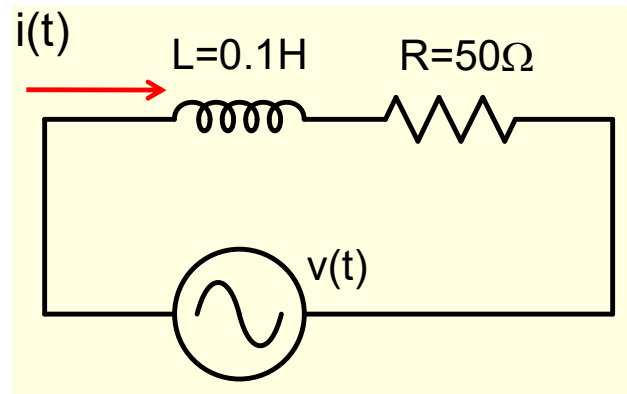

$$v(t) = 2 \cos(200t + 45)$$


$$\omega = 200$$

$$Z_L = j\omega L$$

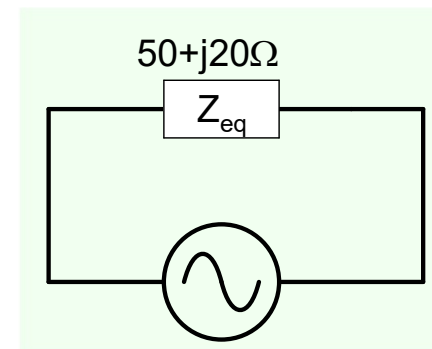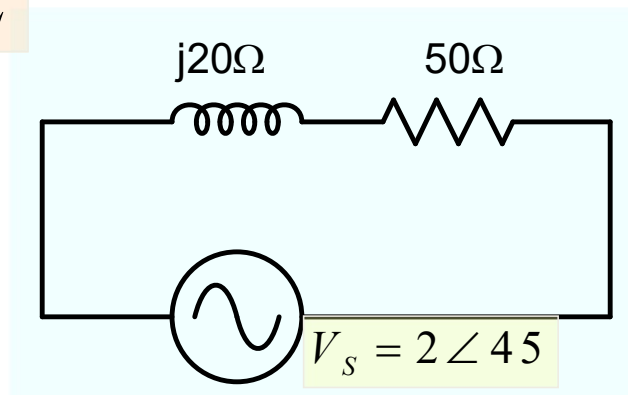

$$I = \frac{2 \angle 45}{50 + j20} = \frac{2 \angle 45}{53.85 \angle 21.8} = 0.037 \angle 23.2$$


$$i(t) = 0.037 \cos(200t + 23.2)$$

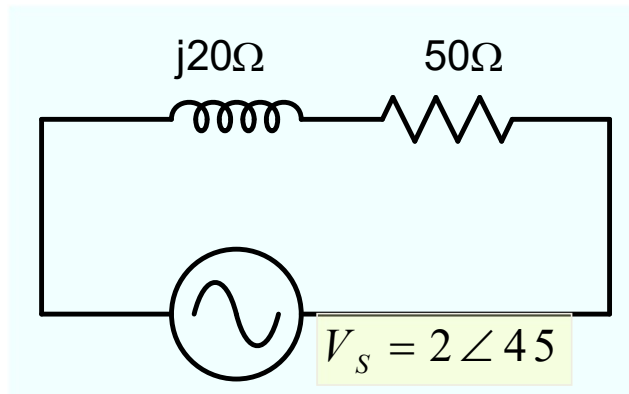


$$V_R = 2 \angle 45 \times \frac{50}{50 + j20}$$

Concept of voltage or current division can be used as before

Thevenin and Norton equivalent circuit

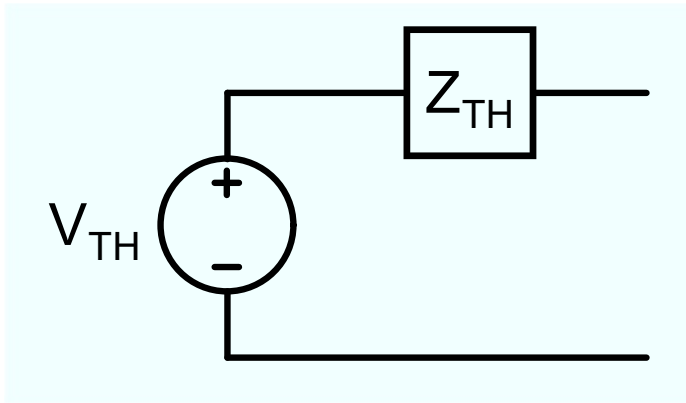


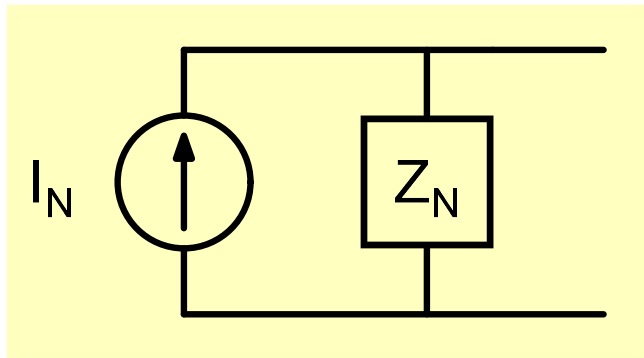Thevenin voltage is a phasor and Thevenin impedance is in general a complex impedance



Similarly Norton current is a phasor and impedances are complex numbers.

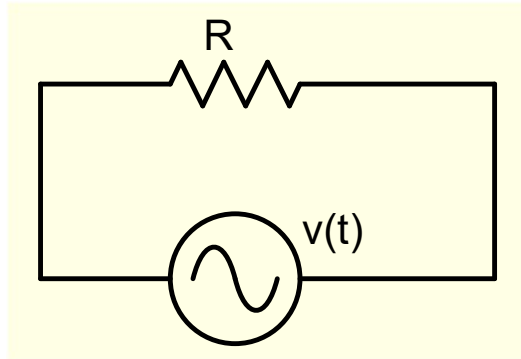Power dissipation with sinusoidal Voltage



$$p = \frac{v(t)^2}{R}$$

$$p_{avg} = \frac{1}{T} \int_0^T \frac{v(t)^2}{R} dt$$

Average


X: $x_1, x_2, x_3, \dots, x_N$

$$x_{avg} = \frac{1}{N} \sum x_i$$

If x is continuous, then its average over a time t_1

$$x_{avg} = \frac{1}{t_1} \int_0^{t_1} x(t) dt$$

For periodic signals

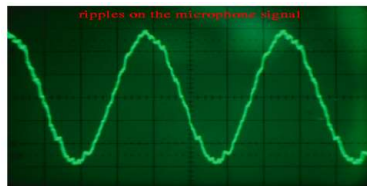

$$x_{avg} = \frac{1}{T} \int_0^T x(t) dt$$

Average Power

$$p_{avg} = \frac{1}{T} \int_0^T \frac{v(t)^2}{R} dt$$

We would like to express it like the dc power dissipated in a resistor

$$p = \frac{V^2}{R}$$

$$p_{avg} = \frac{\left[\sqrt{\frac{1}{T} \int_0^T v(t)^2 dt} \right]^2}{R}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$

$$p_{avg} = \frac{V_{rms}^2}{R}$$

This is true for any periodic waveform

RMS Value of a Sinusoid


$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$

$$v(t) = V_m \cos(\omega t + \theta)$$

$$\begin{aligned} \int_0^T \cos^2(\omega t + \theta) dt &= \int_0^T \frac{1 - \cos(2\omega t + 2\theta)}{2} dt \\ &= 0.5T - \frac{1}{4\omega} \sin(2\omega t + 2\theta) \Big|_0^T = 0.5T \end{aligned}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

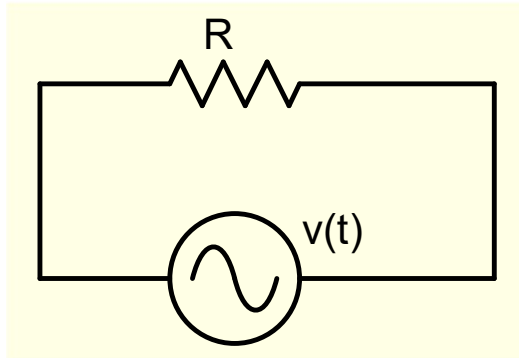Power dissipation with sinusoidal Voltage



$$v(t) = V_m \cos(\omega t + \theta)$$

$$p_{avg} = \frac{V_{rms}^2}{R}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$


$$p_{avg} = \frac{V_m^2}{2R}$$

$$i(t) = I_m \cos(\omega t + \theta)$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt}$$


$$p_{avg} = 0.5 I_m^2 R$$

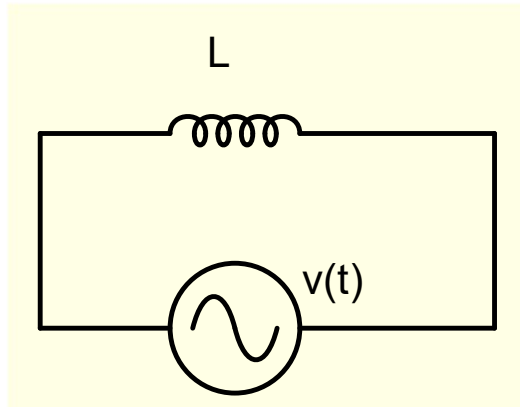

$$v(t) = V_m \cos(\omega t) \quad i(t) = I_m \cos(\omega t - 90^\circ) = I_m \sin(\omega t)$$


$$p(t) = v(t)i(t) = V_m I_m \cos(\omega t) \sin(\omega t)$$
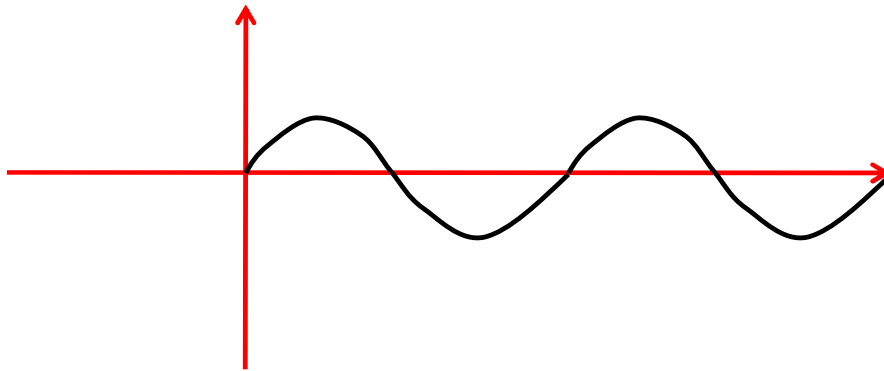
$$= \frac{V_m I_m}{2} \sin(2\omega t) + \frac{V_m I_m}{2} \sin(0)$$
$$= \frac{V_m I_m}{2} \sin(2\omega t)$$



$$p_{avg} = 0$$

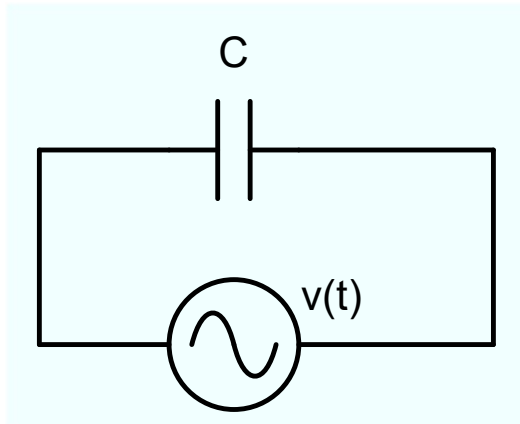- Average power absorbed by
an inductor is zero



$$v(t) = V_m \cos(\omega t) \quad i(t) = I_m \cos(\omega t + 90^\circ) = -I_m \sin(\omega t)$$

$$p(t) = v(t)i(t) = -V_m I_m \cos(\omega t) \sin(\omega t)$$


$$= -\frac{V_m I_m}{2} \sin(2\omega t) - \frac{V_m I_m}{2} \sin(0)$$

$$= -\frac{V_m I_m}{2} \sin(2\omega t)$$

$$p_{avg} = 0$$

- Average power absorbed by
a capacitor is zero

General Rule

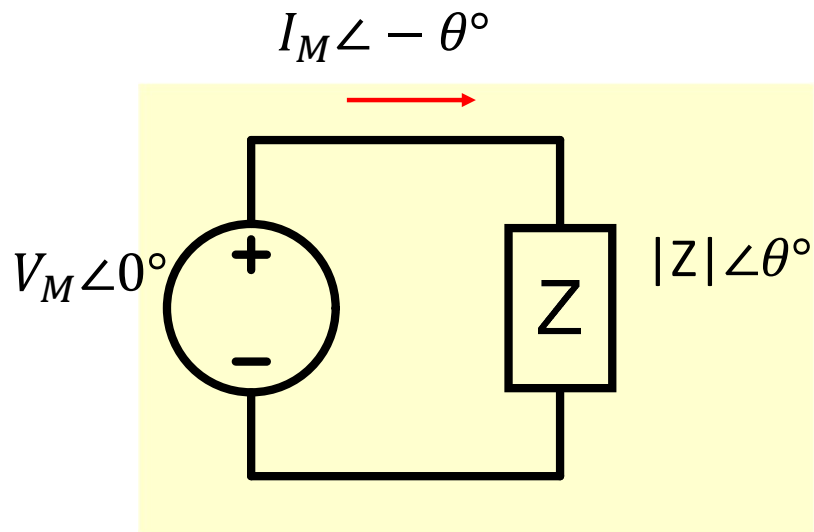

$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t - \theta)$$

Average Power :

$$p = \frac{1}{T} \int_0^T v(t) \times i(t) dt$$

$$P = V_{\text{rms}} I_{\text{rms}} \cos \theta$$


$$\text{Power Factor } PF = \cos \theta$$

For a resistor $PF = 1$, while for inductor and capacitor it is 0

$$j\omega L = \omega L \angle 90^\circ ; -j \frac{1}{\omega C} = \frac{1}{\omega C} \angle -90^\circ$$

Current in phase with voltage gives rise to power dissipation

Maximum Power Transfer for dc circuits

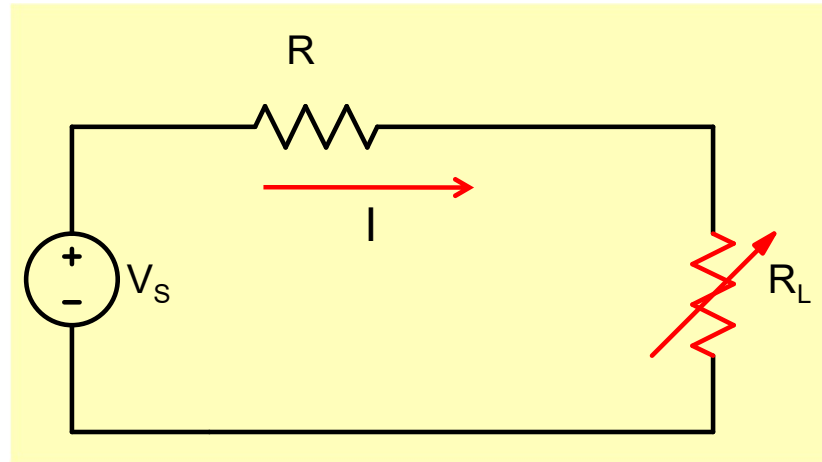

What value of R_L will give rise to maximum load power ?

$$I = \frac{V_s}{R + R_L}$$


$$P_L = I^2 R_L = V_s^2 \times \frac{R_L}{(R + R_L)^2}$$

$$\frac{\partial P_L}{\partial R_L} = 0$$

$$R_L = R$$

$$P_{L_{\max}} = \frac{V_s^2}{4R_L}$$

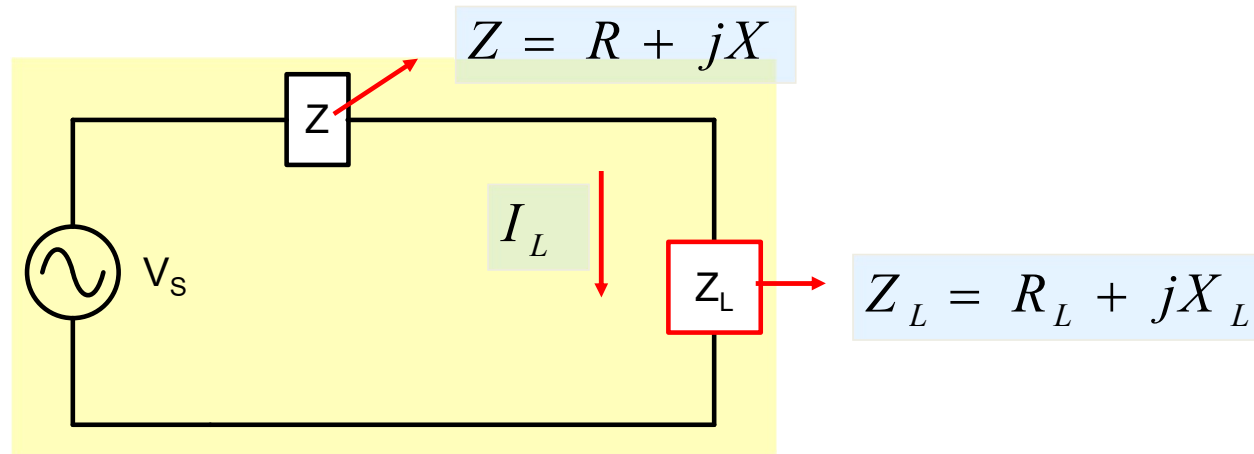Maximum Power Transfer for sinusoidal input



$$I_L = \frac{V_s}{R + R_L + j(X + X_L)}$$

$$P_L = \frac{\frac{V_s^2}{2}}{(R + R_L)^2 + (X + X_L)^2} R_L$$

For maximum load power : $X_L = -X$

$$P_L = 0.5 \times \frac{V_s^2}{(R + R_L)^2} R_L$$



Choose $R_L = R$ to maximize load power

$$Z_L = \bar{Z}$$

Maximum power is transferred to the load when load is complex conjugate of source impedance

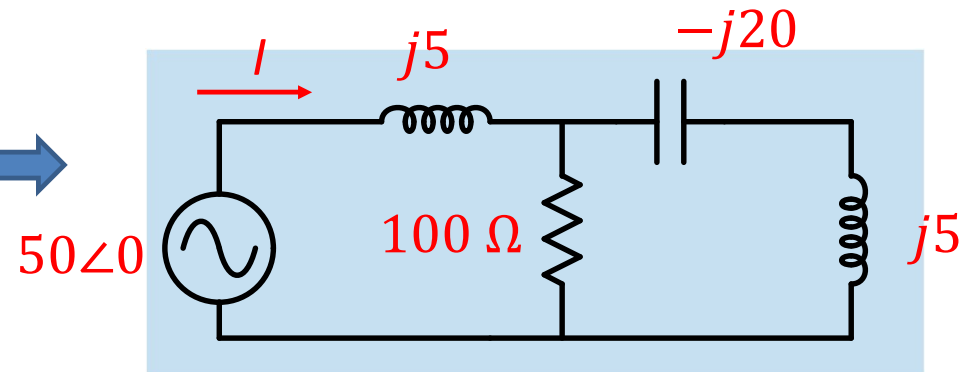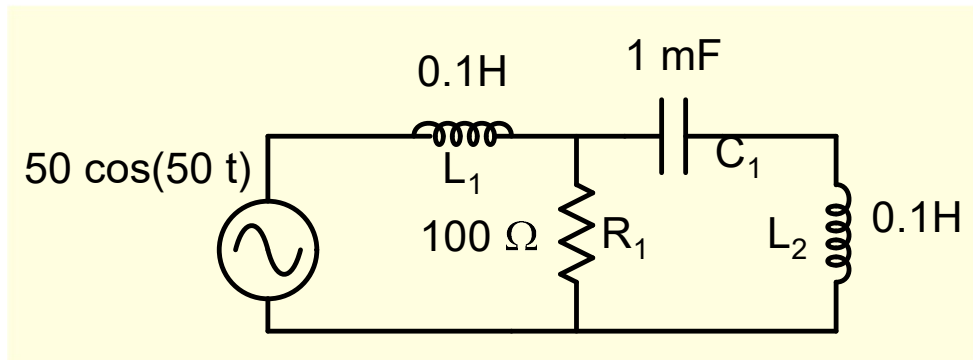Example-3

Determine all you can about the given circuit



$$\omega = 50$$

$$Z = j5 + 100 \parallel (-j15) = 2.2 - j9.67 \quad I = \frac{50}{Z} = 1.12 + j4.96 = 5 \angle 77.2$$

$$P_S = \frac{50}{\sqrt{2}} \times \frac{5}{\sqrt{2}} \times \cos(77.2) = 27.97W$$

Voltage across R_1 ?

$$V_{R1} = I \times (100 \parallel (-j15)) = 74.8 \angle -4.3$$

$$\frac{V_{R1}^2}{2R_1} = 27.97W$$