


ESC201T : Introduction to Electronics

Lecture 25: Amplifiers-1

B. Mazhari
Dept. of EE, IIT Kanpur

“Amplification is the heartbeat of Electronics”




Voltage Amplification

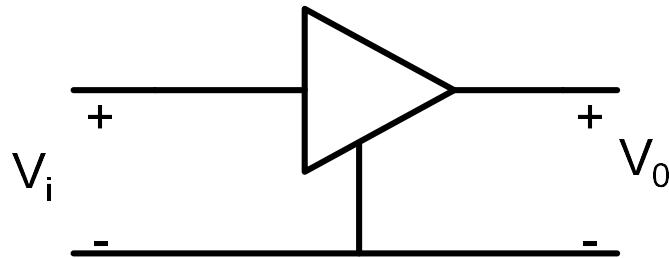

$$V_o = G \times V_i$$

$G > 1$ and constant

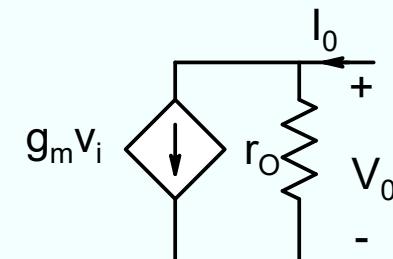
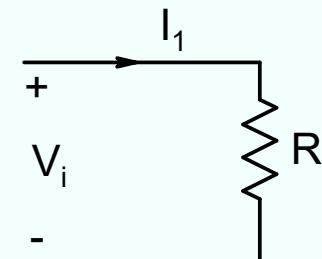
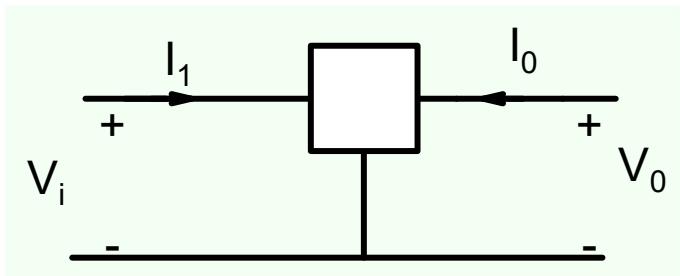
Consider a 3-terminal unilateral linear device




$$R_i = \text{input resistance} = V_i / I_i ; \text{ Transconductance: } g_m = \left. \frac{I_o}{V_i} \right|_{V_o=0}$$

$$\text{Output conductance: } g_o = 1/r_o = \left. \frac{I_o}{V_o} \right|_{V_i=0}$$

Voltage Amplifier

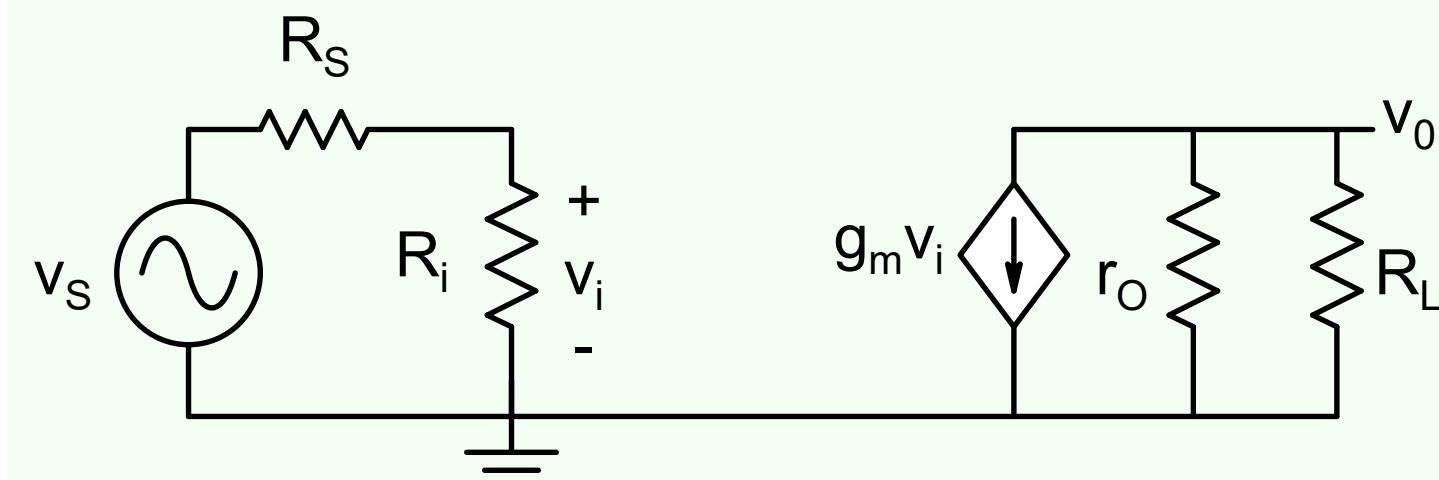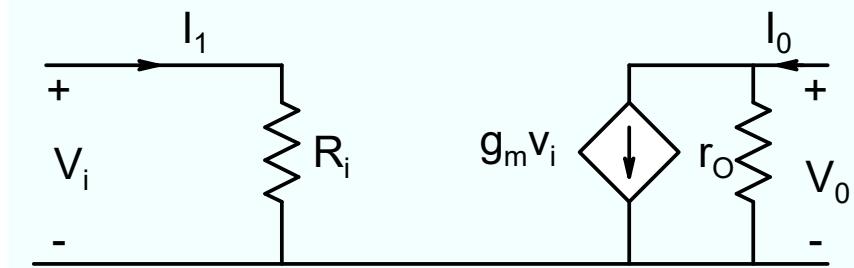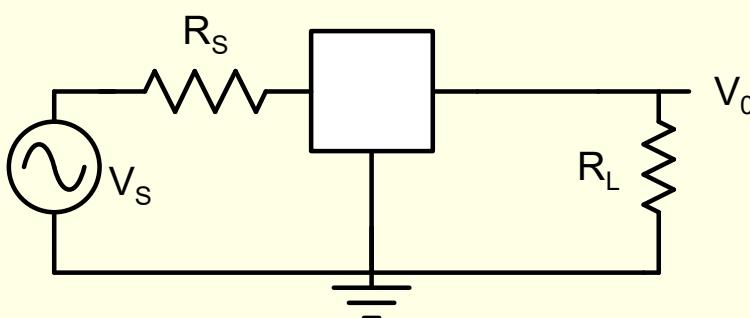

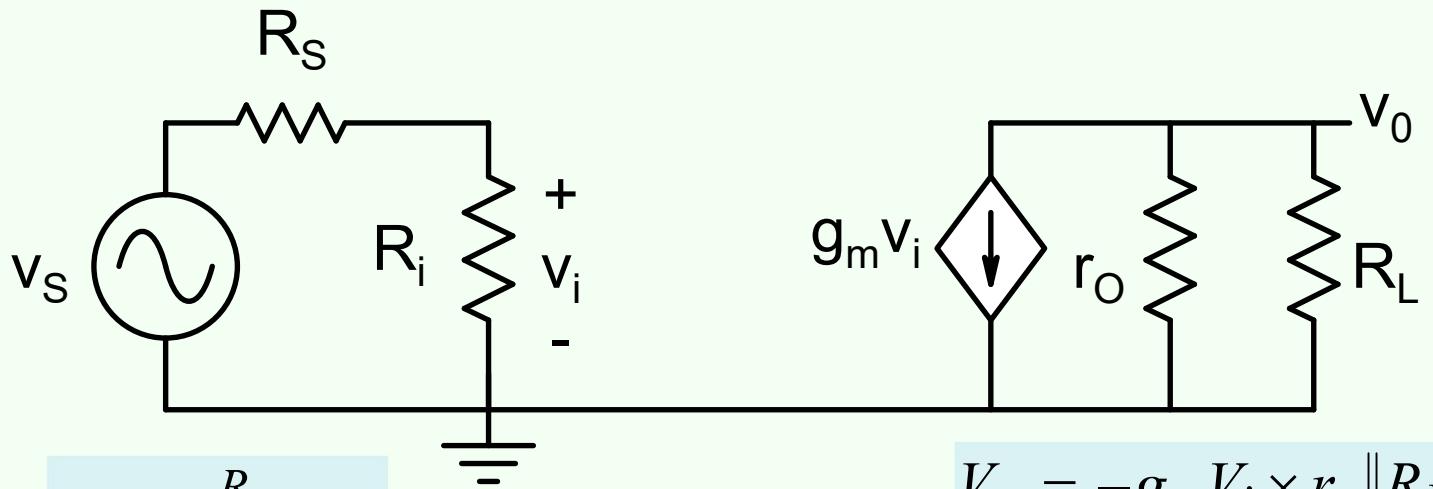

$$V_i = \frac{R_i}{R_i + R_S} V_S$$

$$V_o = -g_m V_i \times r_o \| R_L$$

$$A_V = \frac{V_o}{V_s} = -g_m r_o \times \frac{R_L}{r_o + R_L} \times \frac{R_i}{R_i + R_S}$$

$$|A_V| \leq g_m \times r_o$$



Necessary Condition for Voltage Amplification : $g_m \times r_o > 1$

Voltage Amplification

$$g_m r_o \gg 1$$

$$g_m \gg g_o$$

Transconductance >> Output Conductance

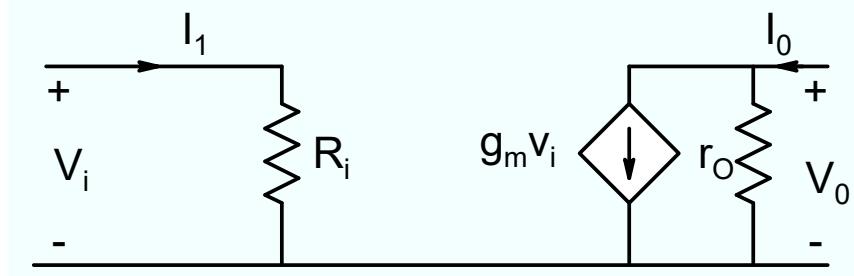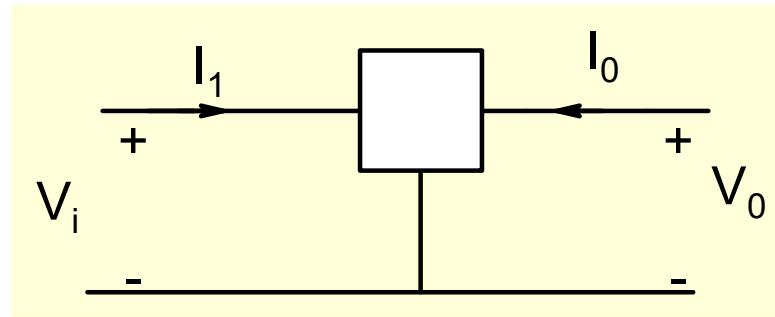



Transistor

Transistor

Trans-resistor




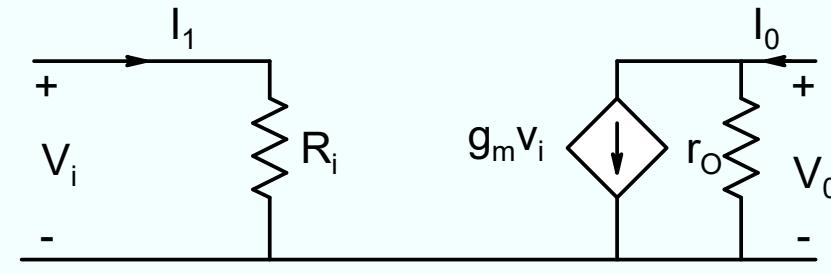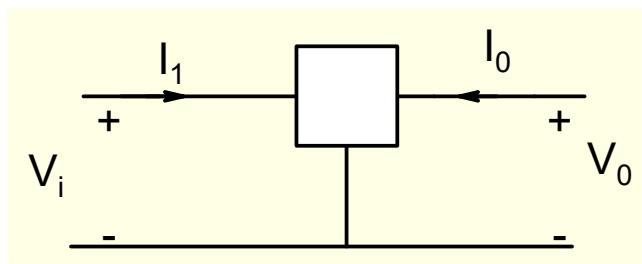Current I_o is much more sensitive to V_{IN} than V_o



$$g_m r_o \gg 1$$

In the ideal case r_o is infinite

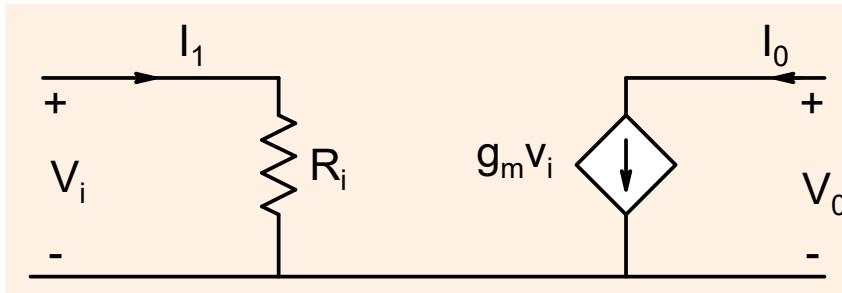





$$A_V = \frac{V_o}{V_s} = -g_m r_o \times \frac{R_L}{r_o + R_L} \times \frac{R_i}{R_i + R_S} = -g_m R_L \times \frac{R_i}{R_i + R_S}$$

We would ideally like input resistance R_i to be infinite as well !

$$A_V = -g_m R_L$$

Note that we have power gain as well which is essential for calling a device as an Amplifier

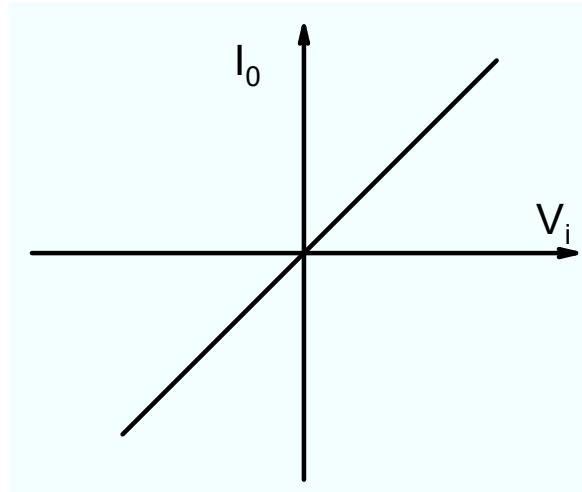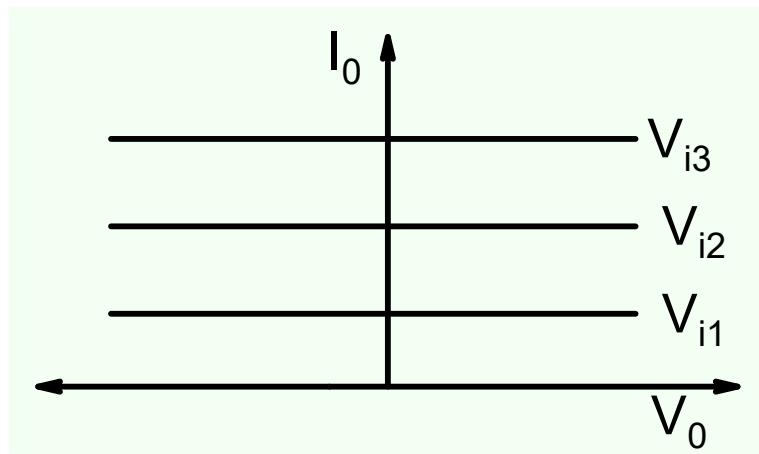
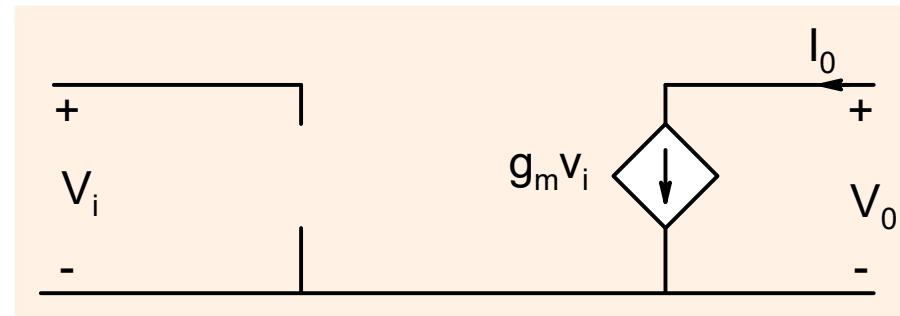
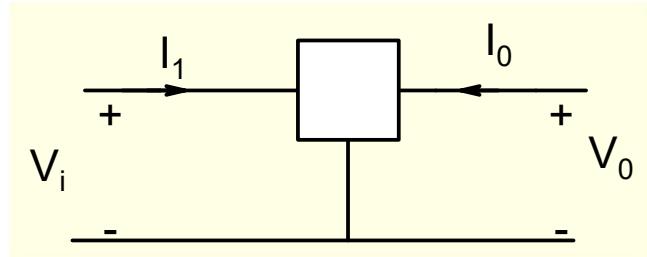
An ideal 3-terminal device for Voltage Amplification



Ideal Transistor Characteristics

Ideal Transistor (IT)

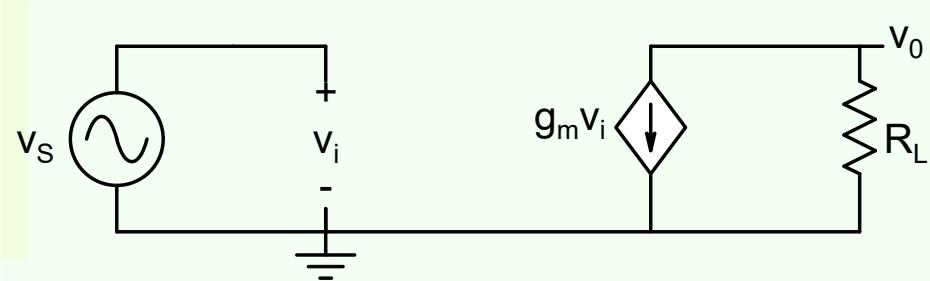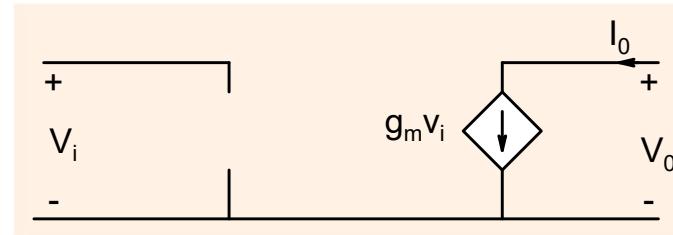
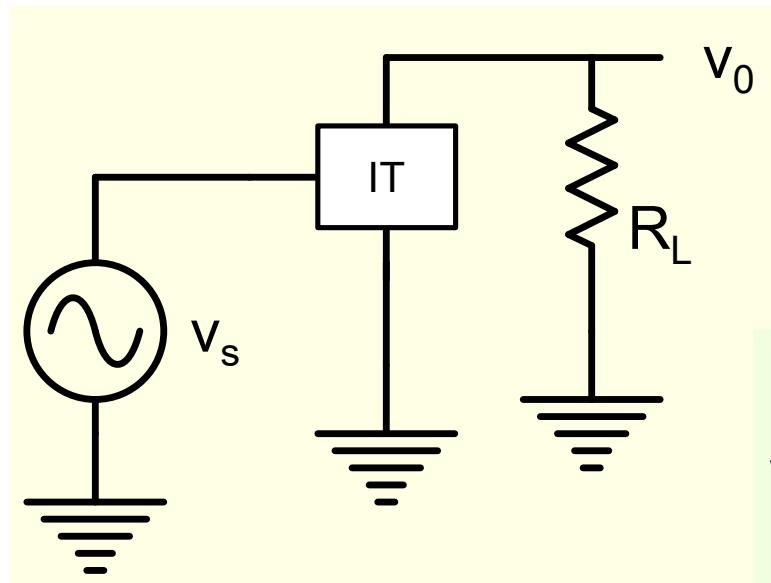
Making a voltage amplifier with an ideal transistor is straightforward





$$A_V = \frac{v_o}{v_s} = -g_m R_L$$

In practice there is no element which has the characteristics of ideal transistor !



Ideal transistor

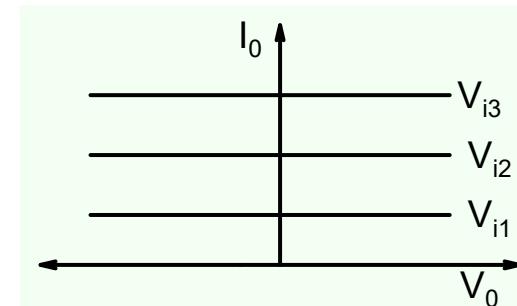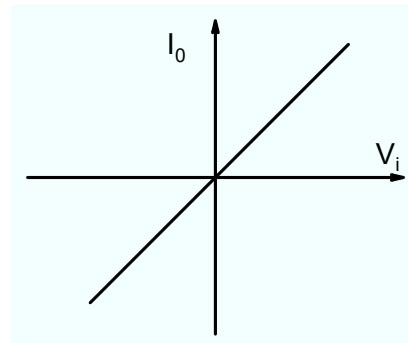

Device X

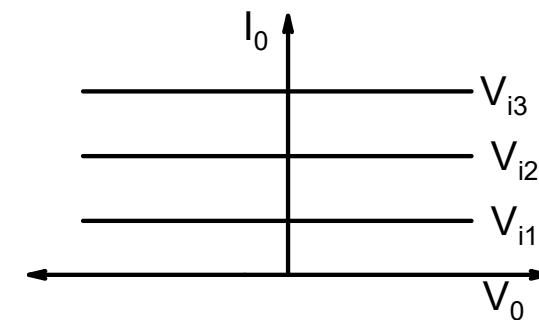
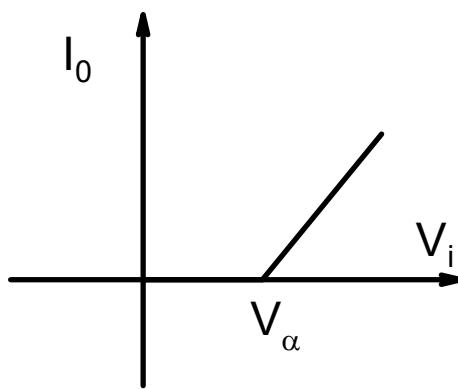


Device Y

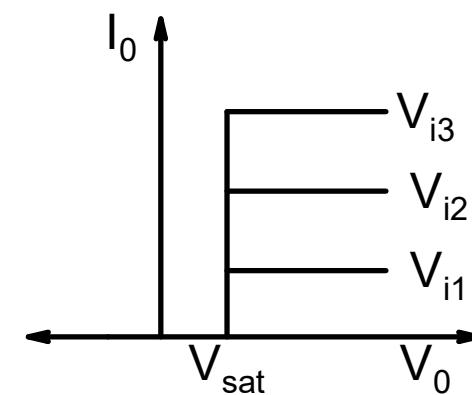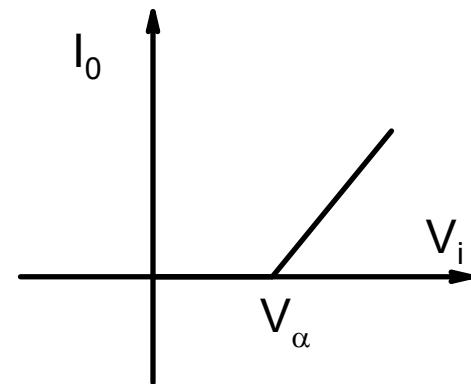


How do we use elements such as X, Y etc to make amplifiers?



Device X

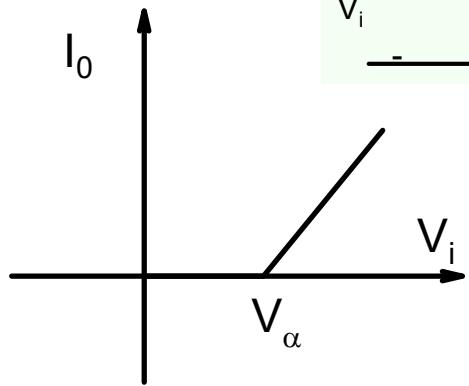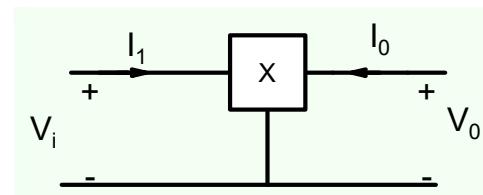



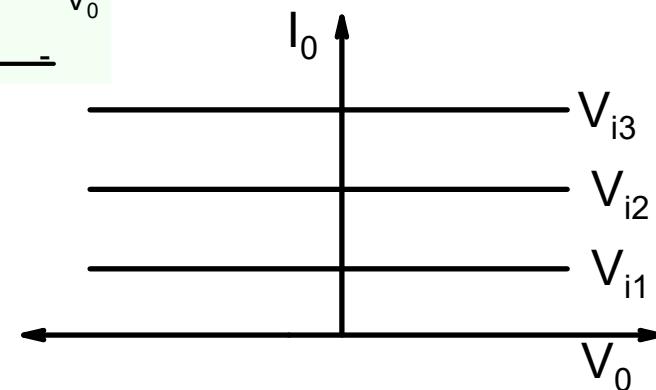
$$I_o = 0 \quad \text{for } V_i \leq V_\alpha$$
$$= g_m \times (V_i - V_\alpha) \quad \text{for } V_i > V_\alpha$$



Ideal Characteristics

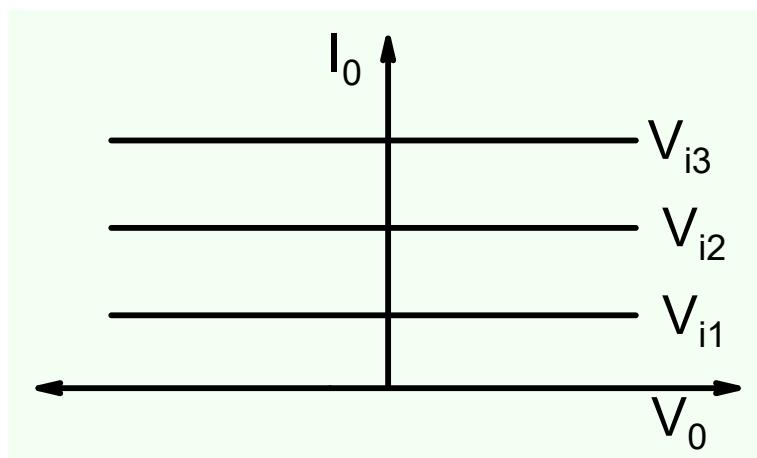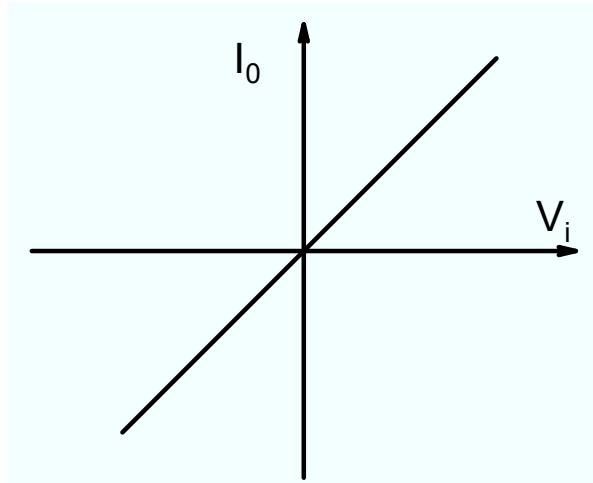

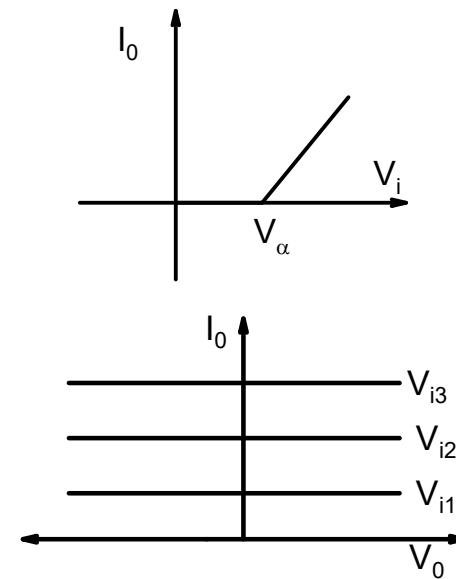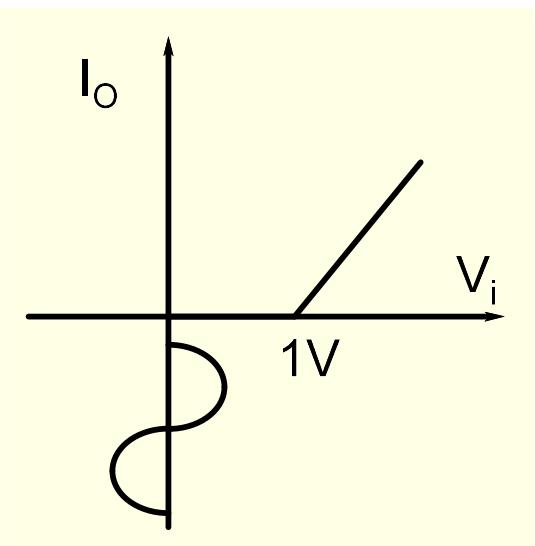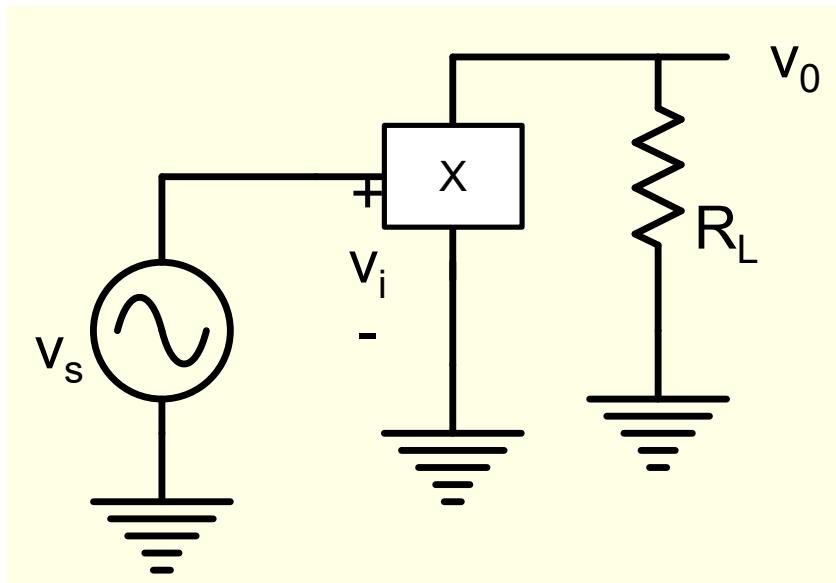How do we use device X to make an amplifier?







$$V_\alpha = 1V; g_m = 0.01\Omega^{-1}$$

$$R_L = 1K ; v_s = 0.5V \sin \omega t$$



$$I_O = 0 \Rightarrow V_O = 0$$

No Amplification

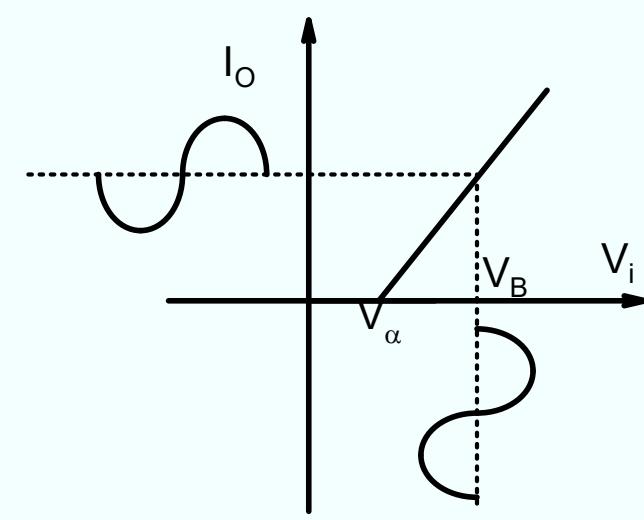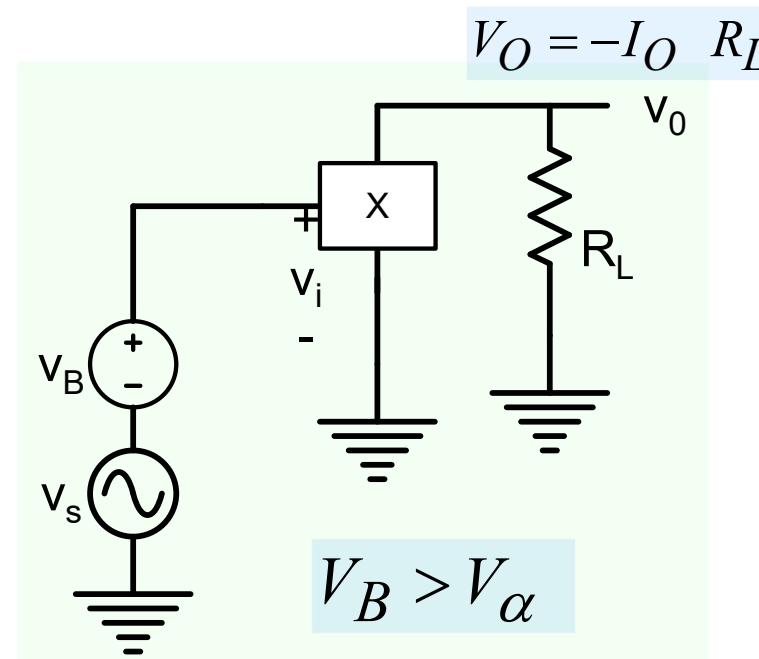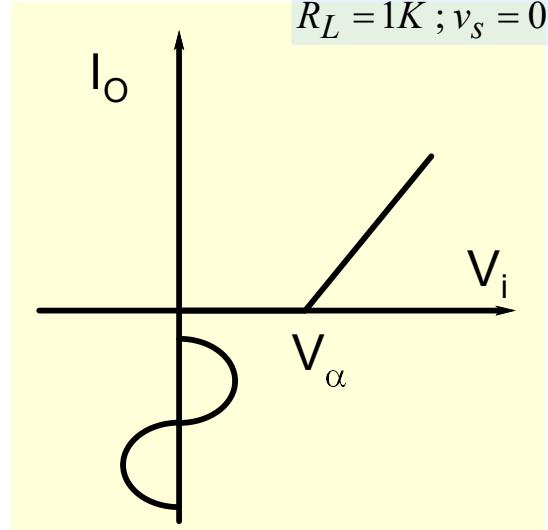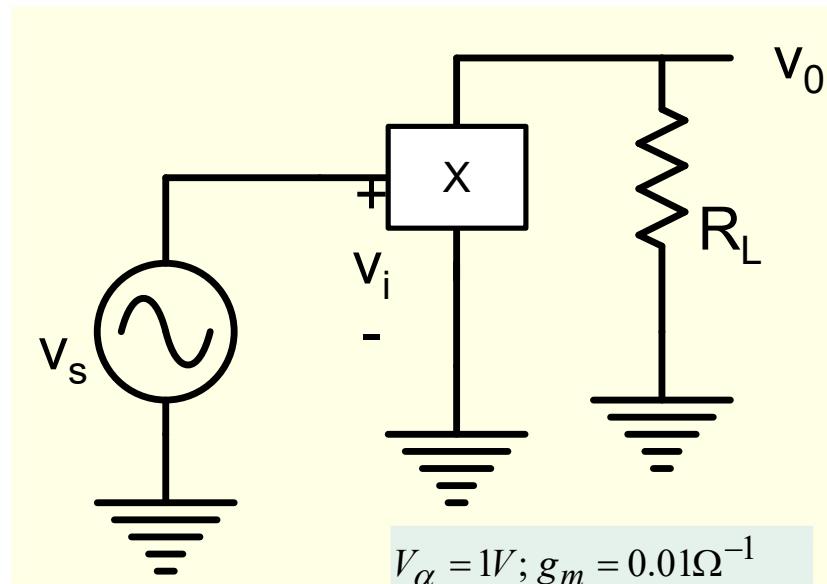
How do we use device X to make an Amplifier?



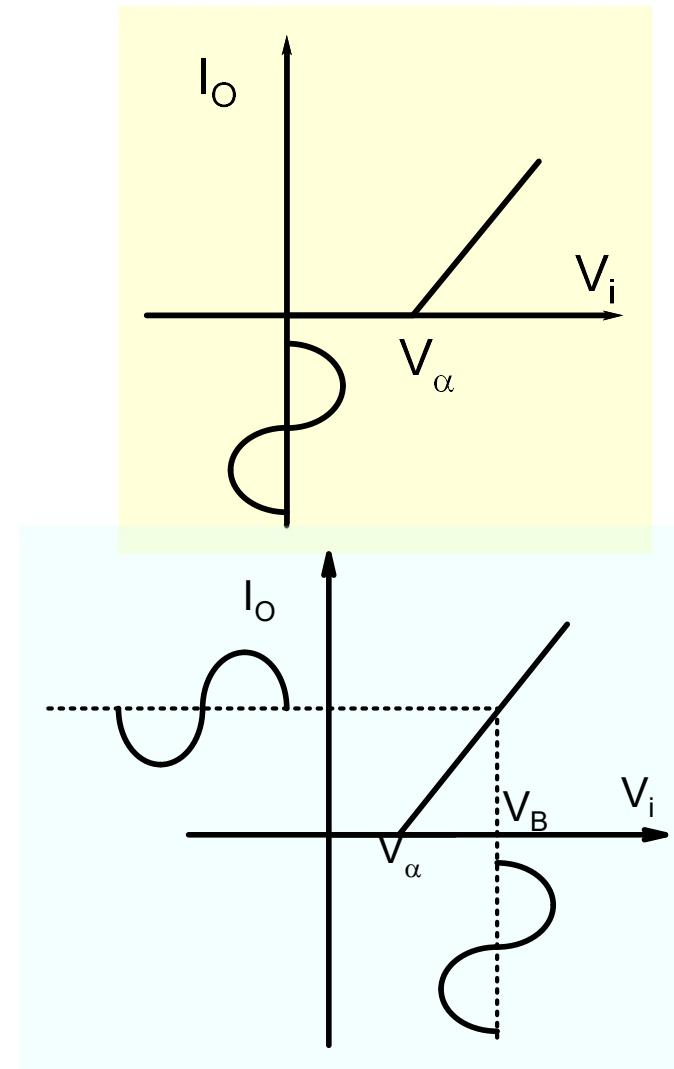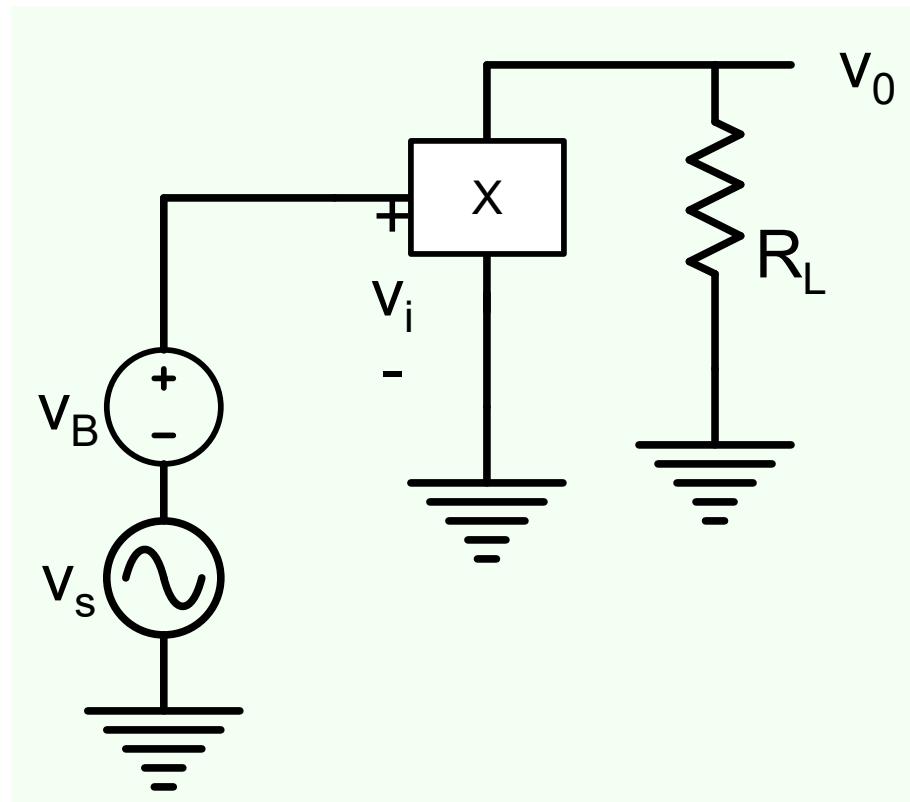
When only a part of device characteristics is suitable for amplification, then we need to push the device into that region by applying suitable bias voltages. This process is called **BIASING**






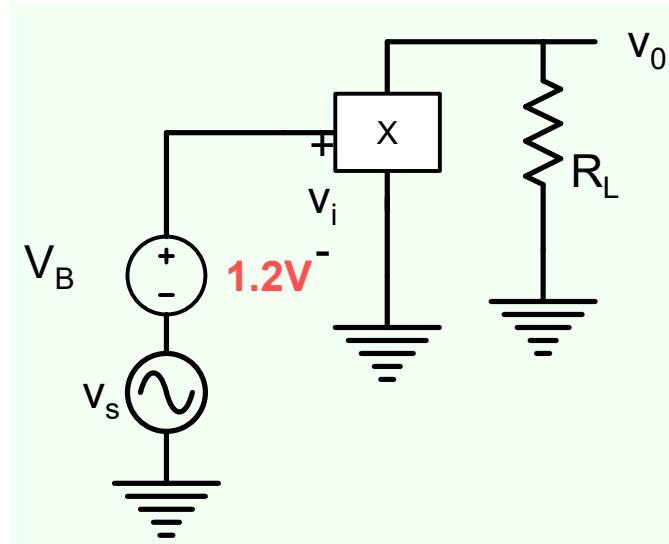
How should one choose the bias voltage V_B ?



$$v_s = 0.5V \sin \omega t$$


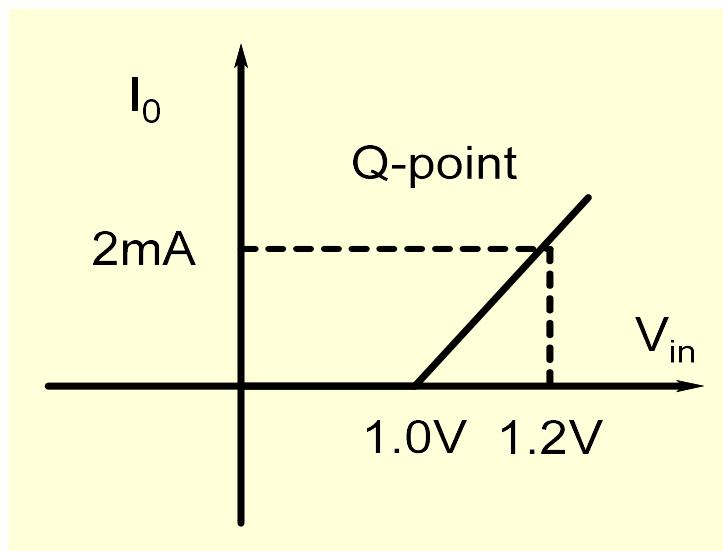


Quiescent point or Bias point

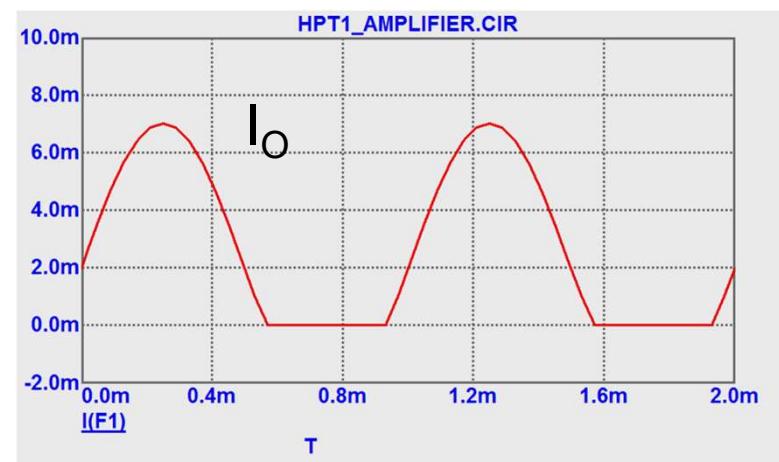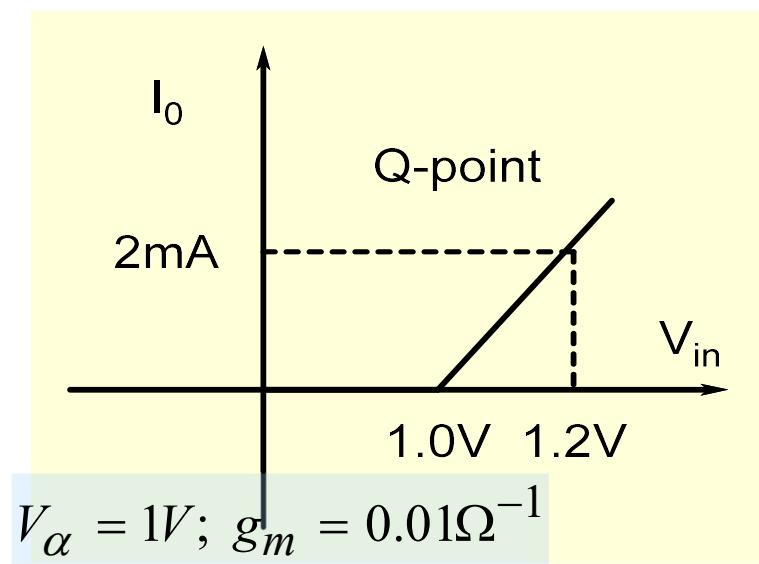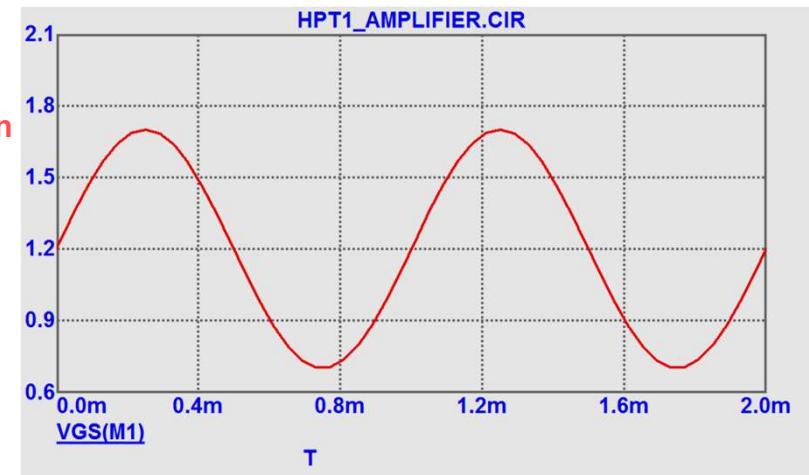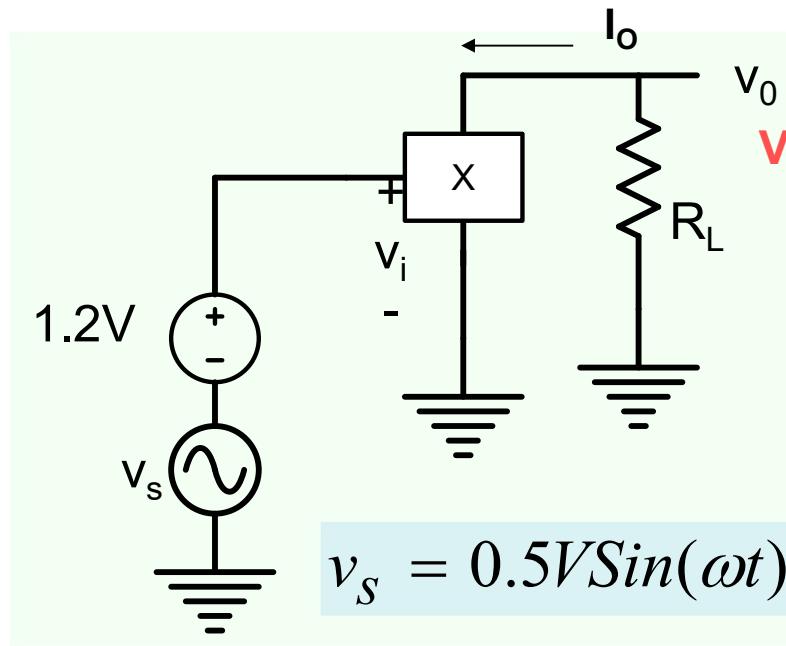


$$V_o = -I_o \cdot R_L$$

Output voltage is distorted !




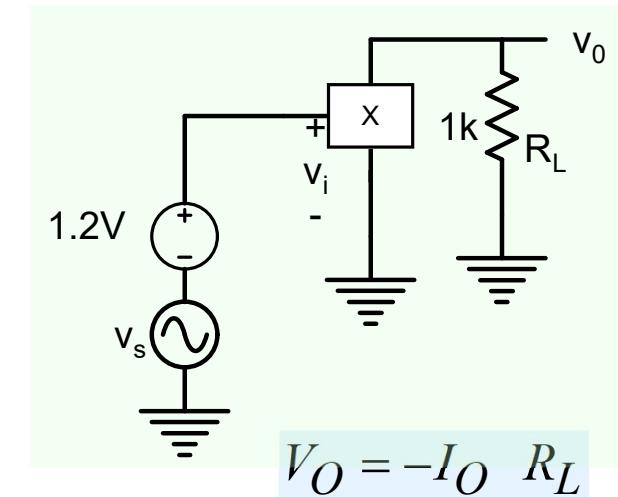
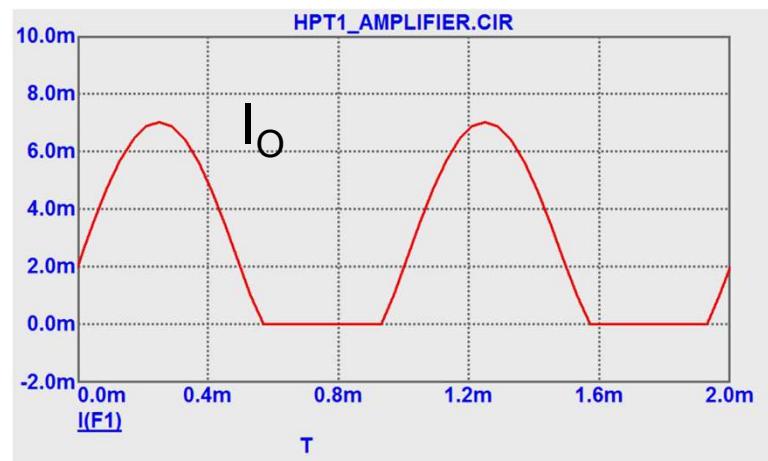


$$V_O = -I_O \cdot R_L$$





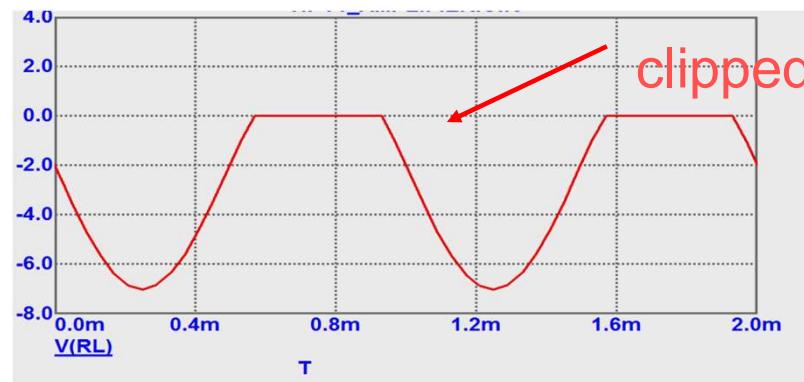


Need to choose a proper value of biasing Voltage





Unnecessary Power Dissipation

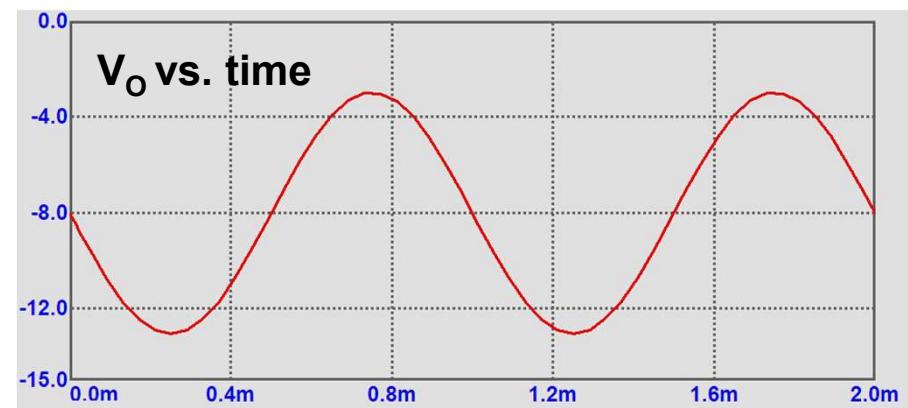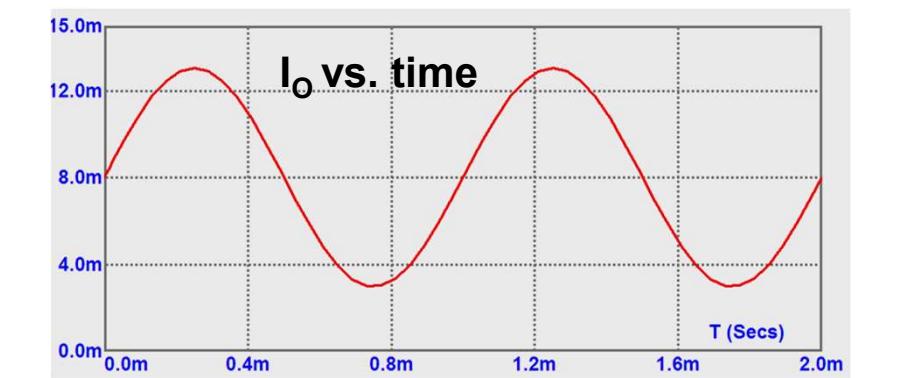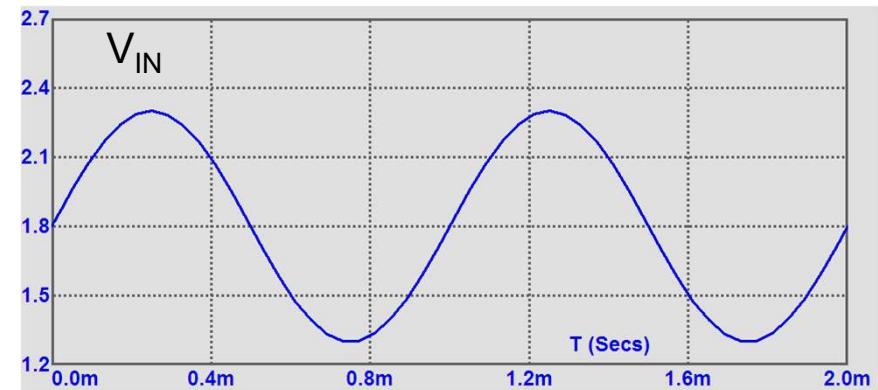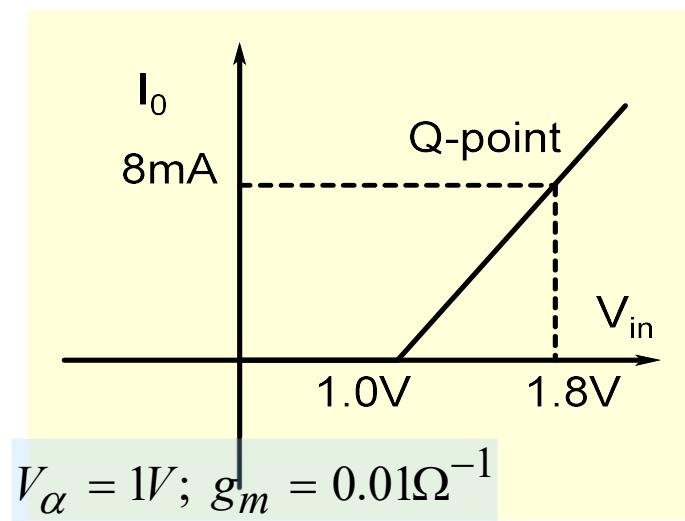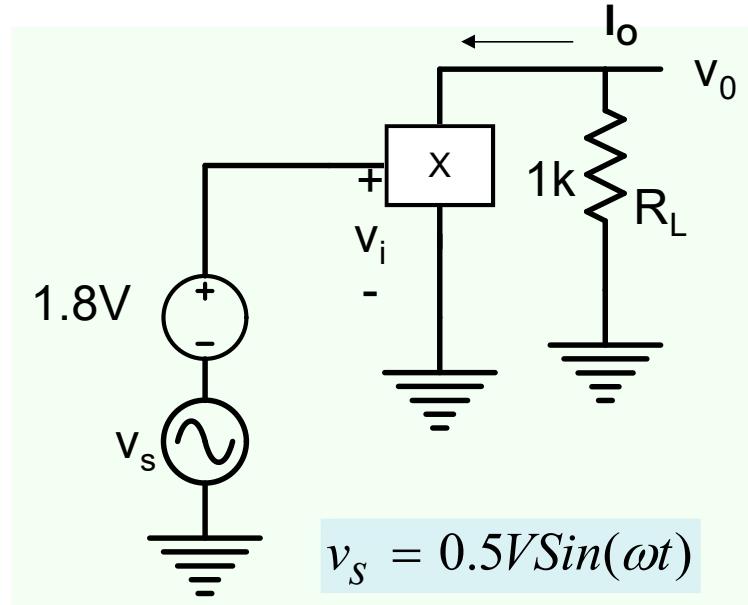



Optimum Biasing ?

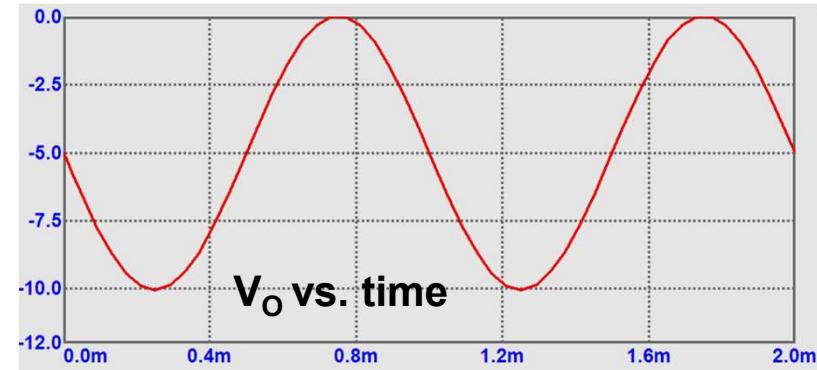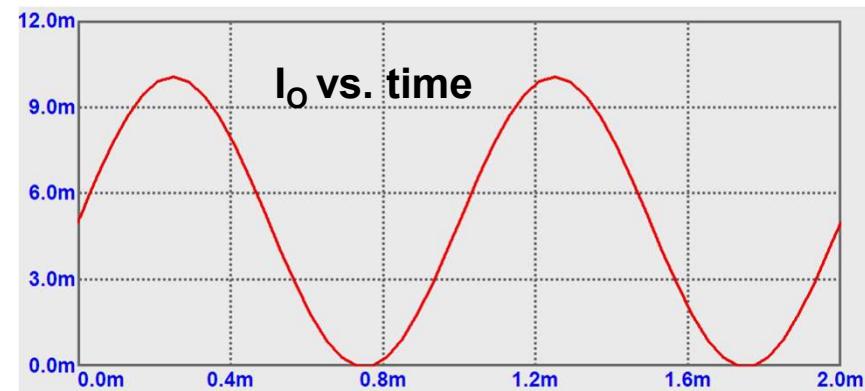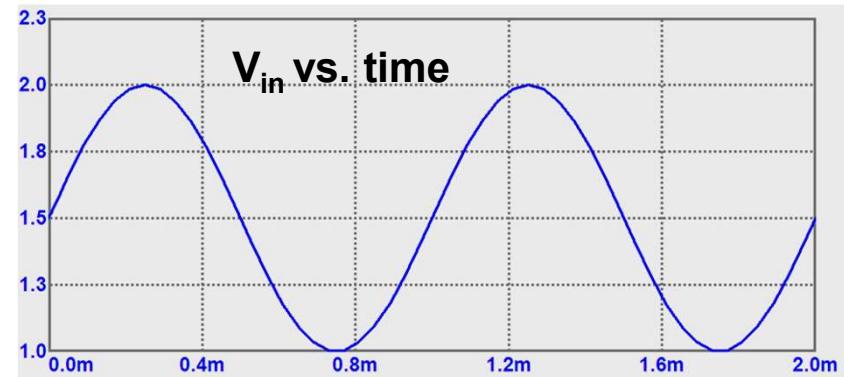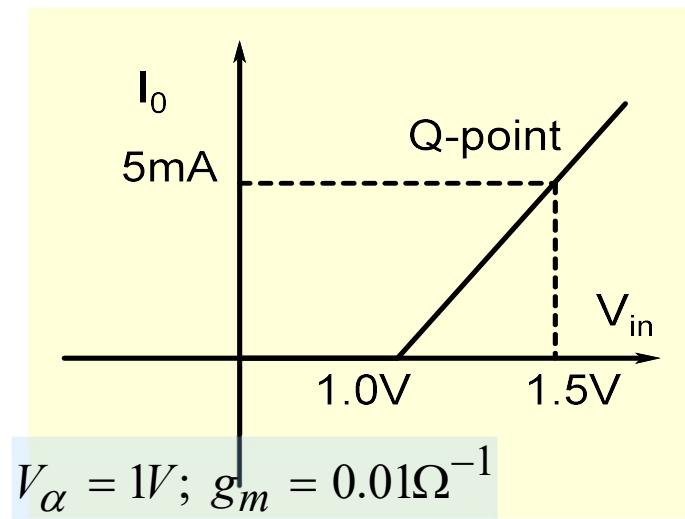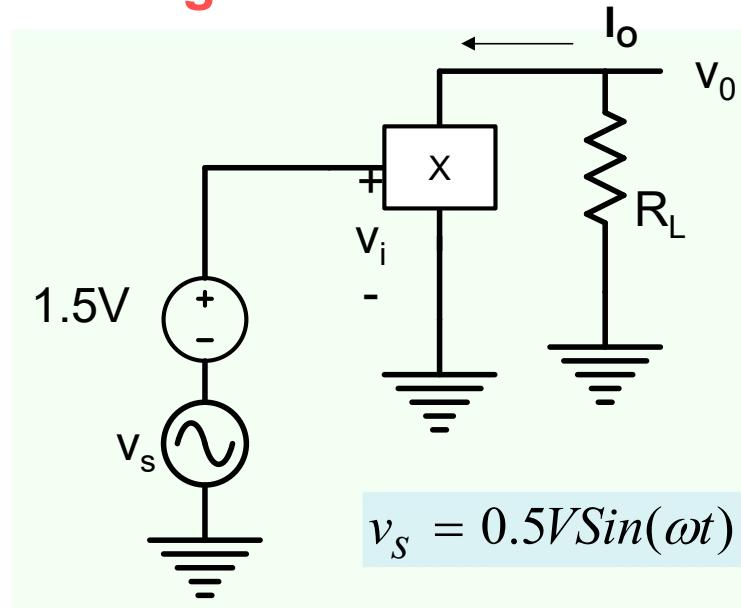

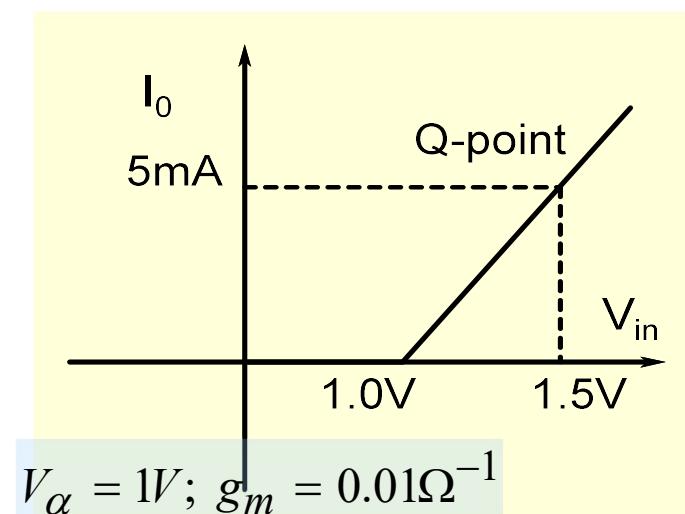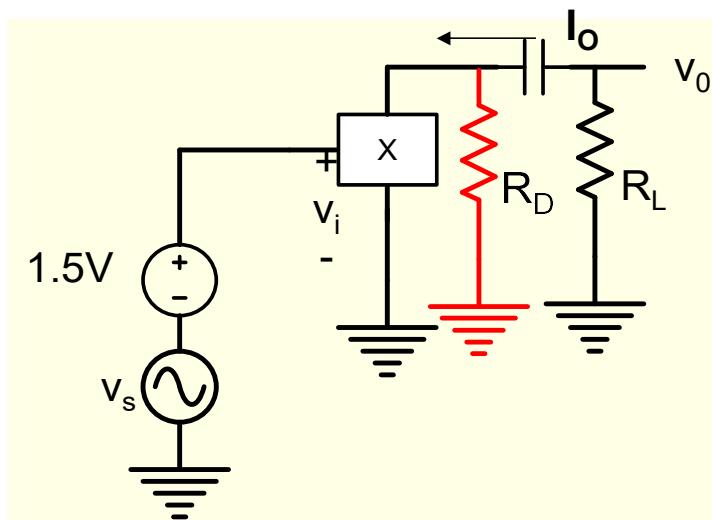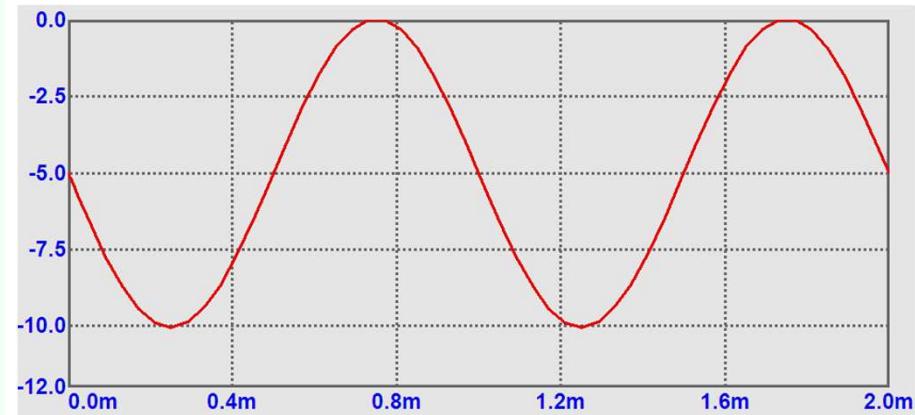
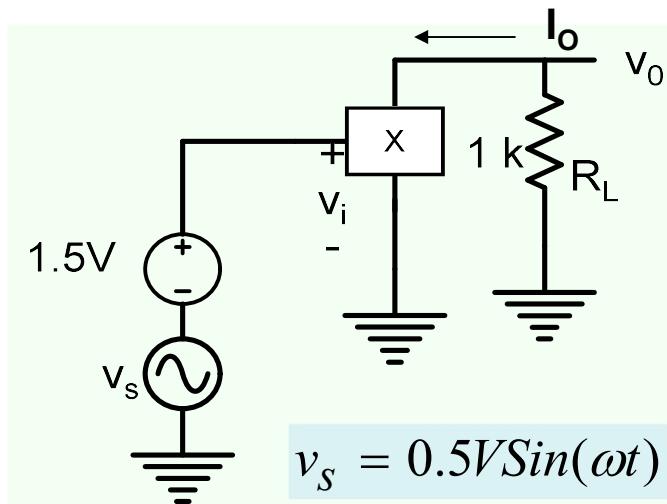
How do we get rid of unwanted dc voltage at the output ?



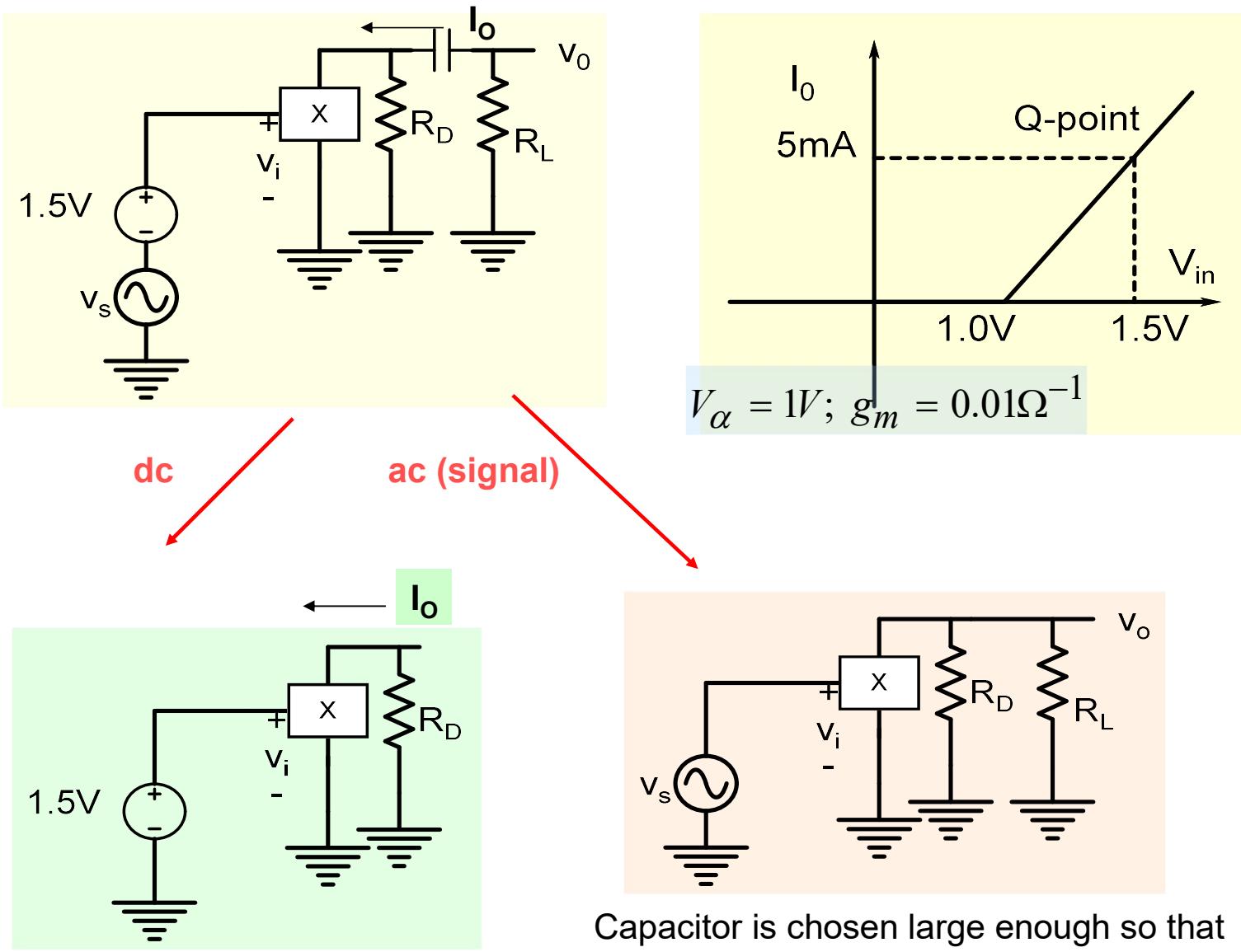






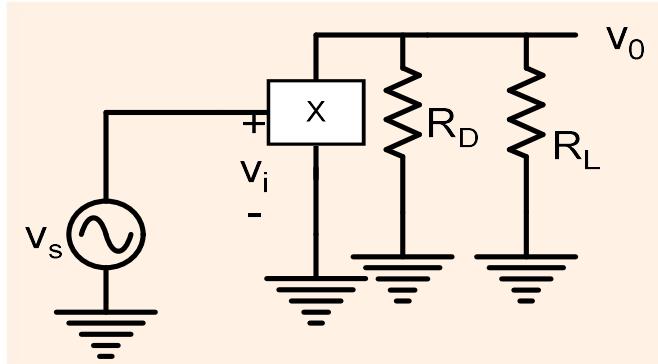

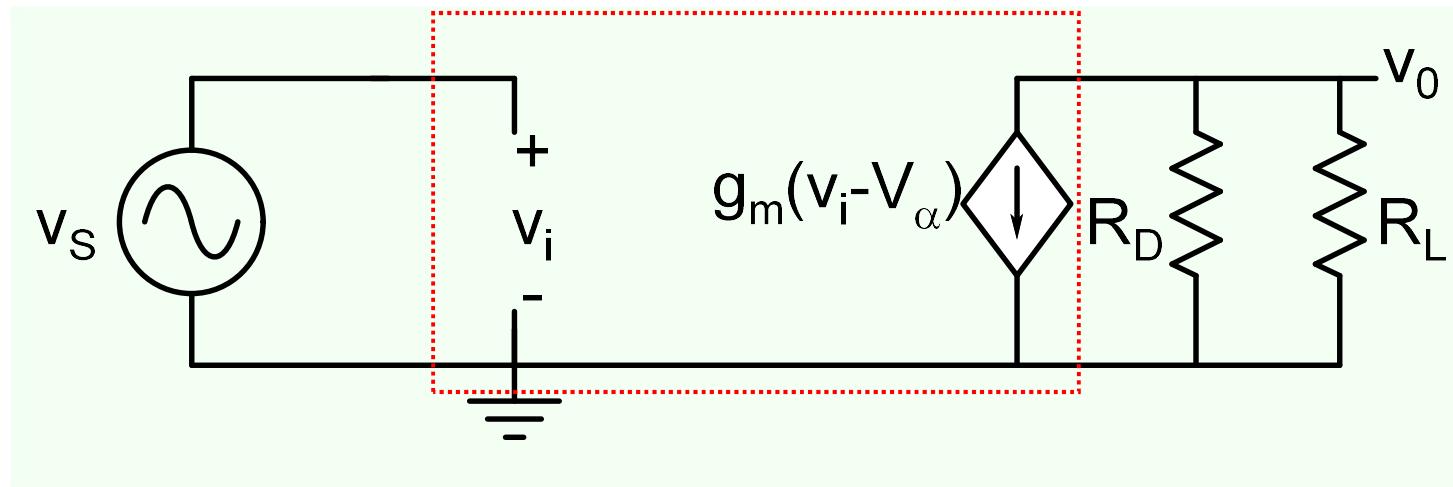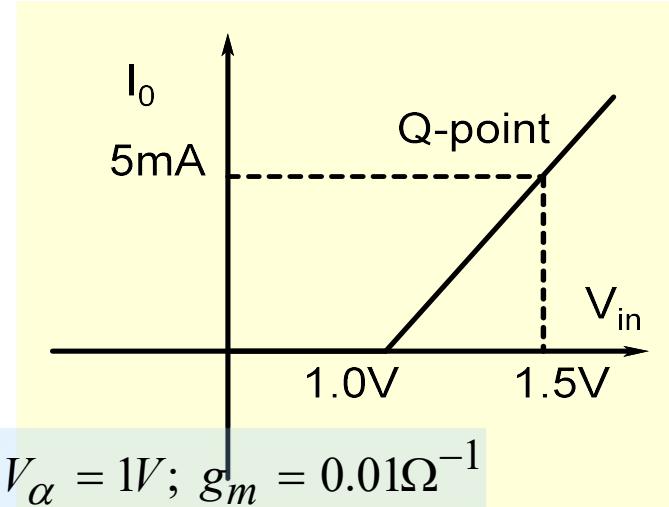
$$I_o = g_m \times (V_i - V_\alpha) \text{ for } V_i > V_\alpha$$





Ac Analysis

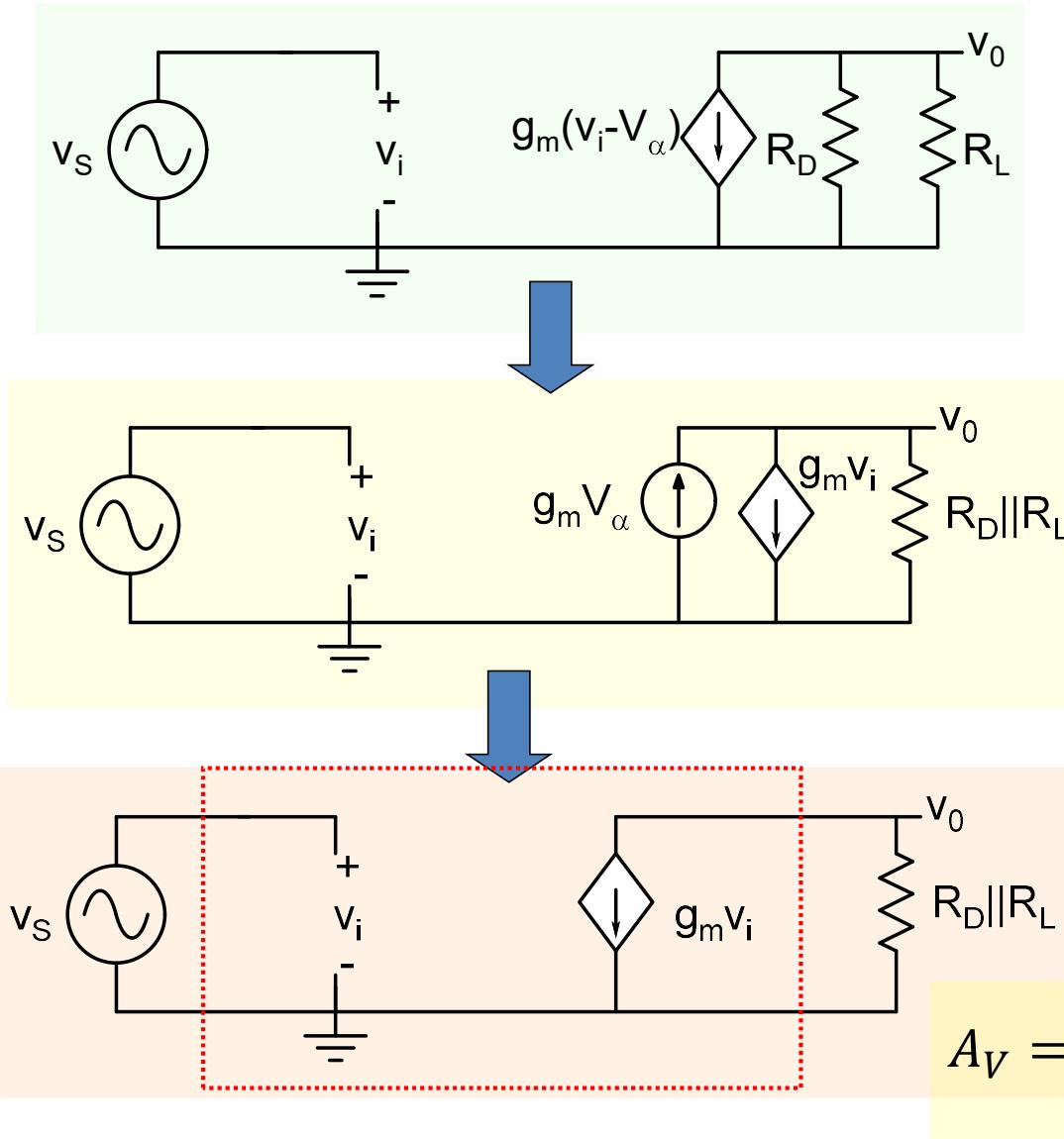

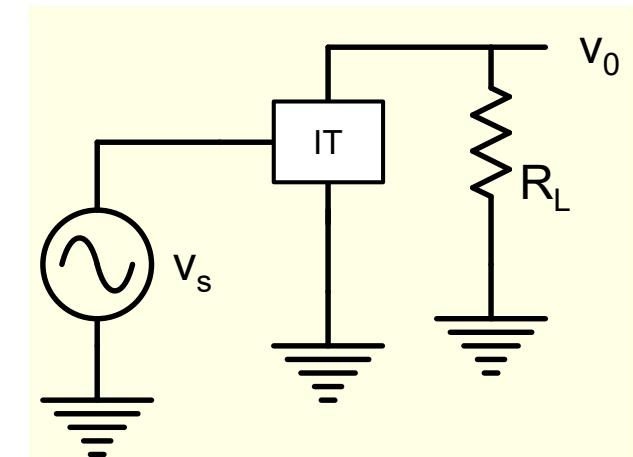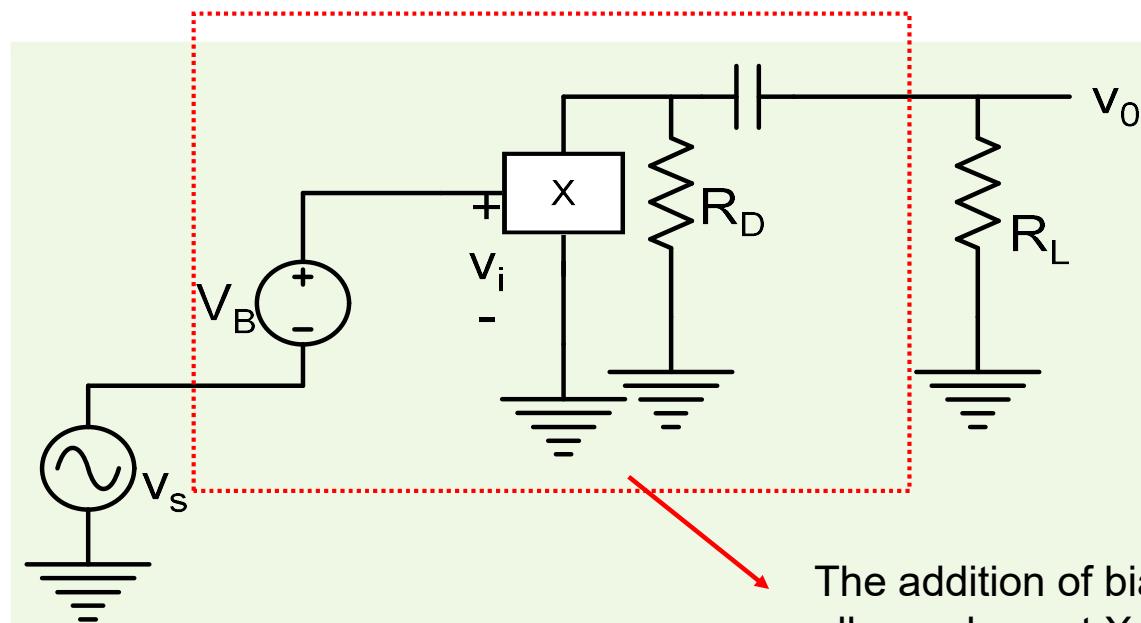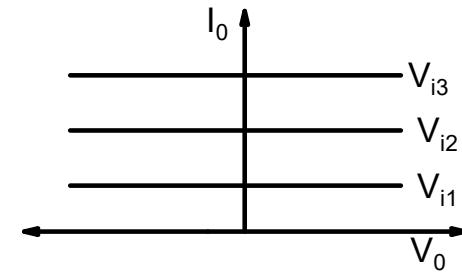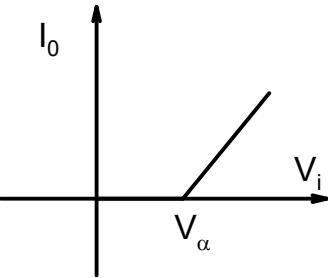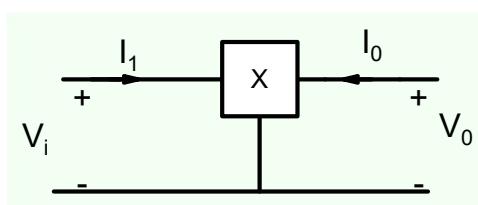


The addition of biasing network allows element X to appear as an ideal transistor to the signal source

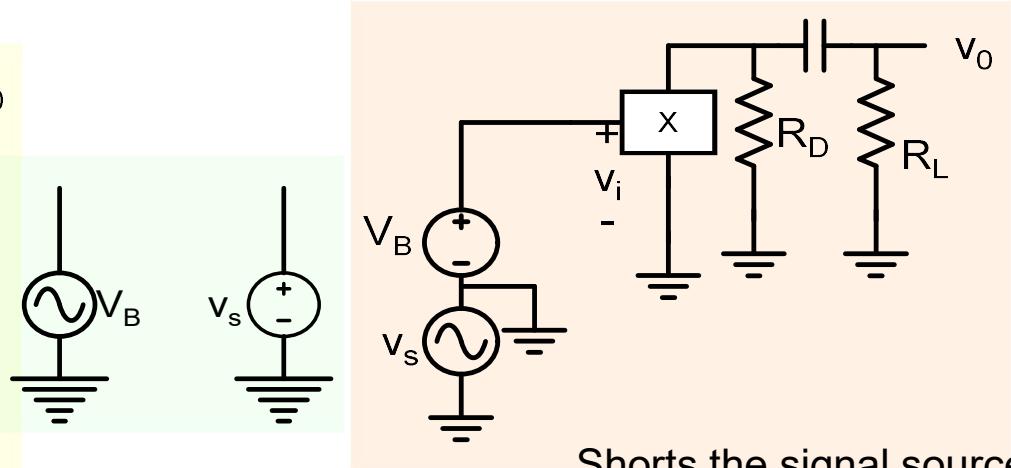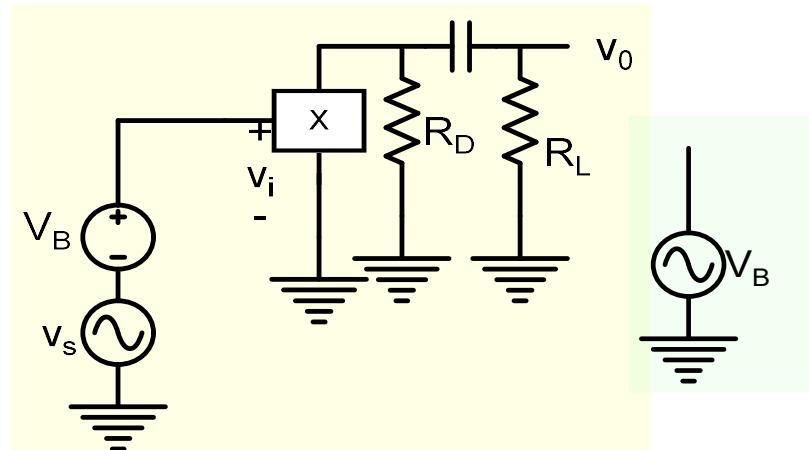What happens if both dc voltage source and signal source have one terminal as ground?





Shorts the signal source

Solution


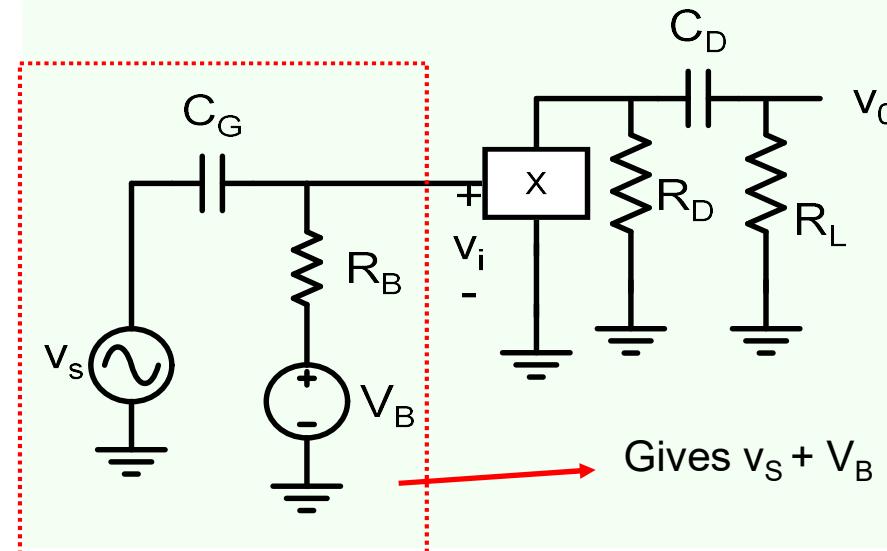


Gives $v_s + V_B$

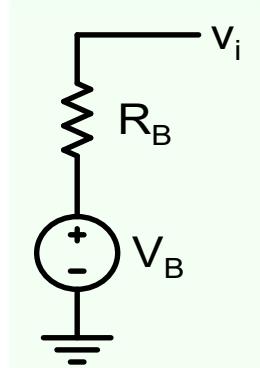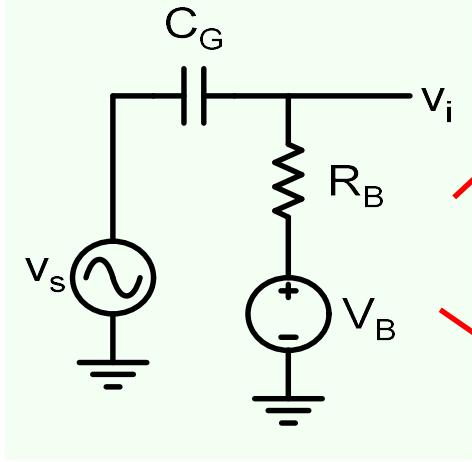

$$v_i = V_B$$

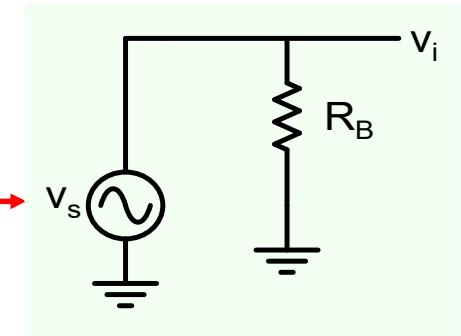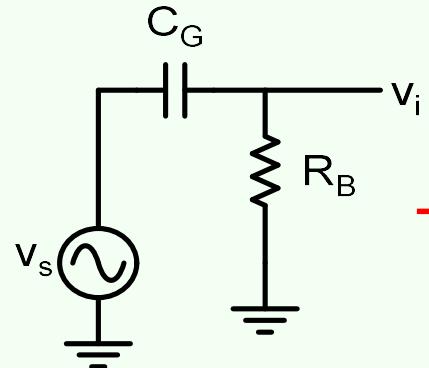Capacitor is chosen large enough so that at the signal frequency $1/j\omega C \sim 0$.





$$v_i = v_s$$

$$v_i(\text{total}) = v_s + V_B$$

Note the role of R_B

Amplifier Schematic

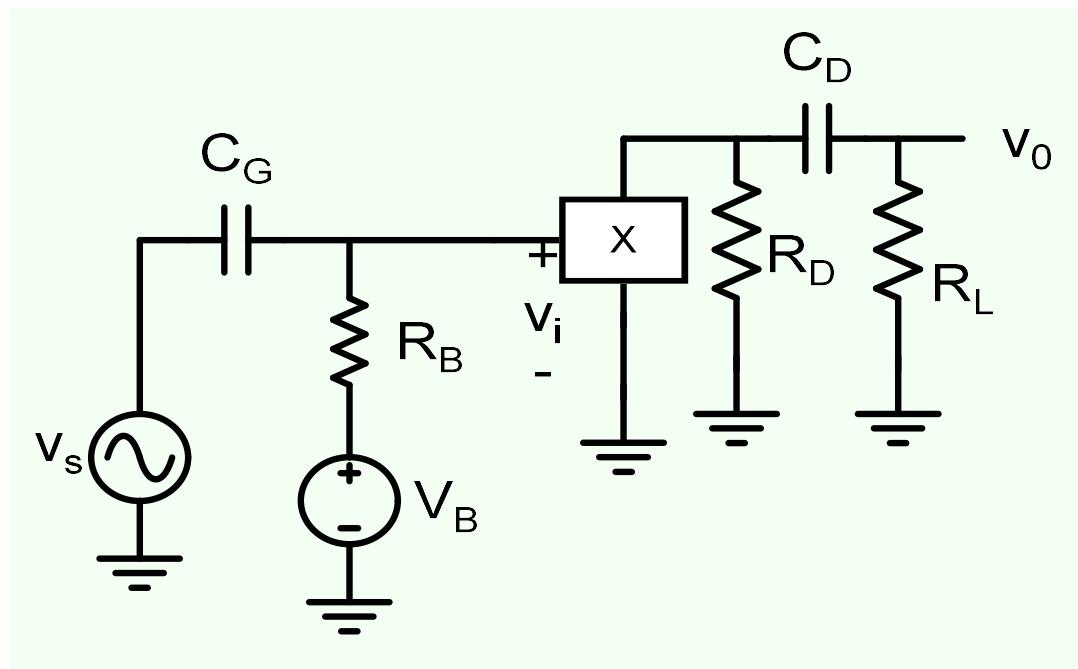
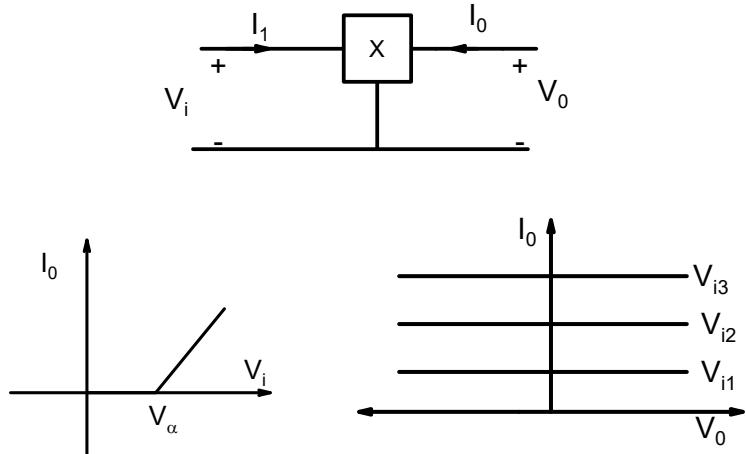


ESC201T : Introduction to Electronics



Lecture 26: Amplifiers-2

B. Mazhari
Dept. of EE, IIT Kanpur


Amplifier Schematic

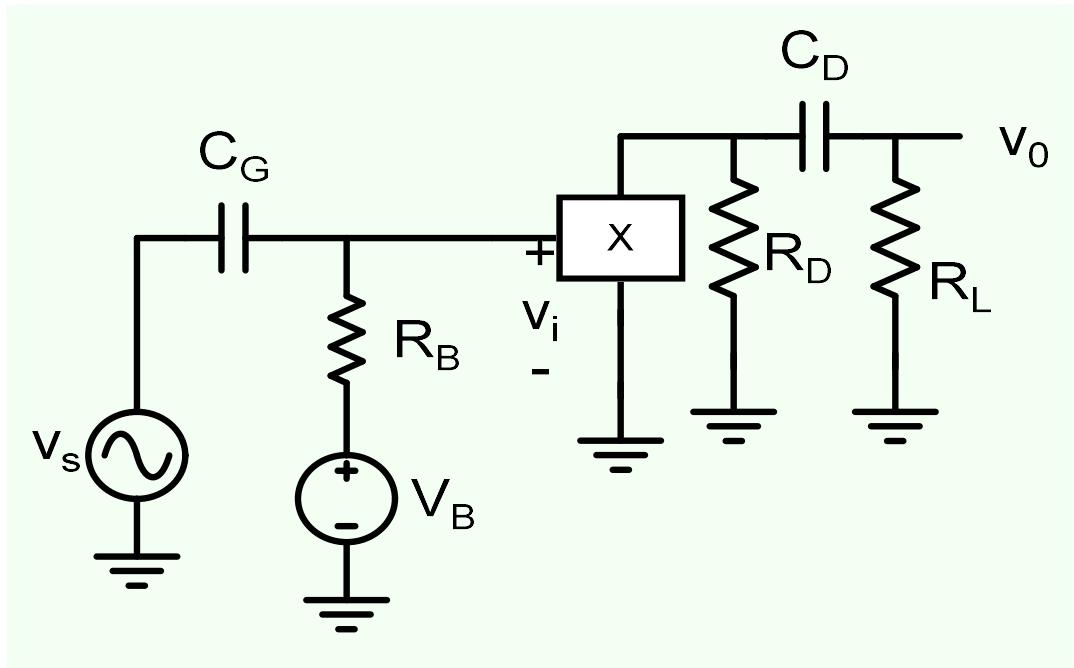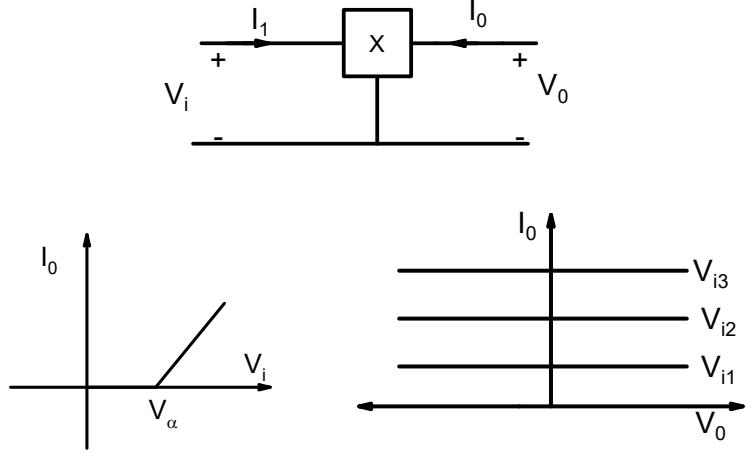



Device Y

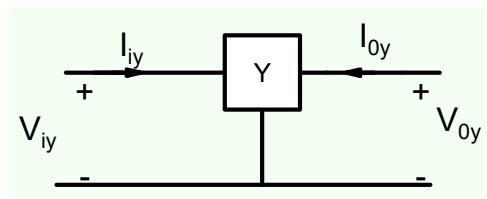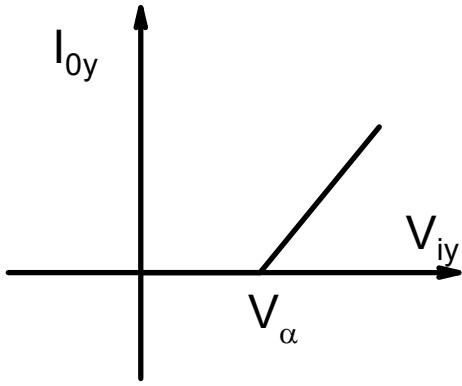


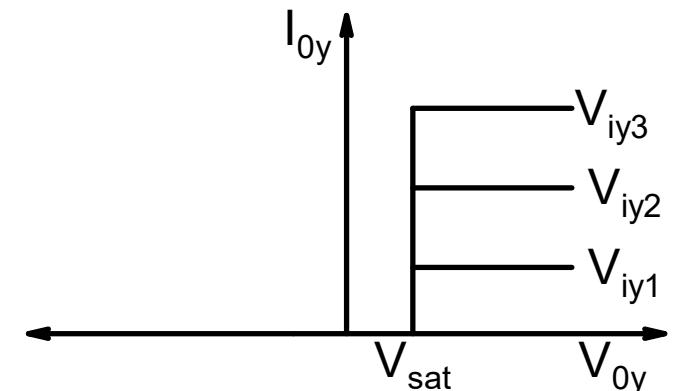
$I_{0y} = 0$ for $V_{OY} < V_{sat}$
 for $V_{OY} \geq V_{sat}$
 $I_{0y} = 0$ for $V_{iy} \leq V_\alpha$
 $= g_m \times (V_{iy} - V_\alpha)$ for $V_{iy} > V_\alpha$




Ideal Characteristics

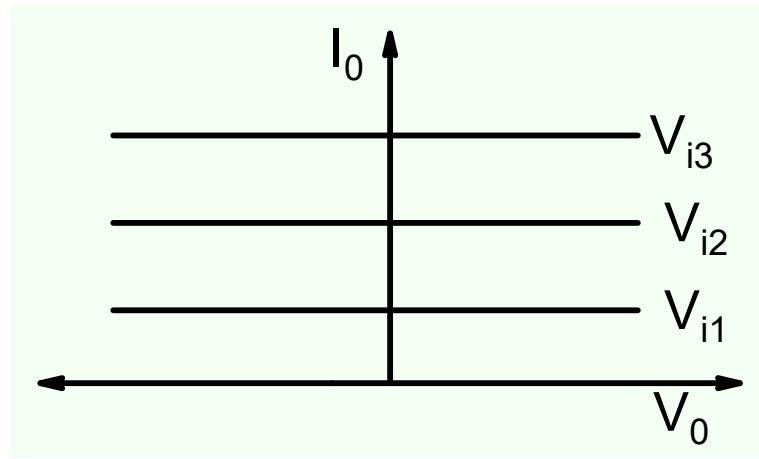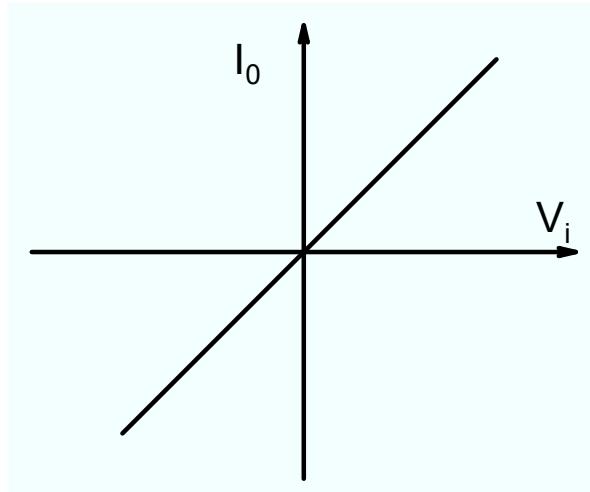

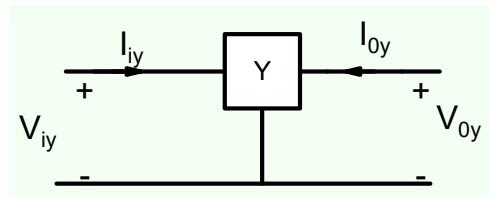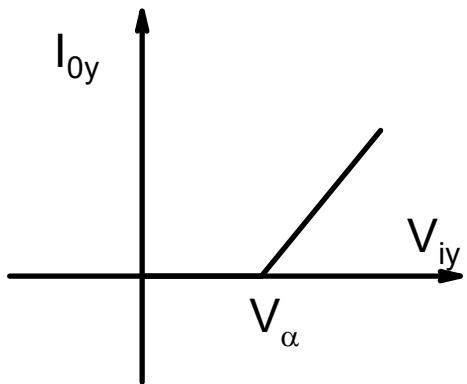
How do we use device Y to make an amplifier?






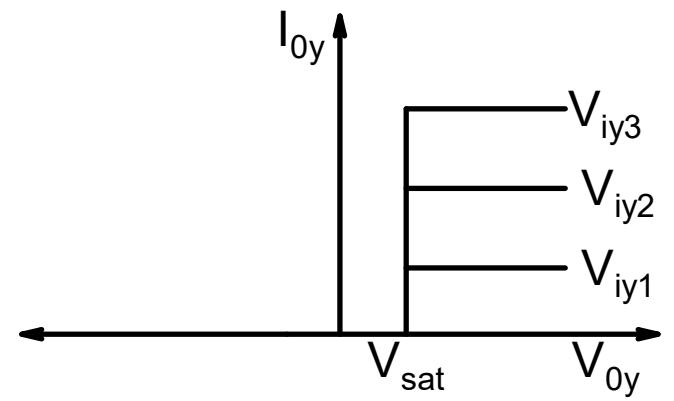
$I_{0y} = 0$ for $V_{OY} < V_{sat}$
 for $V_{OY} \geq V_{sat}$
 $I_{0y} = 0$ for $V_{iy} \leq V_\alpha$
 $= g_m \times (V_{iy} - V_\alpha)$ for $V_{iy} > V_\alpha$







Will the earlier solution work?

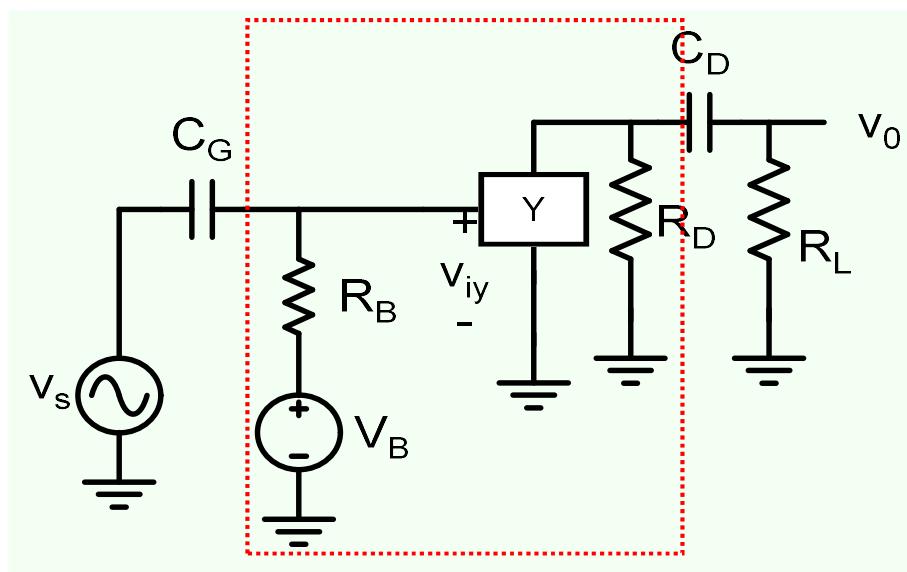

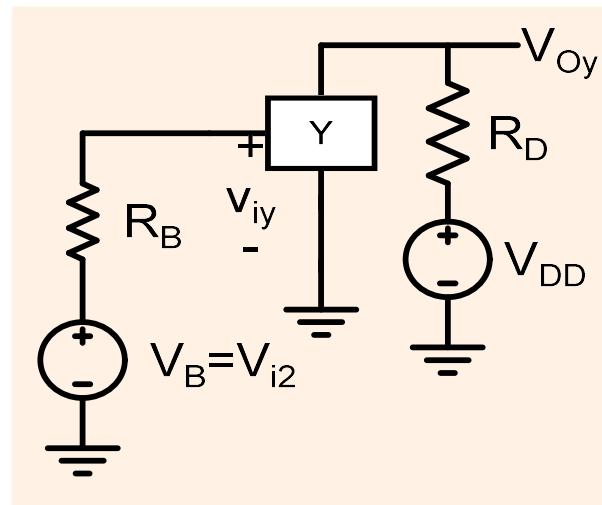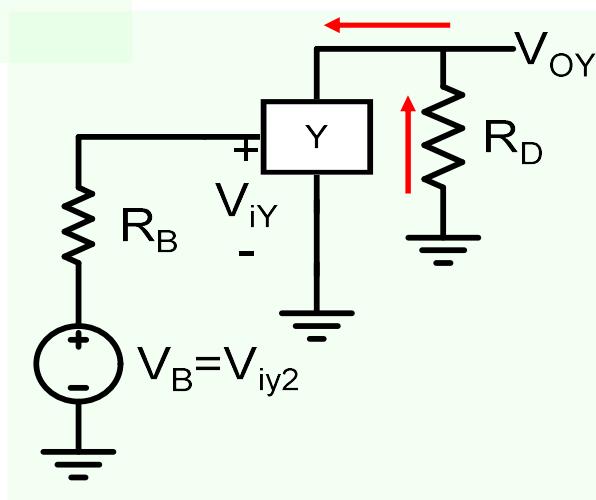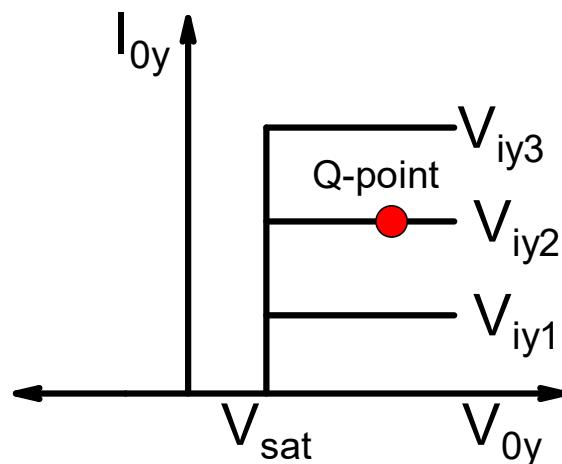
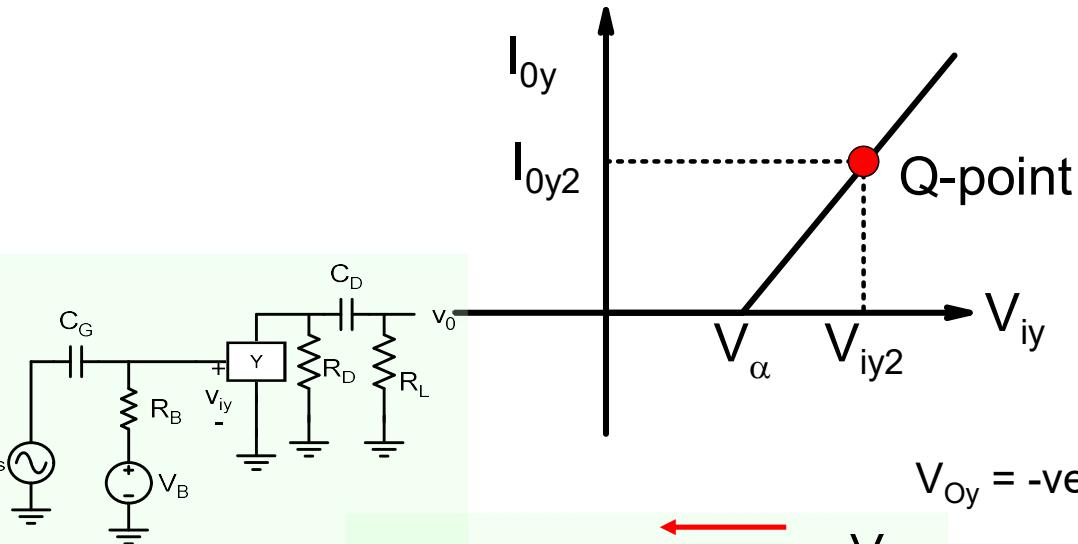
The purpose of biasing network is to operate the device in a region which resembles ideal transistor





Revised Amplifier Schematic

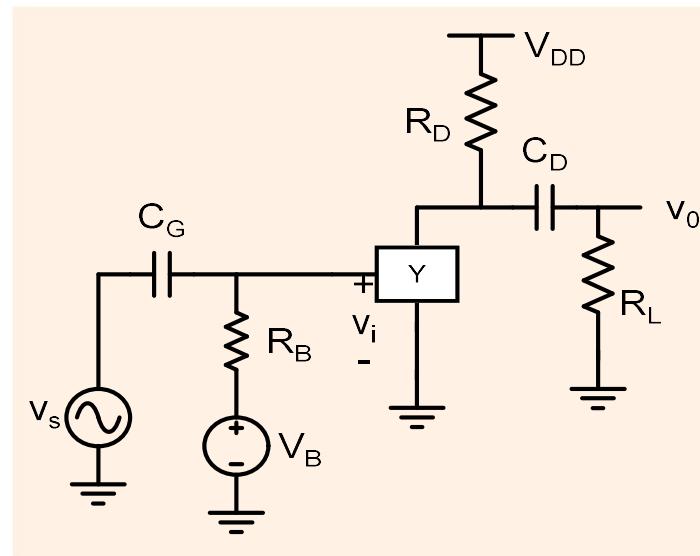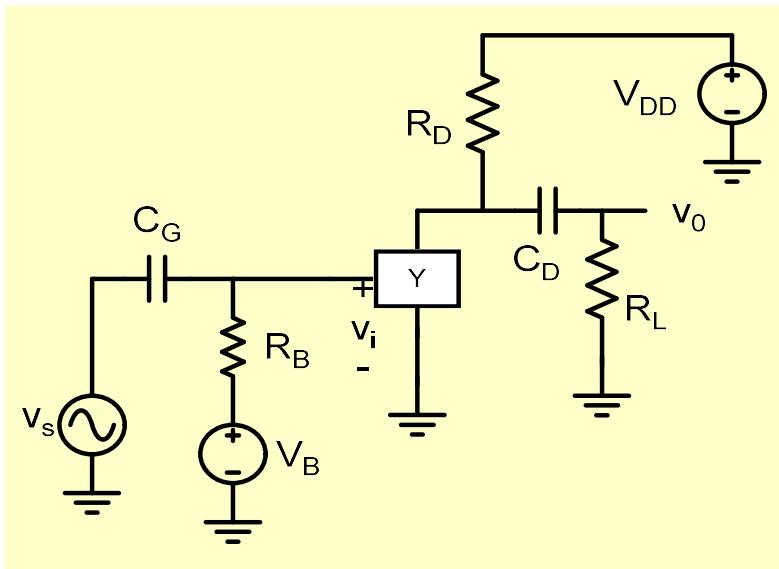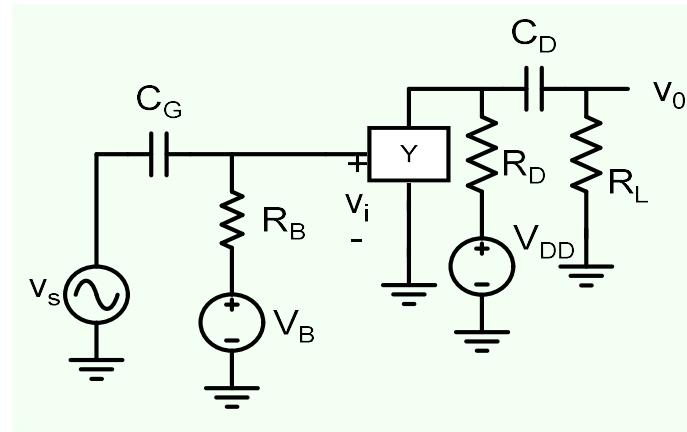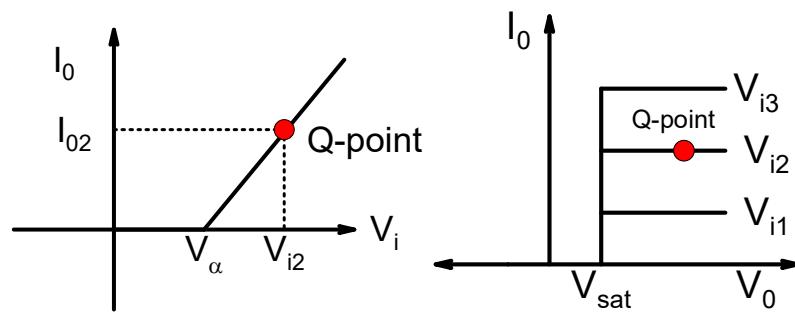

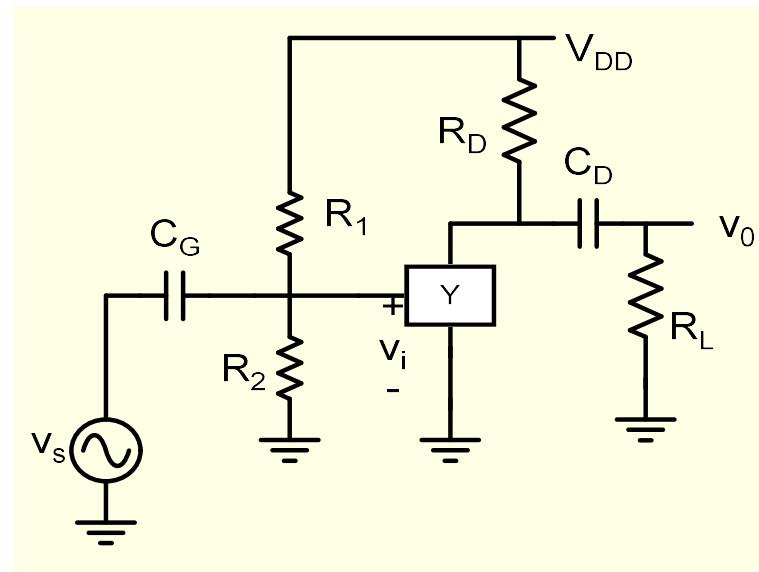
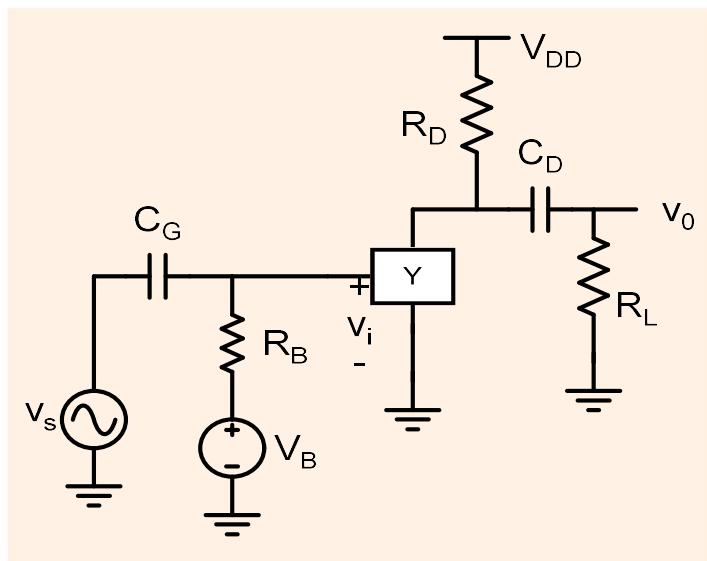
Can we Bias using one dc voltage source only?



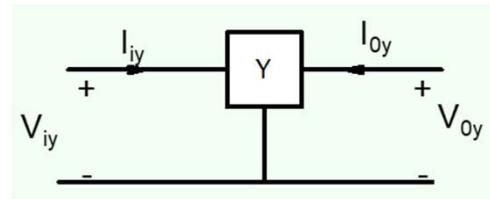
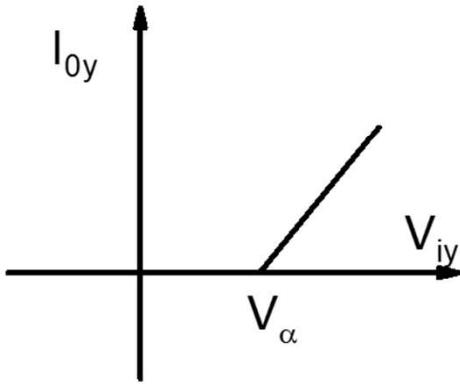
$$V_B = V_{DD} \times \frac{R_2}{R_1 + R_2}$$



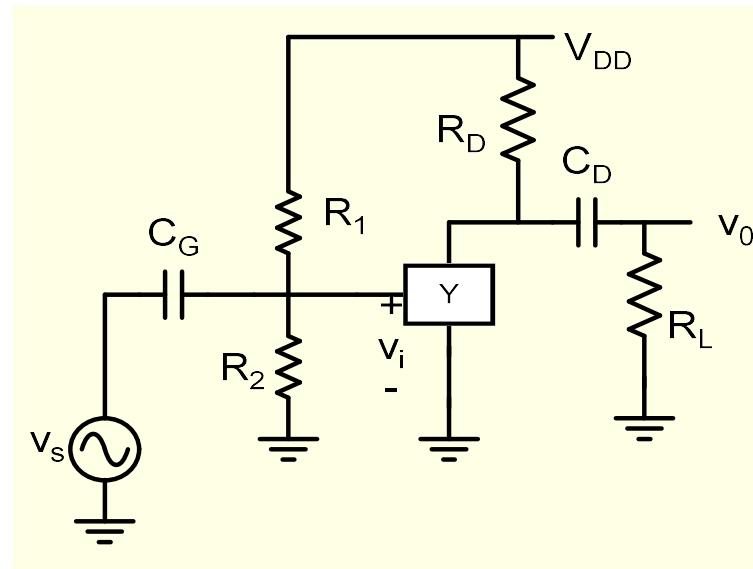
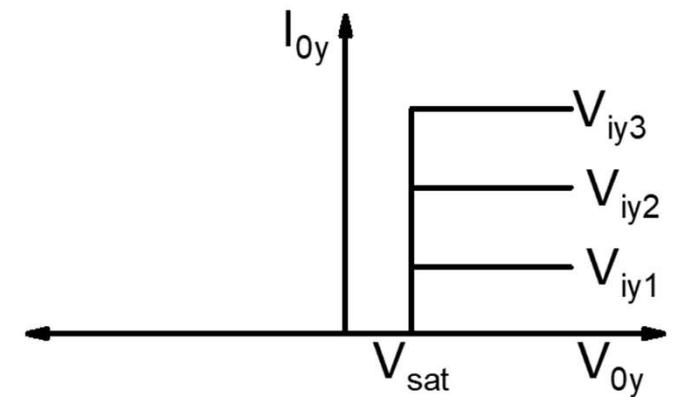
$I_{oy} = 0$ for $V_{OY} < V_{sat}$
 for $V_{OY} \geq V_{sat}$
 $I_{oy} = 0$ for $V_{iy} \leq V_\alpha$
 $= g_m \times (V_{iy} - V_\alpha)$ for $V_{iy} > V_\alpha$



Device Z

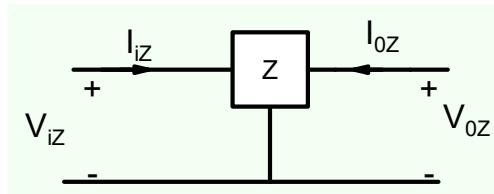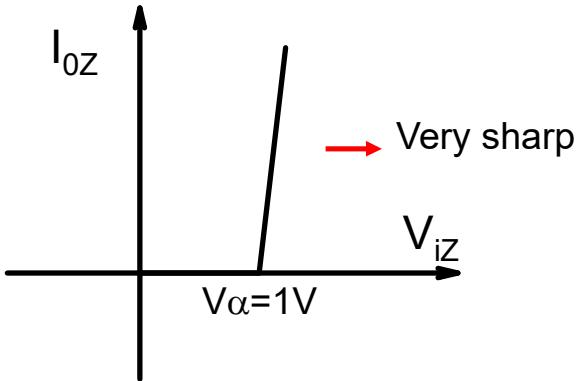

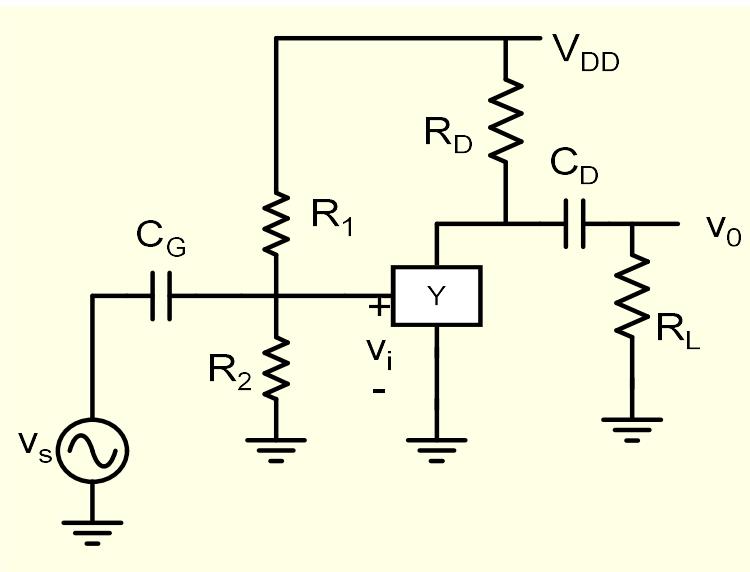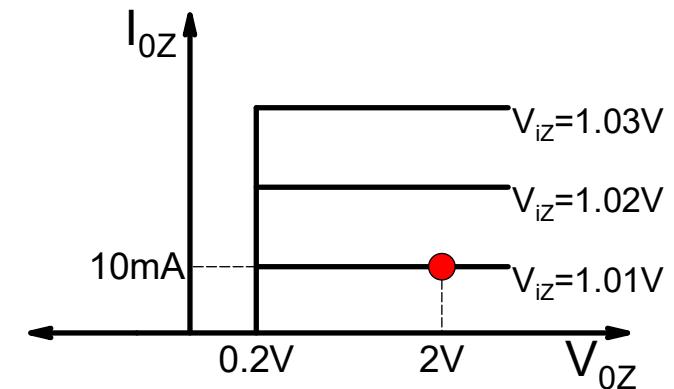$I_{0Z} = 0$ for $V_{OZ} < 0.2V$
 for $V_{OZ} \geq 0.2$
 $I_{0Z} = 0$ for $V_{iz} \leq 1V$
 $= 1 \times (V_{iz} - 1V)$ for $V_{iz} > 1V$





Circuit is very sensitive to variations in resistor values, power supply, device parameters such as V_α

$$V_{DD} = 5V; R_2 = 1K; R_1 = 3.95K \\ \Rightarrow V_{iz} = 1.01 \Rightarrow I_{0Z} = 10mA$$


$$V_{DD} = 5V; R_2 = 0.99K; R_1 = 3.95K \\ \Rightarrow V_{iz} = 1.002 \Rightarrow I_{0Z} = 1.9mA$$

$$V_{DD} = 5V; R_2 = 0.98K; R_1 = 3.95K \\ \Rightarrow V_{iz} = 0.994V \Rightarrow I_{0Z} = 0$$

Solution


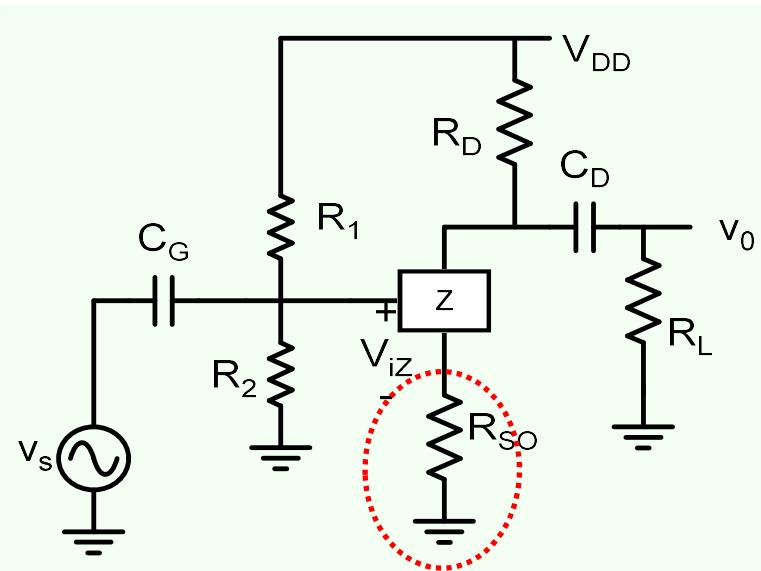
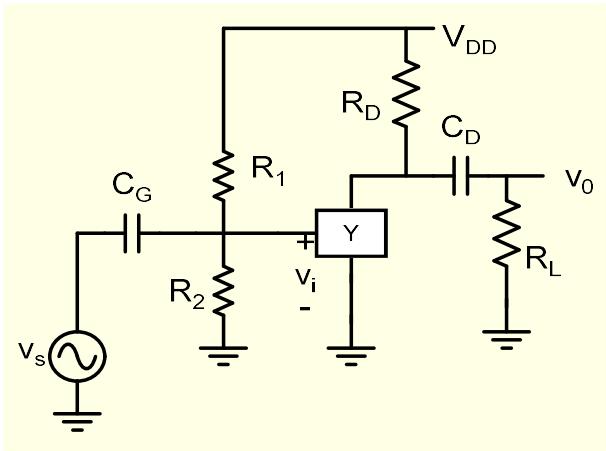


dc Analysis

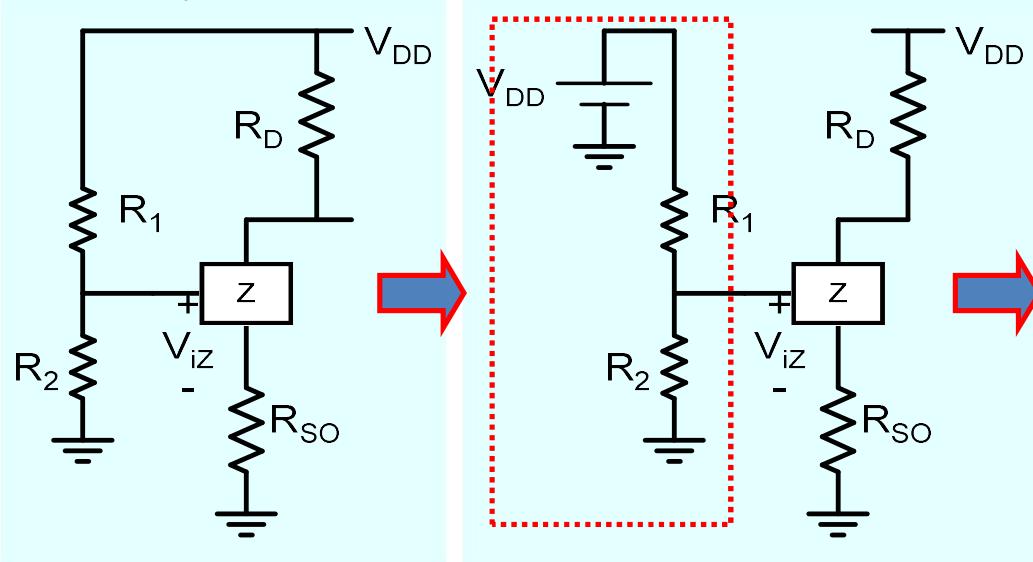

$$R_t = R_1 \parallel R_2$$
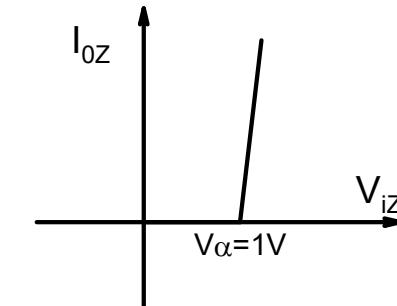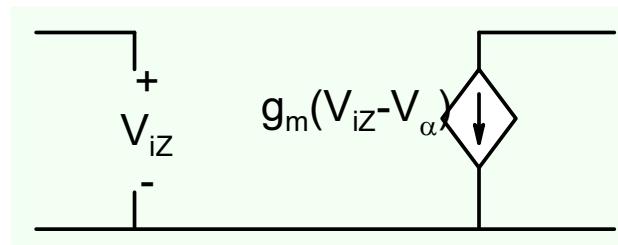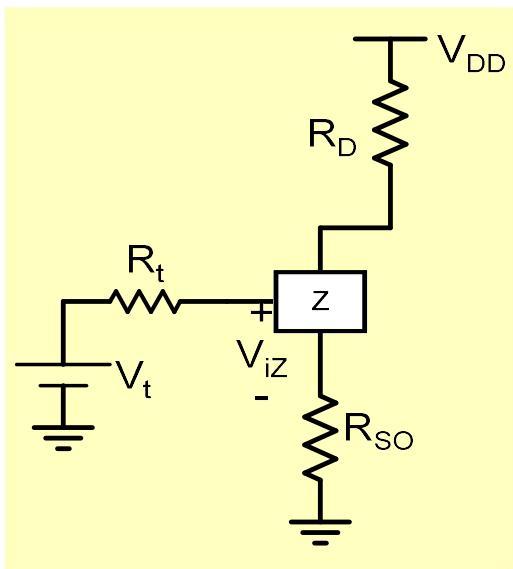
$$V_t = V_{DD} \times \frac{R_2}{R_1 + R_2}$$




$$-V_t + 0 \times R_t + V_{iZ} + I_{OZ}R_{SO} = 0$$

Since I_{OZ} vs. V_{iZ} characteristics is very sharp, $V_{iZ} \sim V_\alpha = 1V$





$$I_{OZ} \cong \frac{V_t - V_\alpha}{R_{SO}}$$



If V_t changes by 1% due to variation in resistor values then the change in output current is proportional.

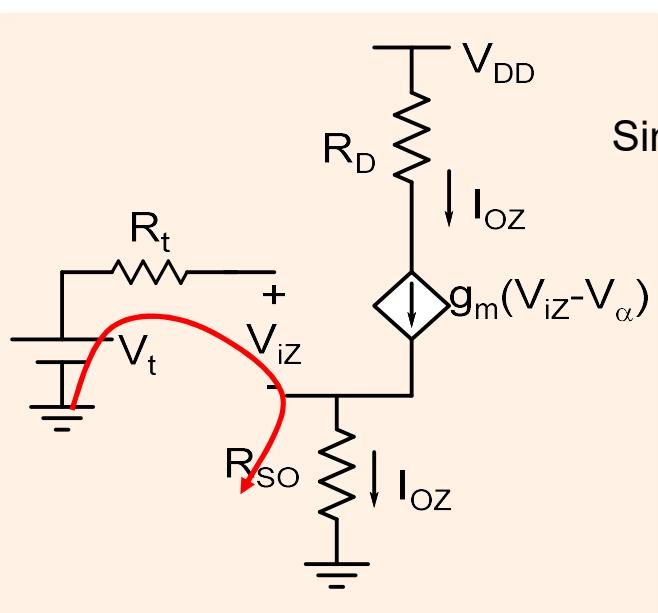Circuit is much less sensitive to variations in circuit parameters



Ac analysis

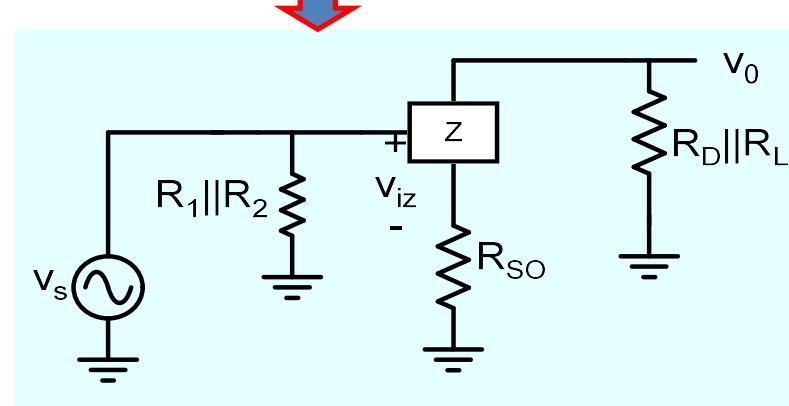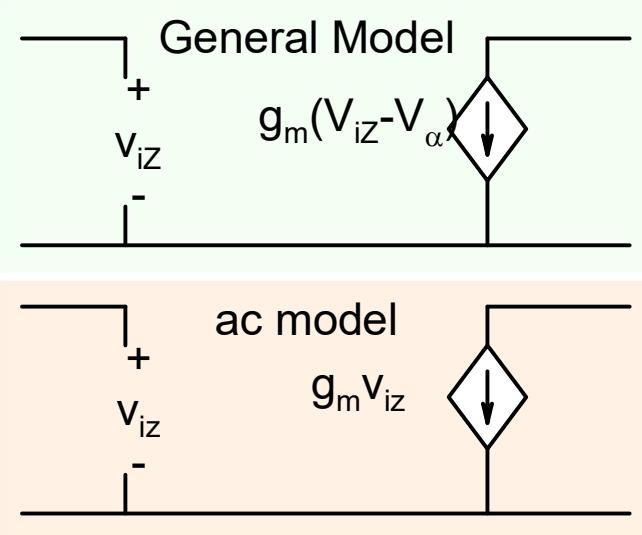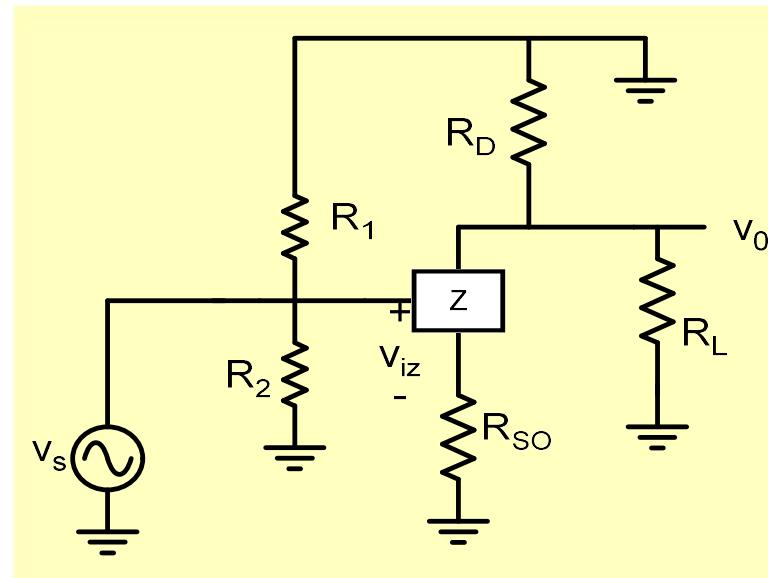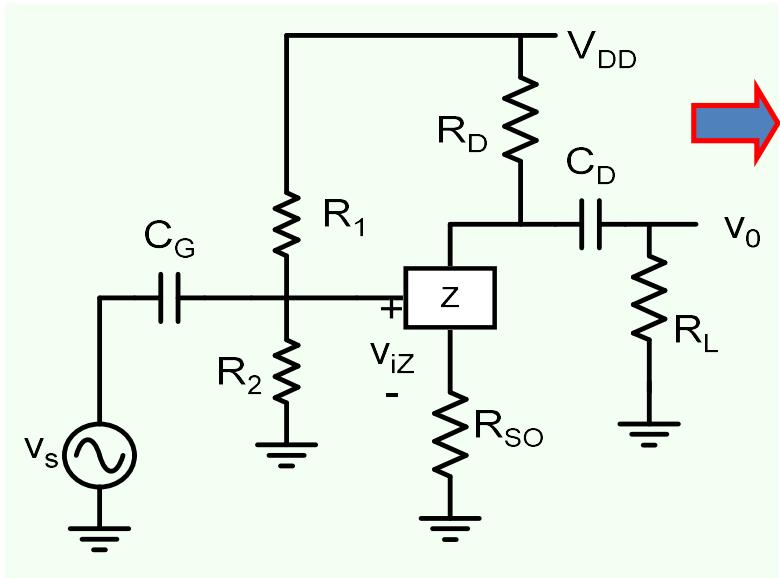


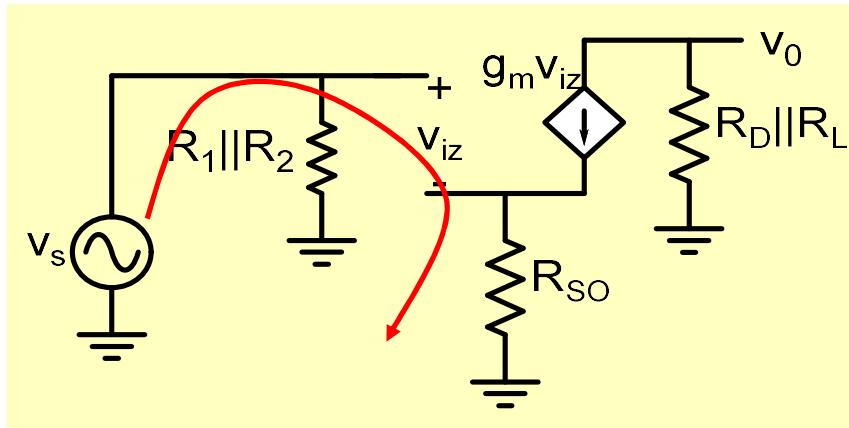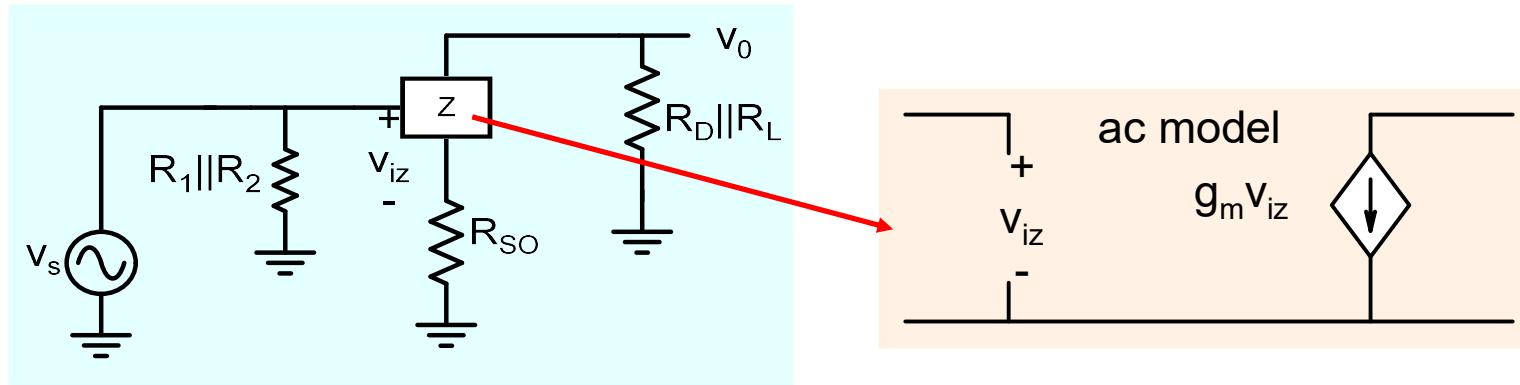

$$v_s = v_{iz} + g_m v_{iz} R_{SO}$$


$$v_o = -g_m \times R_D \parallel R_L$$
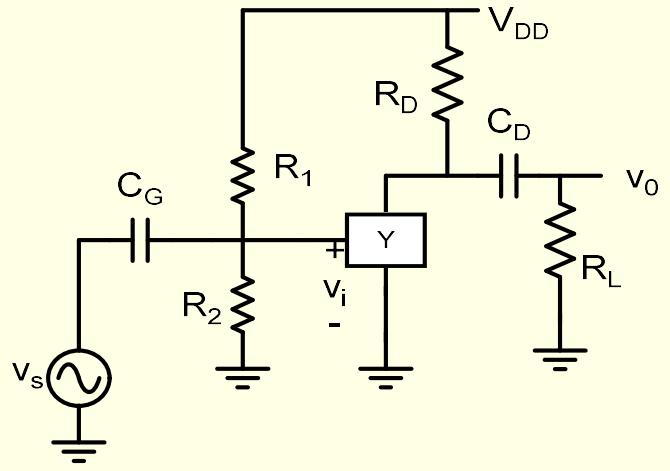
$$A_V = \frac{v_o}{v_s} = -\frac{g_m R_D \parallel R_L}{1 + g_m R_{SO}}$$



Circuit is very sensitive to variations in resistor values, power supply, device parameters such as $V\alpha$
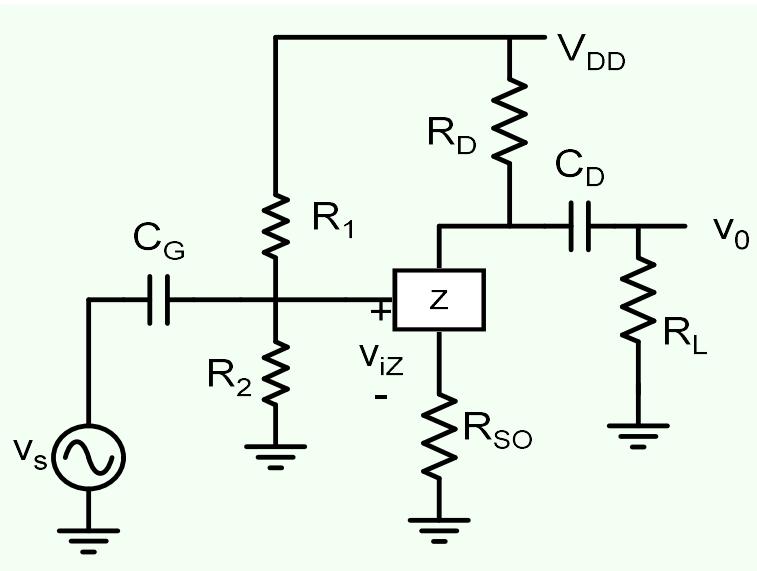
$$A_V = \frac{v_o}{v_s} = -g_m R_D \parallel R_L$$




Circuit is much less sensitive to variations in circuit parameters

$$A_V = \frac{v_o}{v_s} = -\frac{g_m R_D \parallel R_L}{1 + g_m R_{SO}}$$

But gain is smaller



Simple Solution

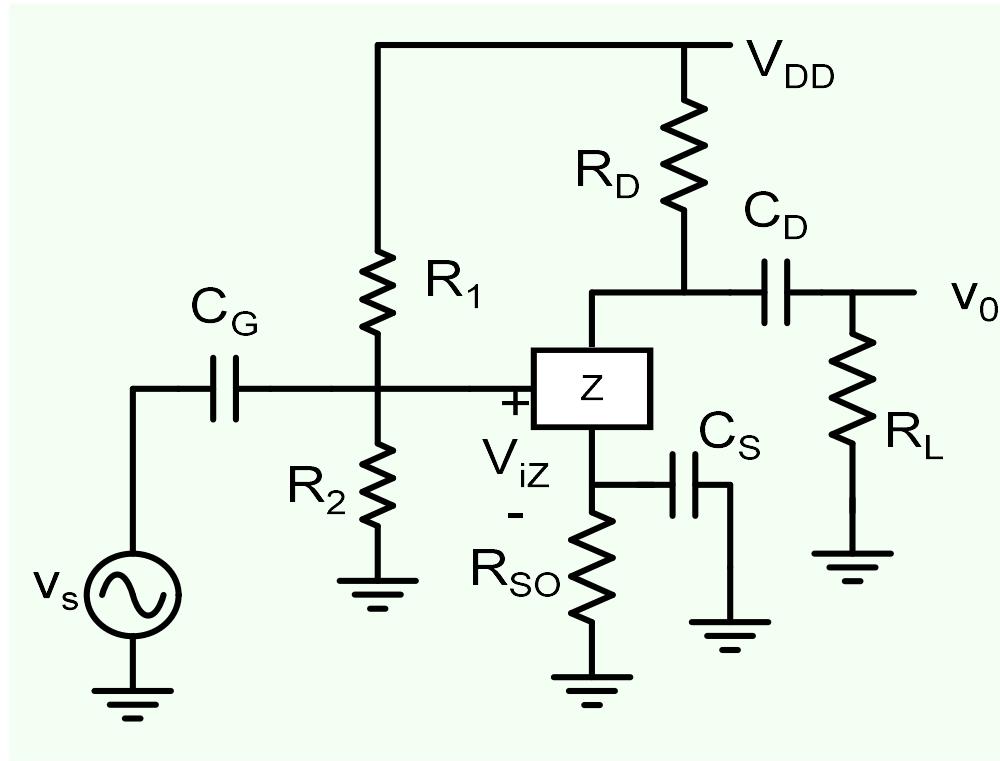

For dc, Capacitor C_S acts as open allowing R_{SO} to reduce variations in current

For ac, Capacitor C_S acts as a short circuit ($1/j\omega C \sim 0$) allowing high voltage gain to be obtained

Device NL:

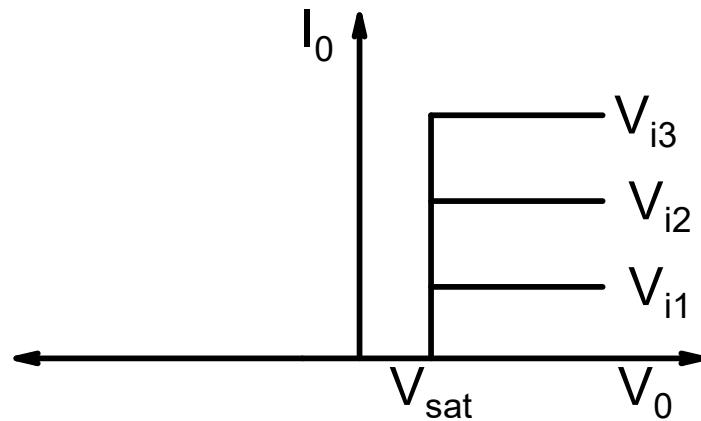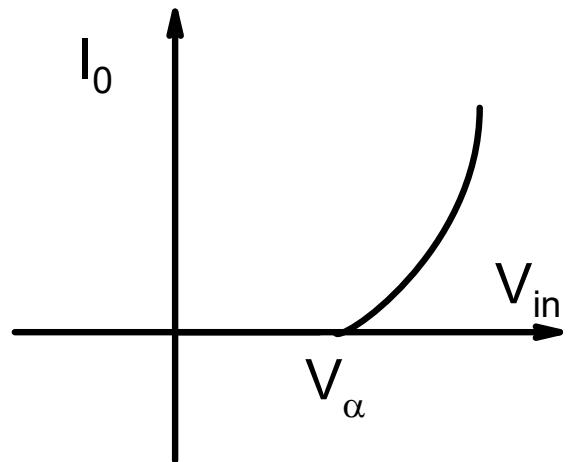





$$I_o = K \times (V_{in} - V_\alpha)^2 \text{ for } V_{in} \geq V_\alpha$$



$$V_\alpha = 1.0V ; K = 0.02$$

$$V_B = 1.5V$$

$$v_s = 0.3V \sin(\omega t)$$

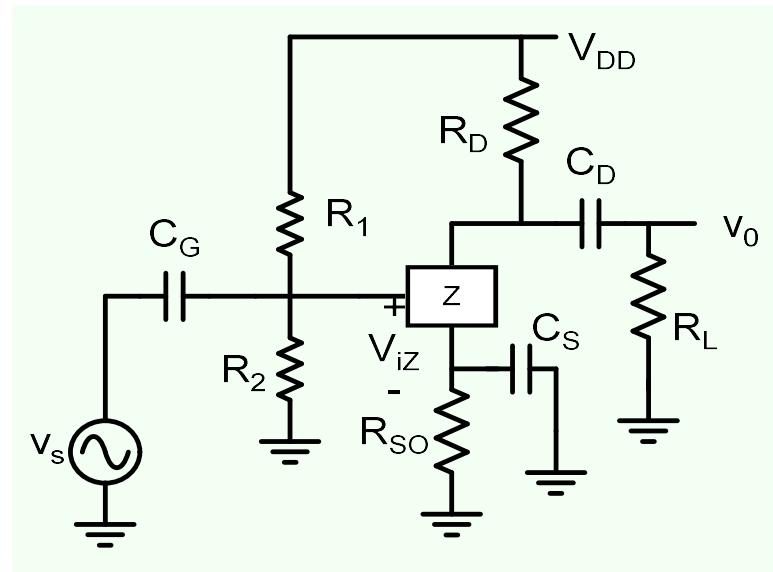


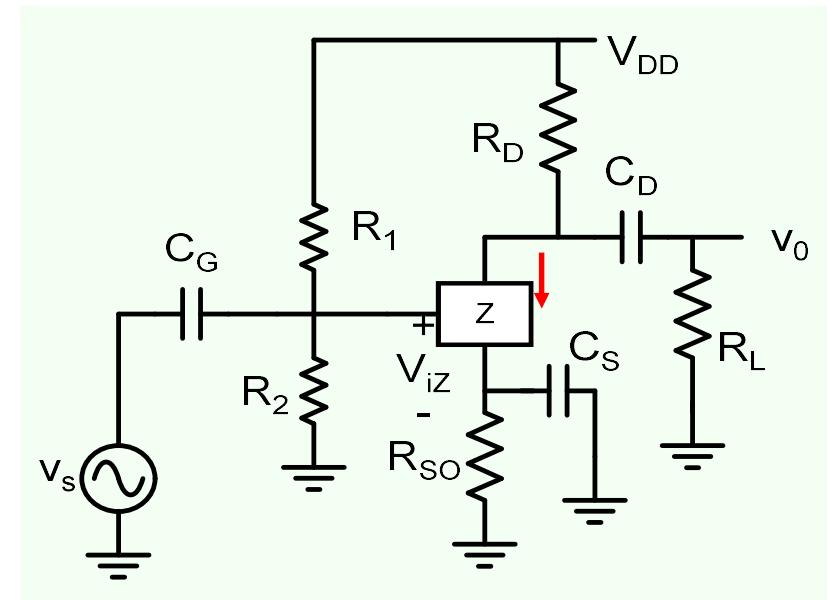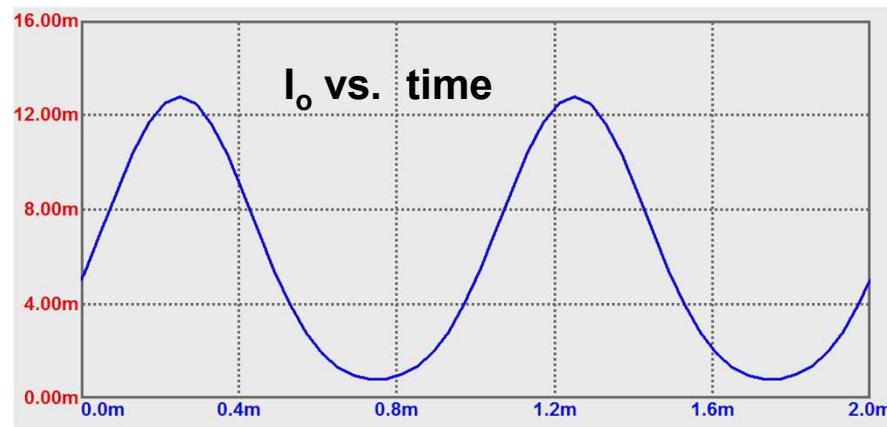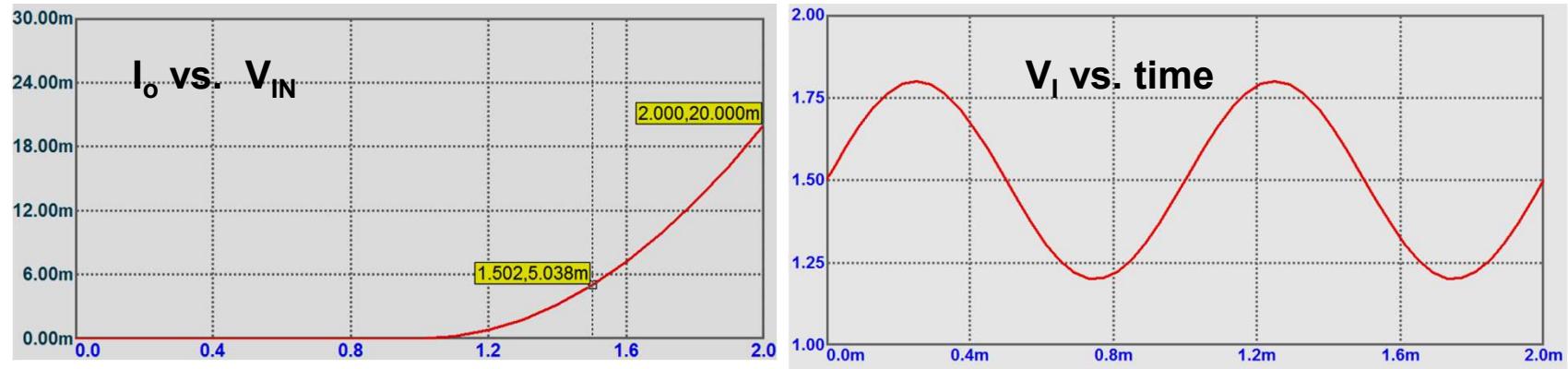

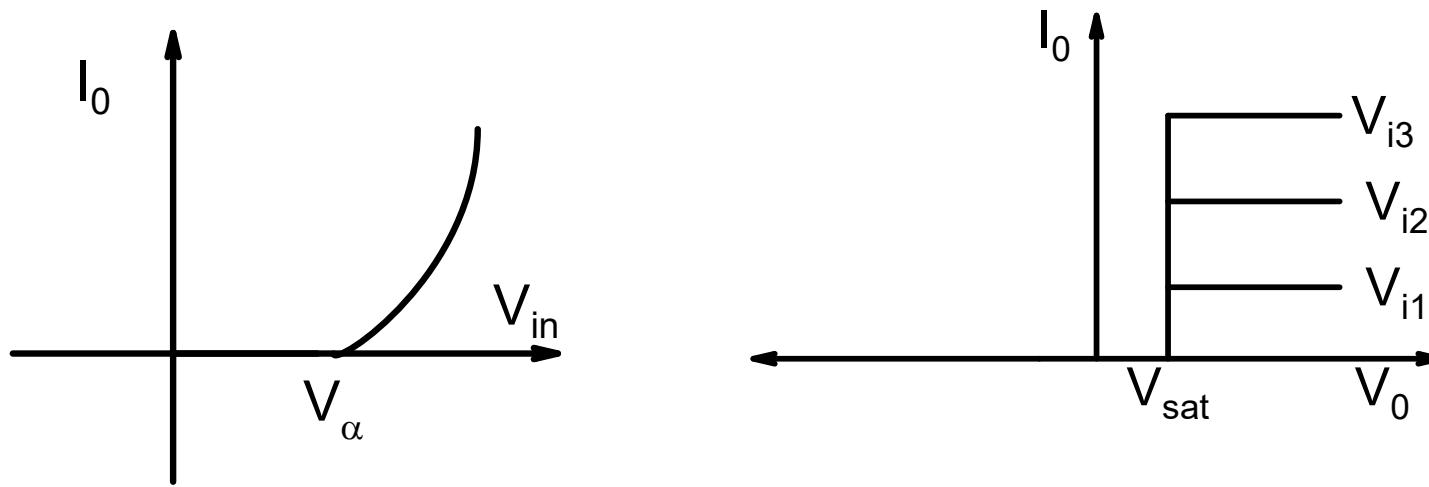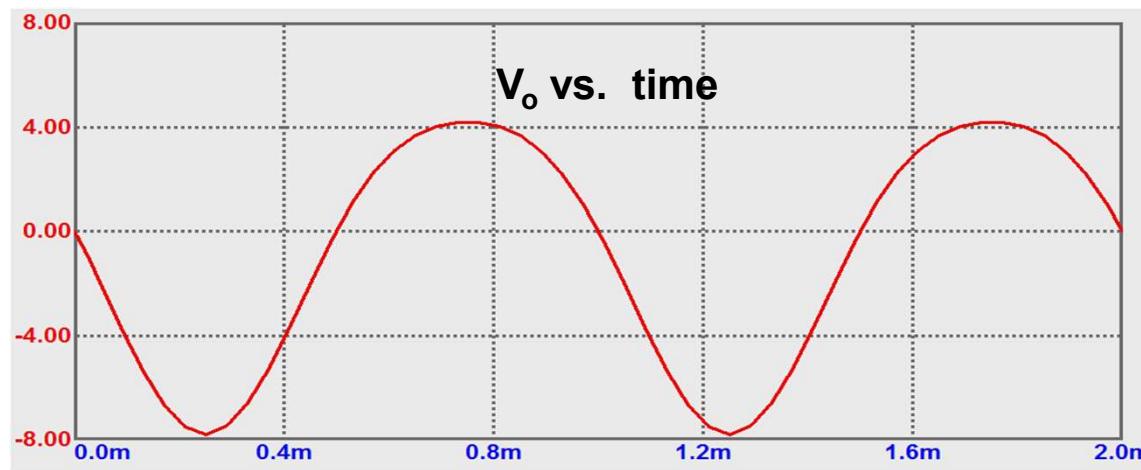



Because of Non-linearity the output waveform is distorted !

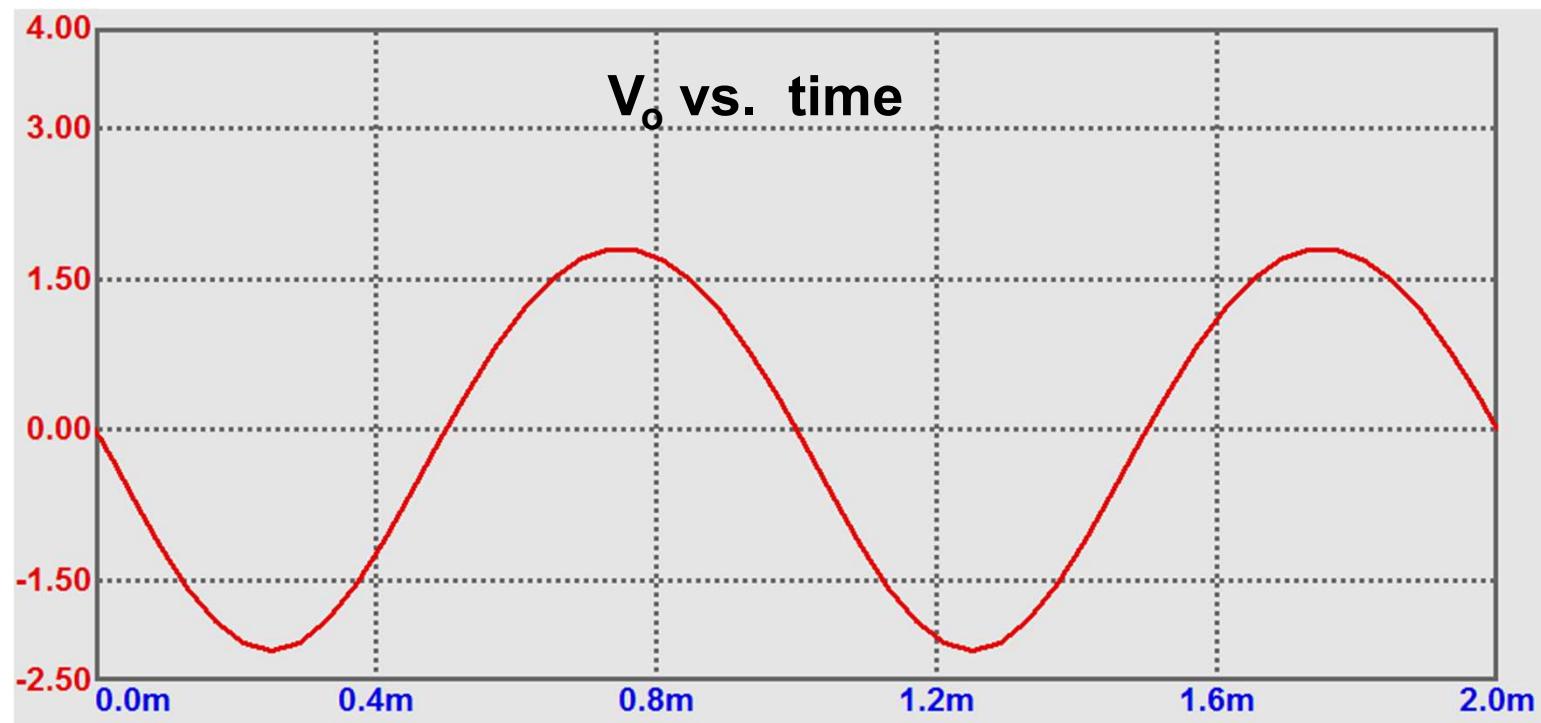Suppose input is reduced to $v_S = 0.1V \ Sin(\omega t)$



Distortion is much smaller if we restrict input voltage to a small value !

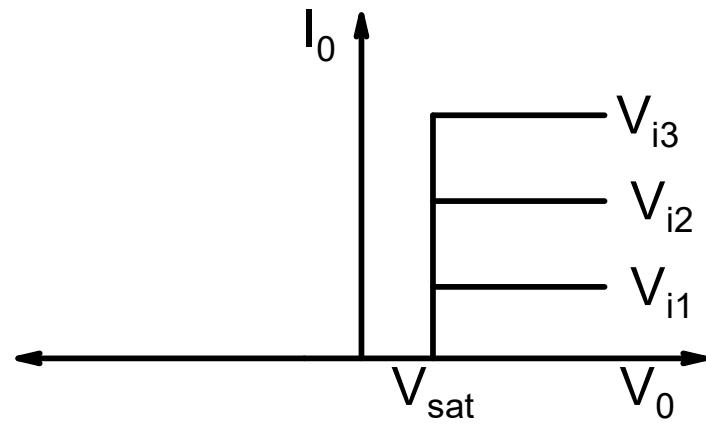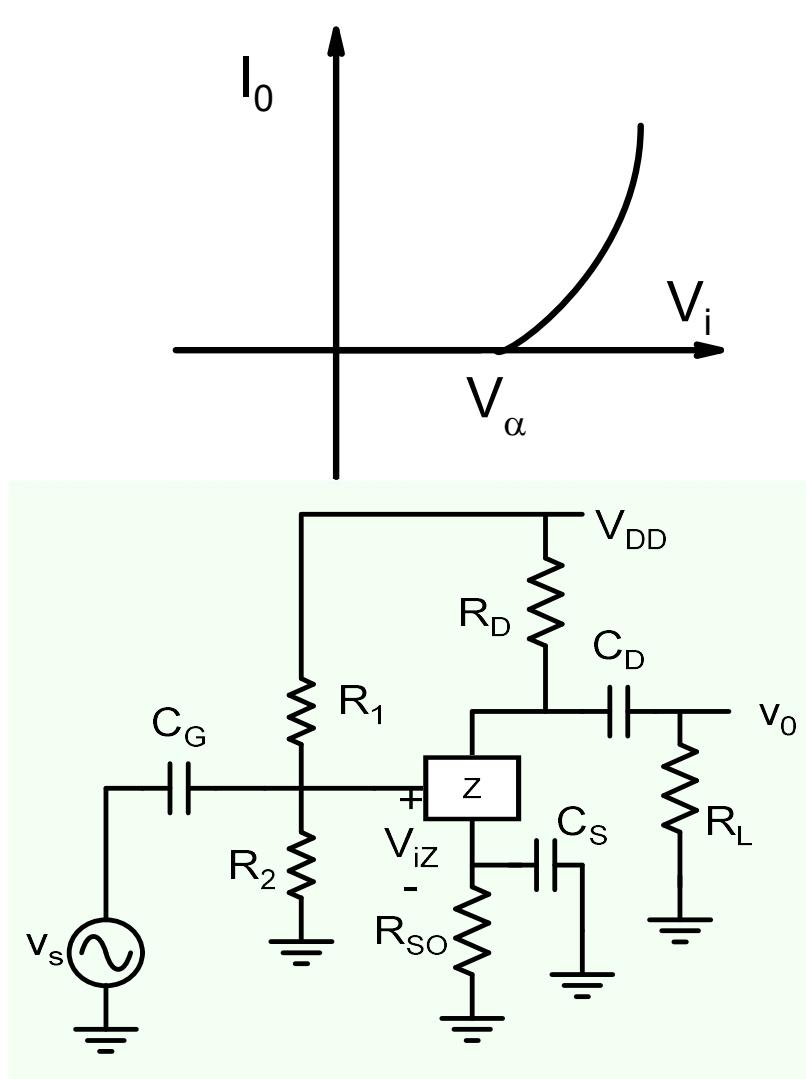Building Amplifiers with non-linear devices



Amplifier will work properly (with small distortion only if we restrict the amplitude of input signal to small values.





How small depends on the nature of non-linearity. The stronger the non-linearity the lesser the signal amplitude.

ESC201T: Introduction to Electronics




Lecture 27: Transistors

B. Mazhari
Dept. of EE, IIT Kanpur

Transistor

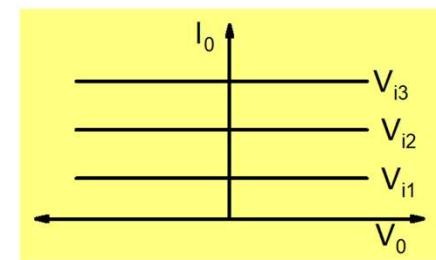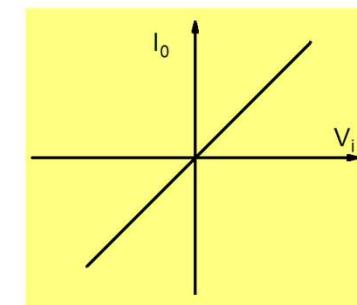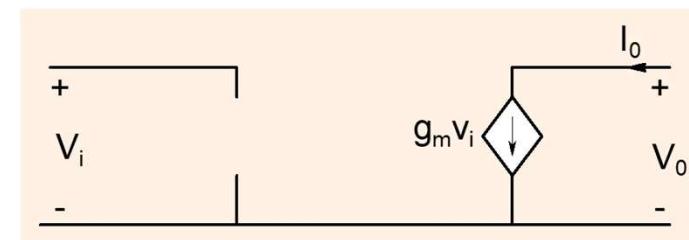
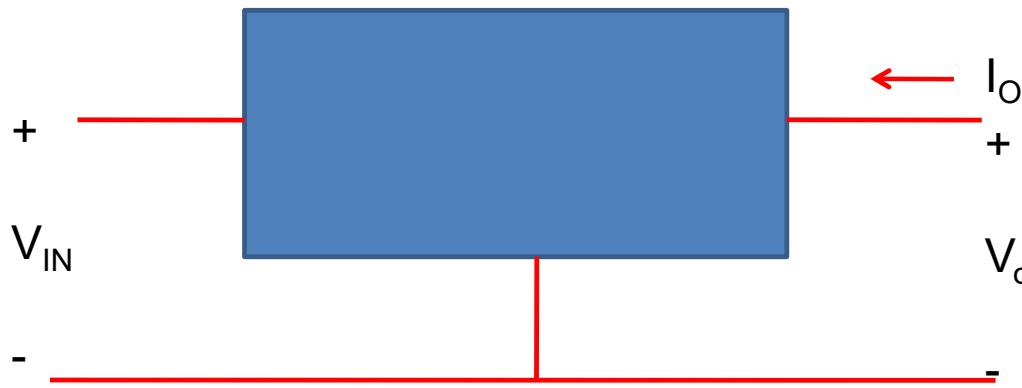


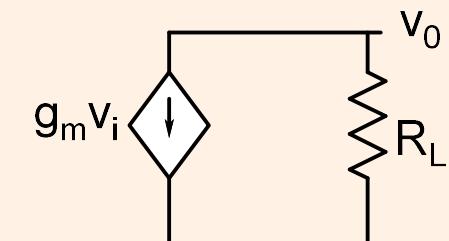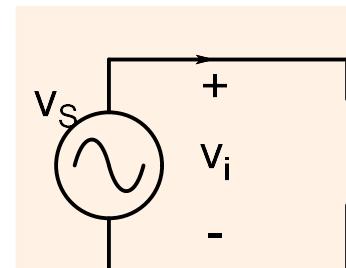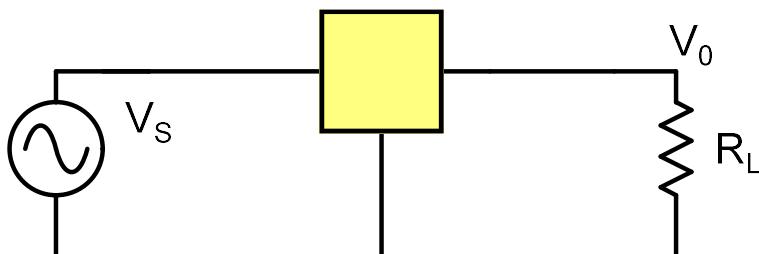Current I_o is much more sensitive to V_{IN} than V_o



$$A_V = \frac{V_o}{V_s} = -g_m \times R_L$$

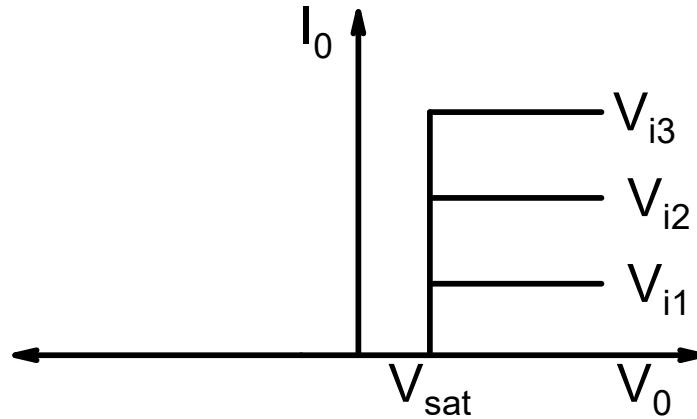
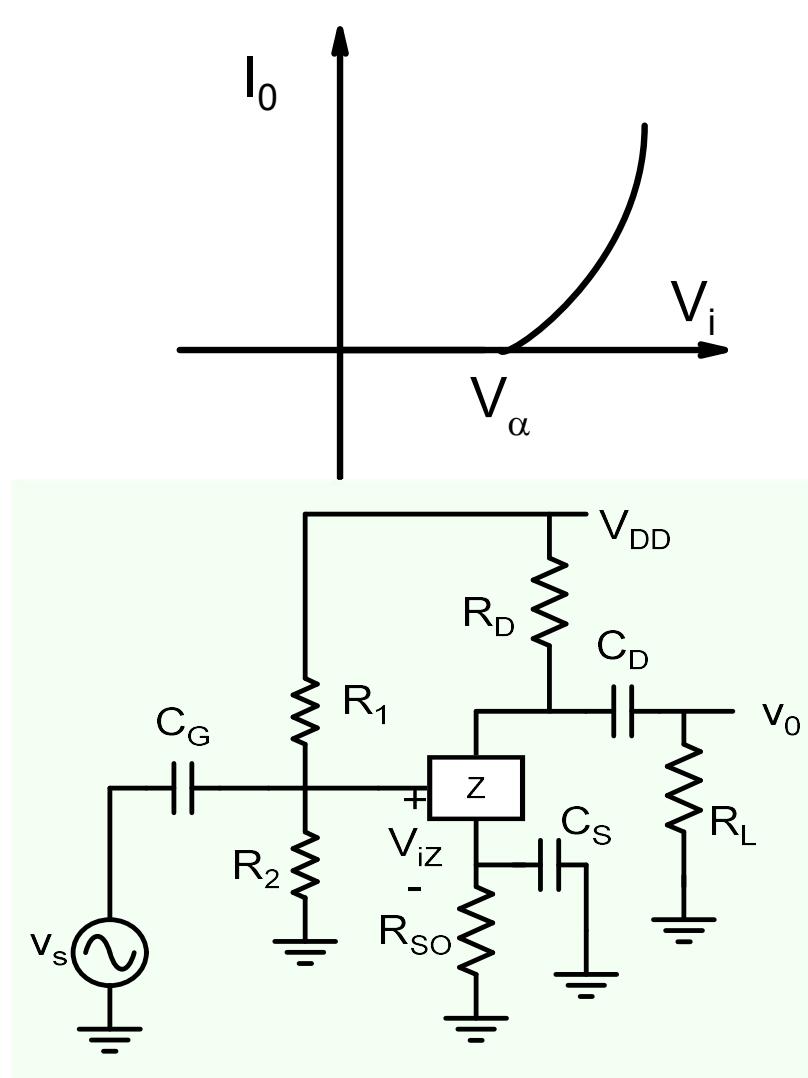
Building Amplifiers with non-linear devices



Amplifier will work properly (with small distortion only if we restrict the amplitude of input signal to small values.



How small depends on the nature of non-linearity. The stronger the non-linearity the lesser the signal amplitude.

Bipolar Junction Transistor (BJT)

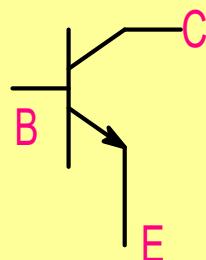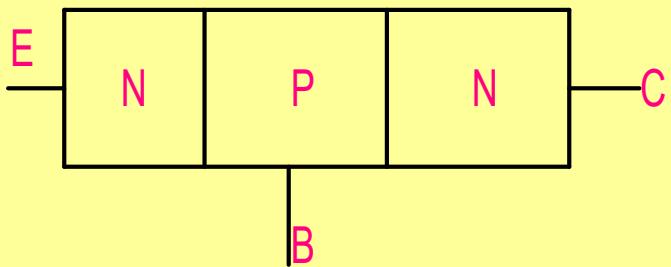

E: Emitter
B: Base
C: Collector



NPN

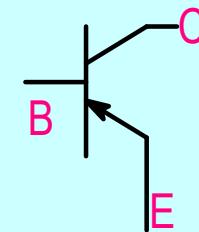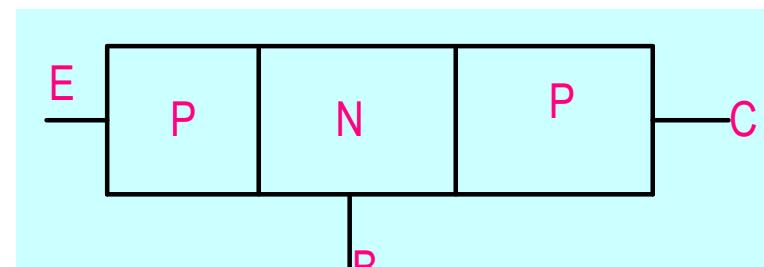

E: Emitter
B: Base
C: Collector

PNP

More Realistic View

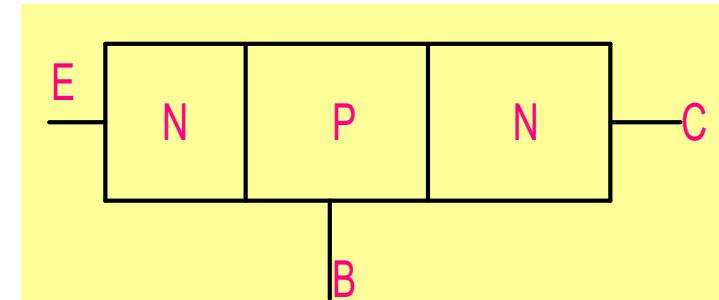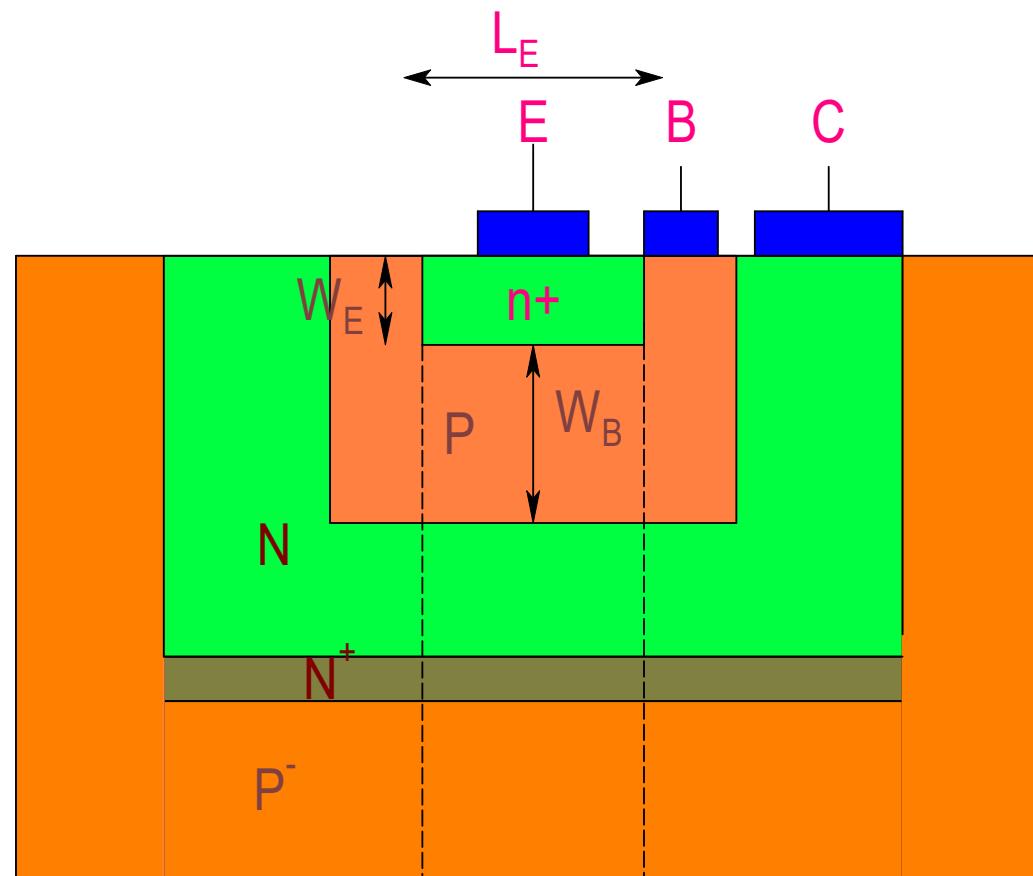

$$N_{DE} \sim 10^{19} \text{ cm}^{-3}$$

$$N_{AB} \sim 10^{17} \text{ cm}^{-3}$$


$$N_{DC} \sim 10^{16} \text{ cm}^{-3}$$

$$W_B \sim 2000 \text{ } \mu\text{m}$$


$$W_E \sim 1000 \text{ } \mu\text{m}$$

$$L_E \sim 1 \mu\text{m}$$

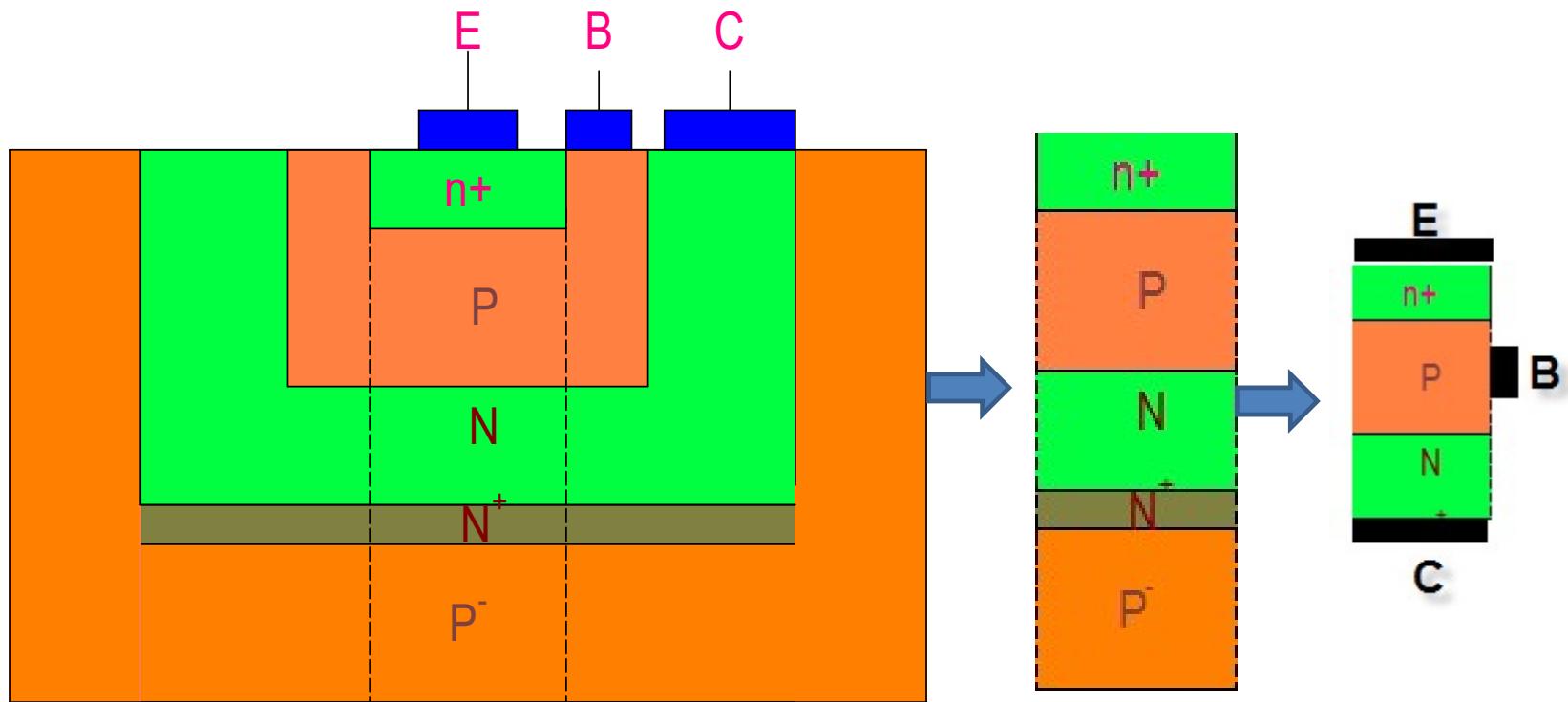
BJT is not symmetric: emitter and collector cannot be simply interchanged



Top View

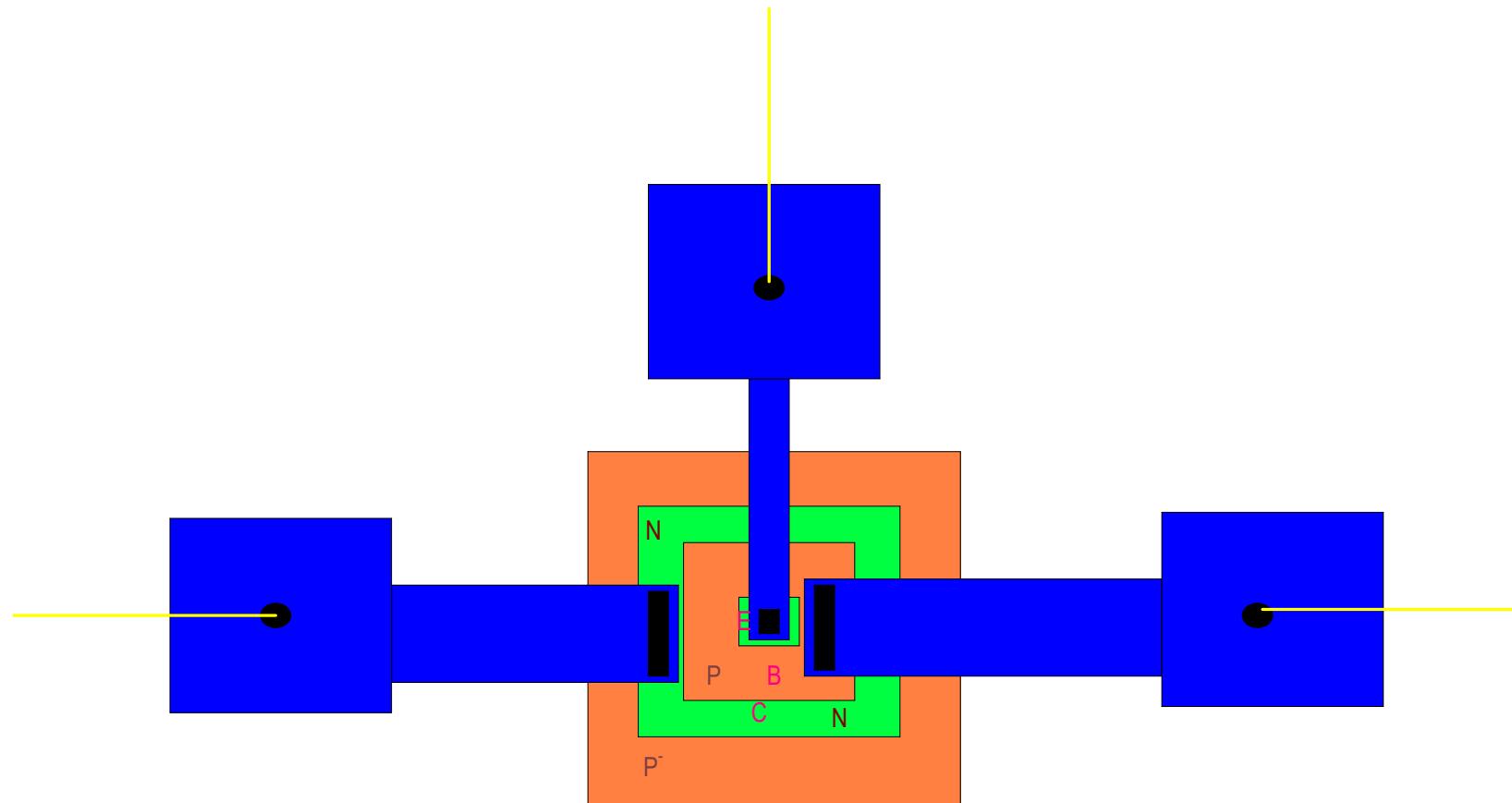


Background

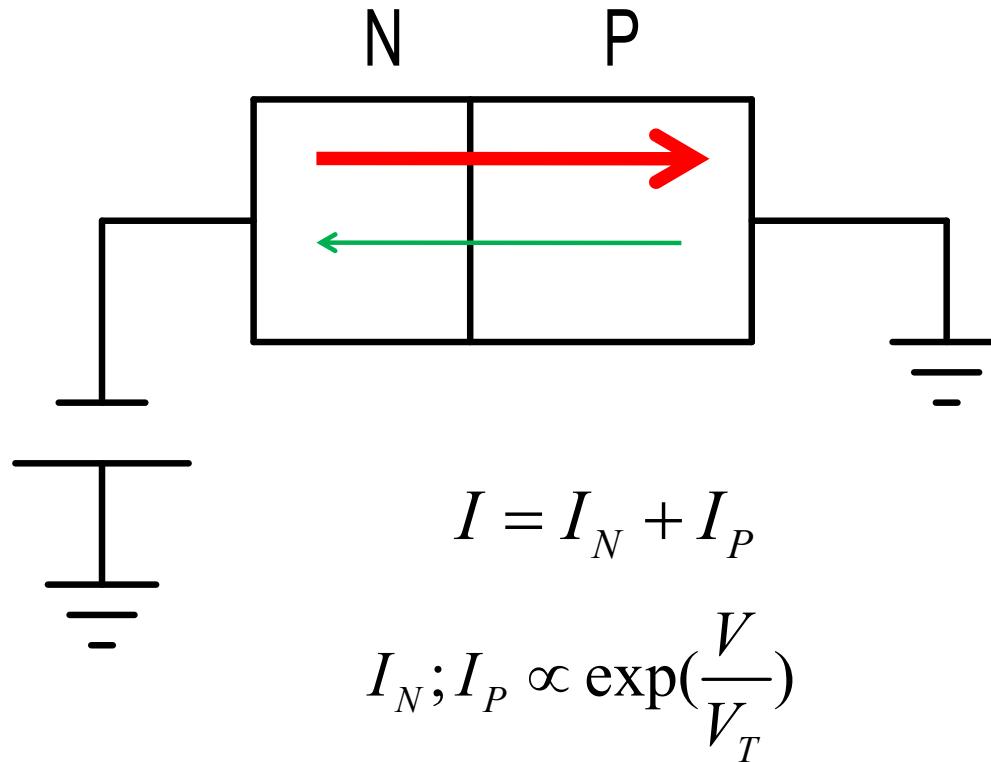

If doping in N region is much larger than doping in p region
then $I_N \gg I_P$

Basic Transistor Operation

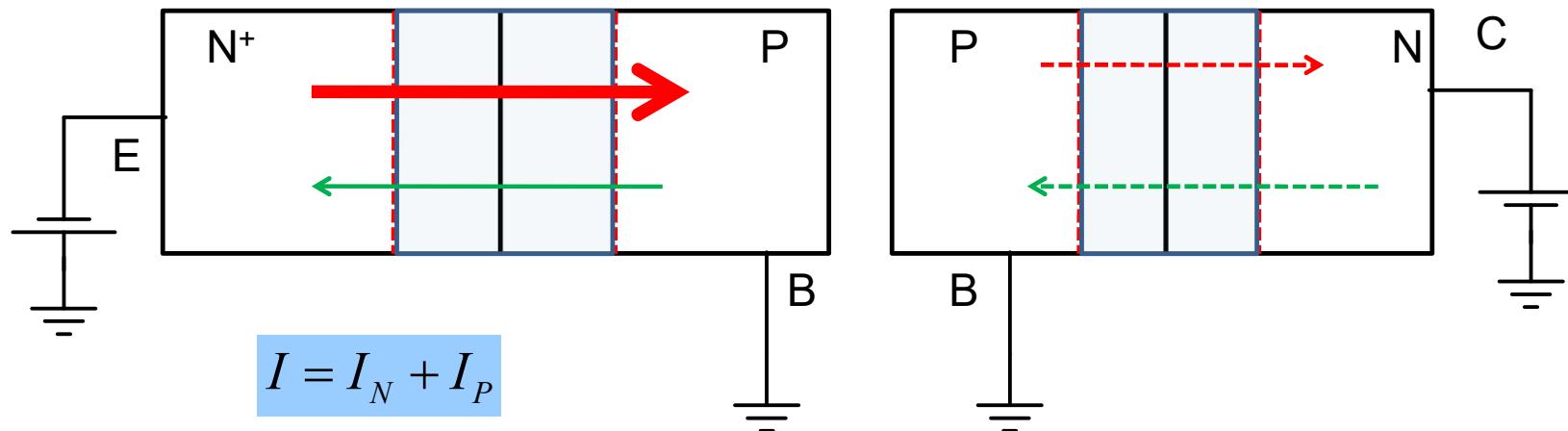



We will assume that doping in emitter is much more than base so that electron current is much larger than hole current


$$I_N \gg I_P$$

In the reverse biased junction current is small because there are very few electrons in P and holes in N-region

Basic Transistor Operation

$$I = I_N + I_P$$

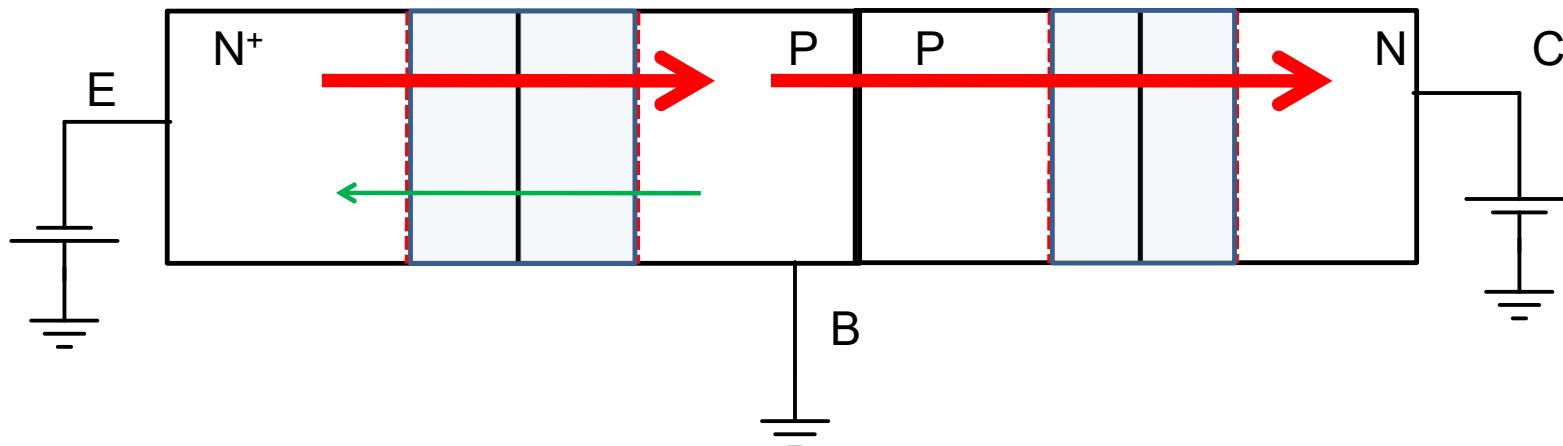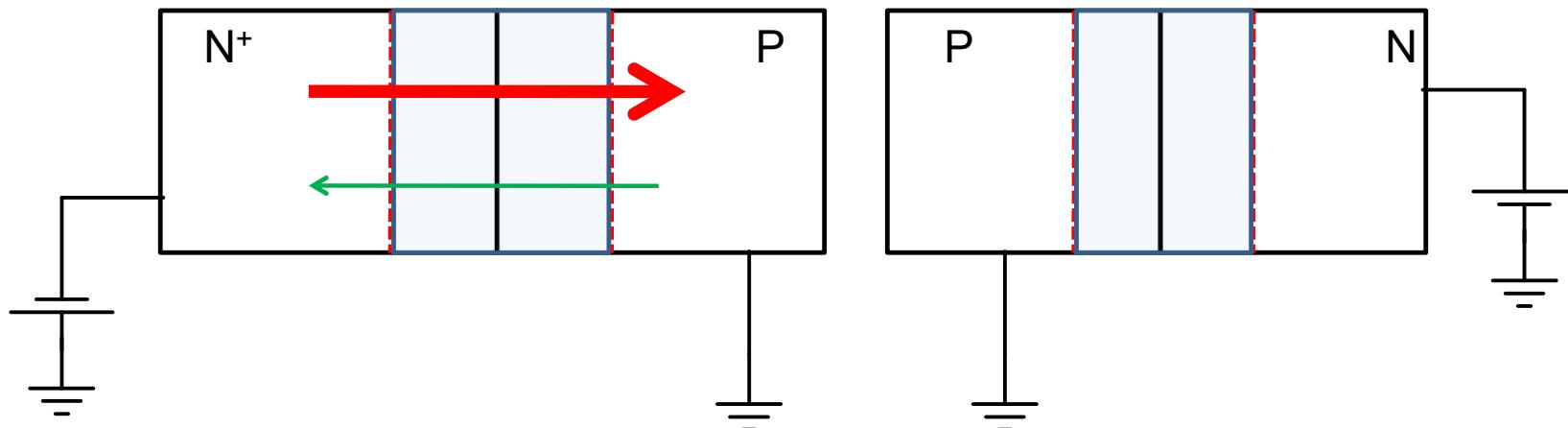


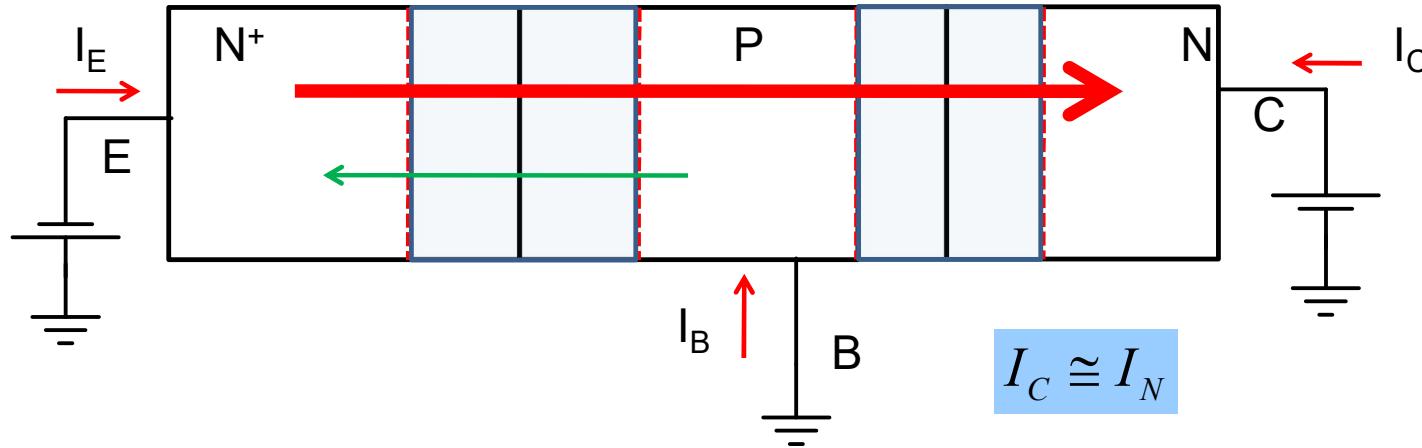

$$I_E = I_N + I_P$$

$$I_B \cong I_P$$

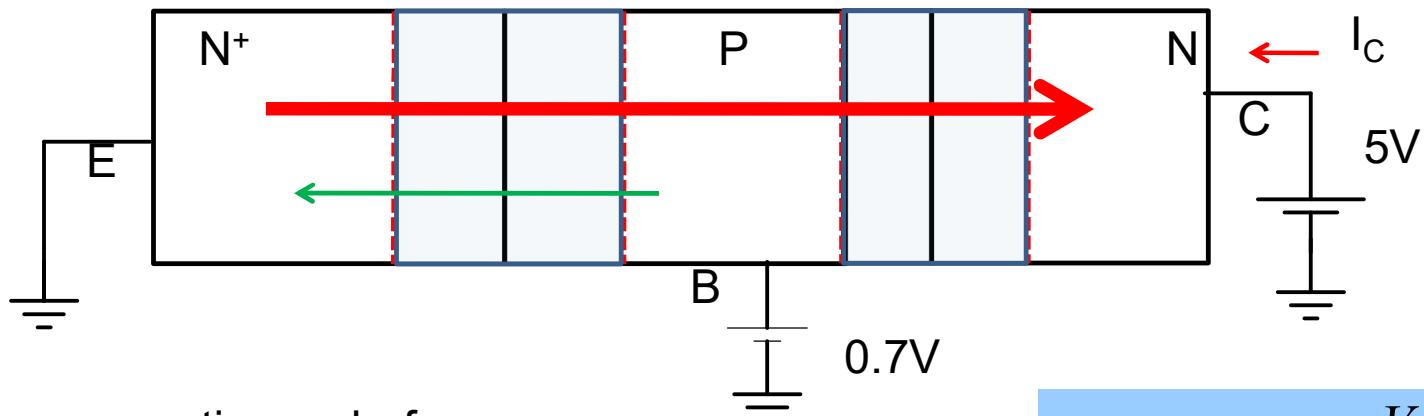Current Gain : $\beta = \frac{I_C}{I_B} = \frac{I_N}{I_P} \gg 1$





Same operation as before


$$I_C = I_N \propto \exp\left(\frac{V_{BE}}{V_T}\right)$$

Transistor action

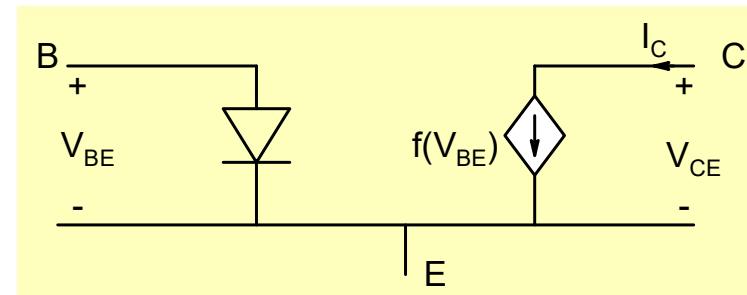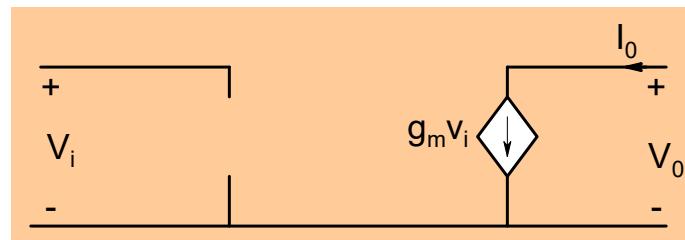Current is affected by base-emitter voltage and not by collector-base voltage





Alternative representation

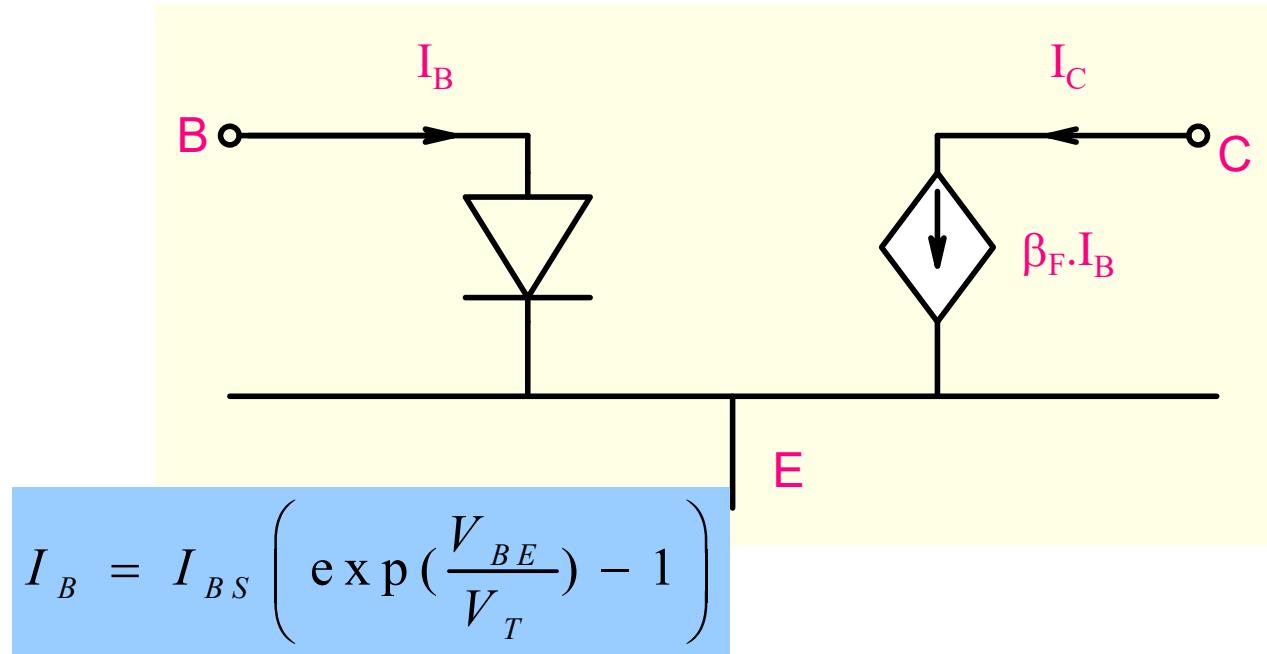


$$\beta = \frac{I_C}{I_B}$$

$$I_C = I_S \left(\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right)$$
$$I_B = \frac{I_C}{\beta_F}$$

Transistor Characteristics

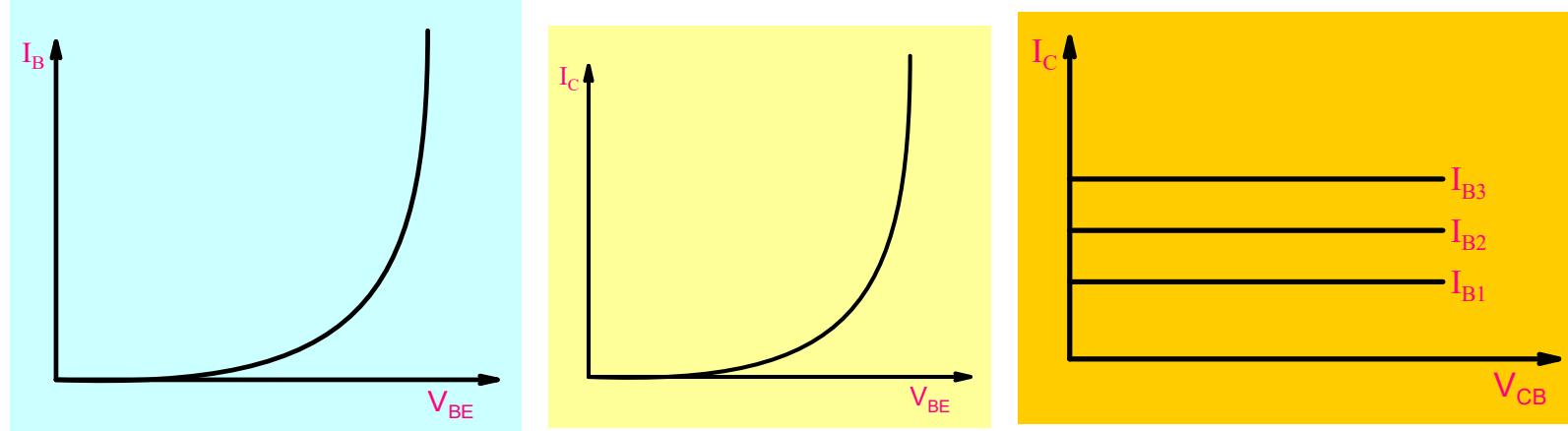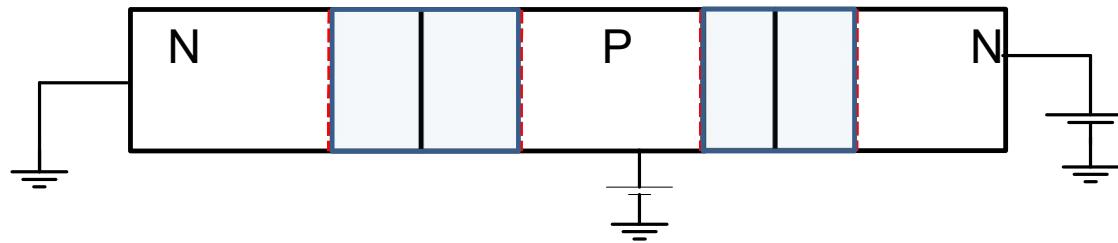


Output Characteristics of the transistor

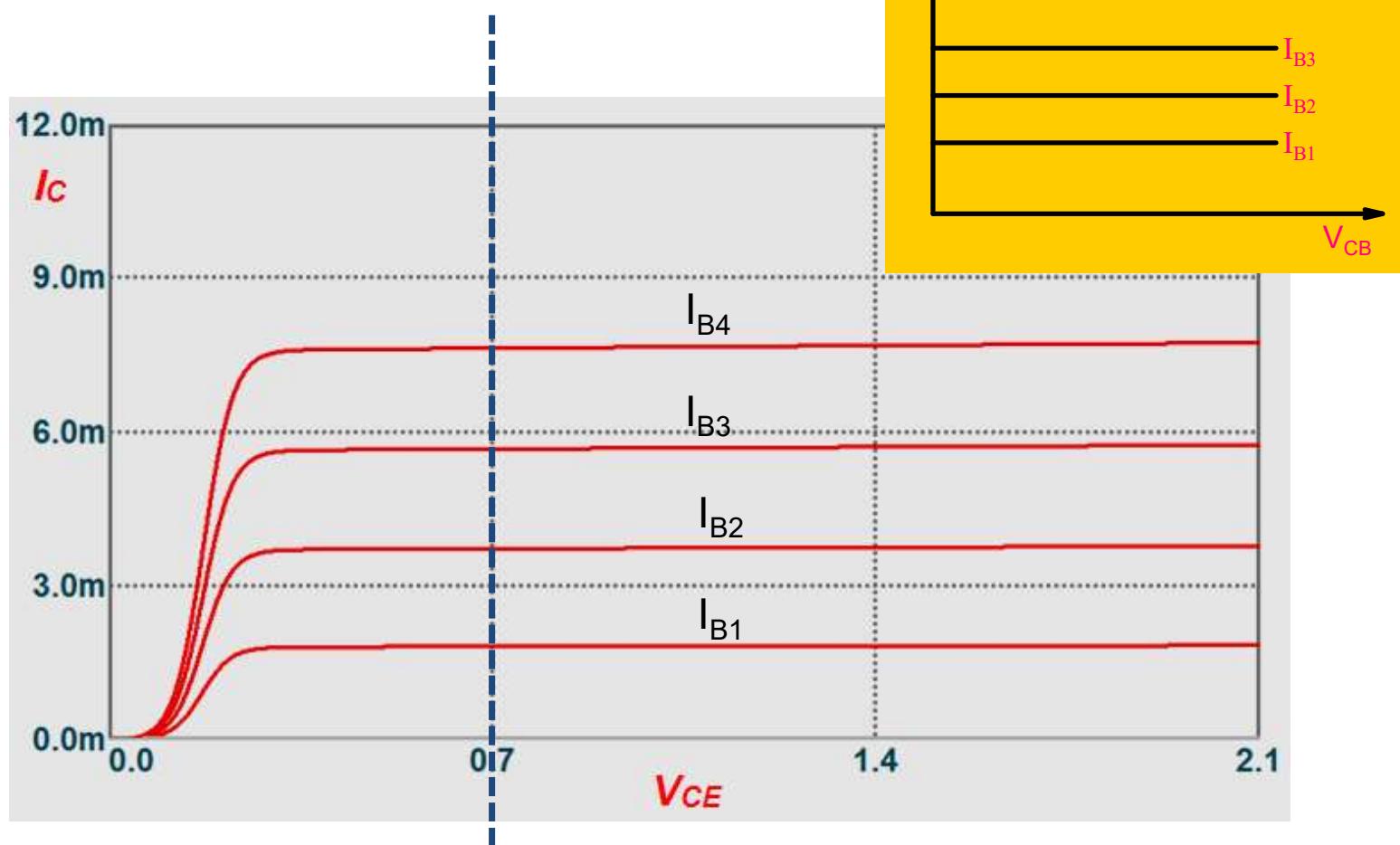


$$\begin{aligned}V_{CE} &= V_{CB} + V_{BE} \\&= V_{BE} - V_{BC}\end{aligned}$$

$$V_{CE} = 0.7 - V_{BC}$$

Transistors

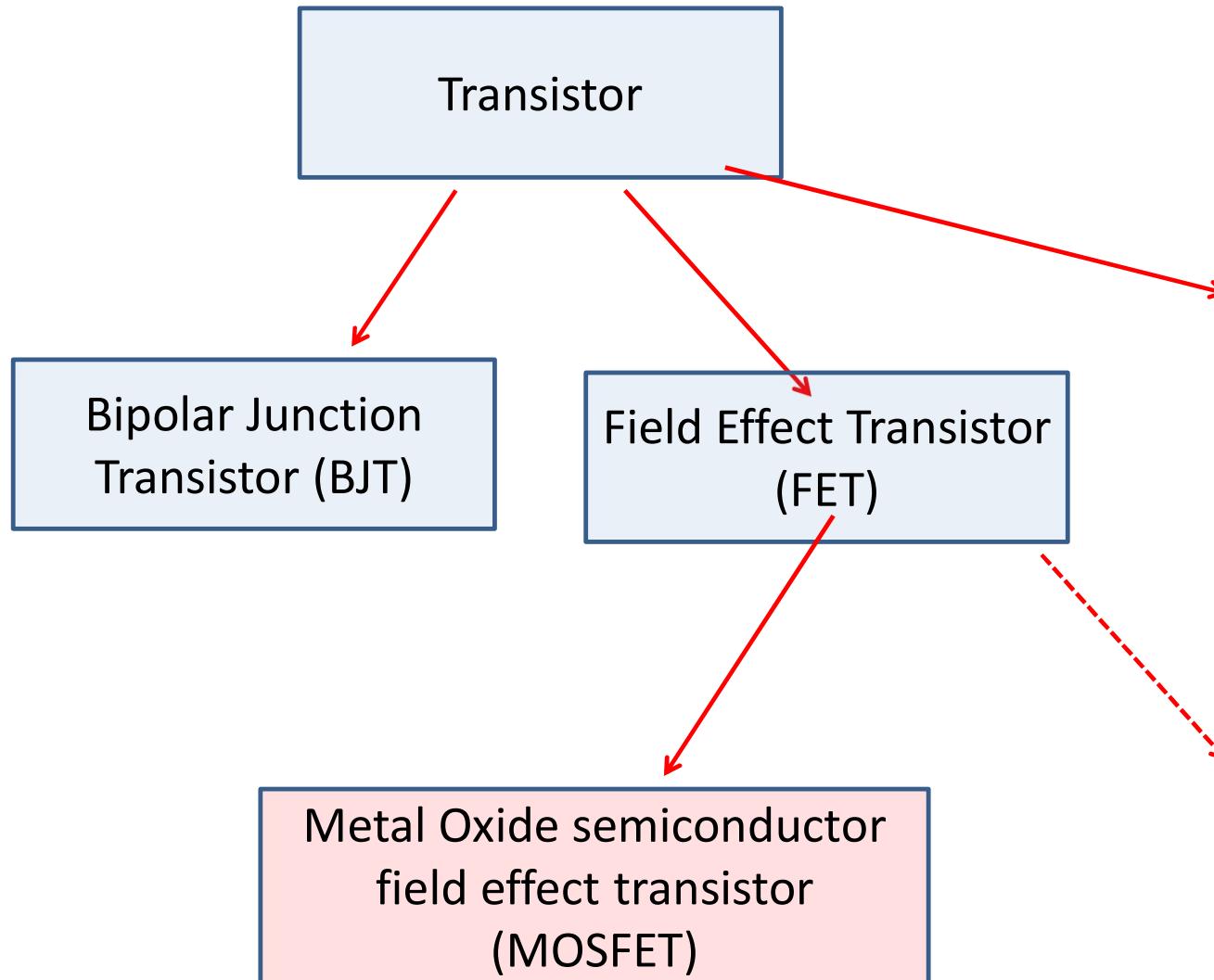

Transistor

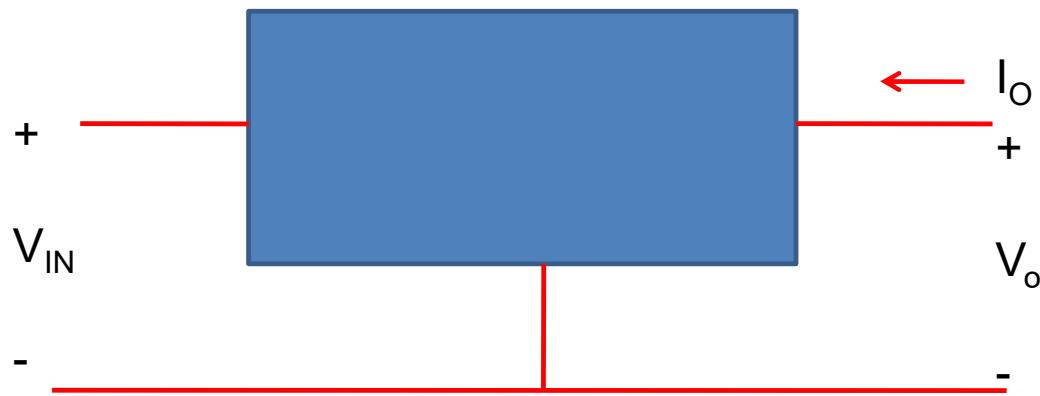


Current I_o is much more sensitive to V_{IN} than V_o

$$\frac{\partial I_o}{\partial V_{in}} \gg \frac{\partial I_o}{\partial V_o}$$

Field Effect Principle
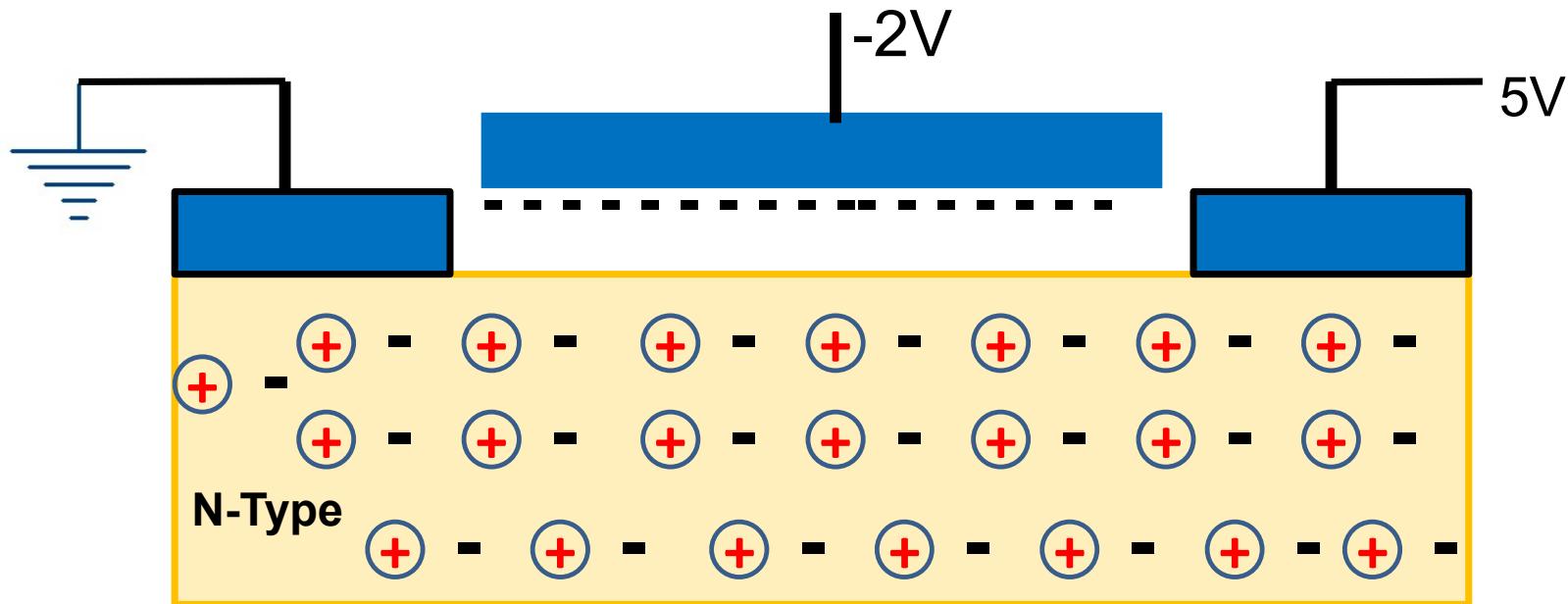
$$\frac{\partial I_o}{\partial V_{in}} \gg \frac{\partial I_o}{\partial V_o}$$



Modulation of conductivity using electric field

Transconductance

Jan. 28, 1930.

J. E. LILIENFELD


1,745,175


METHOD AND APPARATUS FOR CONTROLLING ELECTRIC CURRENTS

Filed Oct. 8, 1926


The invention relates to a method of and apparatus for controlling the flow of an electric current between two terminals of an electrically conducting solid by establishing a
5 third potential between said terminals; and is particularly adaptable to the amplification of oscillating currents such as prevail, for example, in radio communication. Heretofore, thermionic tubes or valves have been
10 generally employed for this purpose; and the present invention has for its object to dispense entirely with devices relying upon the transmission of electrons thru an evacuated space and especially to devices of this char-
15 acter wherein the electrons are given off from an incandescent filament. The invention has for a further object a simple, substantial and inexpensive relay or amplifier not involving the use of excessive voltages, and

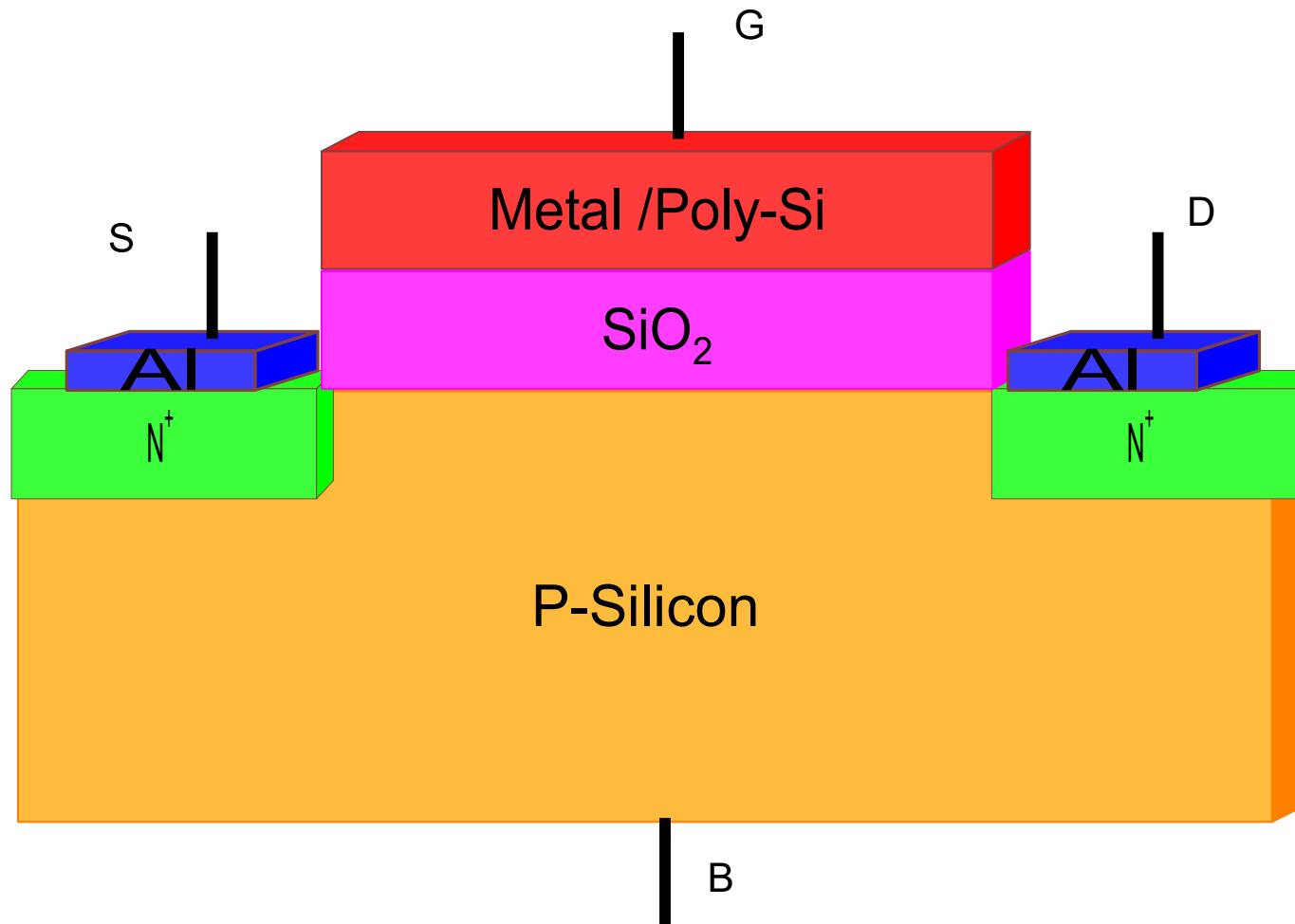NMOS Enhancement mode transistor: Inversion Mode Transistor




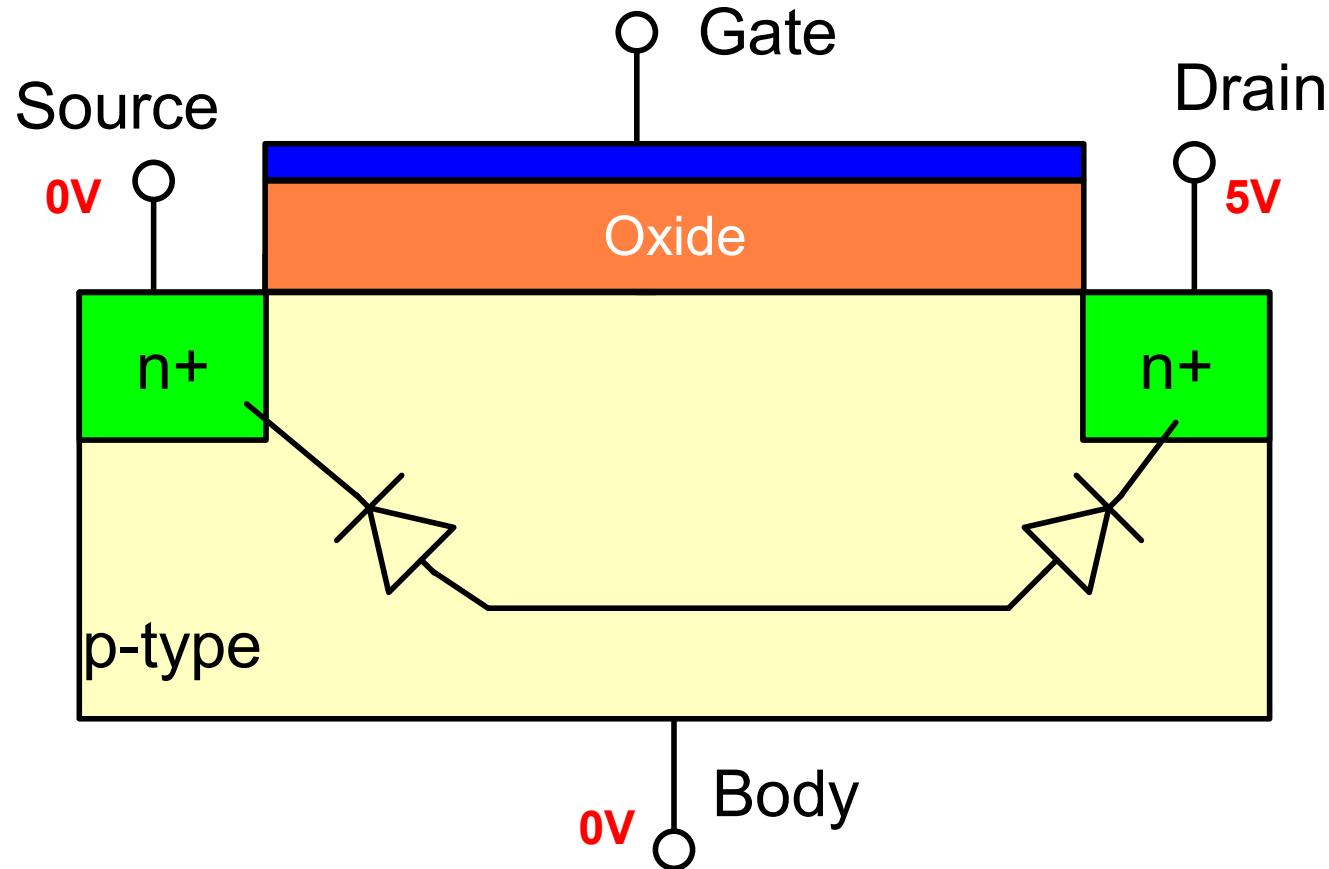

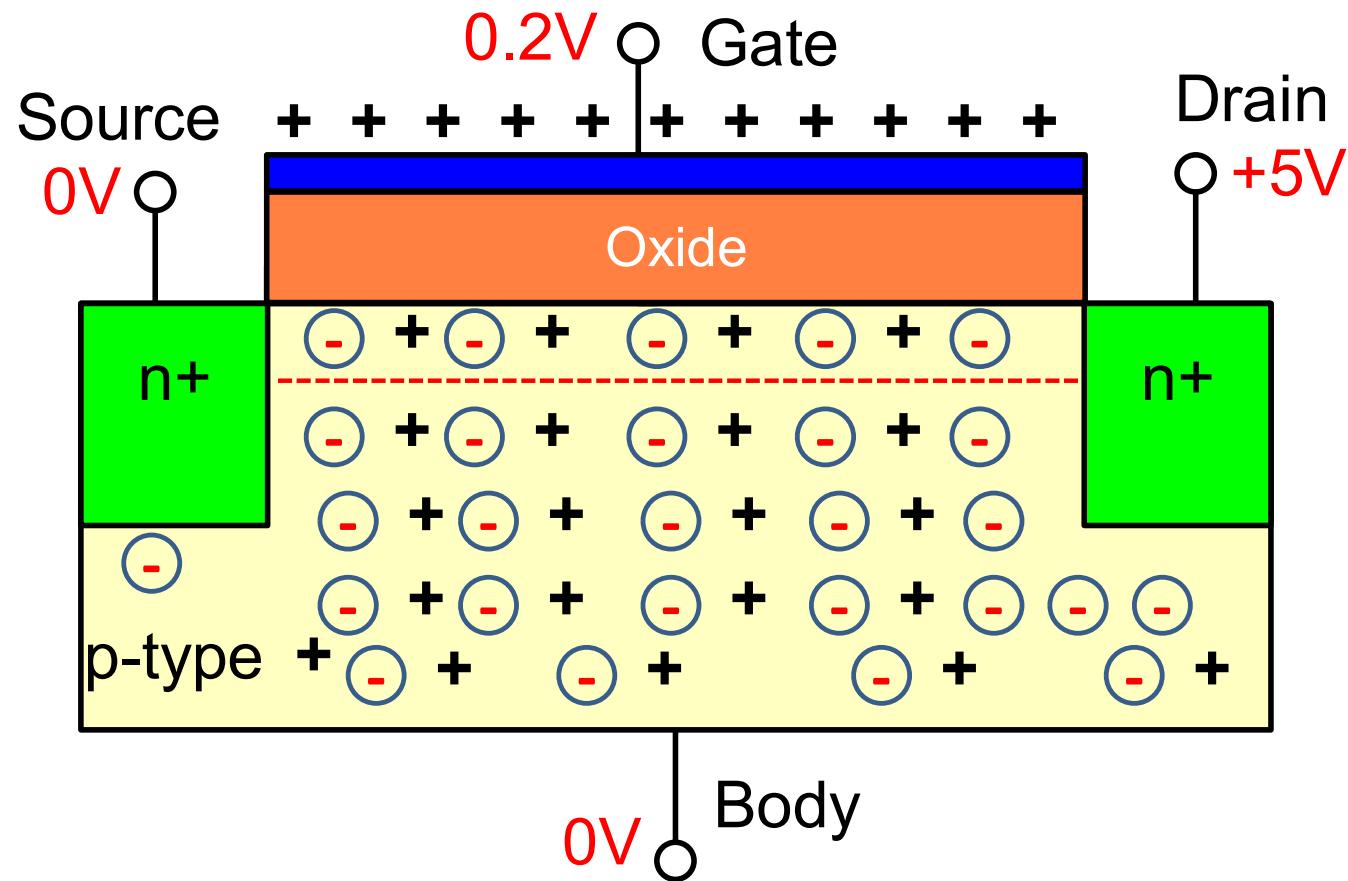No channel exists when gate voltage is zero and current is zero as well.




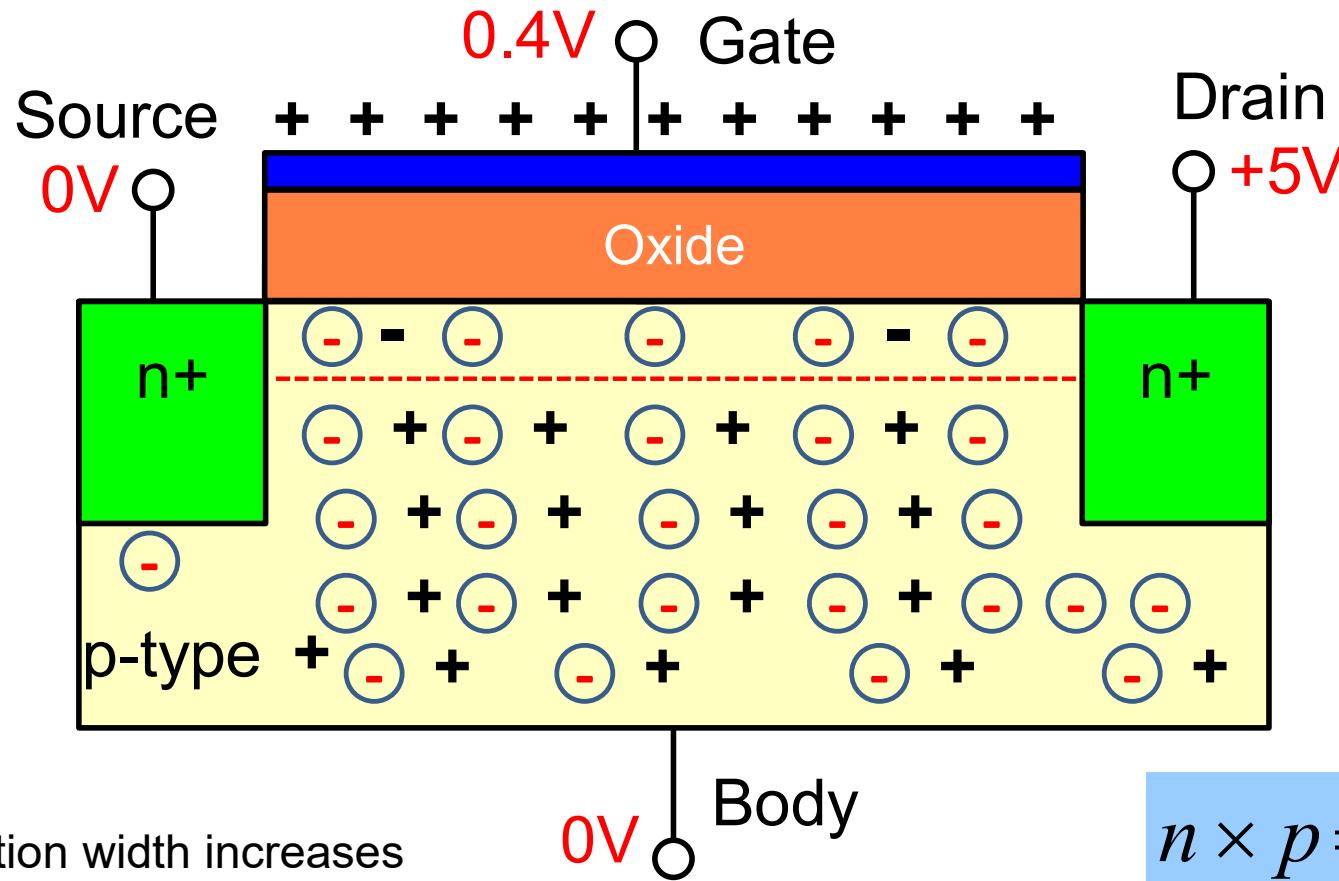Depletion Region is formed near the Si/SiO₂ interface




But something interesting happens: electron density at the surface also increases

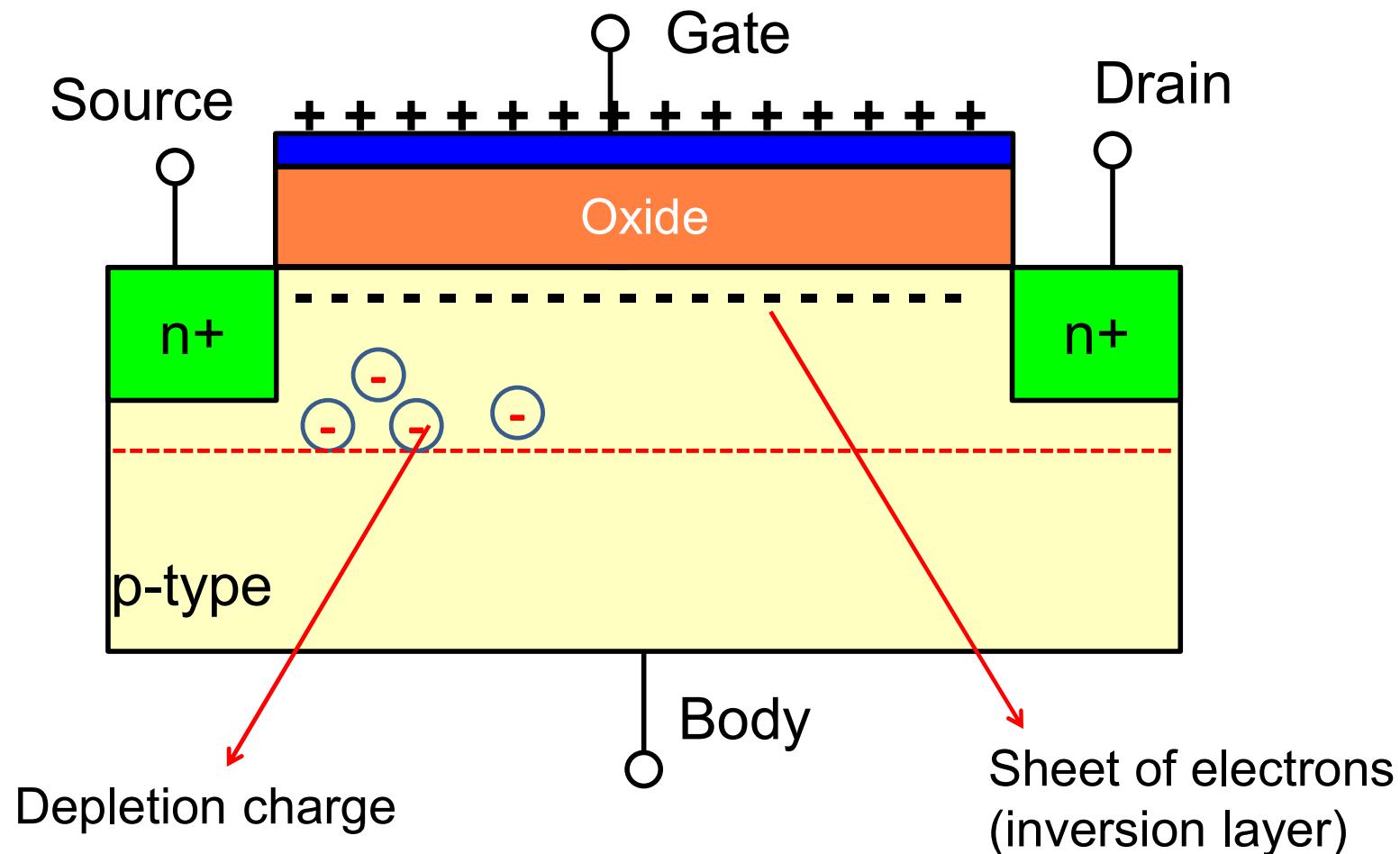At a sufficiently large voltage ($>V_{THN}$) a channel of electrons forms at the Si/SiO₂ interface.



Conductivity modulation at the surface?


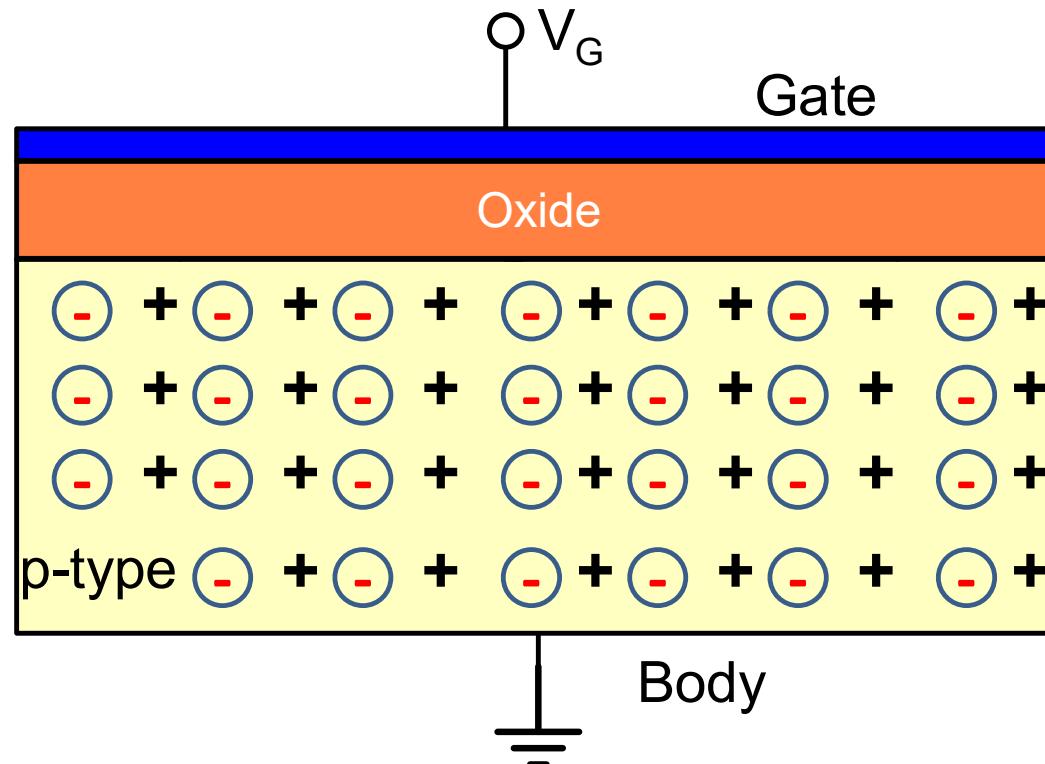


$$p = N_A = 10^{16} \text{ cm}^{-3}$$

$$n = \frac{n_i^2}{p} \cong 10^4 \text{ cm}^{-3}$$


Field Effect...
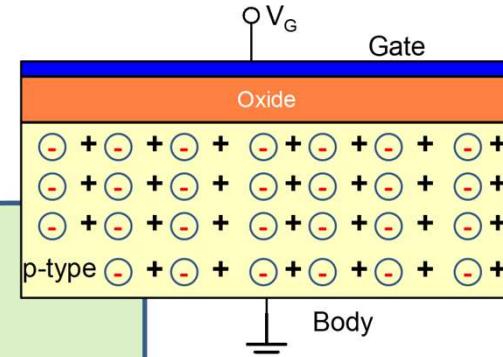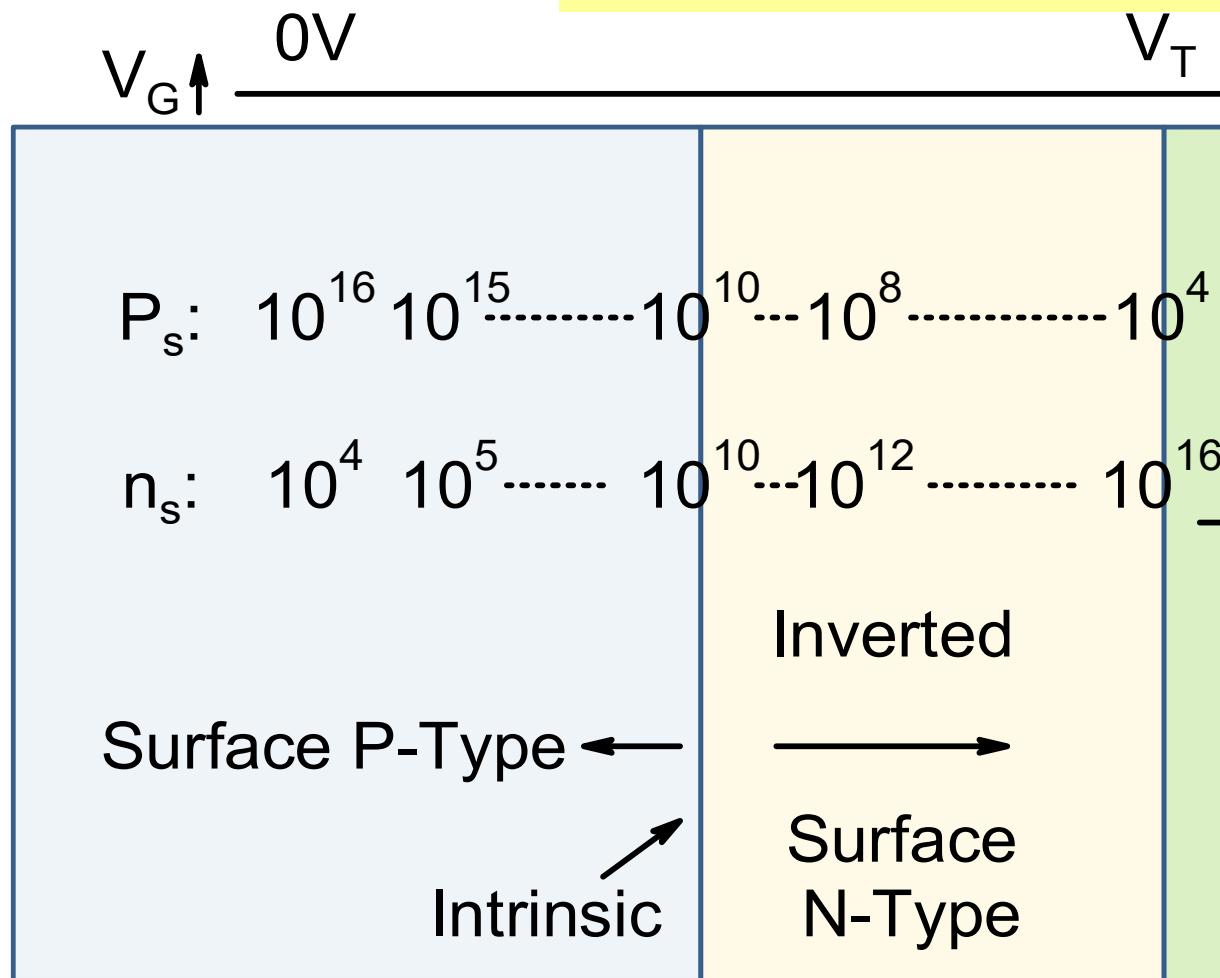
$$n_s \times p_s = n_1^2 \simeq 10^{20} \text{ cm}^{-3}$$




Surface carrier density can be changed from P-type to N-type

Surface Carrier Density

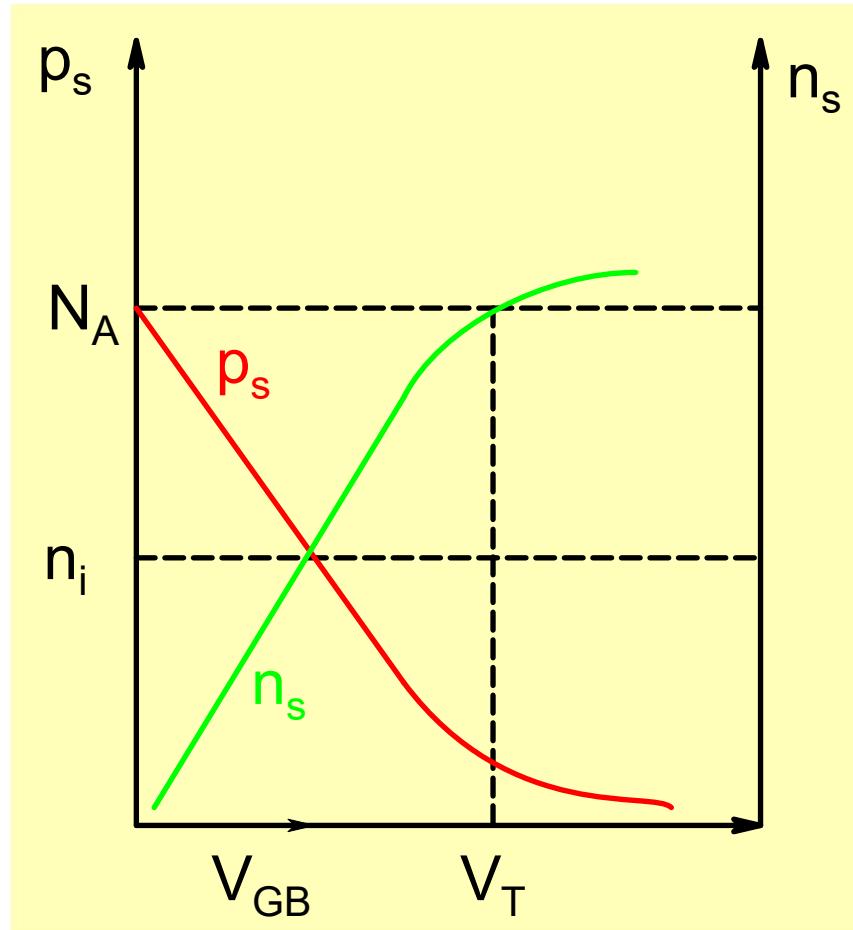



Strong Inversion

$$V_G > V_{THN}$$

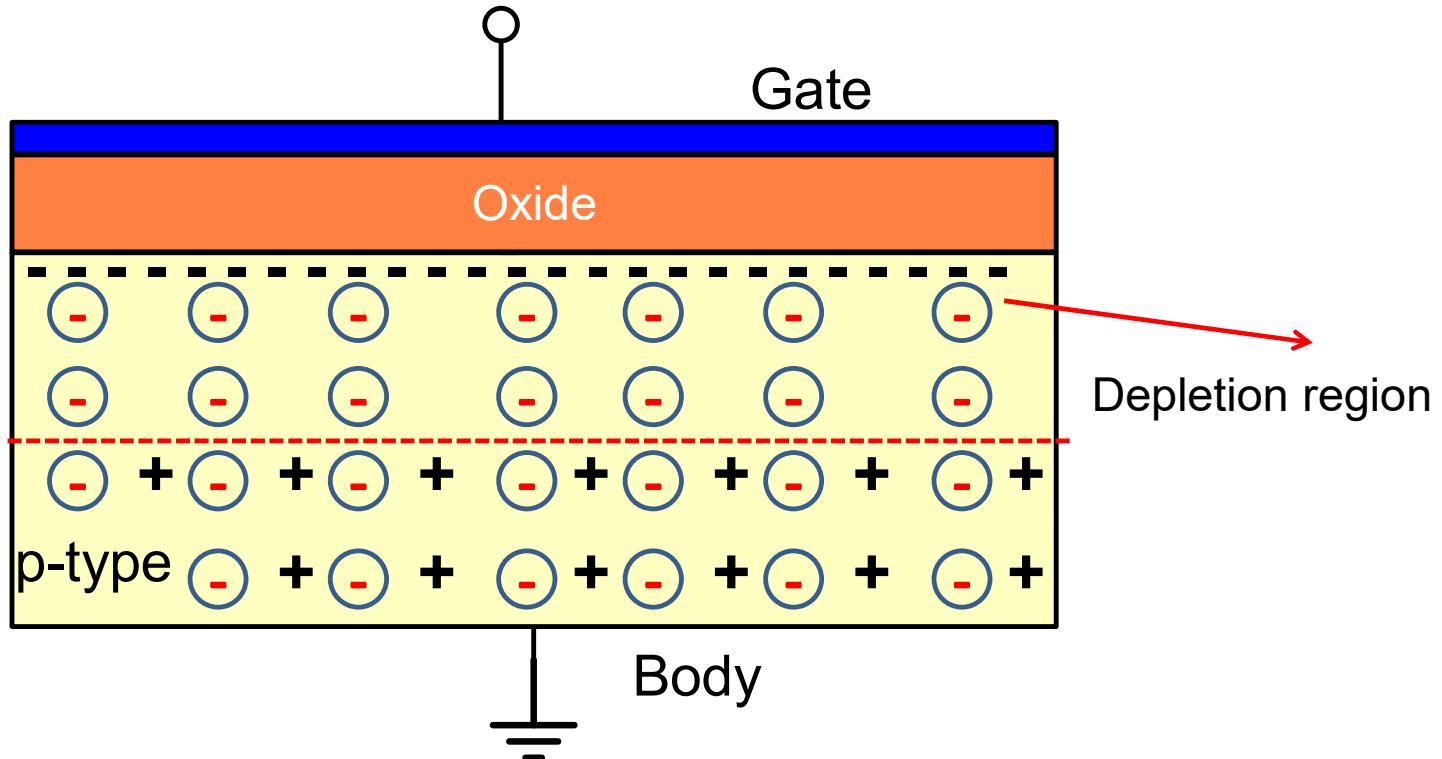


Electrons are accumulated at the surface $n_S \gg N_A$

Simplified Symbols and structure

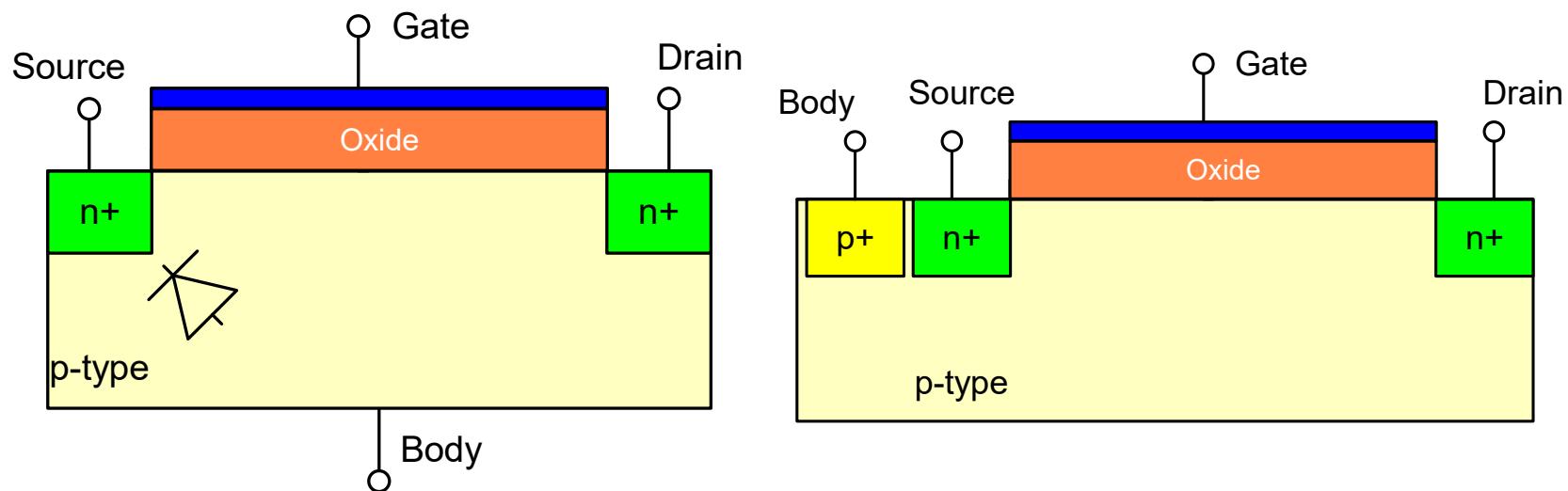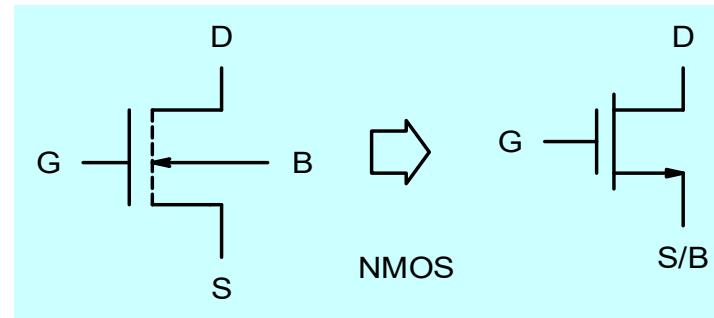


Operation of the MOSFET

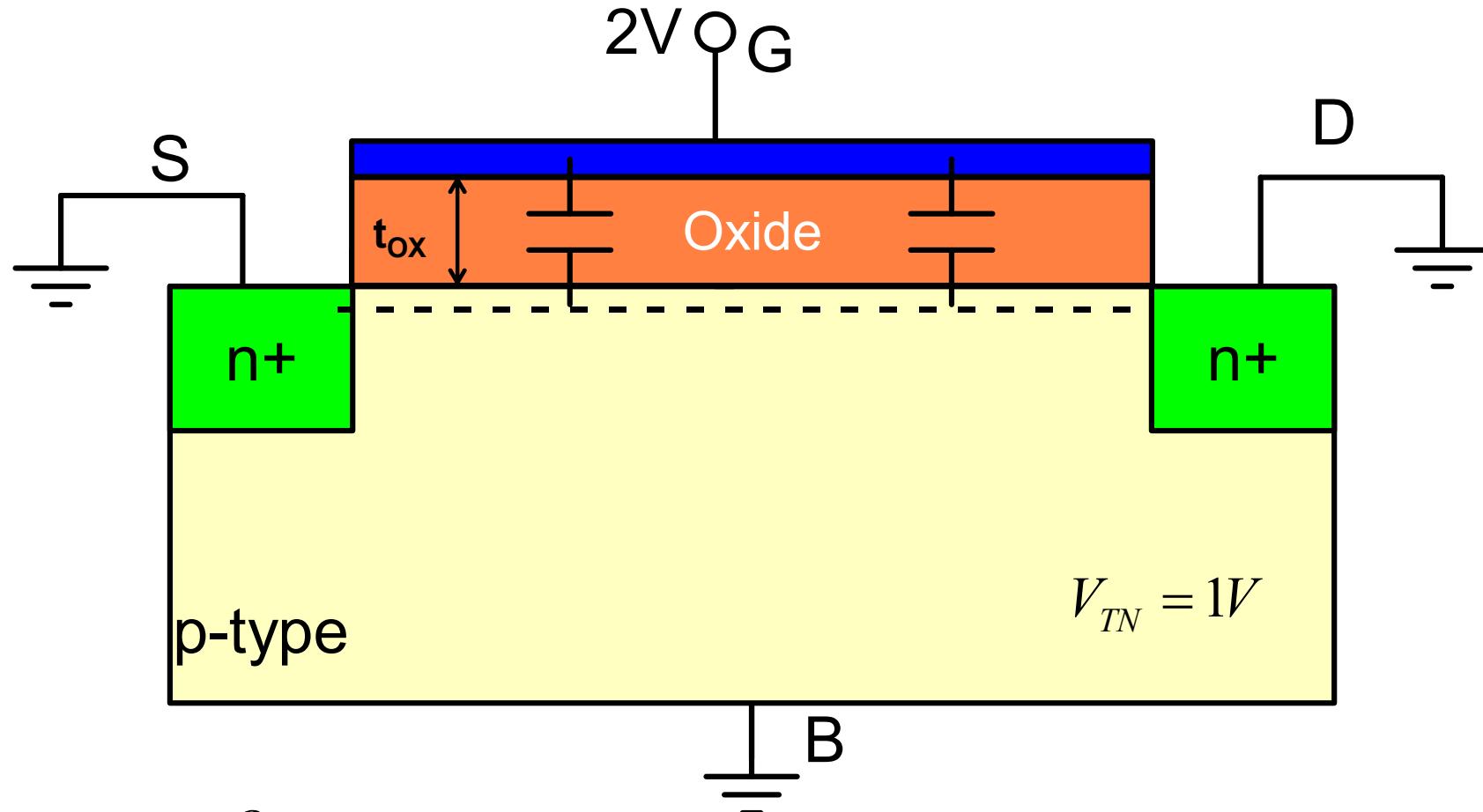




$$C'_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

Inversion charge/area : $Q_{inv} = -C_{ox}(V_{GS} - V_{THN})$

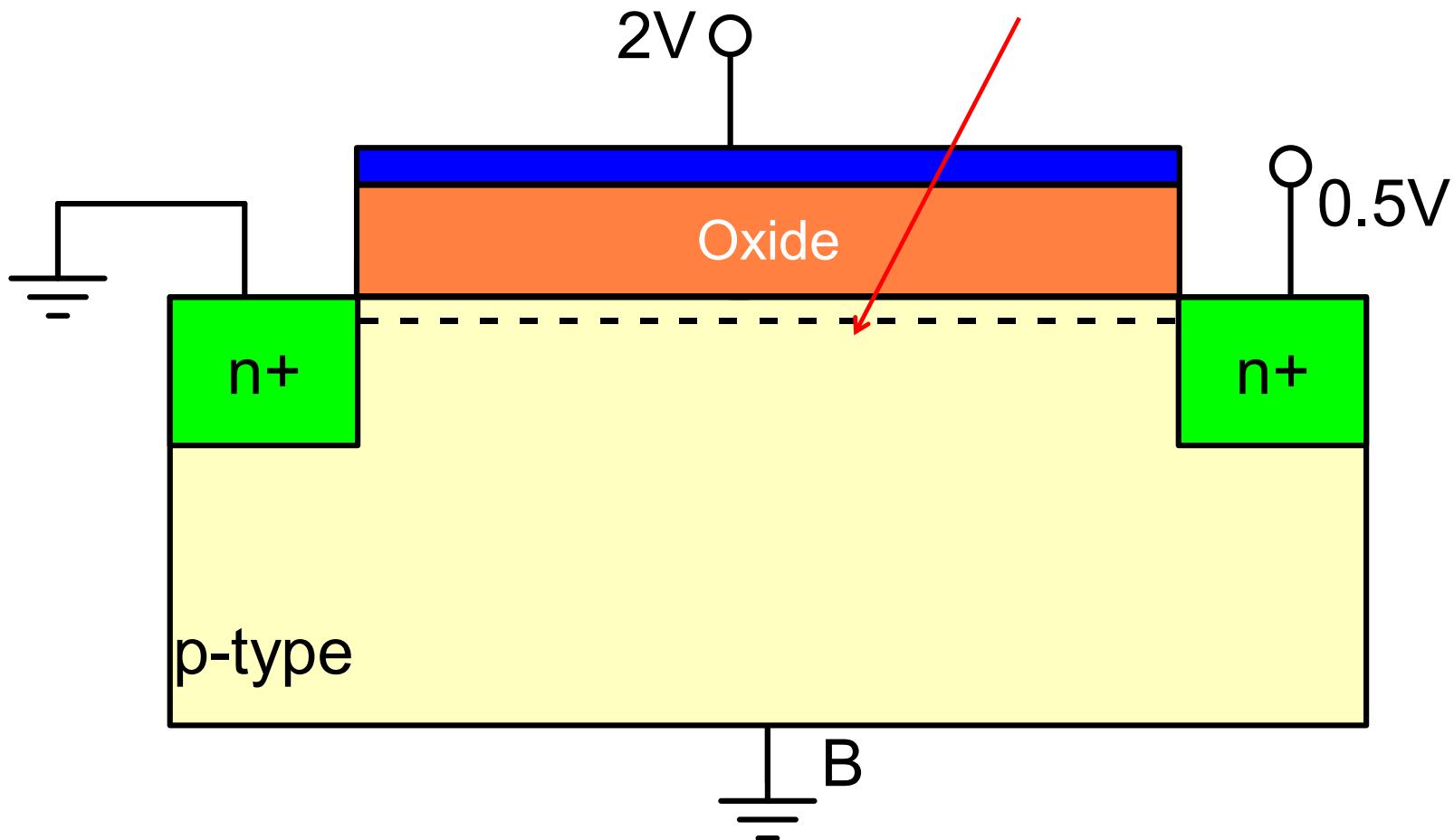
$$Q_{inv}(x) = -C_{ox}(V_{GS} - V_{THN} - V(x))$$



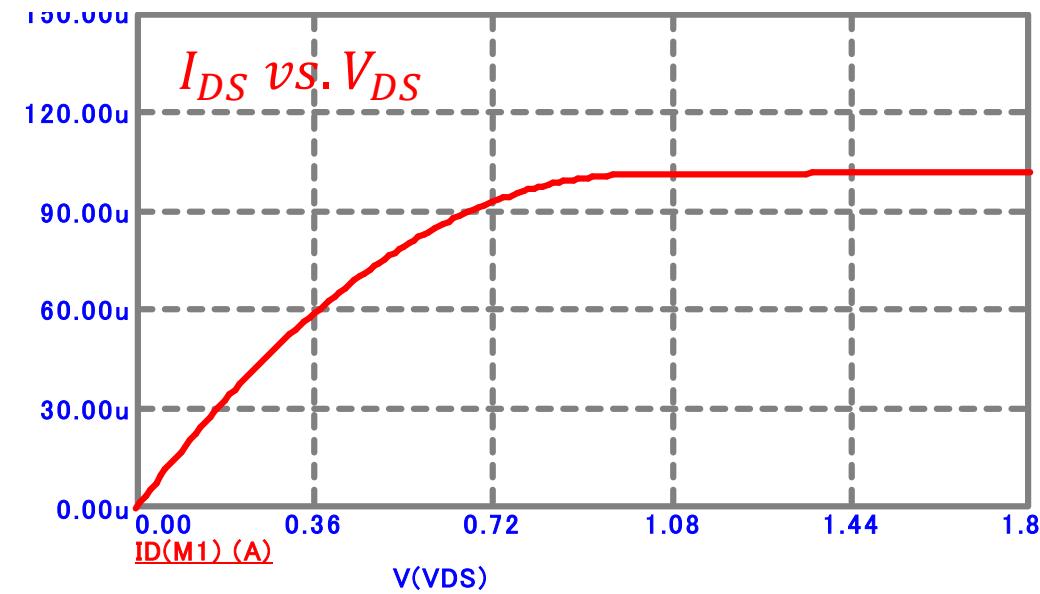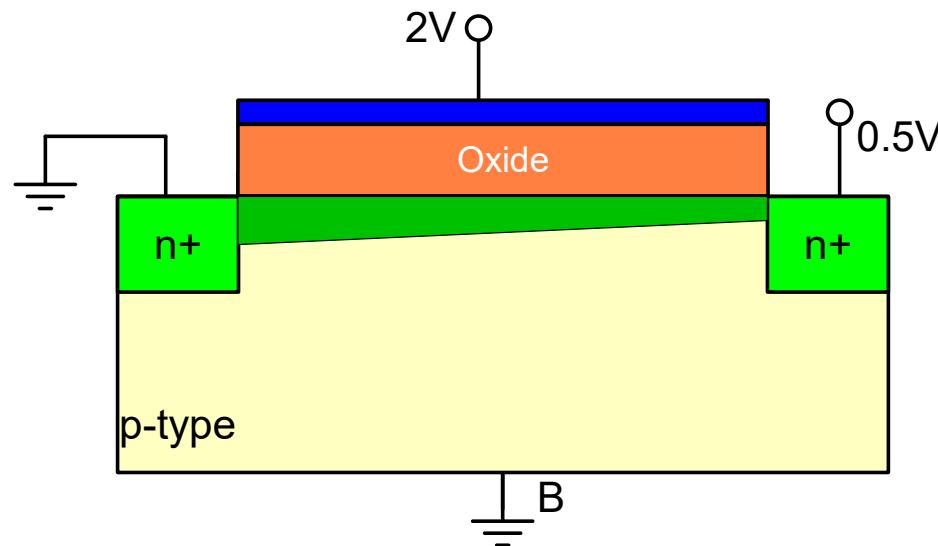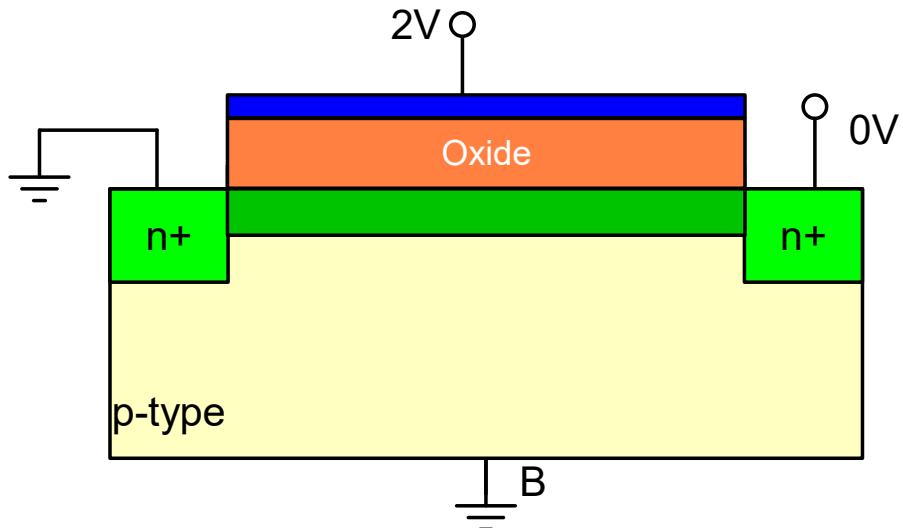When a positive drain voltage is applied, current flows from drain to source and inversion charge density decreases from source to drain end.




$$I_{DS} = \frac{V_{DS}}{R_{ch}} > 0$$





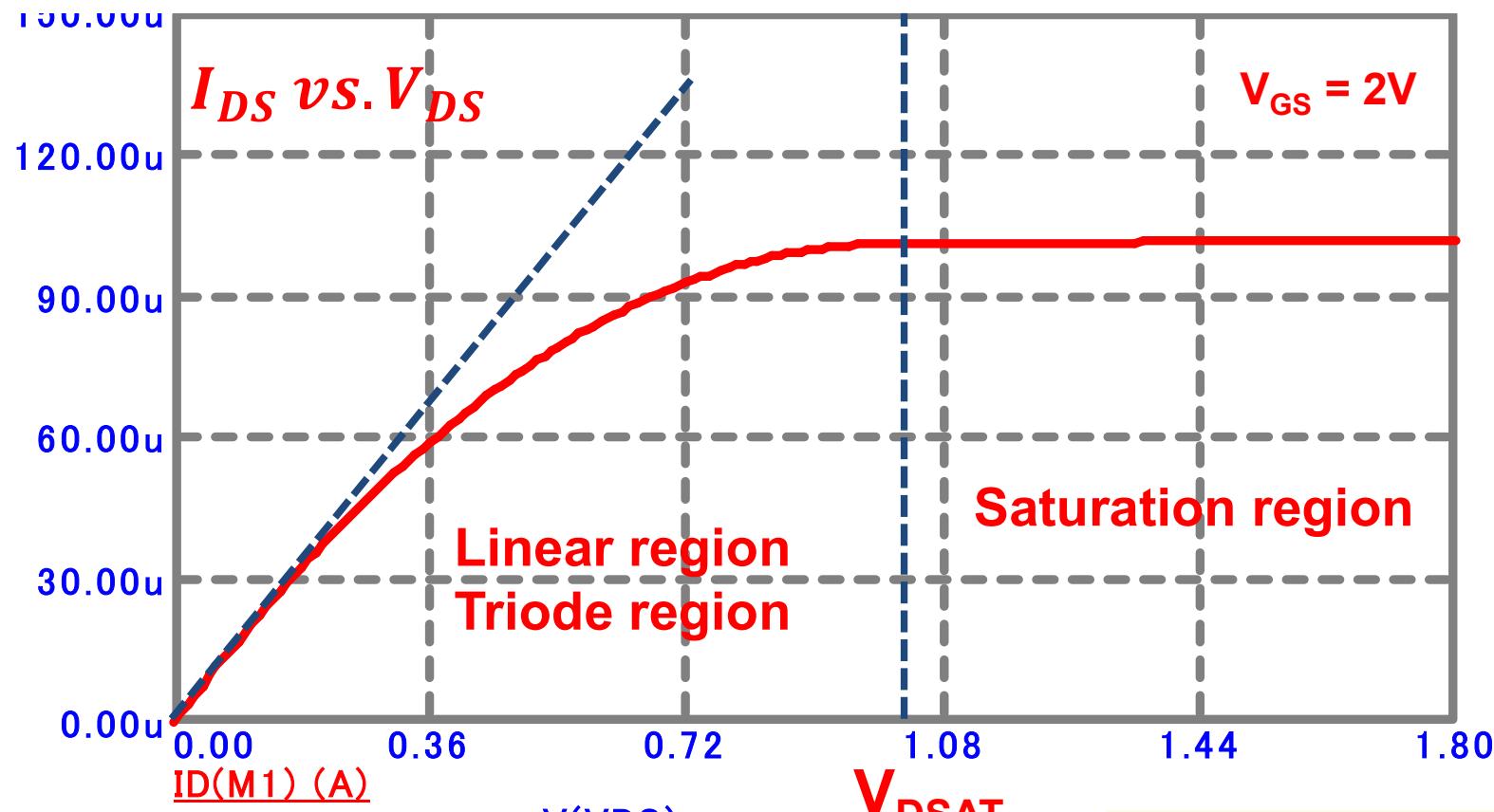


$$V_{DSAT} = V_{GS} - V_{THN}$$
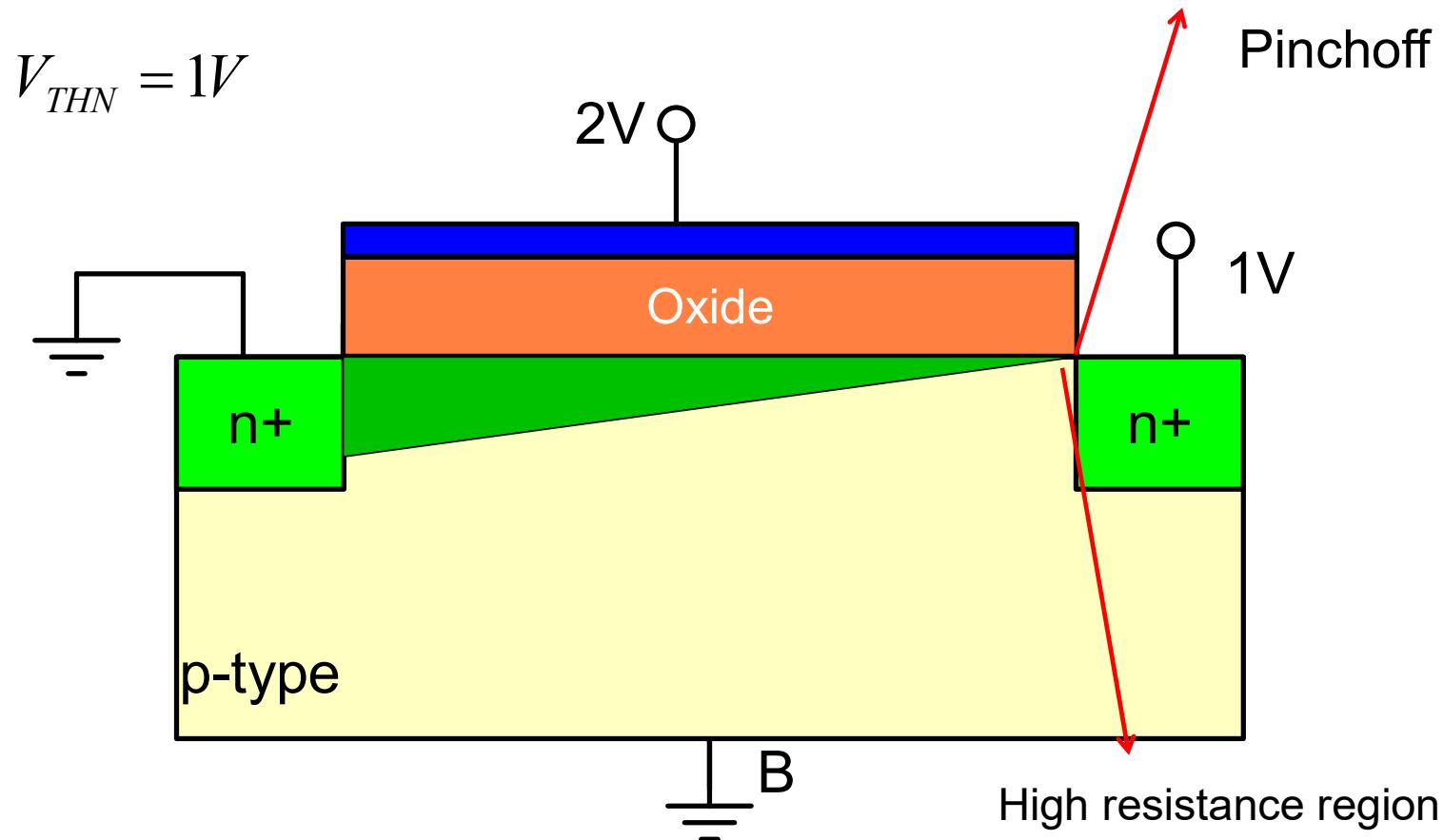
$$Q_{inv}(x) = -C_{ox}(V_{GS} - V_{THN} - V(x)) \cong -C_{ox}(2 - 1 - 1) = 0$$






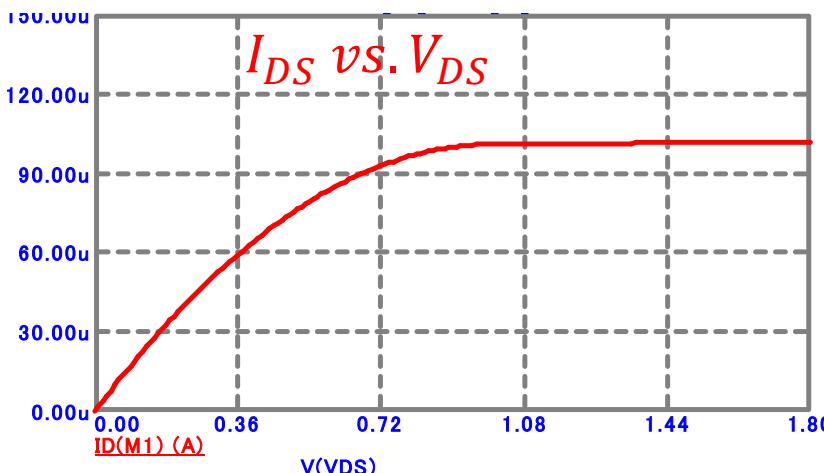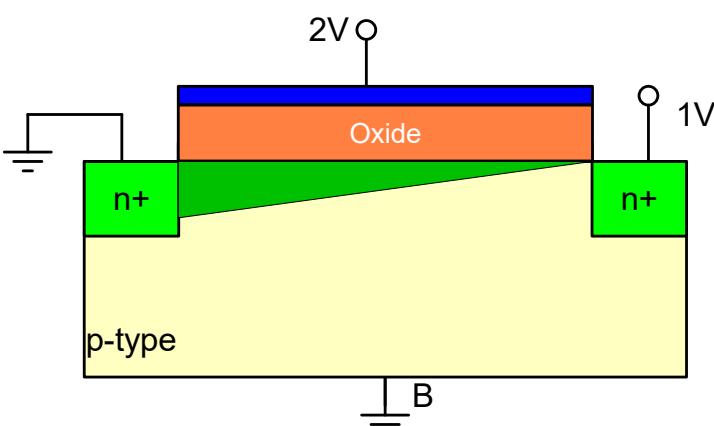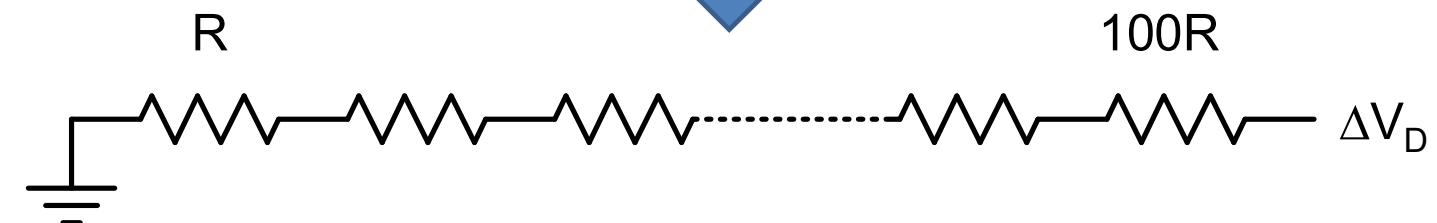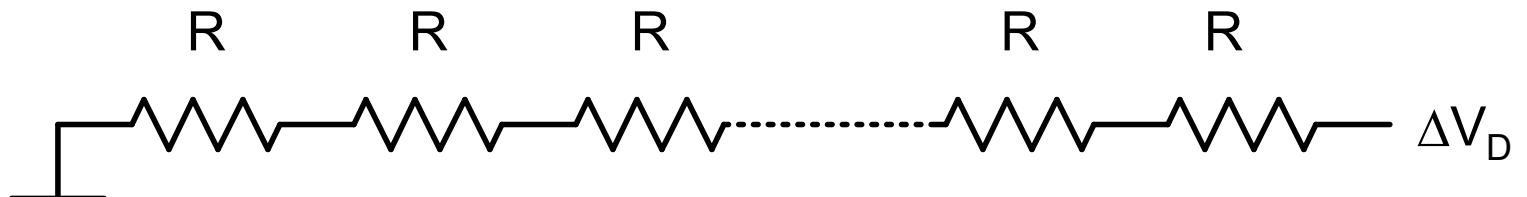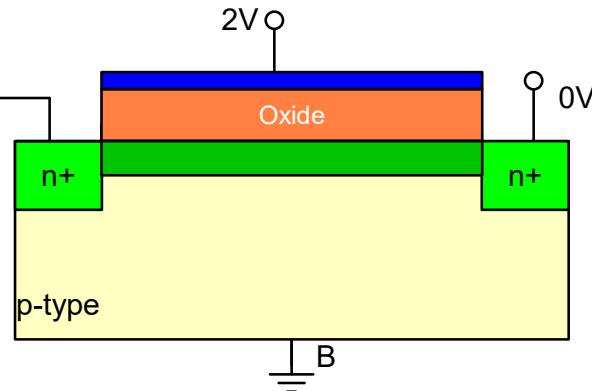Any further increase in drain bias is absorbed in a small region next to the drain and rest of channel is not much affected and thus current becomes constant.








$$\frac{\partial I_{DS}}{\partial V_{GS}} \gg \frac{\partial I_{DS}}{\partial V_{DS}}$$

BJT

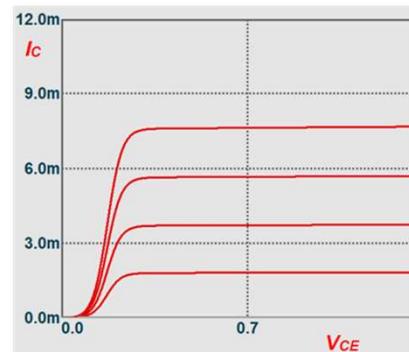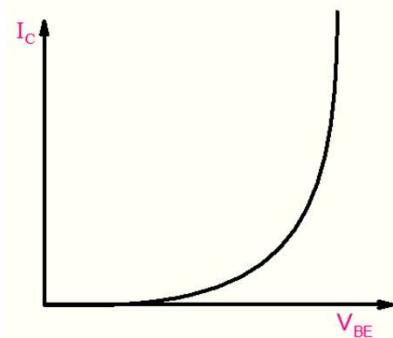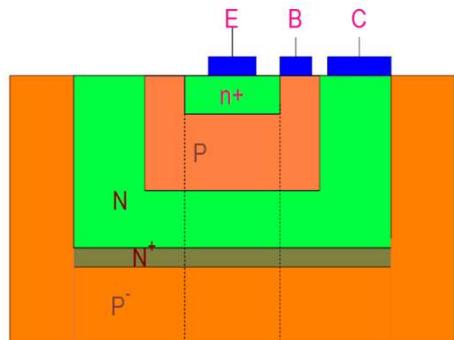

MOSFET



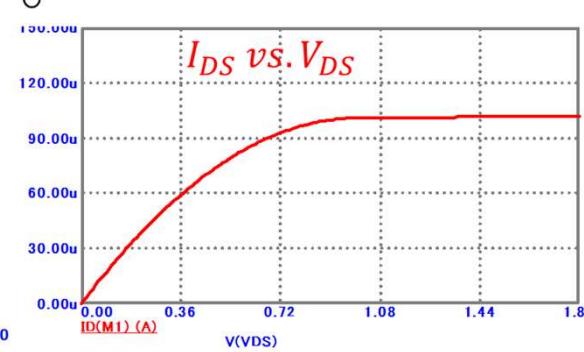
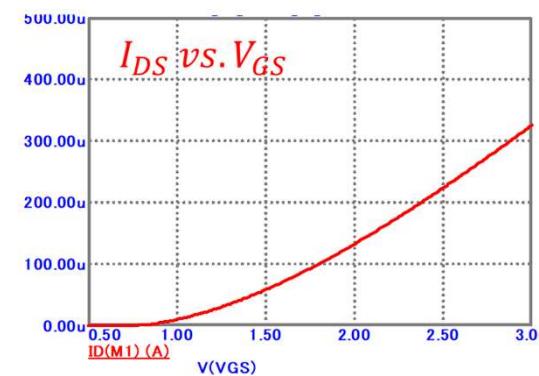
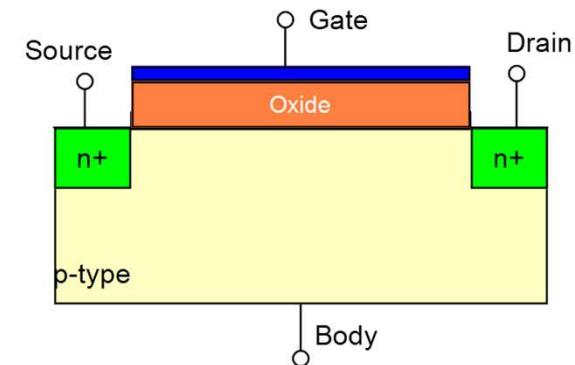


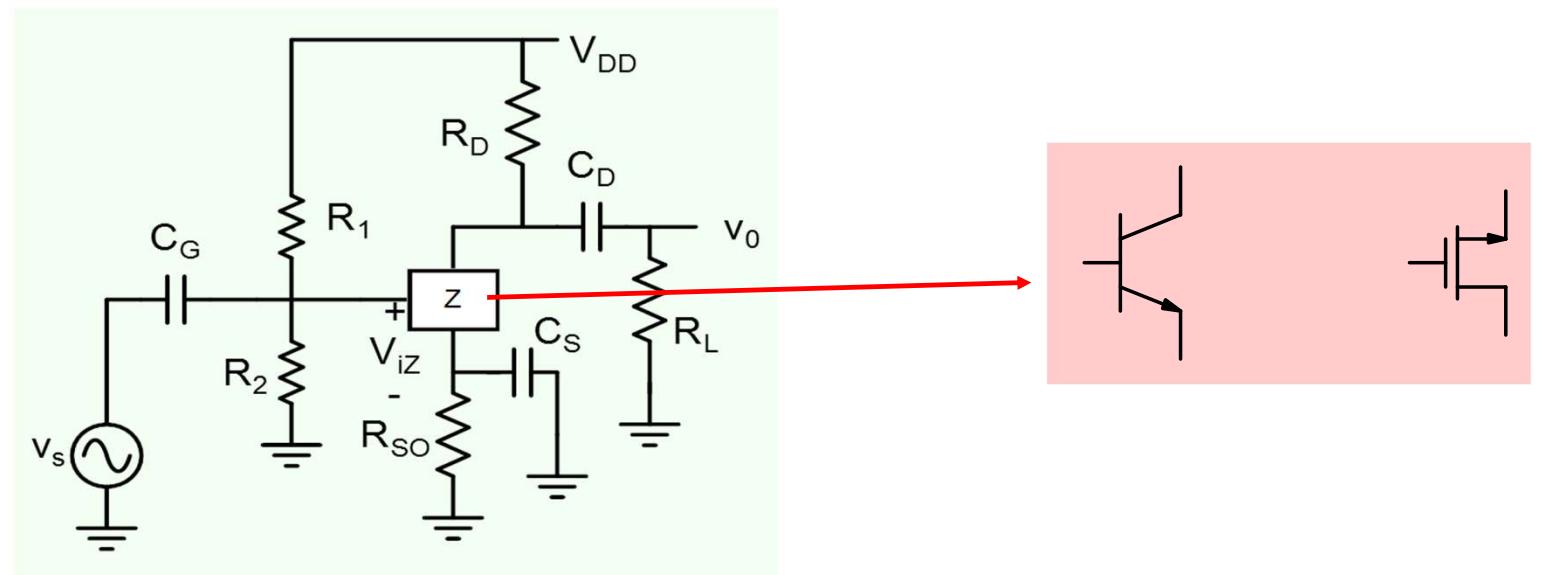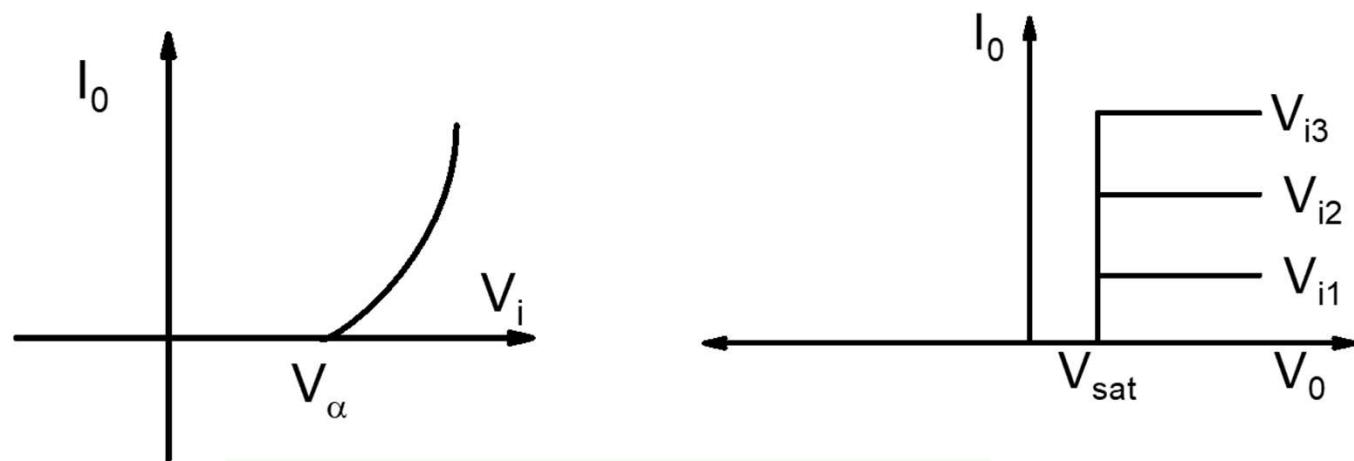



ESC201T: Introduction to Electronics

Lecture 28: Transistor Circuits





B. Mazhari
Dept. of EE, IIT Kanpur

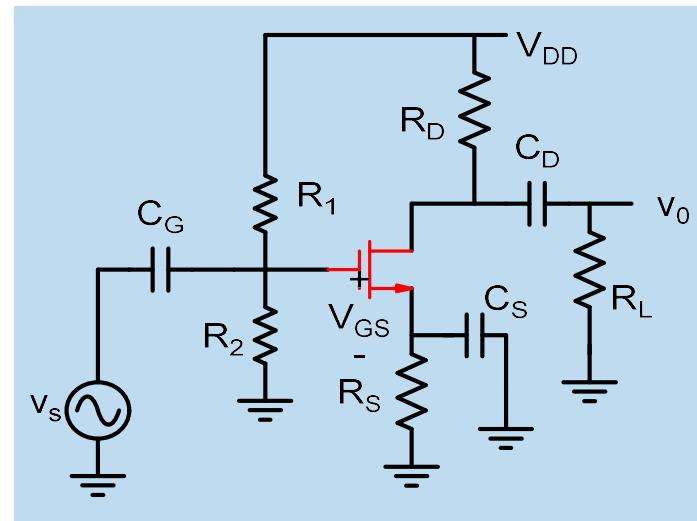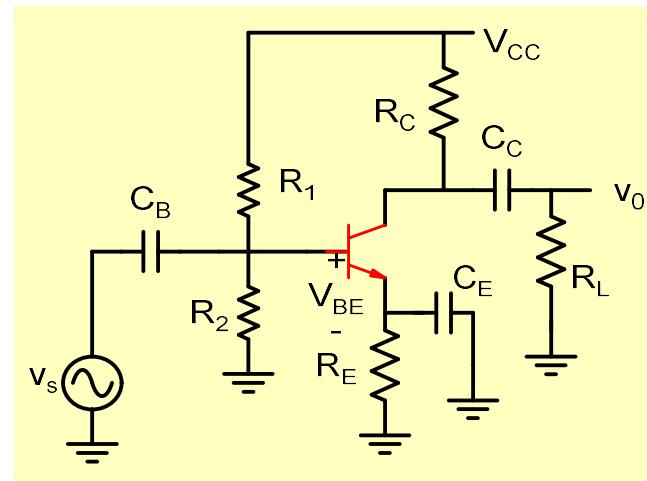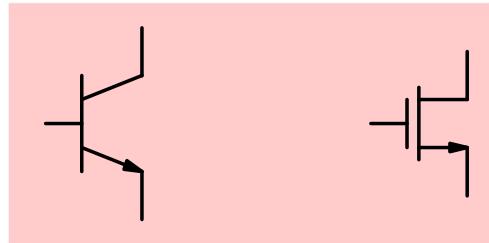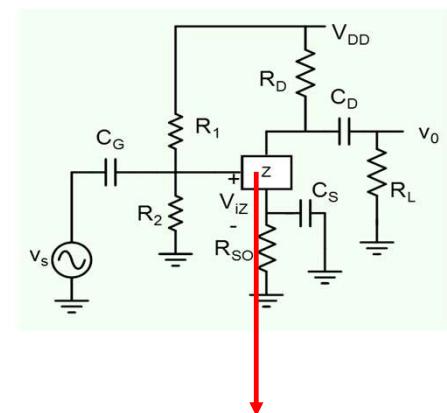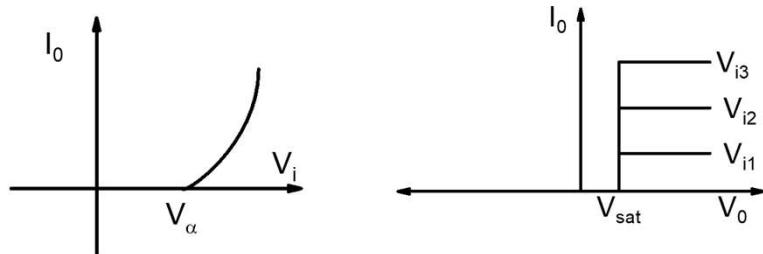



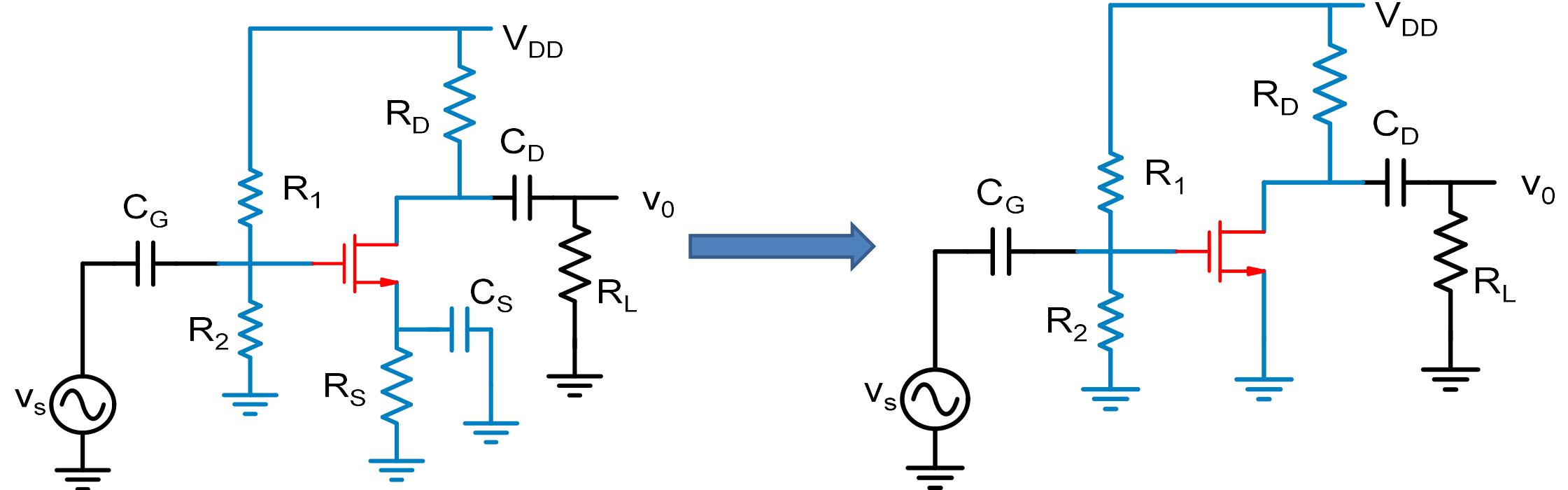


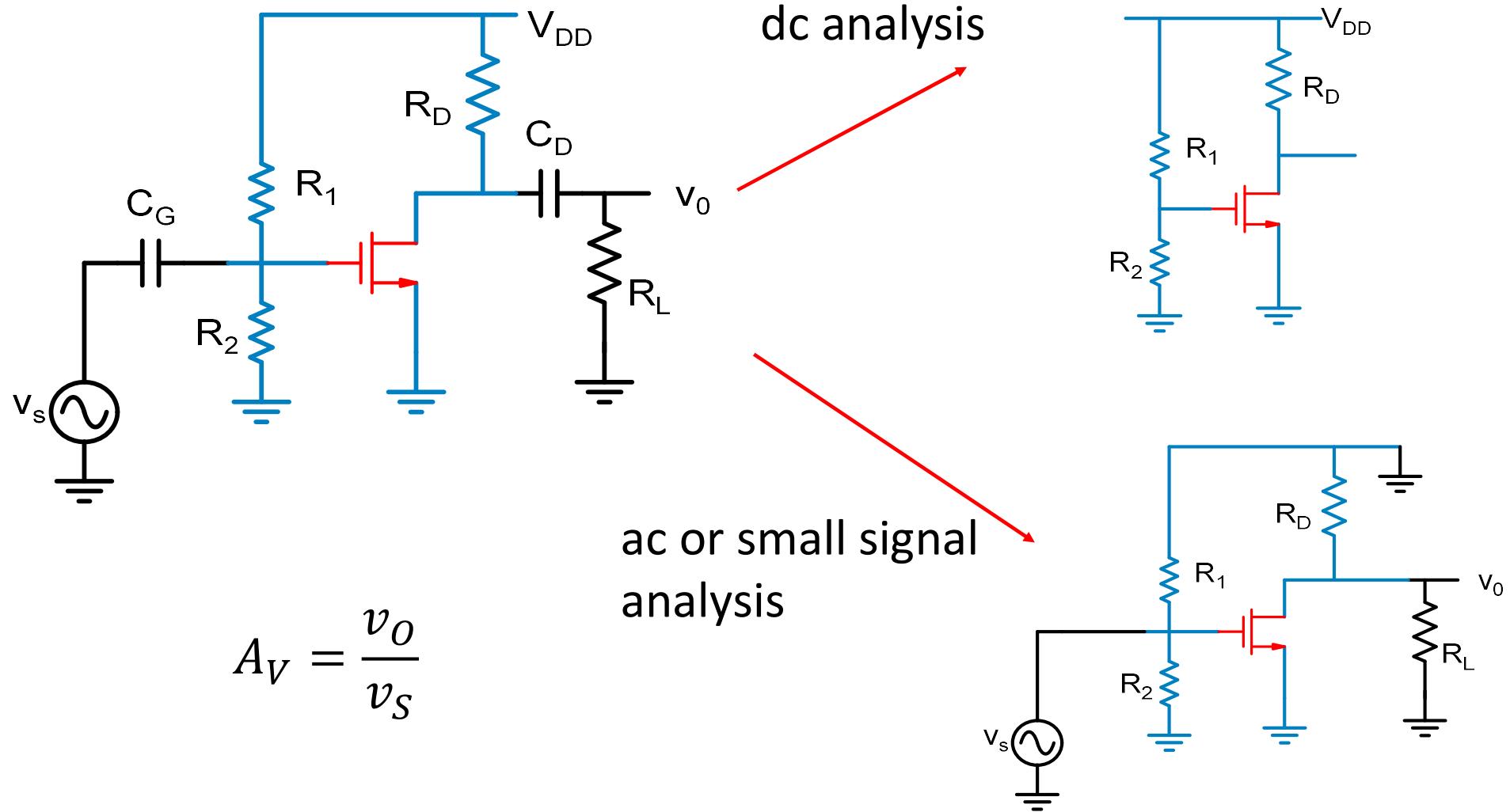

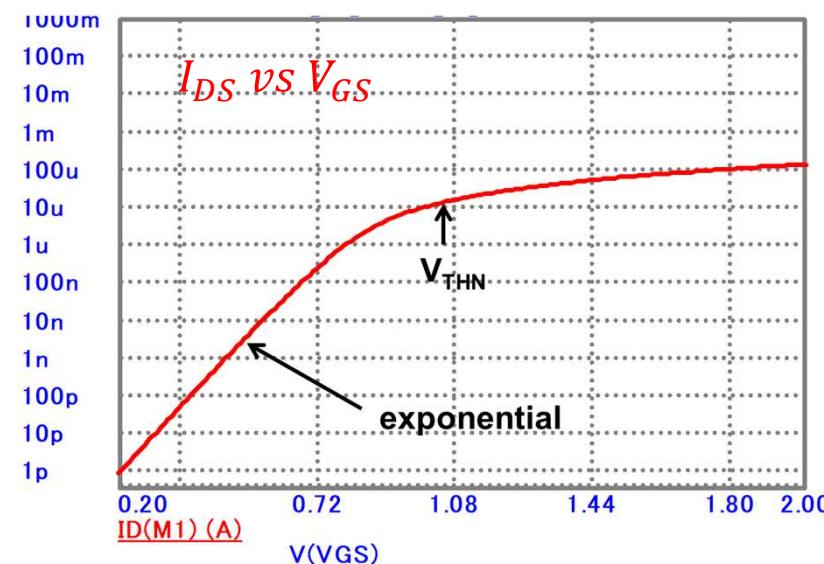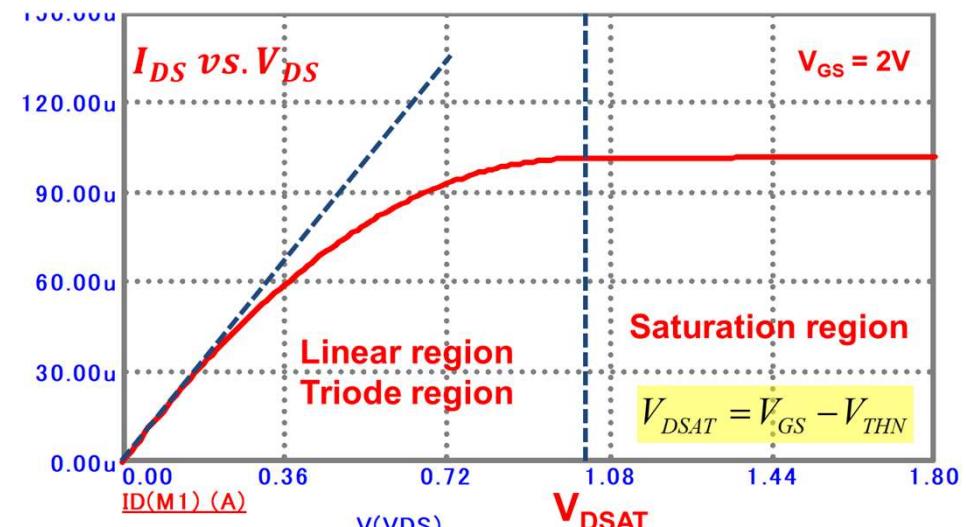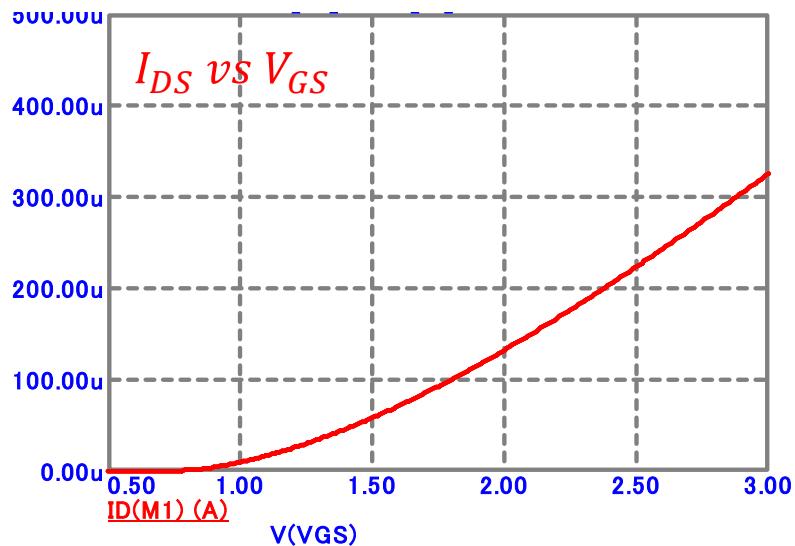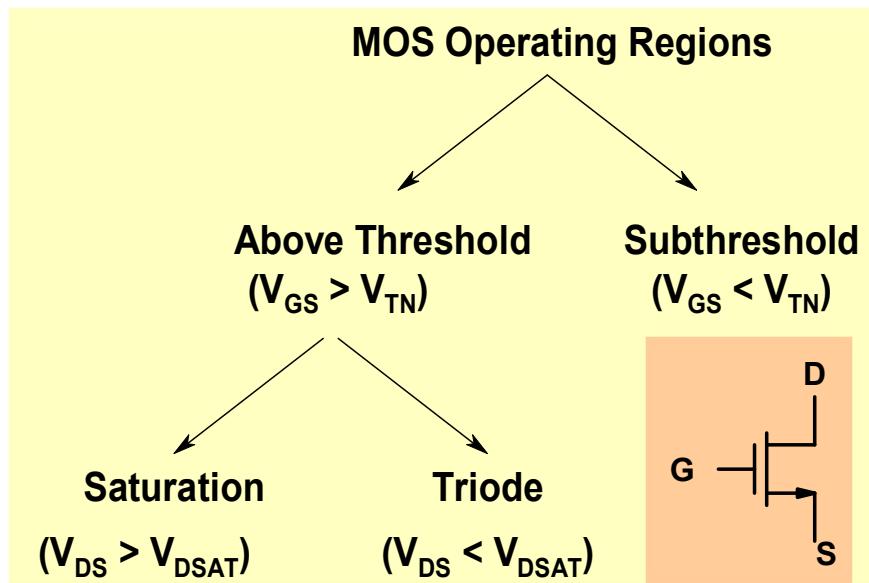Need dc and ac (or small signal incremental) model of the transistors




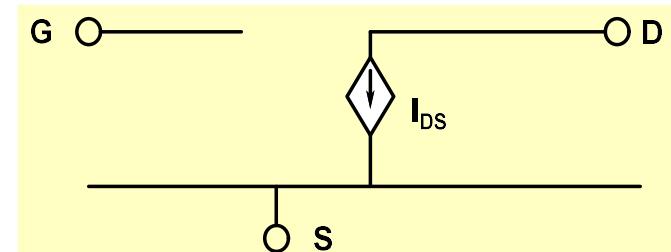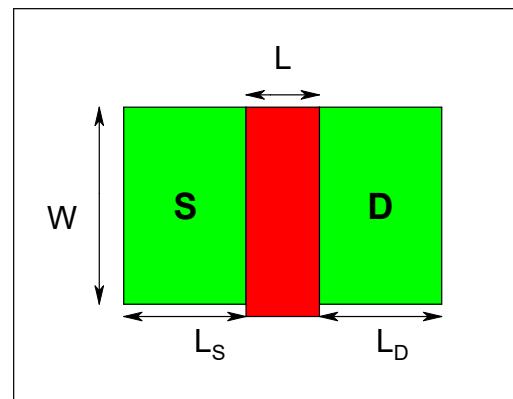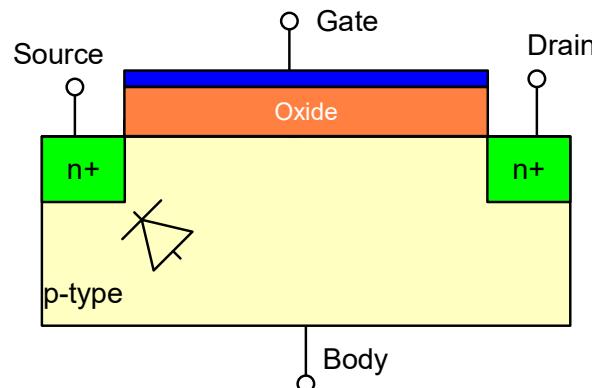The dc and ac models of the transistor in saturation region can be represented in the form of an equivalent circuit:



$$I_{DS} = \frac{\beta_N}{2} (V_{GS} - V_{THN})^2 ; \beta_N = K P_N \times \frac{W}{L}$$

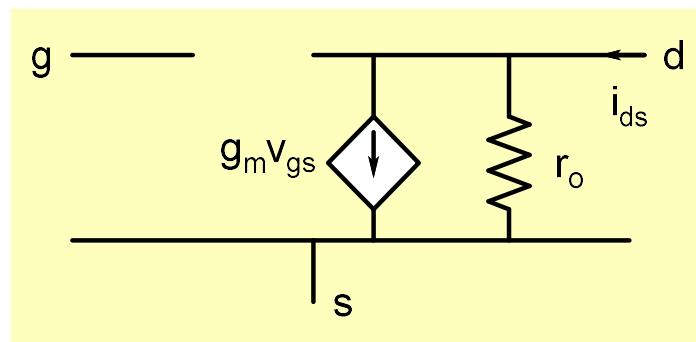kP_N : Transconductance parameter $\frac{\mu A}{V^2}$




$$g_m = \frac{2I_{DSQ}}{V_{GSQ} - V_{THN}} = \sqrt{2I_{DSQ}\beta}$$

$$r_o = \frac{1}{\lambda_n I_{DSQ}}$$

λ_N is the channel length modulation parameter

$$K P_N = 100 \mu A/V^2; V_{THN} = 1V; \lambda_n = 0.01 V^{-1}$$


dc Model: Triode (or Linear)

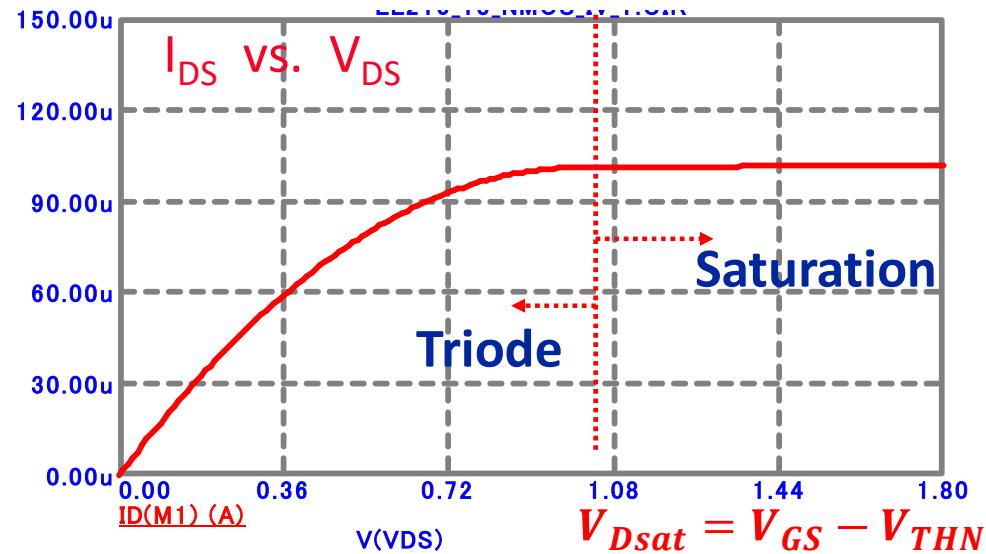


$$I_{DS} = \beta_N \left\{ (V_{GS} - V_{THN})V_{DS} - \frac{V_{DS}^2}{2} \right\}$$

For simplicity we will only consider cases where $I_{DS} \approx K P_N \times \frac{W}{L} \times (V_{GS} - V_{THN}) \times V_{DS}$

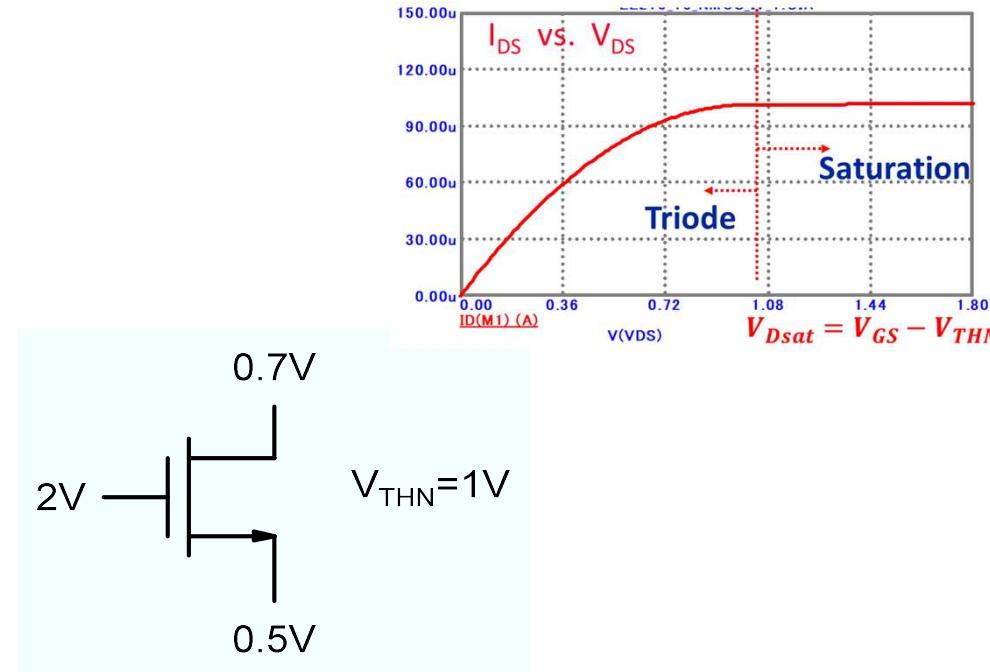Which mode is the transistor operating in ?



$$V_{GS} = 1.5 ; V_{DS} = 0.2$$

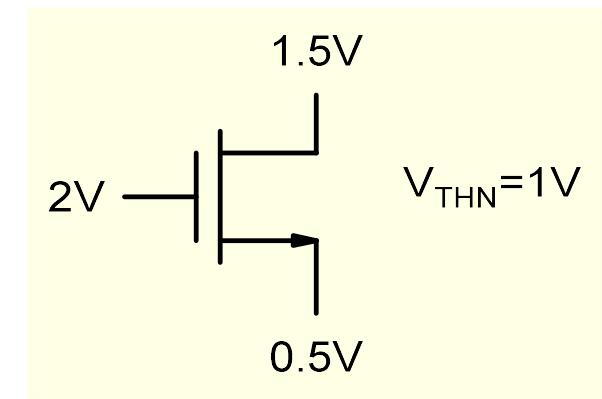


$$V_{DSAT} = 0.5 ; V_{DS} = 1V$$

$$V_{DSAT} = V_{GS} - V_{THN} = 0.5$$


Saturation

$$V_{DS} < V_{DSAT} \Rightarrow Linear$$

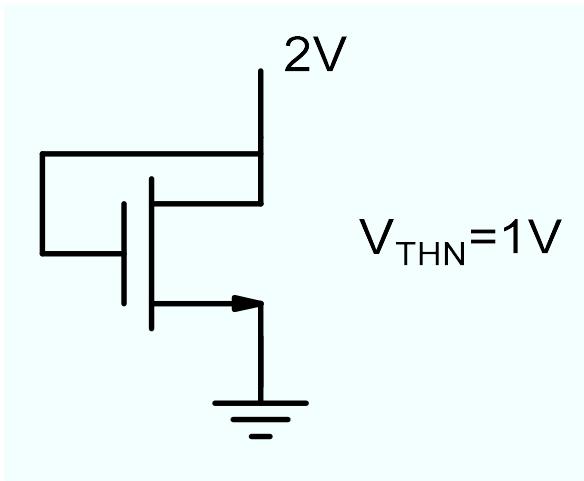



$$V_{GS} = 2 ; V_{DS} = 2$$

Saturation

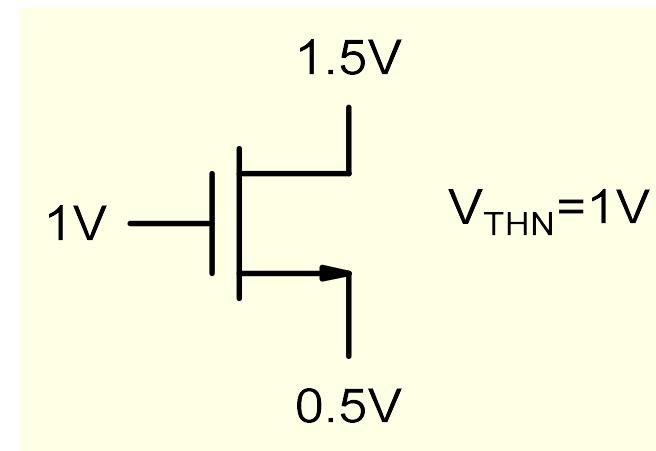


$$V_{GS} = 0.5V < V_{THN}$$

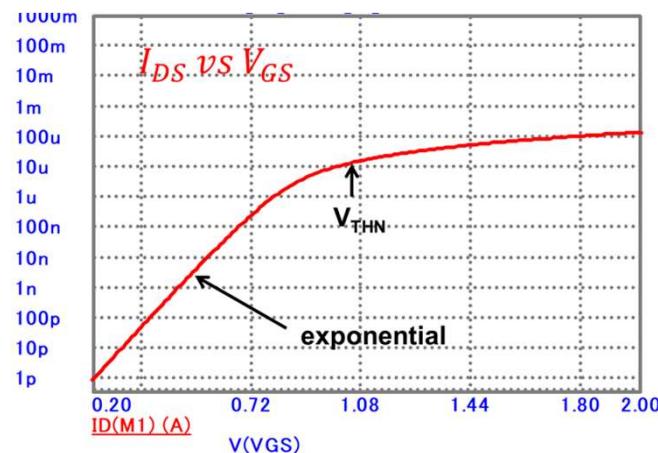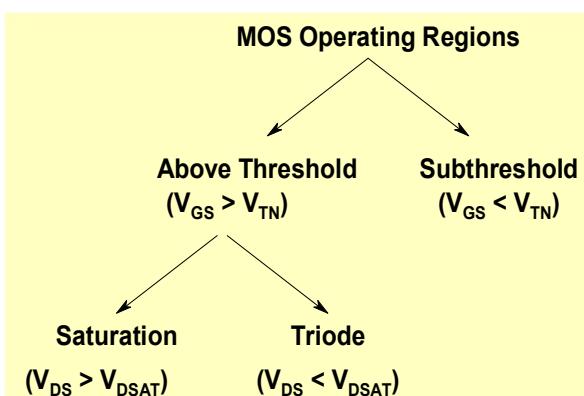Transistor is in sub-threshold mode of operation



MOSFET Circuits

Example-1

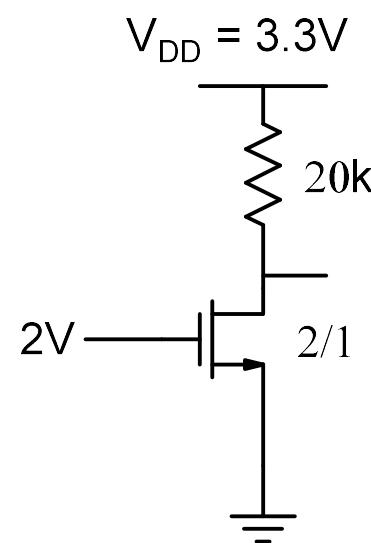

$$KP_N = 100\mu A/V^2; V_{THN} = 1V; \lambda_n = 0.01V^{-1}$$


Determine I_{DS} and V_{DS}

Assume saturation mode of operation

$$I_{DS} = KP_N \times \frac{W}{L} \times \frac{(V_{GS} - V_{THN})^2}{2} = 10^{-4}A$$

$$V_{DS} = V_{DD} - I_{DS} \times R_D = 1.2V$$


$$V_{Dsat} = V_{GS} - V_{THN} = 1V$$

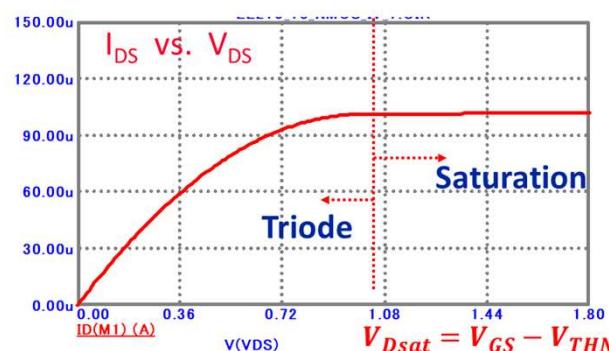

Since $V_{DS} > V_{Dsat}$ our assumption is correct

MOSFET Circuits

Example-2

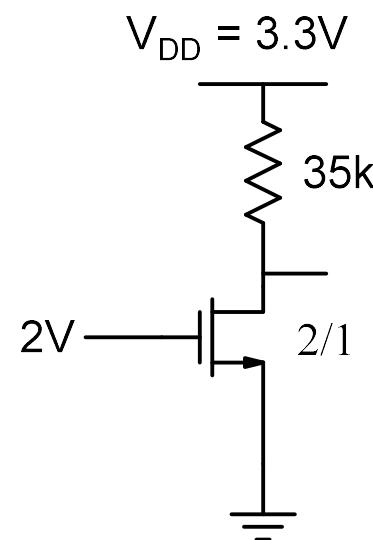


$$KP_N = 100\mu A/V^2; V_{THN} = 1V; \lambda_n = 0.01V^{-1}$$

Determine I_{DS} and V_{DS}

Assume saturation mode of operation

$$I_{DS} = KP_N \times \frac{W}{L} \times \frac{(V_{GS} - V_{THN})^2}{2} = 10^{-4}A$$
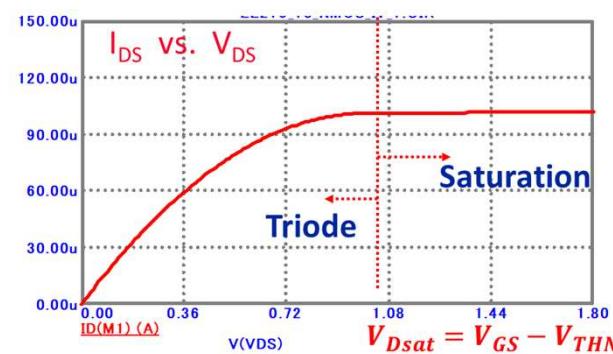
$$V_{DS} = V_{DD} - I_{DS} \times R_D = -0.2V \text{ so assumption incorrect}$$




$$I_{DS} \approx KP_N \times \frac{W}{L} \times (V_{GS} - V_{THN}) \times V_{DS}; V_{DS} = V_{DD} - I_{DS} \times R_D$$
$$\Rightarrow I_{DS} = 8.25 \times 10^{-5} A; V_{DS} = 0.412V$$

$$V_{DSat} = V_{GS} - V_{THN} = 1V$$

Example-3

$$V_{DD} = 3.3V$$

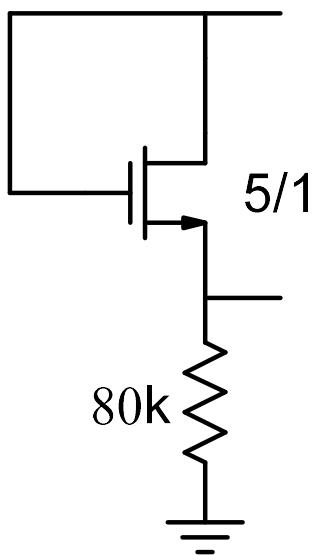

$$KP_N = 100\mu A/V^2; V_{THN} = 1V; \lambda_n = 0.01V^{-1}$$


Determine I_{DS} and V_{DS}

$$\begin{aligned} V_{DS} &= V_{GS} \\ \Rightarrow V_{DS} &> V_{GS} - V_{THN} = V_{DSAT} \Rightarrow \text{Saturation} \end{aligned}$$


$$\begin{aligned} I_{DS} &= KP_N \times \frac{W}{L} \times \frac{(V_{GS} - V_{THN})^2}{2}; V_{GS} = 3.3 - I_{DS} \times 80 \times 10^3 \\ \Rightarrow I_{DS} &= 2.48 \times 10^{-5}A; V_{GS} = 1.315V \end{aligned}$$

For the other solution $V_{GS} = 0.653V$ which is not possible since it is less than V_{THN}

Example-4

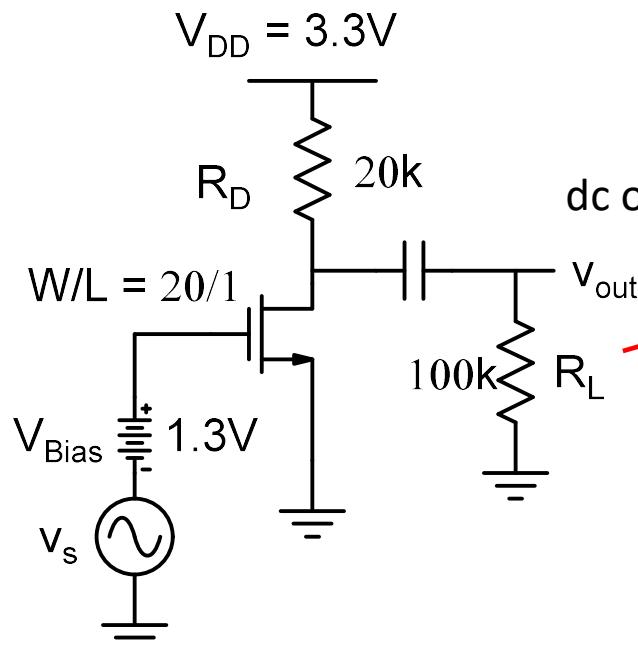
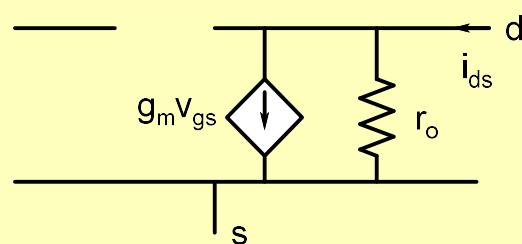
$$KP_N = 100 \mu A/V^2; V_{THN} = 1V; \lambda_n = 0V^{-1}$$




$$g_m = \frac{2I_{DSQ}}{V_{GSQ} - V_{THN}} = \sqrt{2I_{DSQ}\beta}$$

$$= 6 \times 10^{-4} \Omega^{-1}$$

$$r_o = \frac{1}{\lambda_n I_{DSQ}} = \infty$$

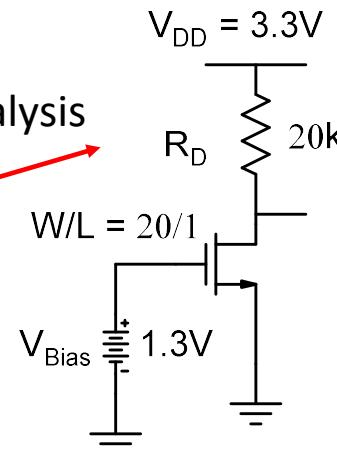Determine the voltage gain of the amplifier $\frac{v_{out}}{v_s}$






$$I_{DS} = KP_N \times \frac{W}{L} \times \frac{(V_{GS} - V_{THN})^2}{2} = 90 \mu A$$

$$V_{DSQ} = V_{DD} - I_{DSQ} \times R_D = 1.5V$$

$$V_{Dsat} = V_{GS} - V_{THN} = 0.3V$$

So Transistor is biased in saturation

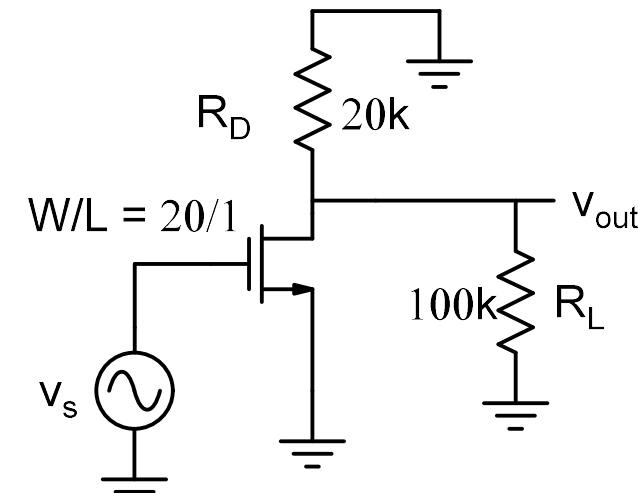


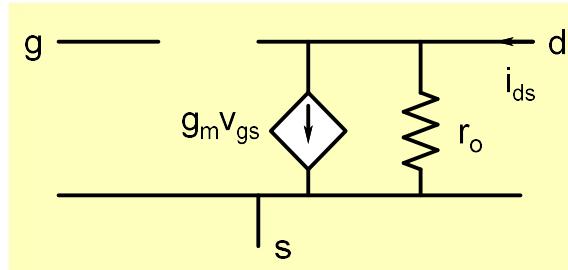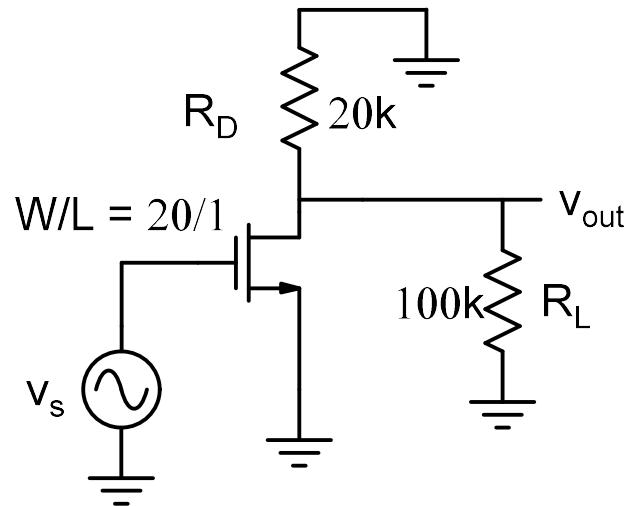

$$g_m = \frac{2I_{DSQ}}{V_{GSQ} - V_{THN}} = \sqrt{2I_{DSQ}\beta}$$


$$= 6 \times 10^{-4} \Omega^{-1}$$
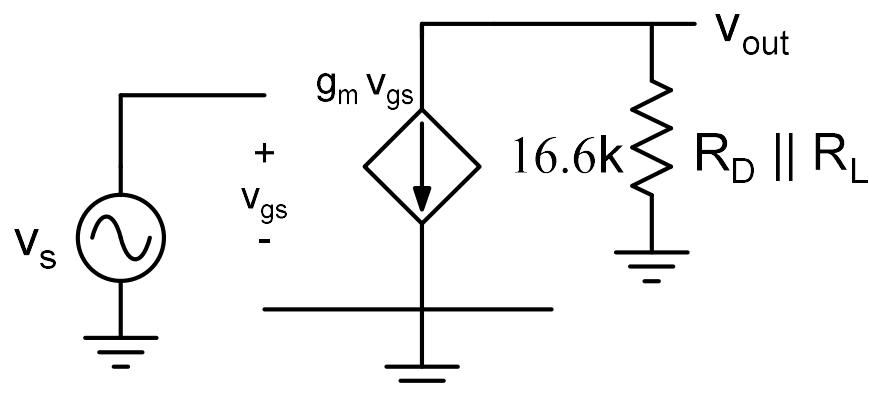
$$r_o = \frac{1}{\lambda_n I_{DSQ}} = \infty$$



$$\frac{v_{out}}{v_s} = -g_m \times R_D \parallel R_L = -10$$

Example-5 Plot V_{OUT} vs. V_{IN} curve.



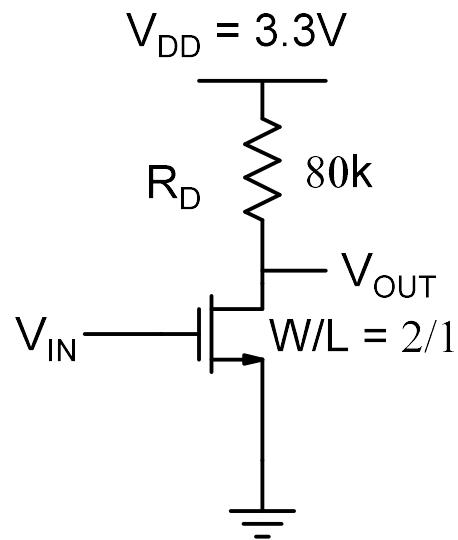


$$KP_N = 100\mu A/V^2; V_{THN} = 1V; \lambda_n = 0.01V^{-1}$$

$$V_{out} = V_{DD} - I_{DS} \times R_D$$

$$I_{DS} = KP_N \times \frac{W}{L} \times (V_{IN} - V_{THN}) \times V_{out}$$

MOS Digital NOT gate

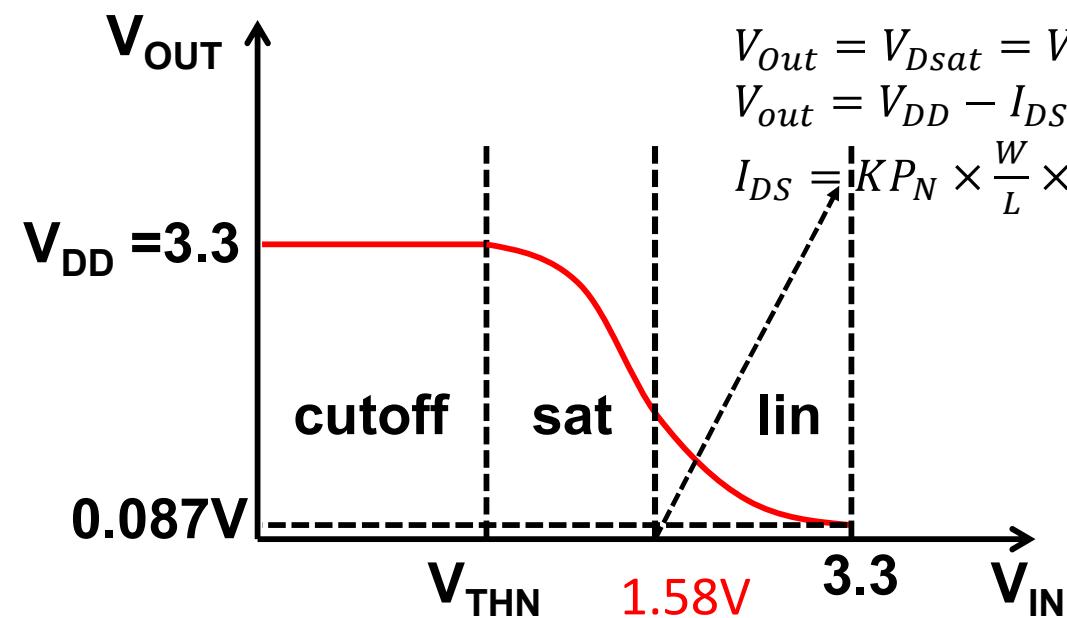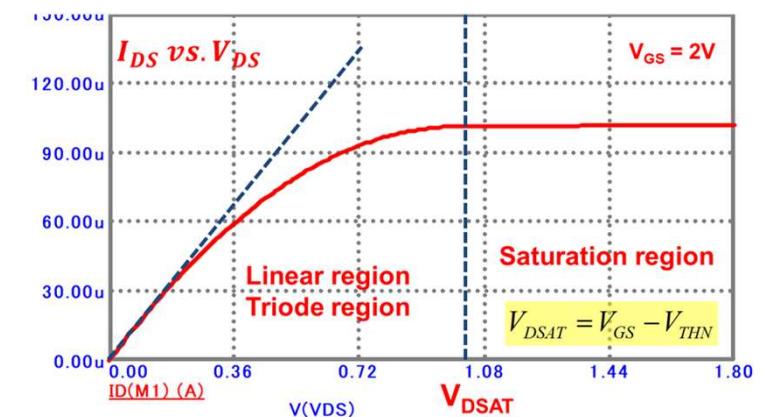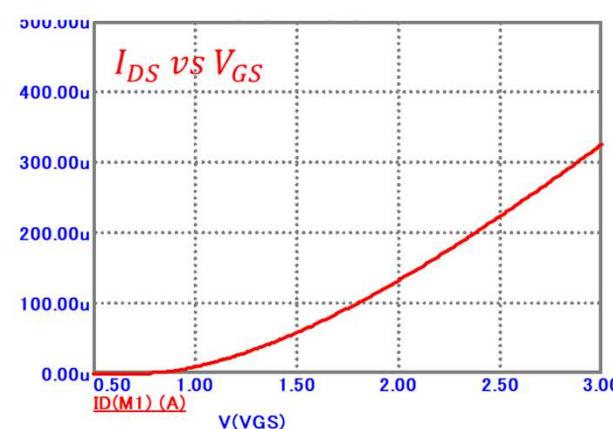

$$V_{out} = V_{DSAT} = V_{IN} - V_{THN}$$

$$V_{out} = V_{DD} - I_{DS} \times R_D$$



$$I_{DS} = KP_N \times \frac{W}{L} \times \frac{(V_{GS} - V_{THN})^2}{2}$$

ESC201T : Introduction to Electronics

Lecture 29: Operational Amplifier

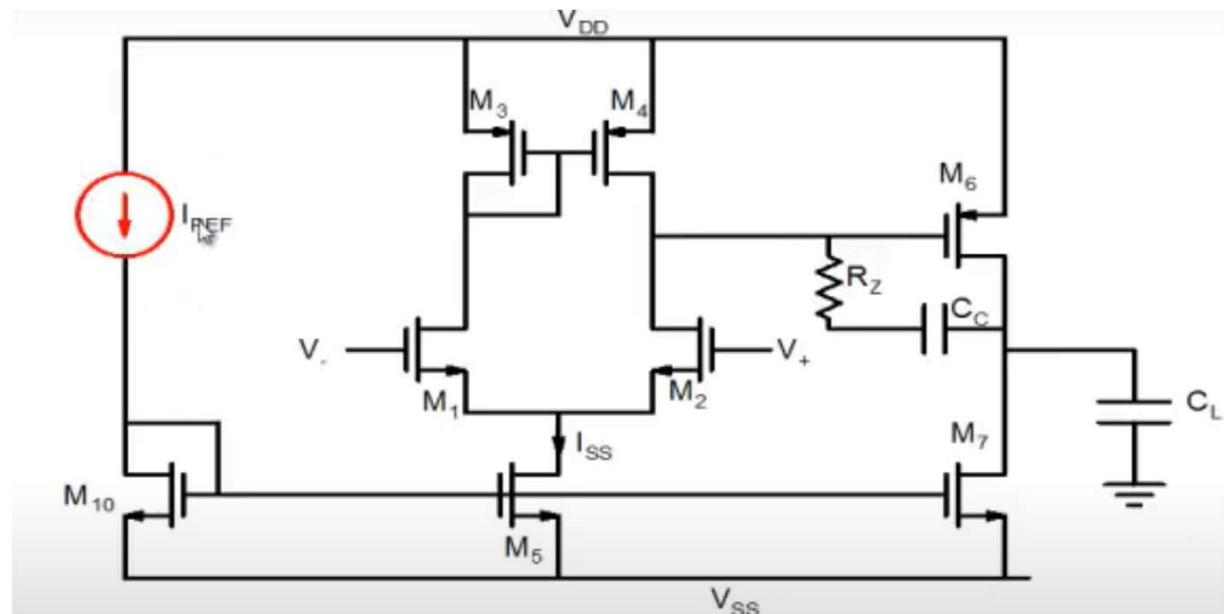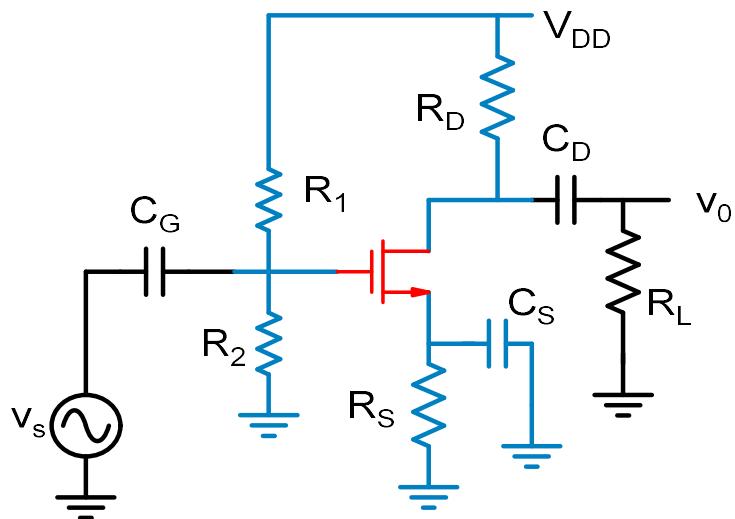B. Mazhari
Dept. of EE, IIT Kanpur


Amplifier Design requires specialized knowledge



It is not possible for every user to design his/her own amplifier !

Why can't we have experts design and implement amplifiers and make it available to everybody else !

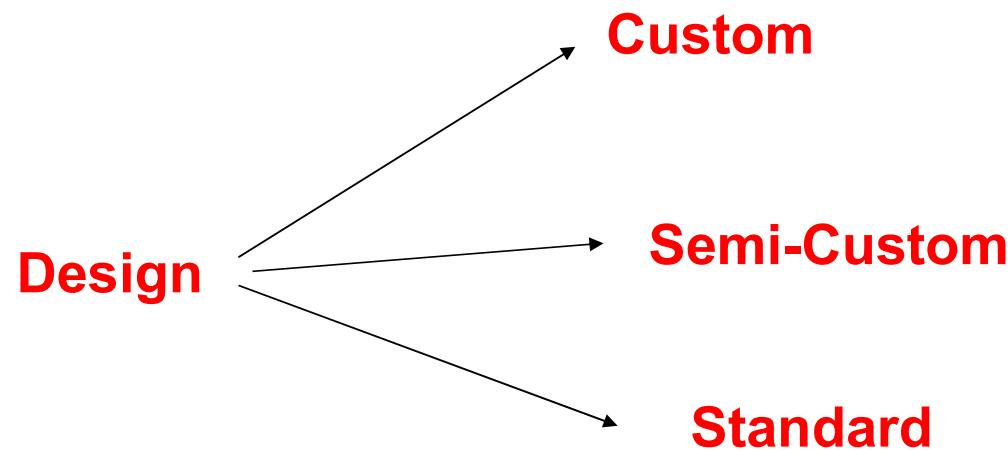Although this is done, it does not satisfy all the users due to diverse requirements




Semi-custom: partially completed design which is customized by the user

Opamp is a good illustration of the advantages of semi-custom approach

Difference Amplifier

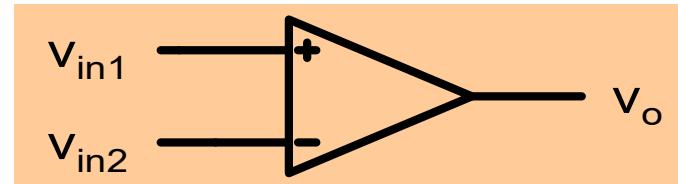-An amplifier that is sensitive to difference in input voltages and insensitive to what is common.



$$v_{id} = v_{in1} - v_{in2}$$

$$v_{ic} = \frac{v_{in1} + v_{in2}}{2}$$


$$v_o = A_d v_{id} + A_{cm} v_{ic}$$

A_d : Differential mode gain

A_{cm} : Common mode gain

$$A_d \gg A_{cm}$$
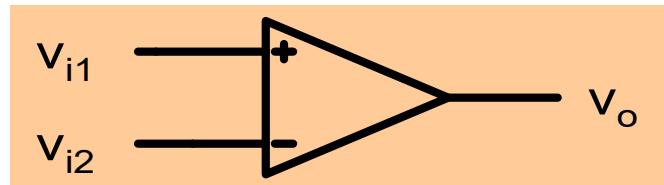
$$\text{Common Mode Rejection Ratio: } CMRR = \frac{A_d}{A_{cm}}$$



$$A_d = 100; \quad A_{cm} = 0.01$$

$$v_{i1} = 1V + 5mV \times \sin(\omega t); \quad v_{i2} = 1V - 5mV \times \sin(\omega t)$$


$$v_{id} = v_{in1} - v_{in2} = 10mV \times \sin(\omega t)$$

$$v_{ic} = \frac{v_{in1} + v_{in2}}{2} = 1V$$

$$\begin{aligned} v_o &= A_d v_{id} + A_{cm} v_{ic} \\ &= 1V \times \sin(\omega t) + 10mV \end{aligned}$$

Whatever is common is rejected and whatever is different is amplified !


Operational Amplifier

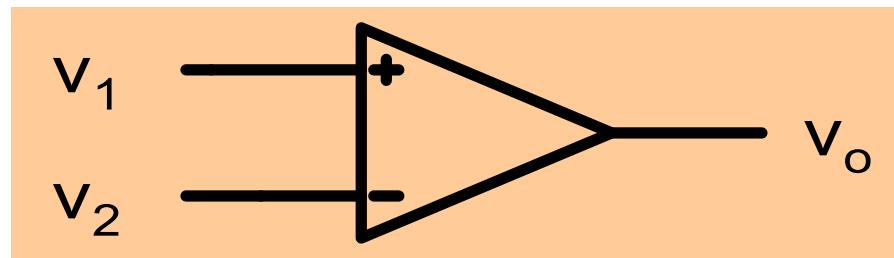

A **special** kind of difference amplifier

1. Very High Differential-mode voltage gain
2. Very High Common mode Rejection ratio
3. Very High Input Resistance
4. Very Low output Resistance
5.

Ideal Operational Amplifier

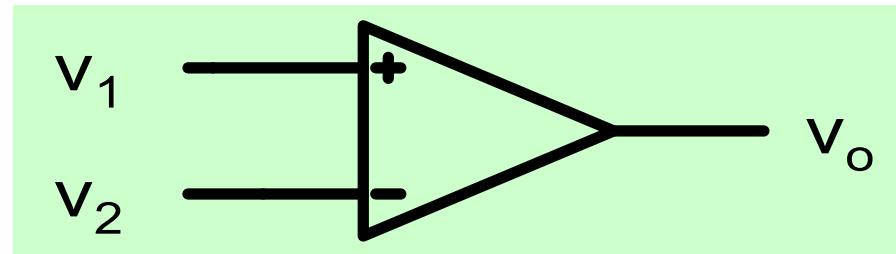

1. Infinite Differential-mode voltage gain
2. Infinite Common mode Rejection ratio
3. Infinite Input Resistance
4. Zero output Resistance
5.

Example: LM 741

LM741

Operational Amplifier


General Description

The LM741 series are general purpose operational amplifiers which feature improved performance over industry standards like the LM709. They are direct, plug-in replacements for the 709C, LM201, MC1439 and 748 in most applications.

The amplifiers offer many features which make their application nearly foolproof: overload protection on the input and output, no latch-up when the common mode range is exceeded, as well as freedom from oscillations.

The LM741C is identical to the LM741/LM741A except that the LM741C has their performance guaranteed over a 0°C to +70°C temperature range, instead of -55°C to +125°C.


Dual-In-Line or S.O. Package

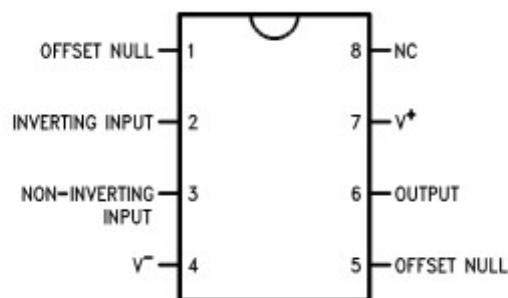



Parameter	Conditions	LM741A			LM741			LM741C			Units
		Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	
Input Resistance	$T_A = 25^\circ\text{C}$, $V_s = \pm 20\text{V}$	1.0	6.0		0.3	2.0		0.3	2.0		MΩ
	$T_{A\text{MIN}} \leq T_A \leq T_{A\text{MAX}}$, $V_s = \pm 20\text{V}$	0.5									MΩ
Large Signal Voltage Gain	$T_A = 25^\circ\text{C}$, $R_L \geq 2\text{ k}\Omega$ $V_s = \pm 20\text{V}$, $V_o = \pm 15\text{V}$ $V_s = \pm 15\text{V}$, $V_o = \pm 10\text{V}$	50			50	200		20	200		V/mV
Common-Mode Rejection Ratio	$T_{A\text{MIN}} \leq T_A \leq T_{A\text{MAX}}$ $R_s \leq 10\text{ k}\Omega$, $V_{CM} = \pm 12\text{V}$ $R_s \leq 50\Omega$, $V_{CM} = \pm 12\text{V}$	70	90		70	90		70	90		dB

Inside the opamp, there is a complicated circuit containing several transistors and resistors.




Schematic Diagram




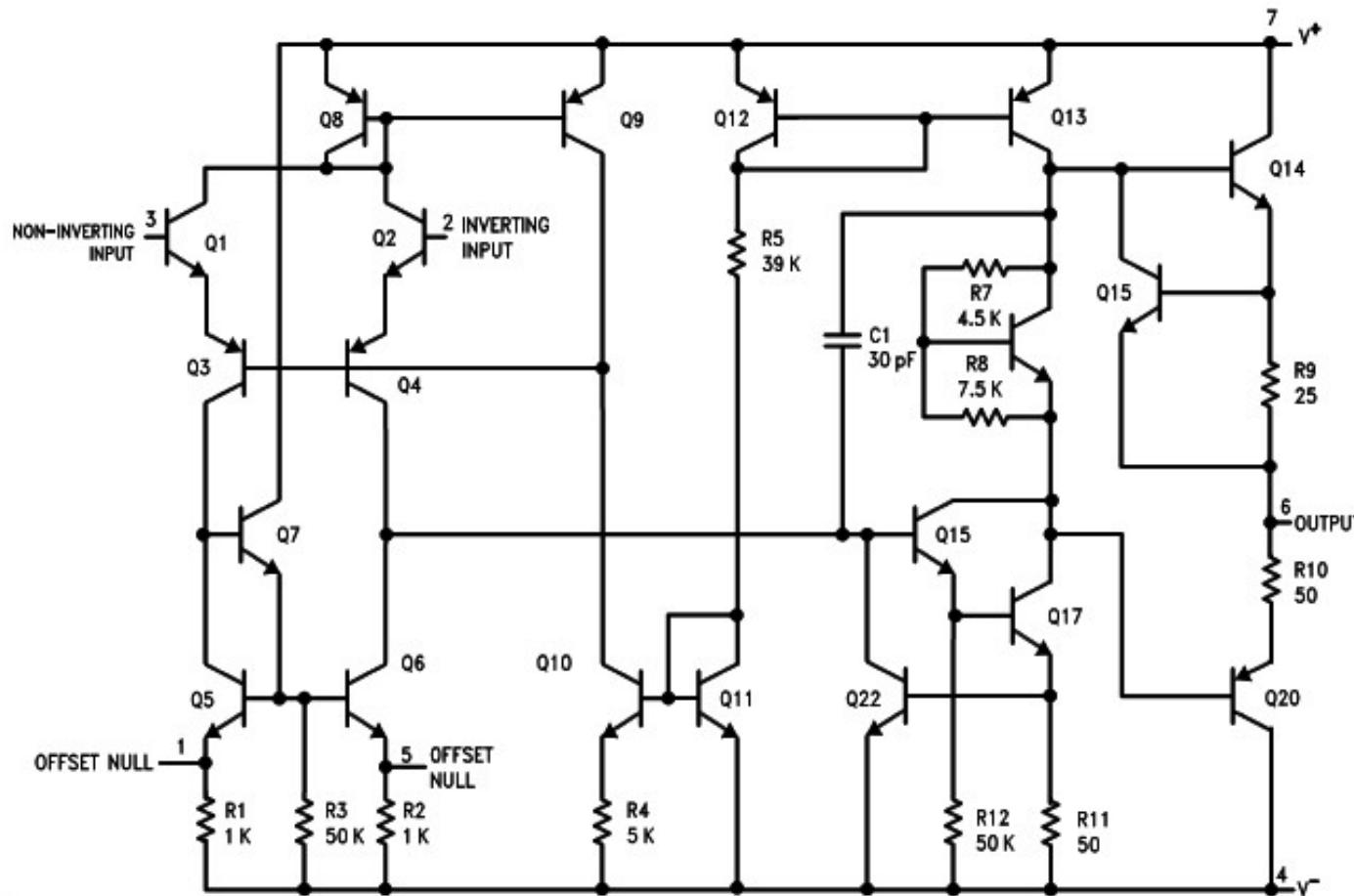


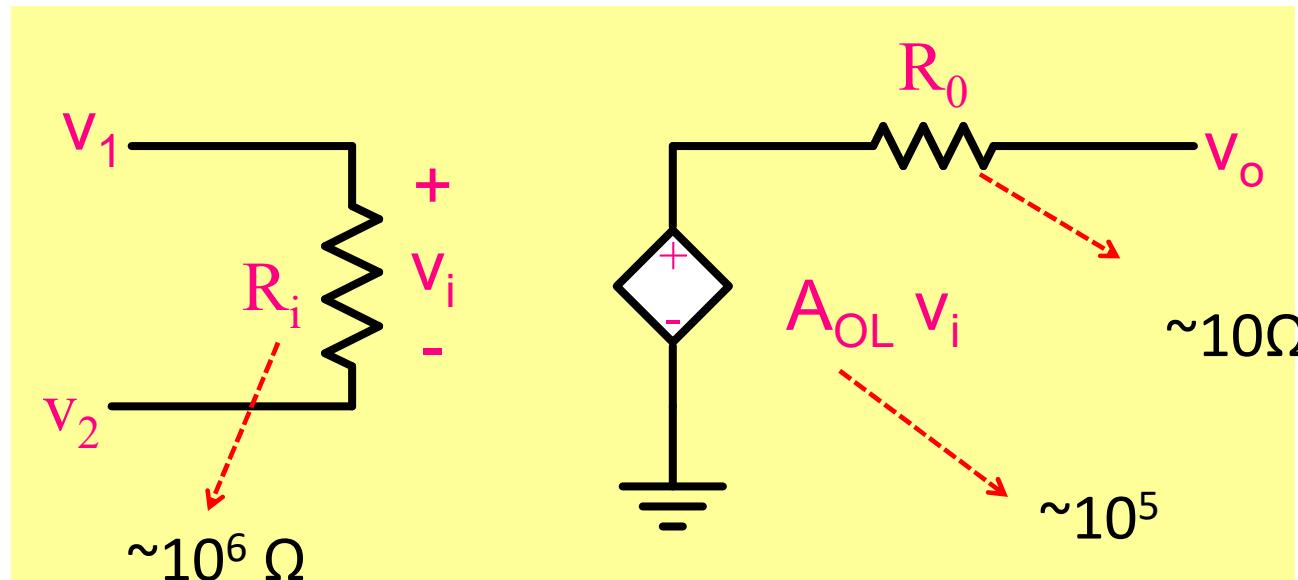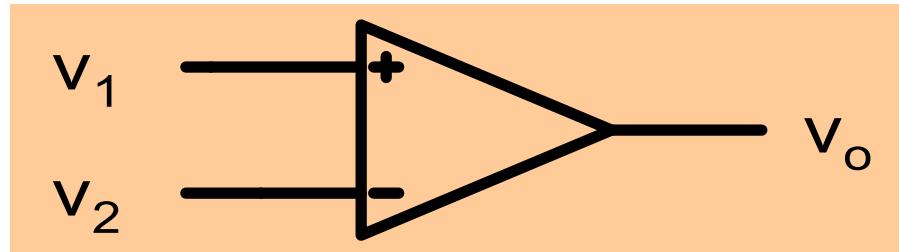Simple equivalent circuit model of an opamp




This assumes very high CMRR

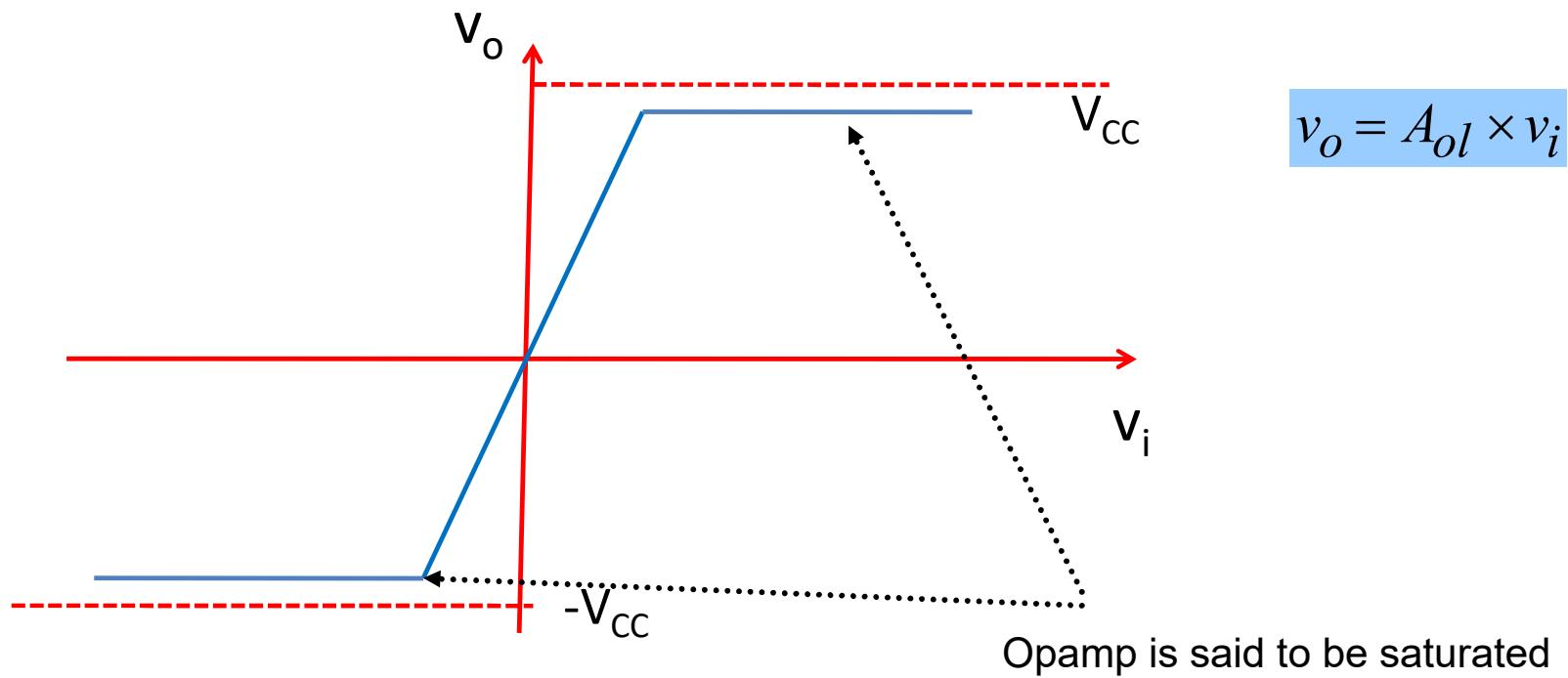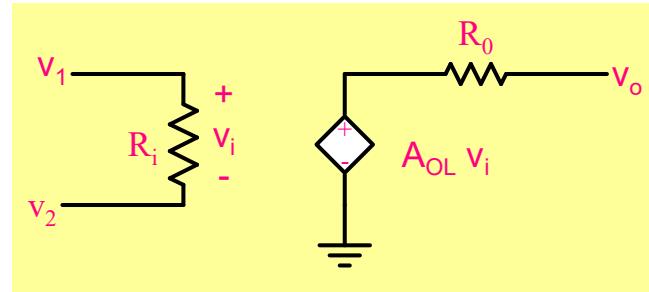
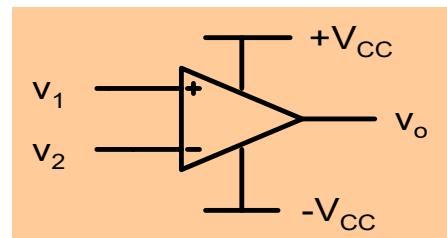


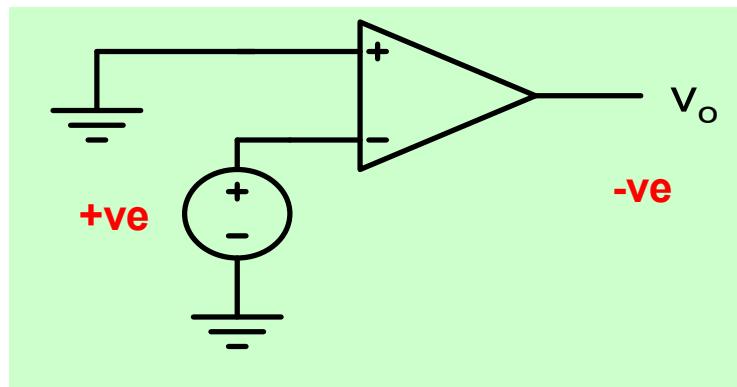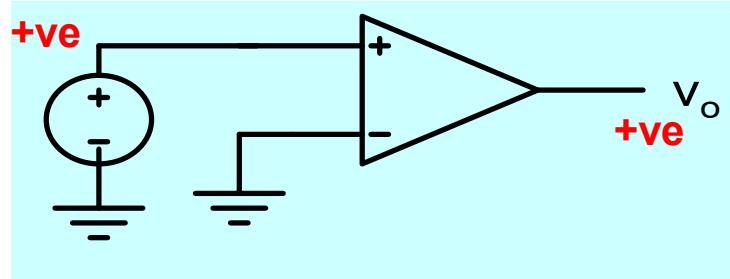
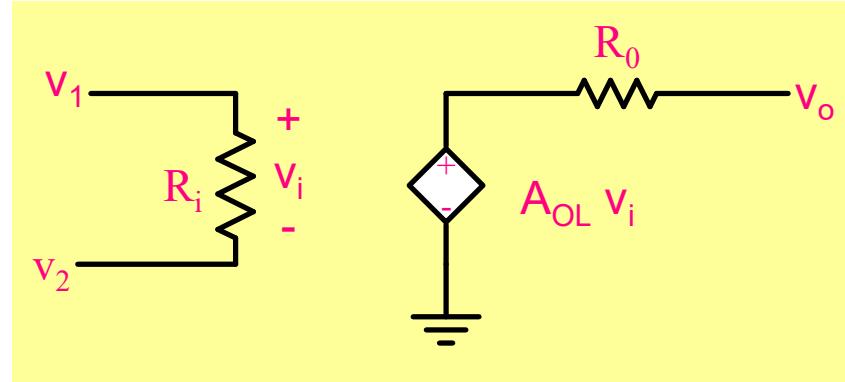
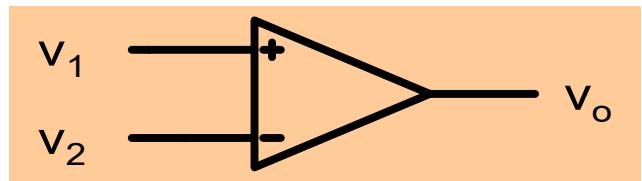


How do we amplify this signal?

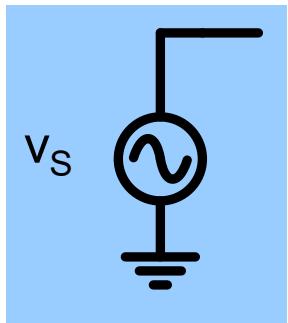

$$v_s = 1mV \sin(\omega t)$$


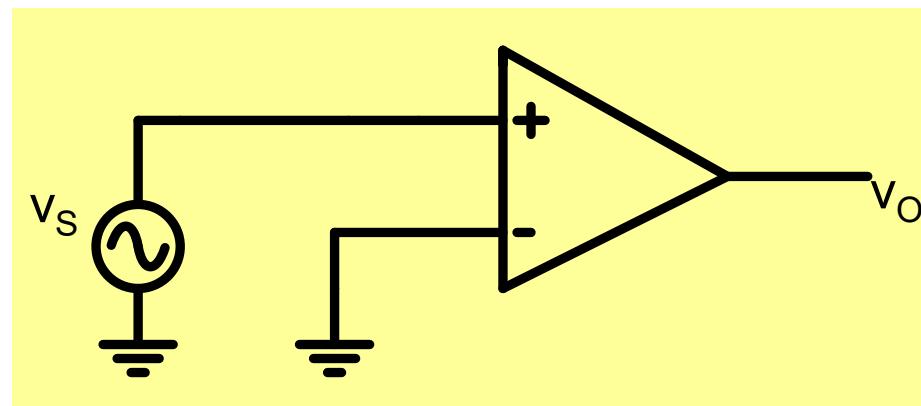
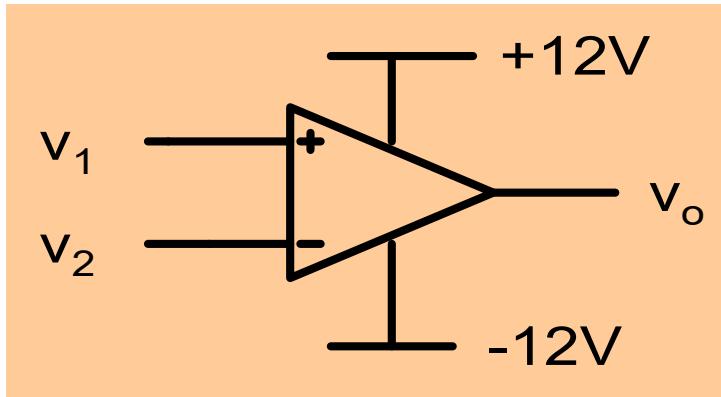


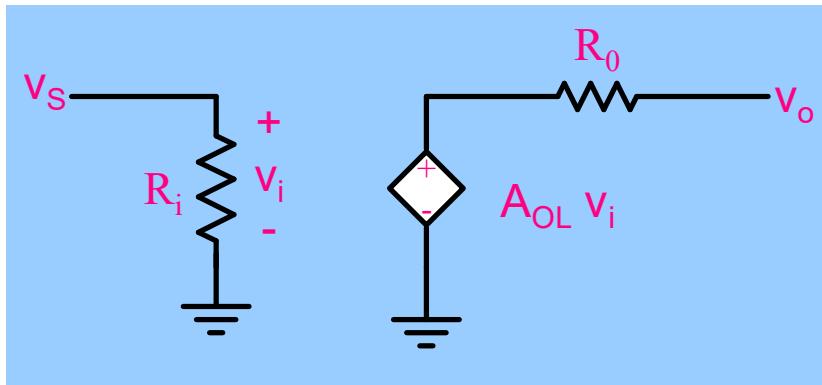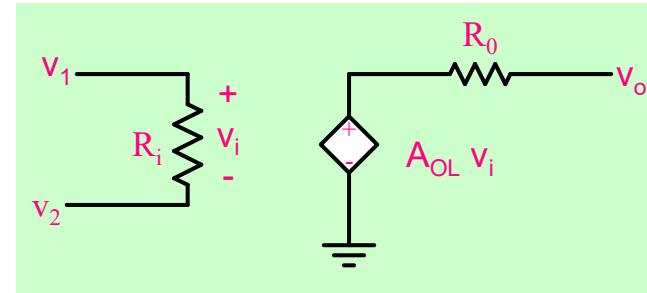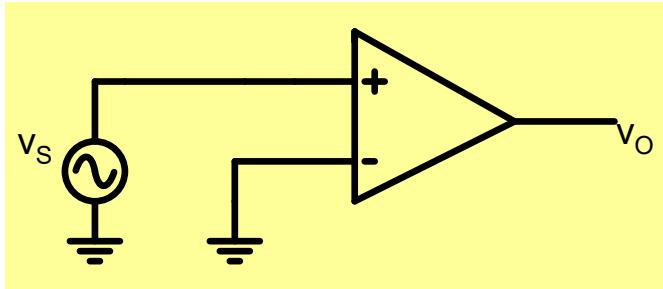


$$v_o = A_{ol} \times v_s = 10^2 \sin(\omega t)$$

But opamp voltage is limited to $\pm 12V$



Simulation Results

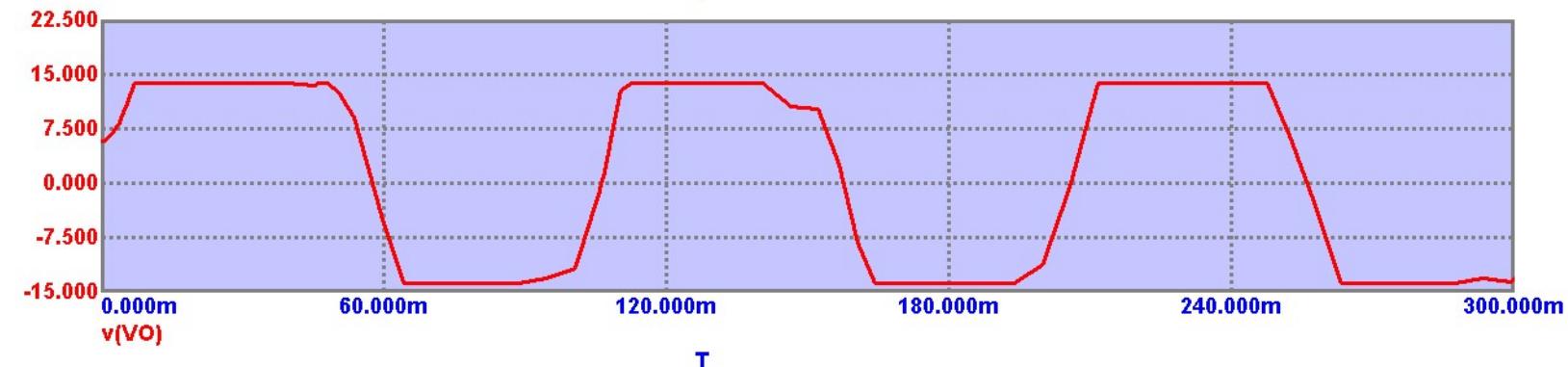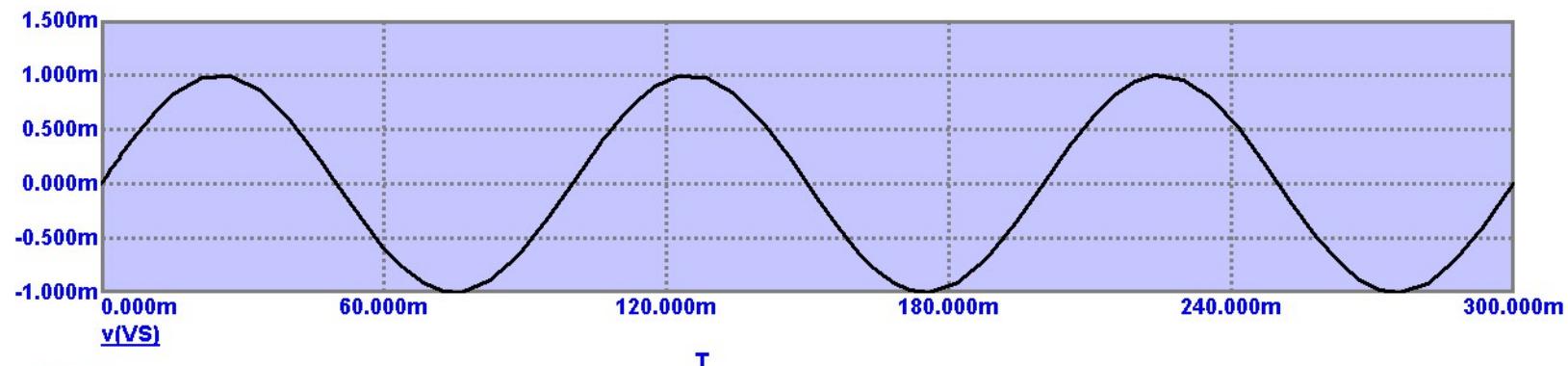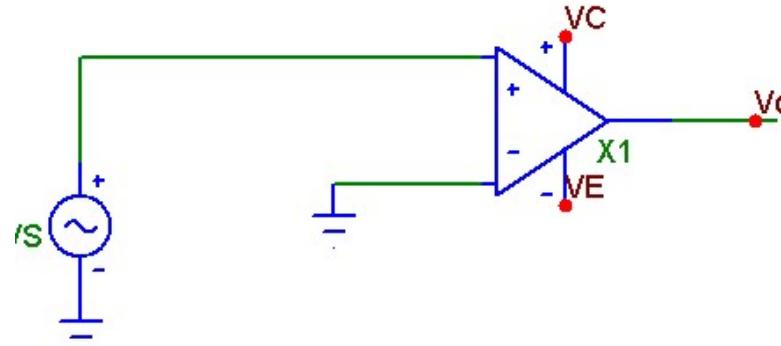

How do we amplify this signal then ?

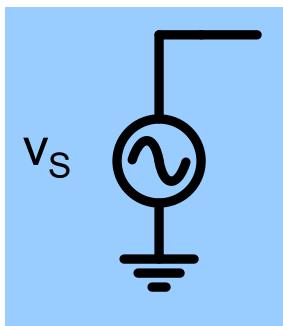


$$v_s = 1mV \sin(\omega t)$$

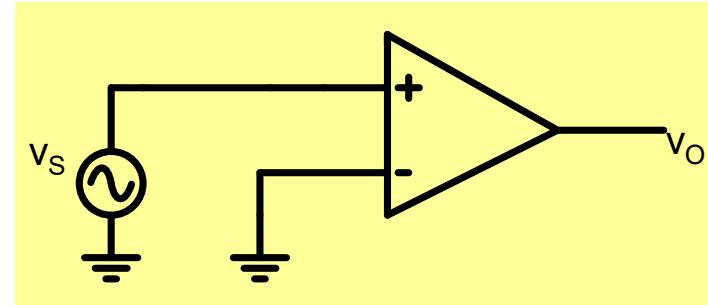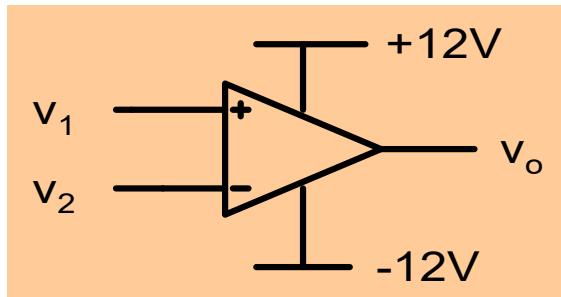

1. Attenuate the signal to 0.1mV and then amplify ?
2.

A Better Solution


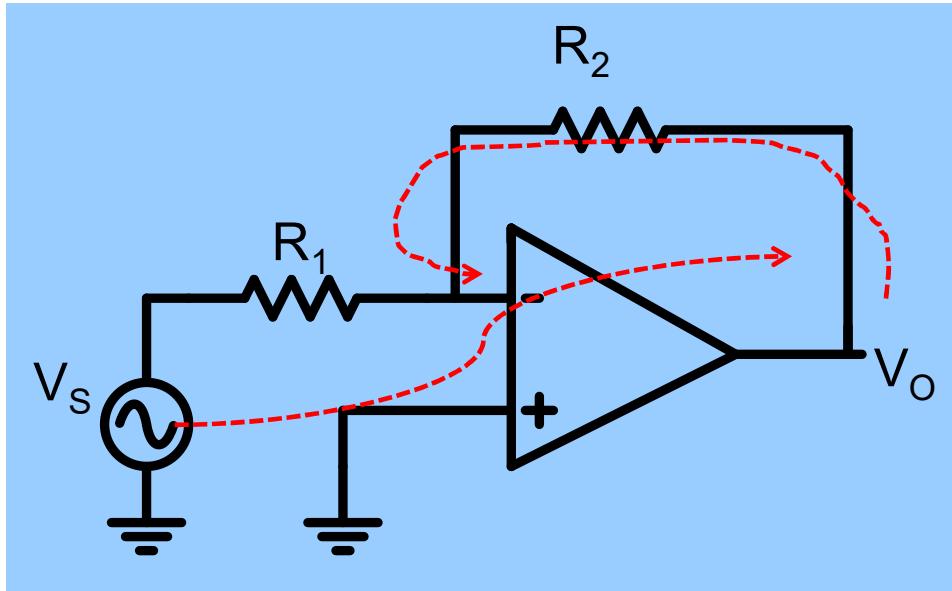


$$\frac{v_o}{v_s} = -\frac{R_2}{R_1}$$



Amplifier has feedback

If the feedback signal helps the input voltage we have positive feedback, otherwise negative.



Feedback

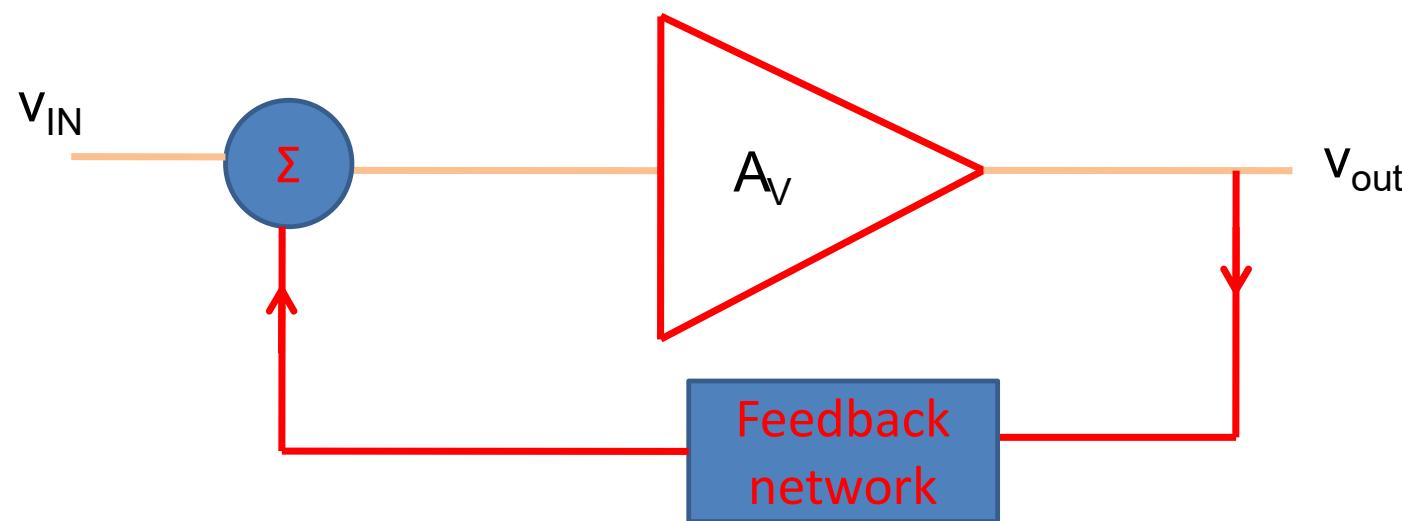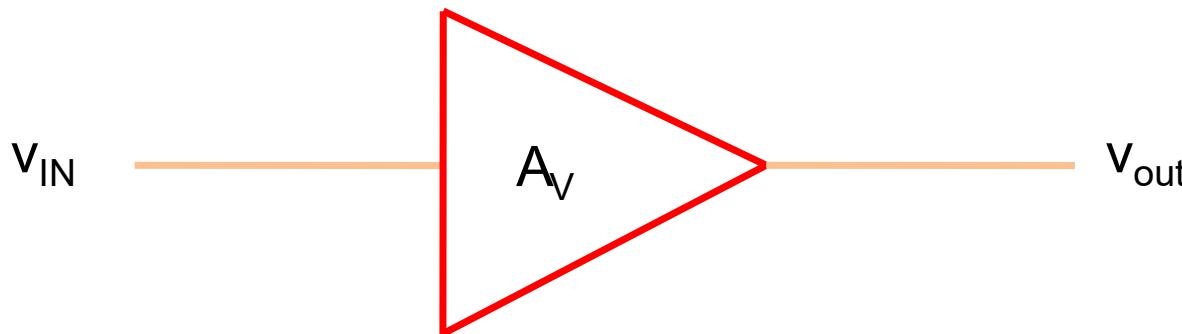


Negative and Positive feedback

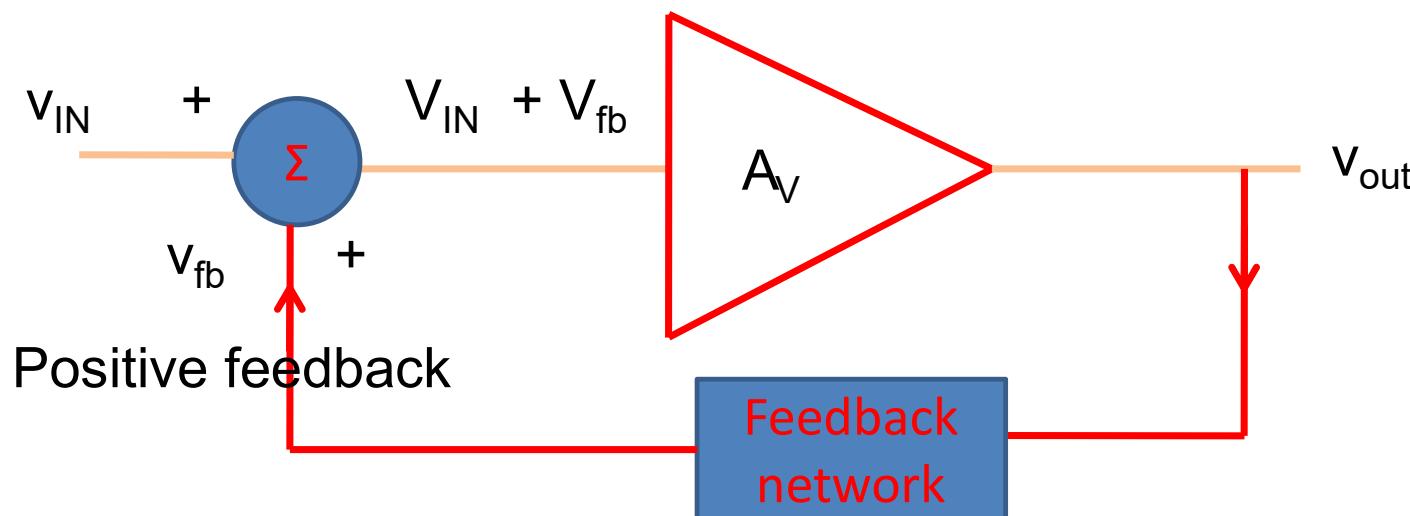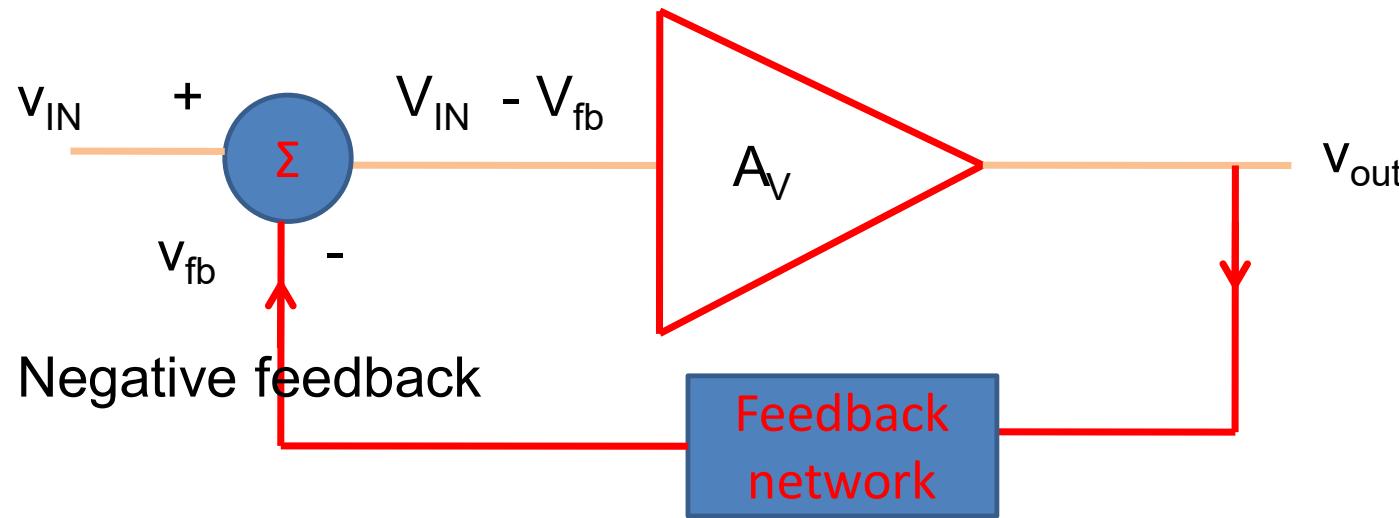

Negative and positive feedback



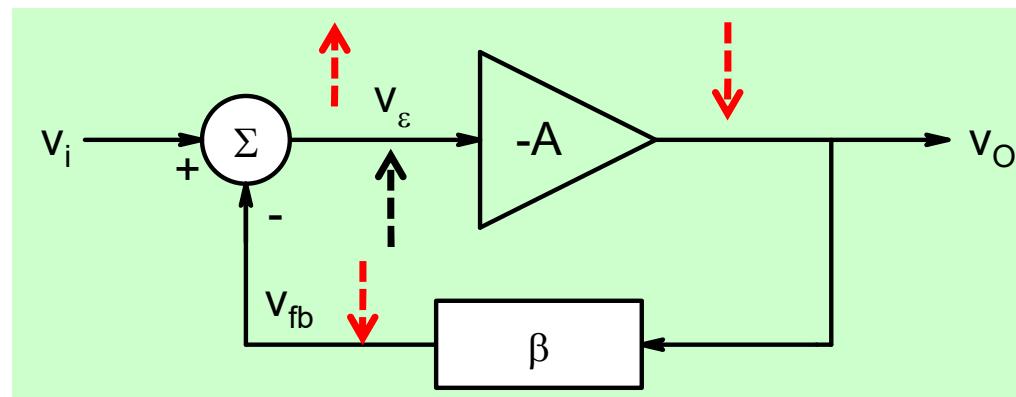
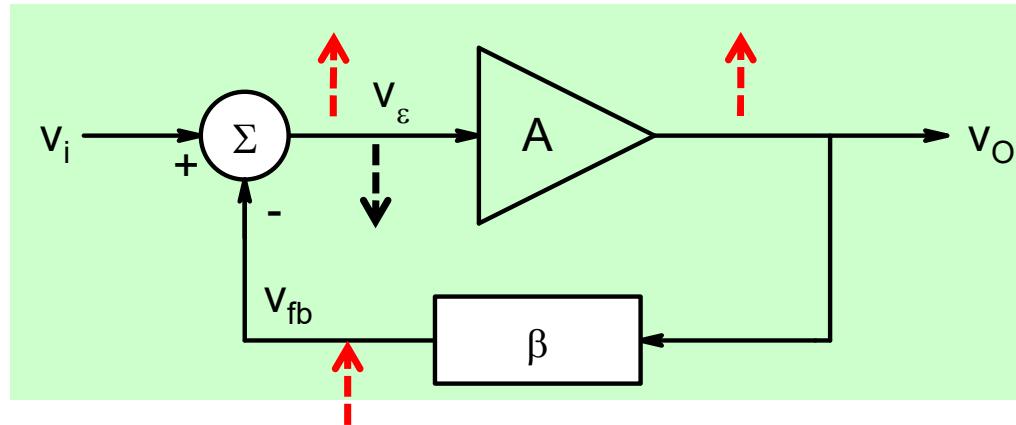



Opamp circuits classification

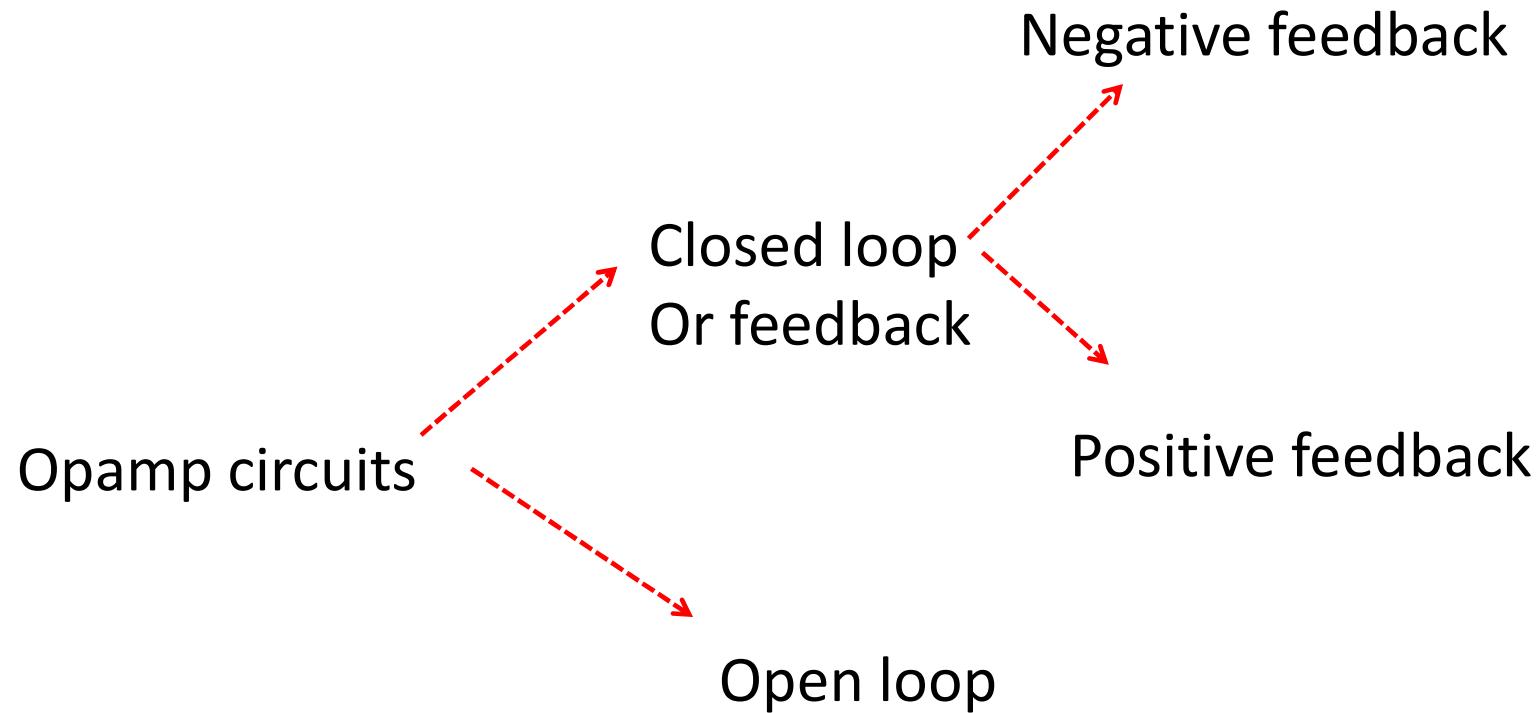

Most Opamp Circuits employ negative feedback

Inverting amplifier

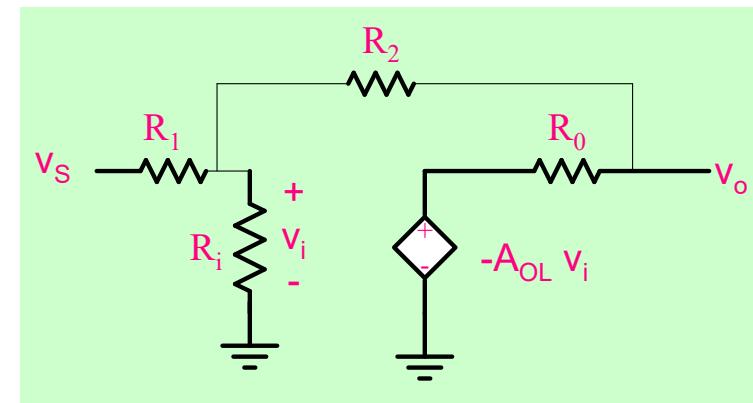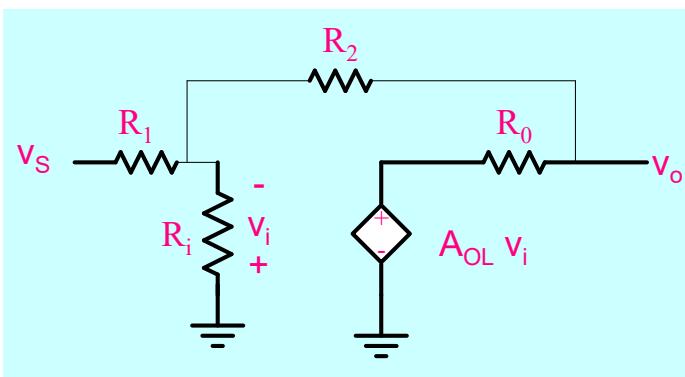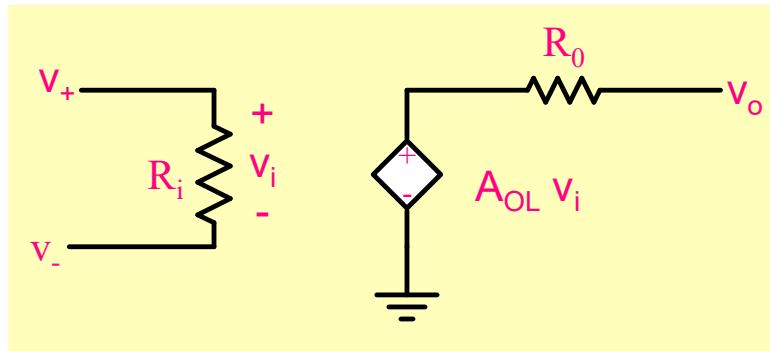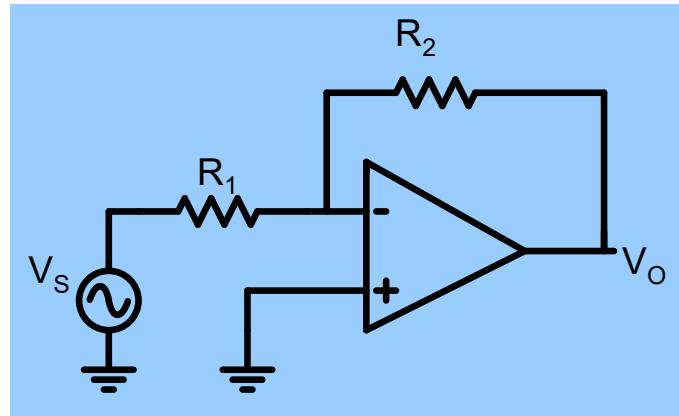

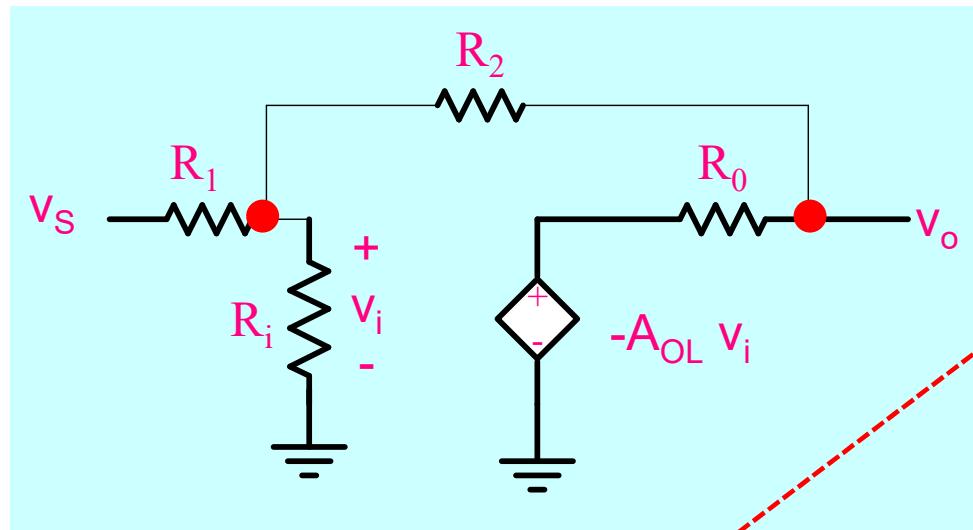

Nodal Analysis

$$\frac{v_s - v_i}{R_1} = \frac{v_i}{R_i} + \frac{v_i - v_o}{R_2} \quad (1)$$


$$\frac{-A_{OL}v_i - v_o}{R_o} = \frac{v_o - v_i}{R_2} \quad (2)$$

$$v_i = v_o \frac{\frac{1}{R_o} + \frac{1}{R_2}}{\frac{-A_{OL}}{R_o} + \frac{1}{R_2}} \quad (4)$$

$$\frac{v_s}{R_1} = -\frac{v_o}{R_2} + v_i \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_o} \right) \quad (3)$$

As $A_{OL} \rightarrow \infty$ $v_i \rightarrow 0$


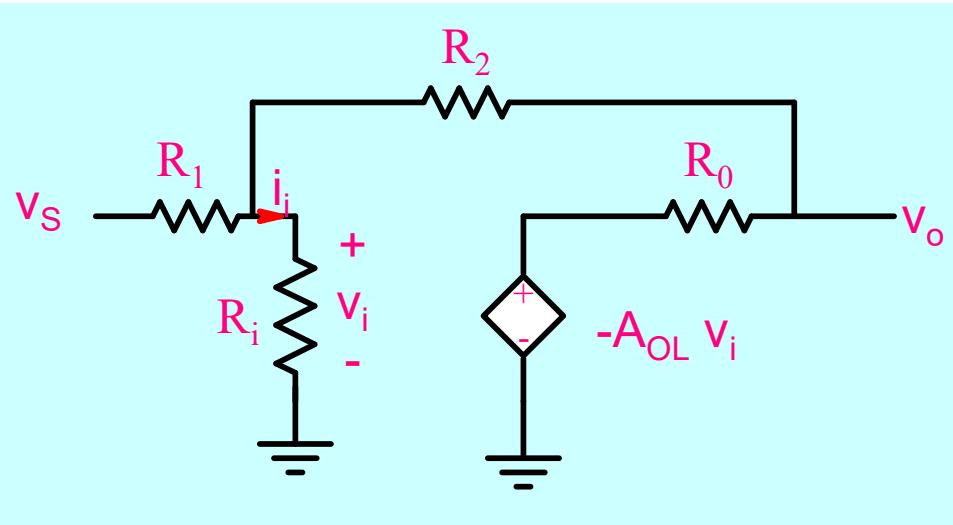
This is called the **Virtual Ground** property





As $A_{OL} \rightarrow \infty$ $v_i \rightarrow 0$

This implies that : $i_i \rightarrow 0$

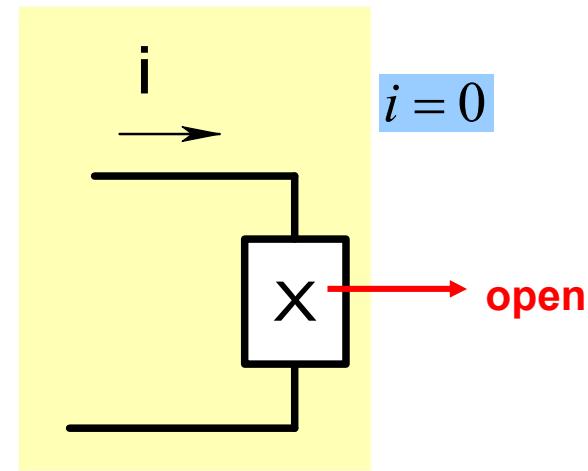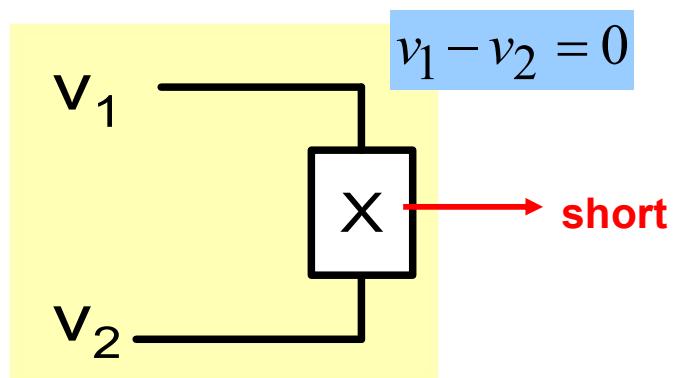No current flows in or out of either inverting or non-inverting terminals of an ideal opamp




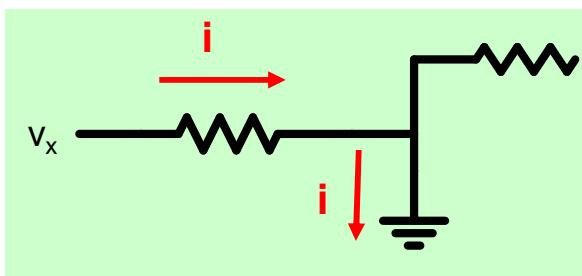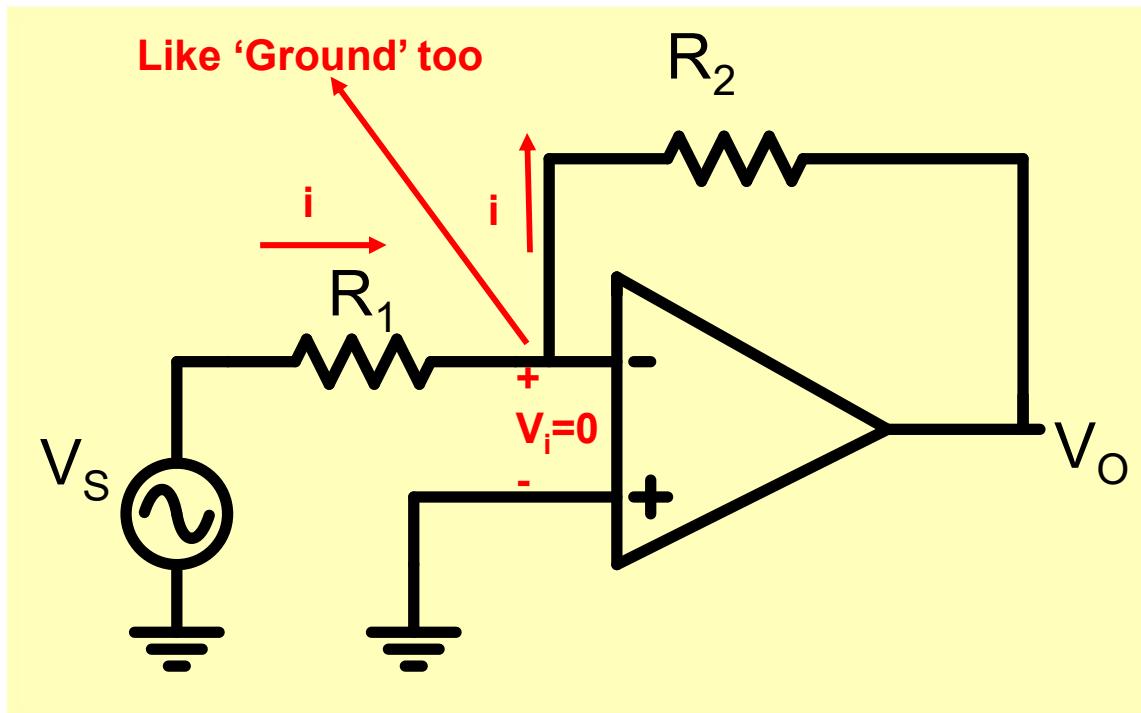Can something be both a short as well as open circuit ?



Hence the name Virtual ground

Virtual Ground Property

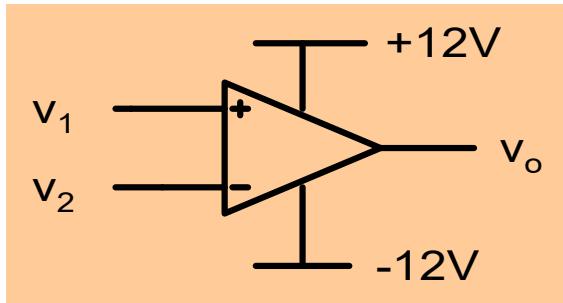


$$v_1 \approx v_2$$

In an opamp with **negative feedback**, the voltage of the inverting terminal is equal to the voltage of the non-inverting terminal if the **gain of the opamp is sufficiently high**

This property **does not** hold under certain conditions such as

- open loop,
- positive feedback
- or if the opamp is saturated.

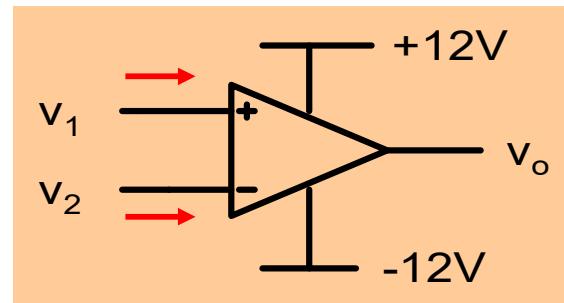Two important property for analyzing ideal opamp circuits under negative feedback




$$1. \quad v_1 = v_2$$

$$2. \quad i_1 = i_2 = 0$$

At the input side opamp appears to be like a short and an open circuit simultaneously !

Inverting amplifier

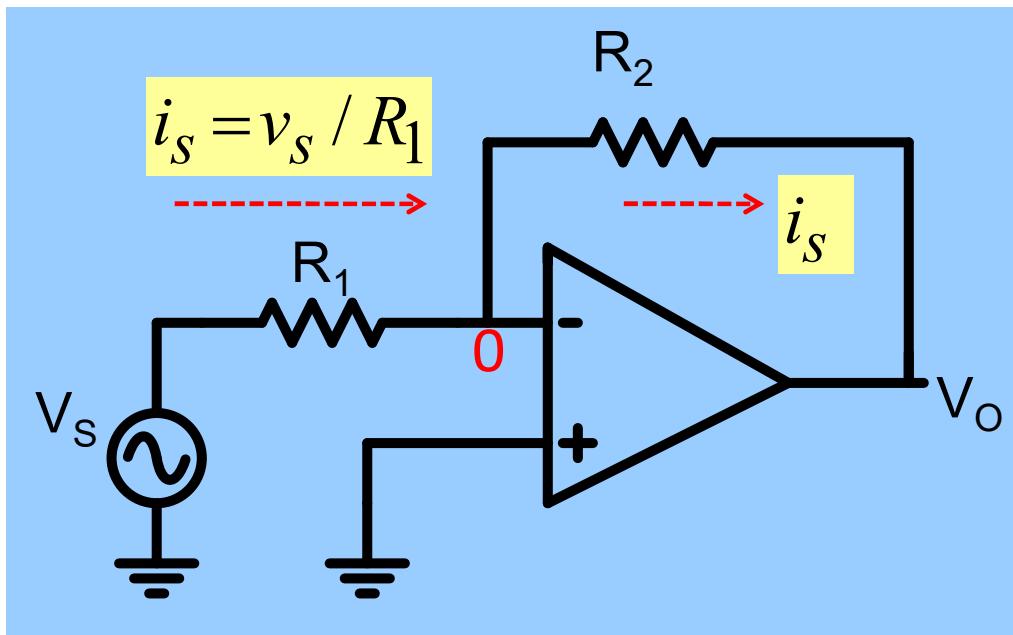Re-analyze inverting amplifier with these properties




$$\frac{0 - v_o}{R_2} = i_s = \frac{v_s}{R_1}$$

$$\frac{v_o}{v_s} = -\frac{R_2}{R_1}$$

Non-Inverting Amplifier

$$1. \quad v_1 = v_2$$


$$2. \quad i_1 = i_2 = 0$$

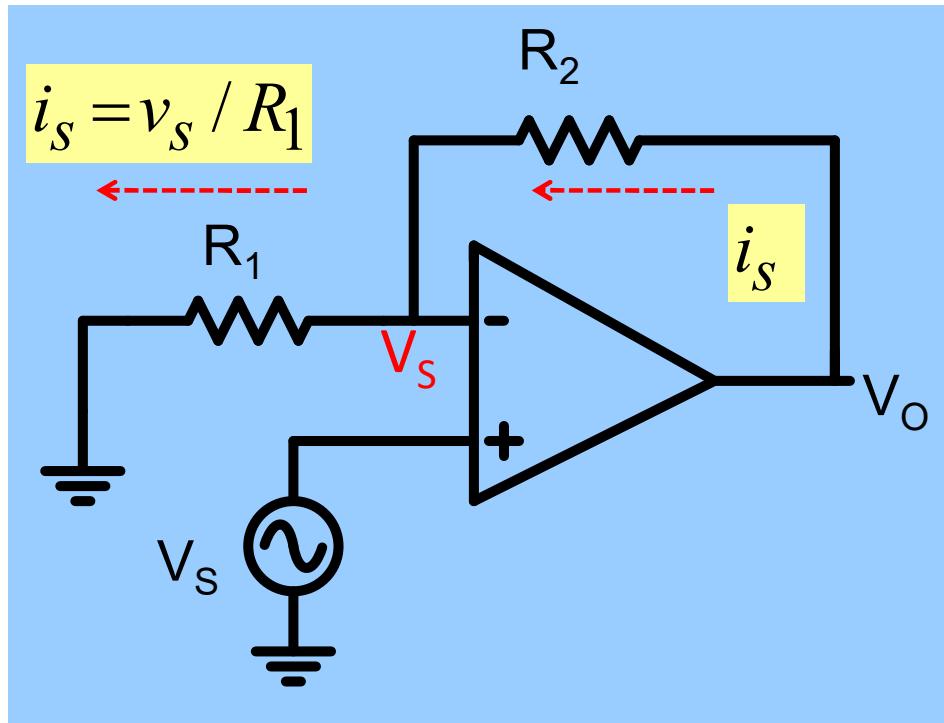


$$\frac{v_o - v_s}{R_2} = i_s = \frac{v_s}{R_1}$$

$$\frac{v_o}{v_s} = 1 + \frac{R_2}{R_1}$$


Examples

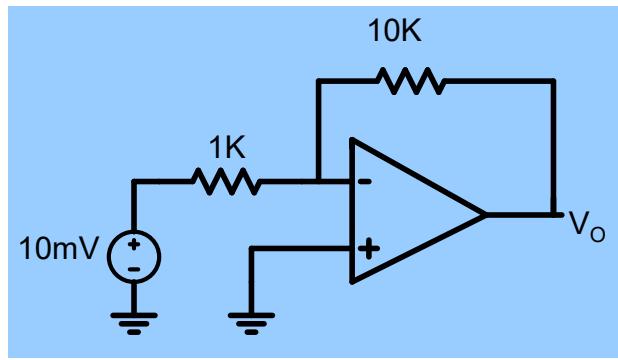
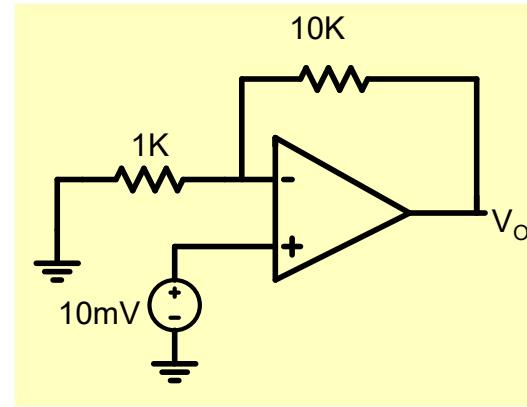
$$\frac{v_o}{v_s} = -\frac{R_2}{R_1} \Rightarrow v_o = -100mV$$



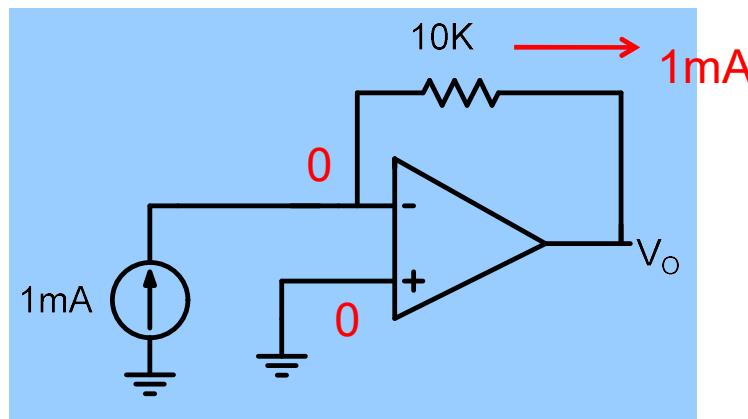
$$\frac{v_o}{v_s} = 1 + \frac{R_2}{R_1} \Rightarrow v_o = 110mV$$



$$\frac{0 - v_o}{10K} = 1mA$$

$$v_o = -10V$$

Adder


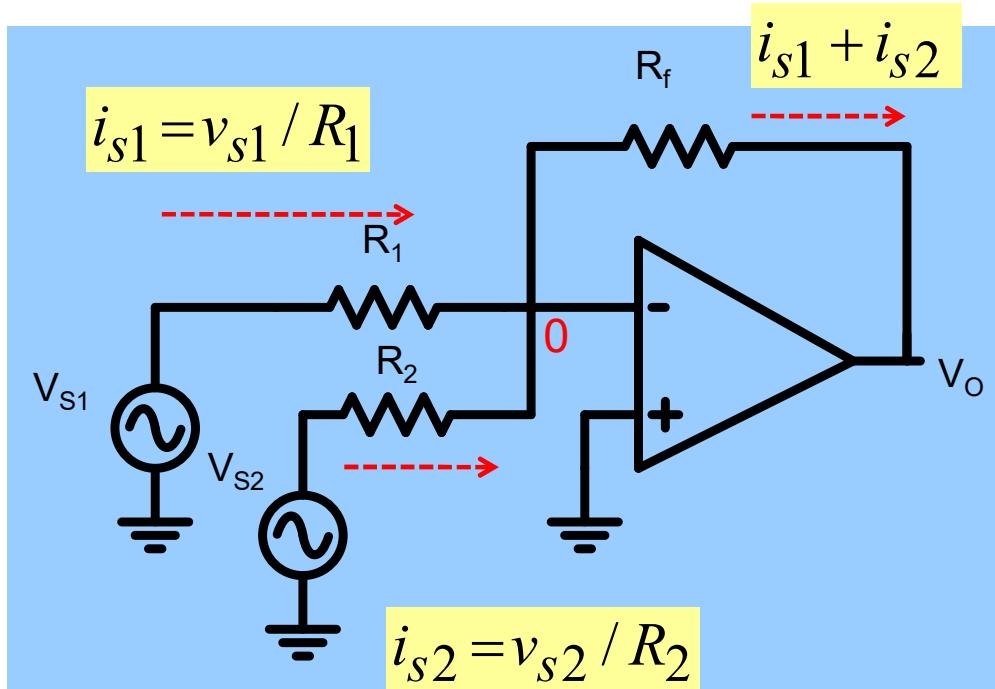


$$\frac{0 - v_o}{R_f} = i_{s1} + i_{s2} = \frac{v_{s1}}{R_1} + \frac{v_{s2}}{R_2}$$


$$v_o = -\left(\frac{R_f}{R_1}v_{s1} + \frac{R_f}{R_2}v_{s2}\right)$$

For $R_1 = R_2 = R$ $v_o = -\frac{R_f}{R}(v_{s1} + v_{s2})$

Alternative Analysis

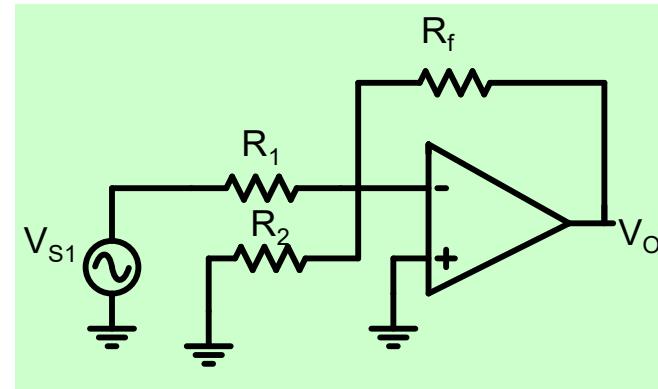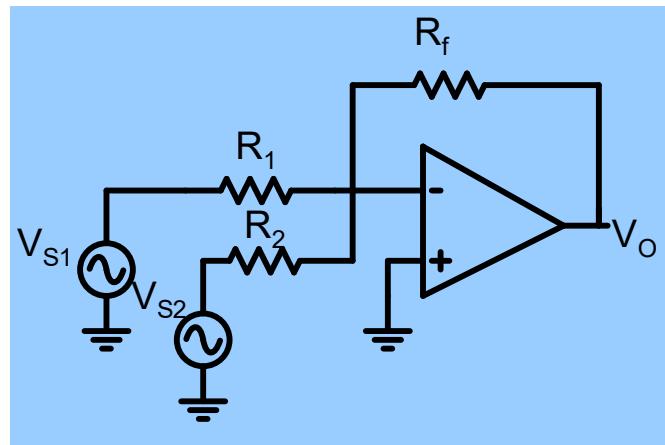

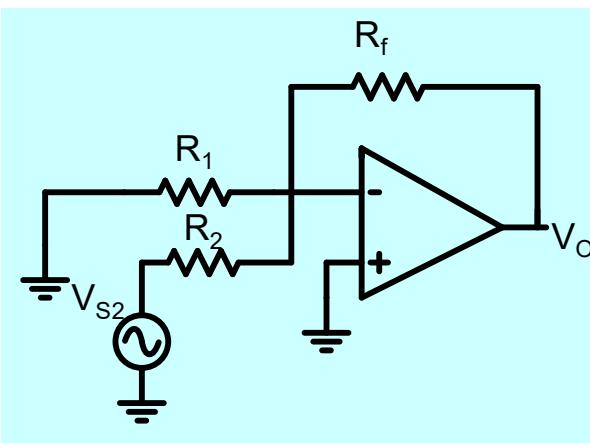
$$v_o = -\left(\frac{R_f}{R_1}\right)v_{s1} + -\left(\frac{R_f}{R_2}\right)v_{s2}$$




Design Example

Design a circuit that would generate the following output given three input voltages v_{s1} , v_{s2} and v_{s3} .

$$v_o = -10v_{s1} - 4v_{s2} - 5v_{s3}$$

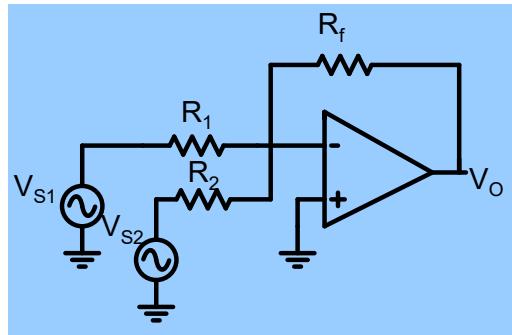
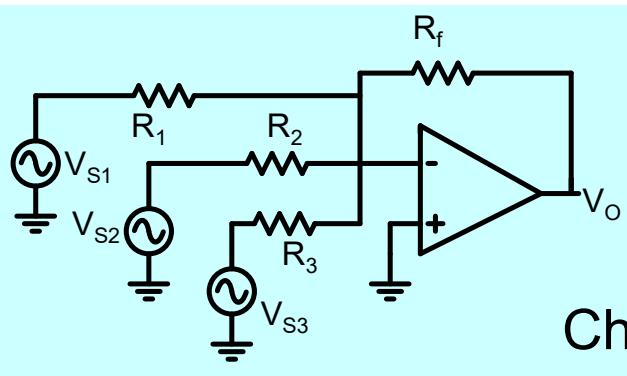
$$v_o = -\frac{R_f}{R_1}v_{s1} - \frac{R_f}{R_2}v_{s2}$$



$$v_o = -\frac{R_f}{R_1}v_{s1} - \frac{R_f}{R_2}v_{s2} - \frac{R_f}{R_3}v_{s3}$$




Choose : $R_f = 10K$

$$\Rightarrow R_1 = 1K$$

$$\Rightarrow R_2 = 2.5K$$

$$\Rightarrow R_3 = 2K$$


Adder

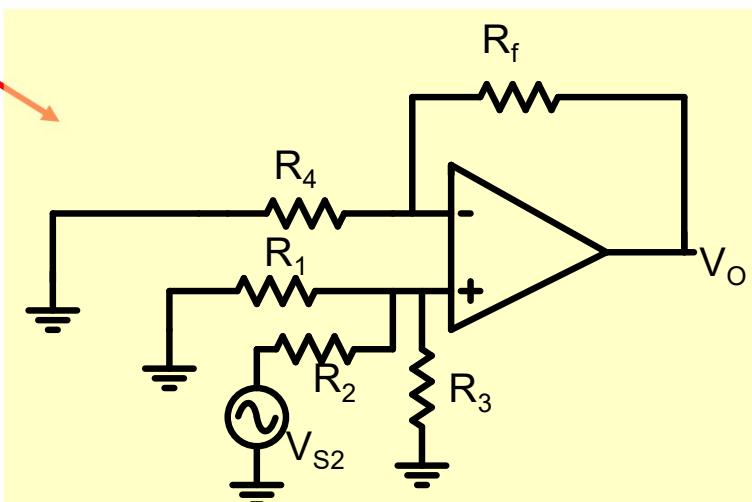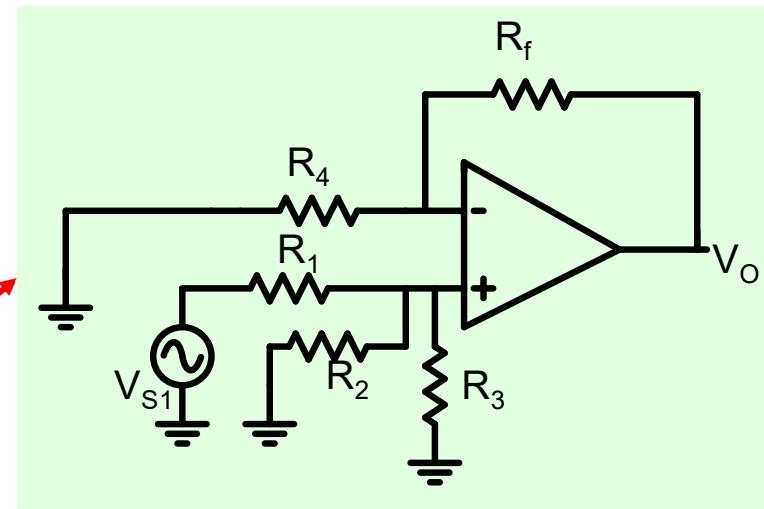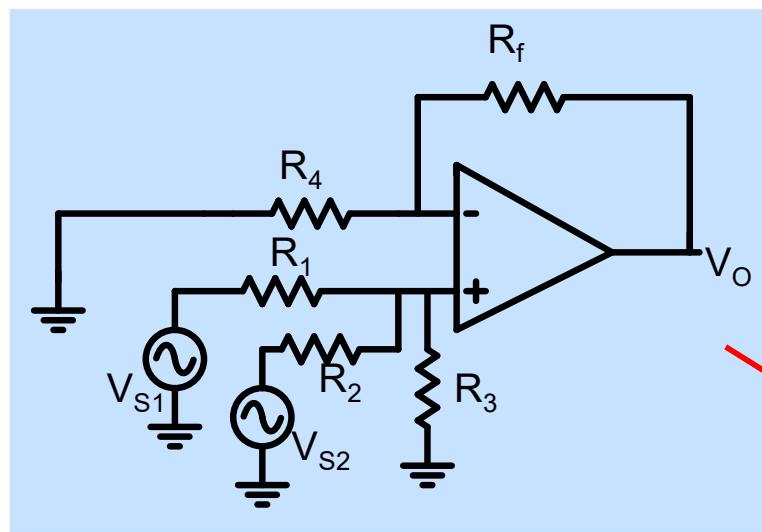

$$v_o = v_{s1} \frac{R_2 \| R_3}{R_2 \| R_3 + R_1} \times \left(1 + \frac{R_f}{R_4}\right)$$

$$+ v_{s2} \frac{R_1 \| R_3}{R_1 \| R_3 + R_2} \times \left(1 + \frac{R_f}{R_4}\right)$$

Adder

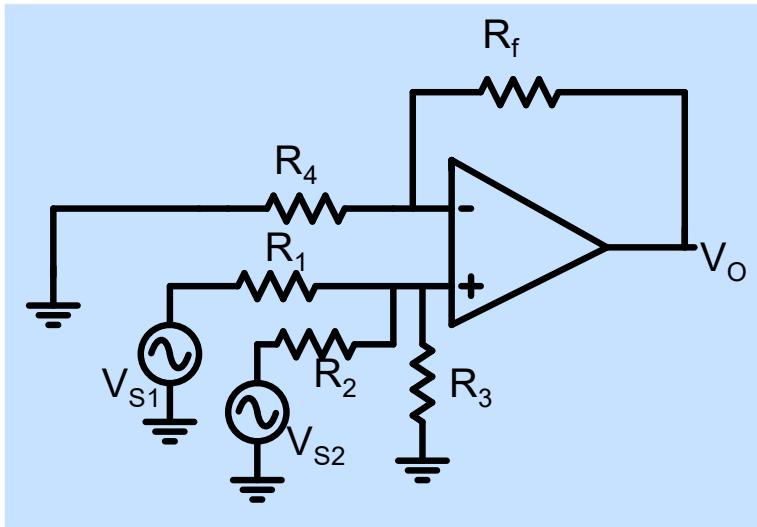

$$v_o = v_{s1} \frac{R_2 \| R_3}{R_2 \| R_3 + R_1} \times \left(1 + \frac{R_f}{R_4}\right)$$

$$+ v_{s2} \frac{R_1 \| R_3}{R_1 \| R_3 + R_2} \times \left(1 + \frac{R_f}{R_4}\right)$$

High entropy expression !

$$R_P = R_1 \| R_2 \| R_3$$


$$v_o = \left(\frac{R_p}{R_1} v_{s1} + \frac{R_p}{R_2} v_{s2} \right) \times \left(1 + \frac{R_f}{R_4}\right)$$

Low entropy expression !

Design Example

Design a circuit that would generate the following output given three input voltages v_{s1} , v_{s2} and v_{s3} .


$$v_o = 10v_{s1} + 4v_{s2}$$

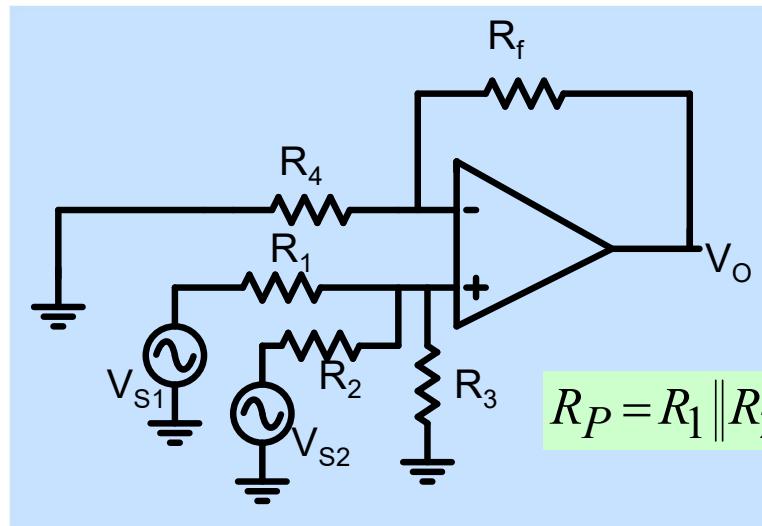


$$v_o = \left(\frac{R_p}{R_1} v_{s1} + \frac{R_p}{R_2} v_{s2} \right) \times \left(1 + \frac{R_f}{R_4} \right)$$

$$R_p = R_1 \parallel R_2 \parallel R_3$$

Homework problem !

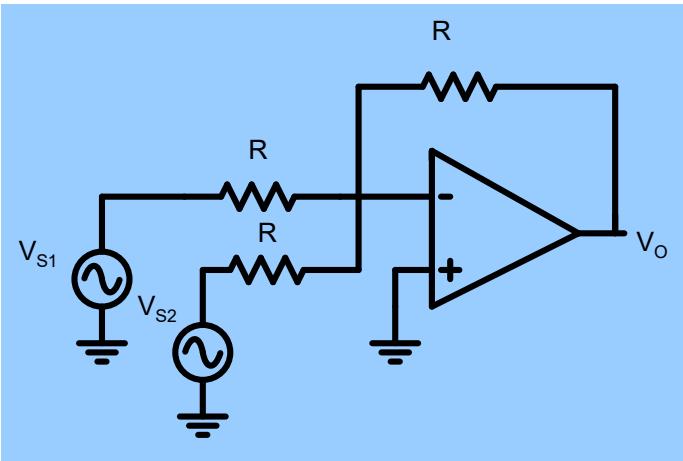

$$v_o = -(v_{s1} + v_{s2})$$

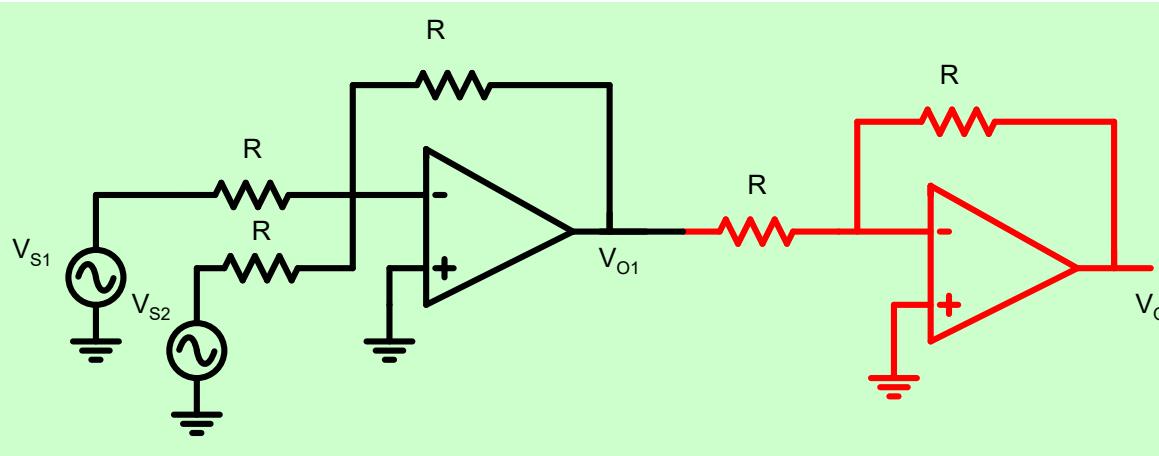



$$v_{o1} = -(v_{s1} + v_{s2})$$

$$v_o = -v_{o1}$$

$$v_o = (v_{s1} + v_{s2})$$

Have we made some assumption here ?

Example

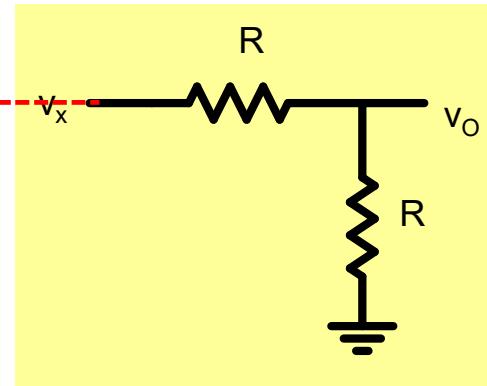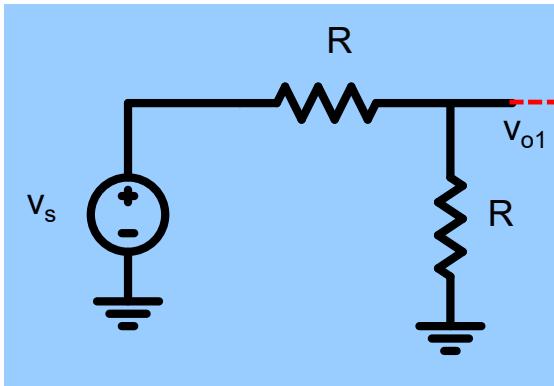

$$\frac{v_{o1}}{v_s} = 0.5$$


$$\frac{v_o}{v_x} = 0.5$$

$$v_{o1} = v_x$$

$$\frac{v_o}{v_x} = \frac{v_o}{v_{o1}} = 0.5$$


$$\frac{v_o}{v_s} = \frac{v_o}{v_{o1}} \times \frac{v_{o1}}{v_s} = 0.5 \times 0.5 = 0.25$$

BUT

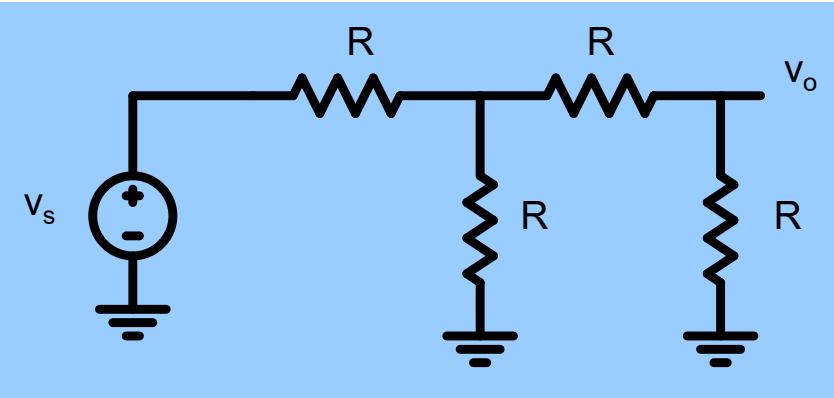


$$\frac{v_o}{v_s} = 0.2$$

Where is the error ?

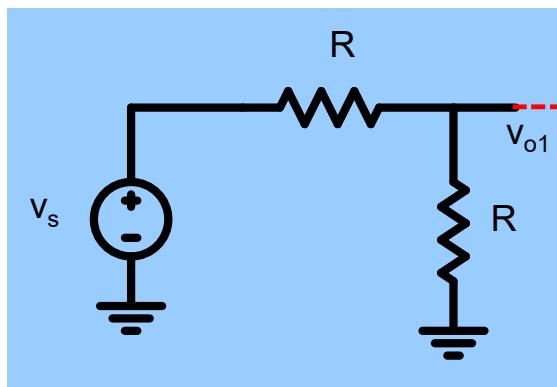

$$v_{o1} = v_x$$

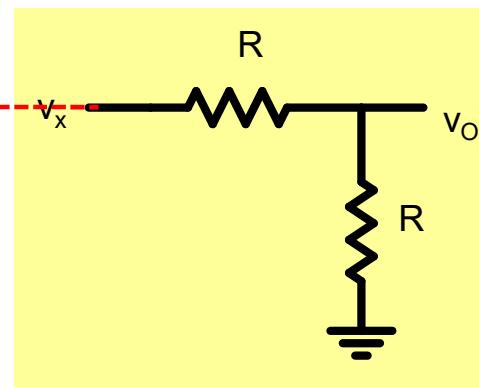


$$\frac{v_{o1}}{v_s} = 0.5$$

$$\frac{v_{o1}}{v_s} \neq 0.5$$

$$\frac{v_o}{v_x} = 0.5$$

Circuit-1 gets 'loaded' by circuit-2 and its output vs. input characteristics get modified.



Loading Effect

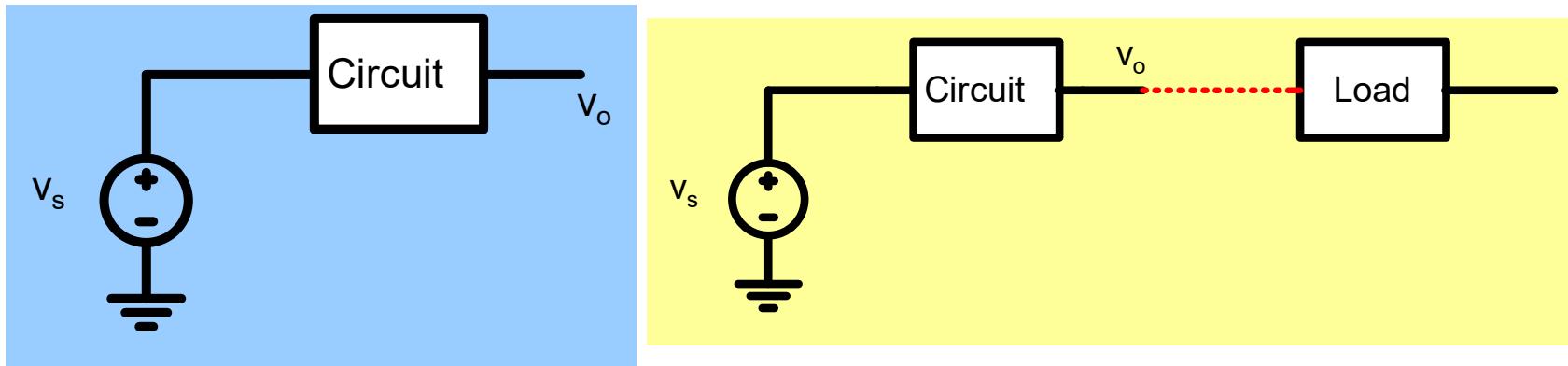

V_o in general gets altered when we connect a load to it

Under what conditions is change in V_o small upon connection of a load ?


Example

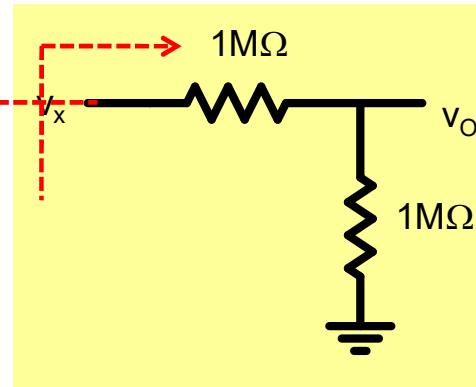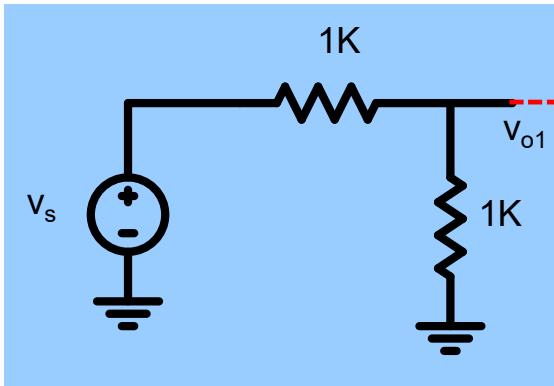

$$\frac{v_{o1}}{v_s} = 0.5$$

$$\frac{v_{o1}}{v_s} \approx 0.5$$

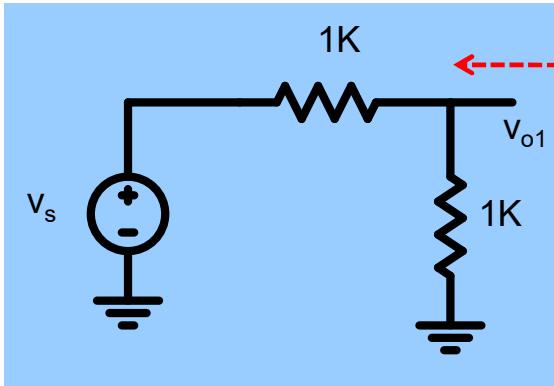We can describe this effect in terms of output resistance




$$R_o = 0.5K$$

$$R_L = 2M\Omega$$


Loading Effect

Whenever output resistance of a circuit is much smaller than the load resistance, the loading effect is minimal.

$$R_o \ll R_L$$

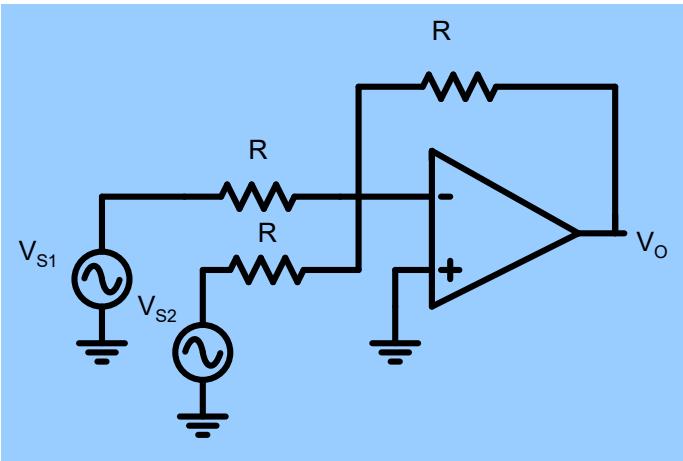

$$v_o = -(v_{s1} + v_{s2})$$

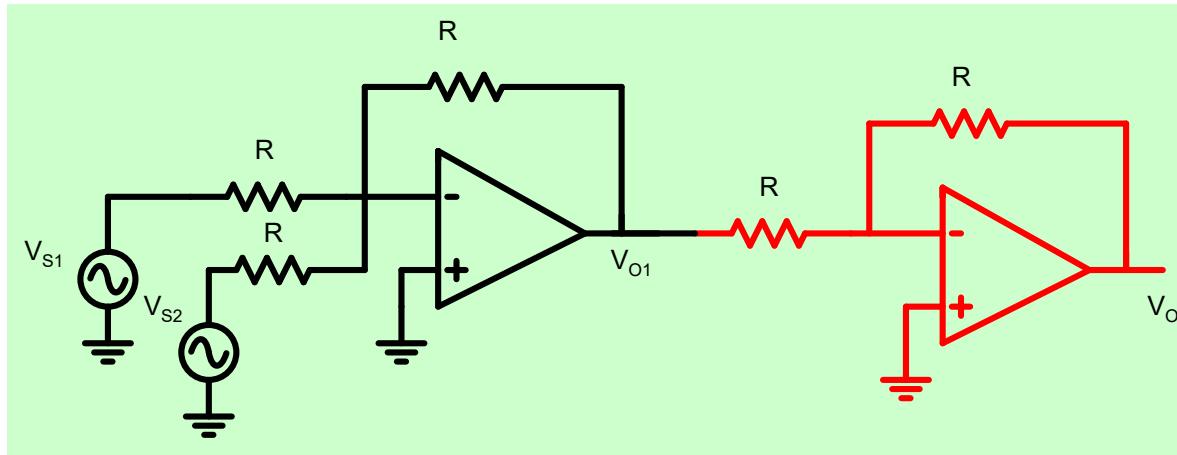


$$v_{o1} = -(v_{s1} + v_{s2})$$

$$v_o = -v_{o1}$$

$$v_o = (v_{s1} + v_{s2})$$

The assumption made here is that there is no loading which is reasonable because opamps have very low resistance


Example

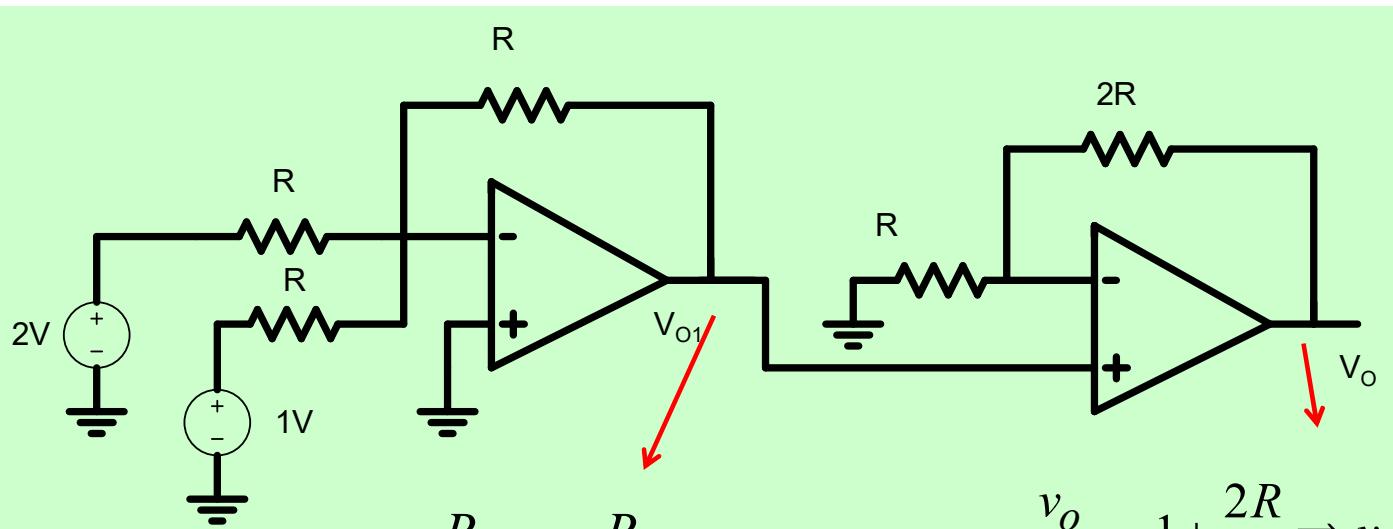

$$v_{o1} = -\left\{ \frac{R}{R} \times 1 + \frac{R}{R} \times 2 \right\} = -3V$$


$$\frac{v_o}{v_{o1}} = 1 + \frac{2R}{R} \Rightarrow v_o = -9V$$

Subtractor

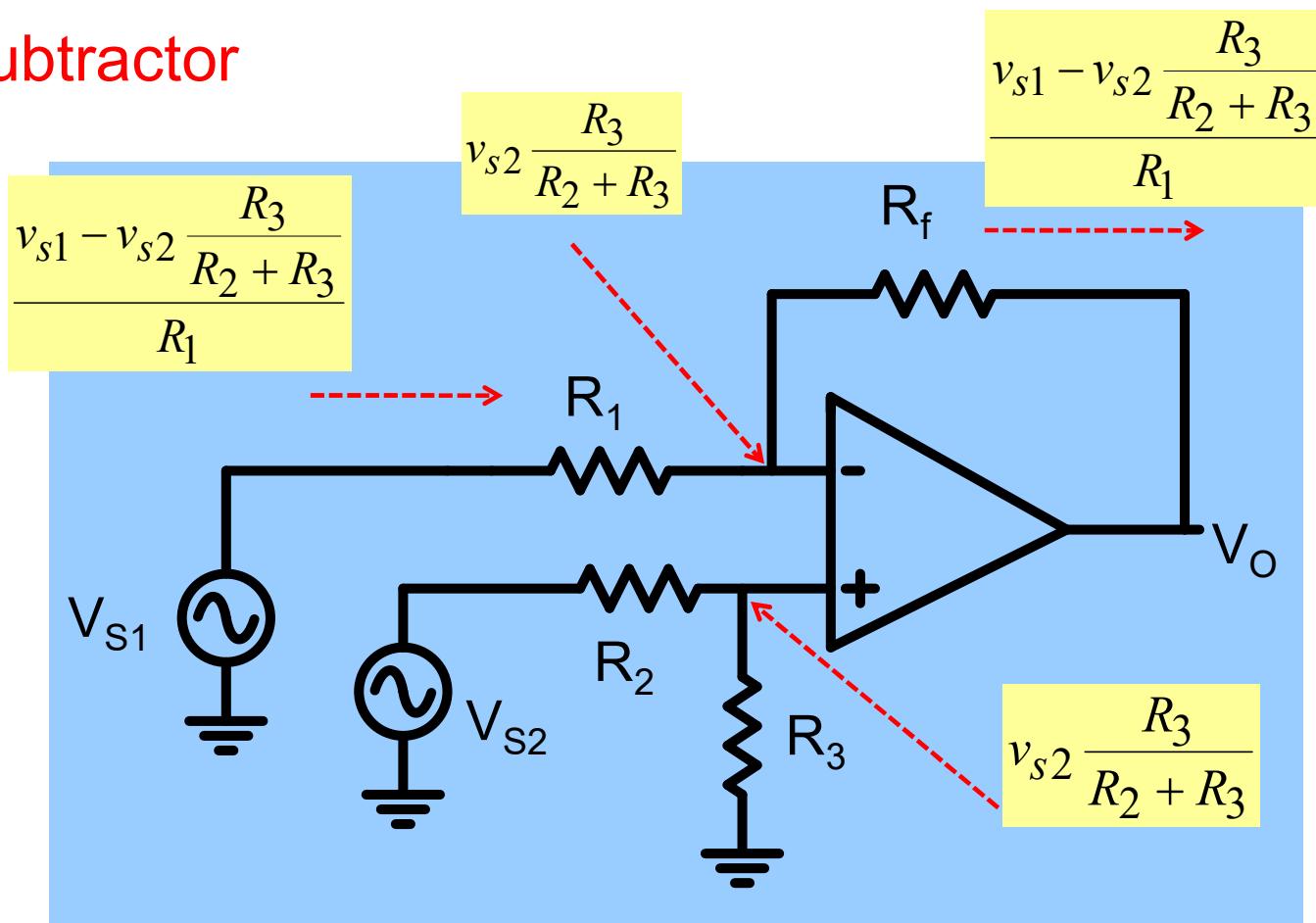

$$\frac{v_{s2} \frac{R_3}{R_2 + R_3} - v_o}{R_f} = \frac{v_{s1} - v_{s2} \frac{R_3}{R_2 + R_3}}{R_1}$$
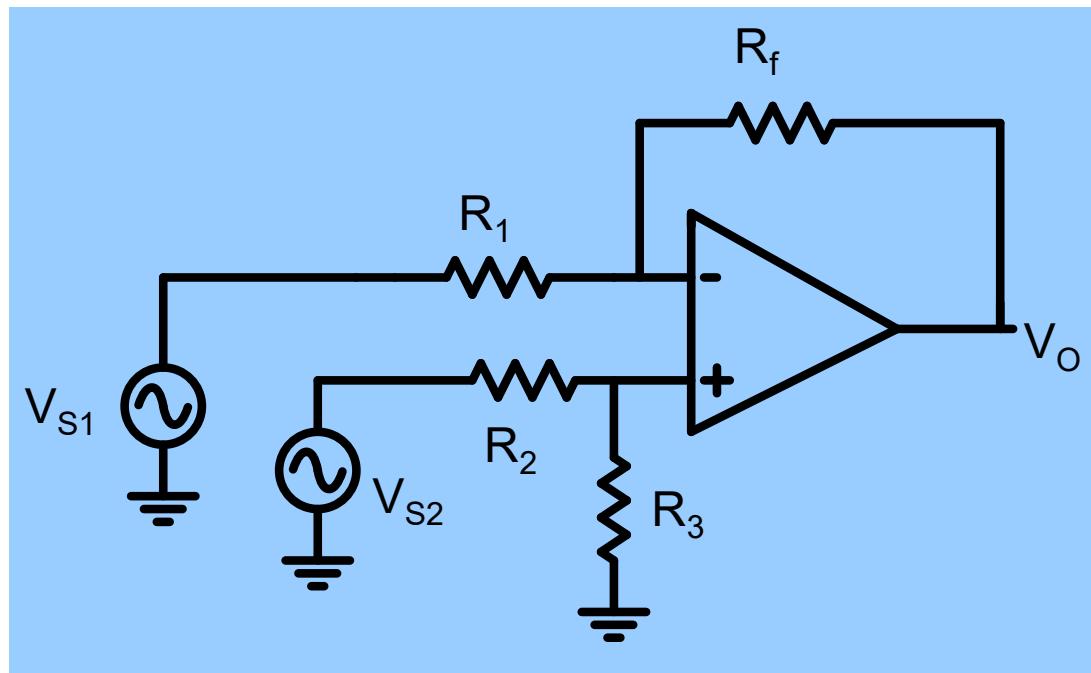
$$v_o = v_{s2} \frac{\frac{R_3}{R_2}}{(1 + \frac{R_3}{R_2})} (1 + \frac{R_f}{R_1}) - (\frac{R_f}{R_1}) v_{s1}$$




$$v_o = v_{s2} \frac{\frac{R_3}{R_2}}{\left(1 + \frac{R_3}{R_2}\right)} \left(1 + \frac{R_f}{R_1}\right) - \left(\frac{R_f}{R_1}\right) v_{s1}$$

Choose $\frac{R_3}{R_2} = \frac{R_f}{R_1}$


$$v_o = \frac{R_f}{R_1} (v_{s2} - v_{s1})$$

Subtractor: Alternative Analysis

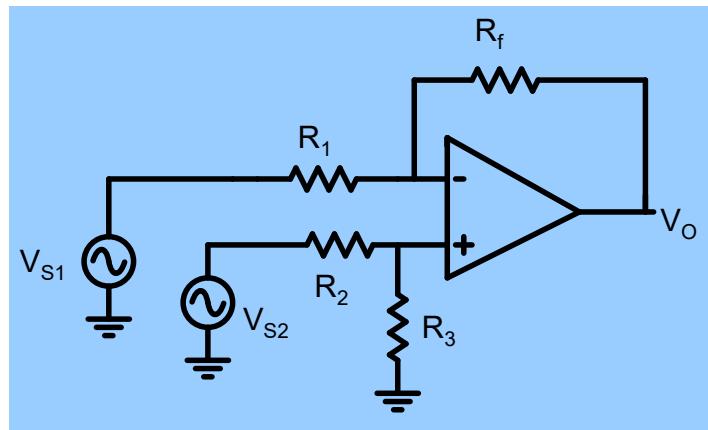


Use superposition theorem
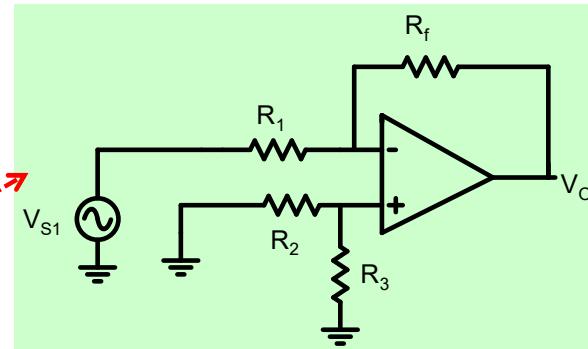
$$v_o = -\left(\frac{R_f}{R_1}\right)v_{s1} + v_{s2} \frac{R_3}{(R_3 + R_2)} \times \left(1 + \frac{R_f}{R_1}\right)$$




Inverting amplifier

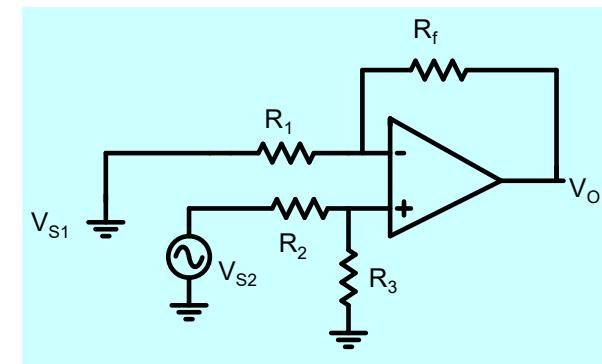

Non-inverting amplifier


Analysis is made simpler by **Re-Using** results derived earlier

Adder/Subtractor

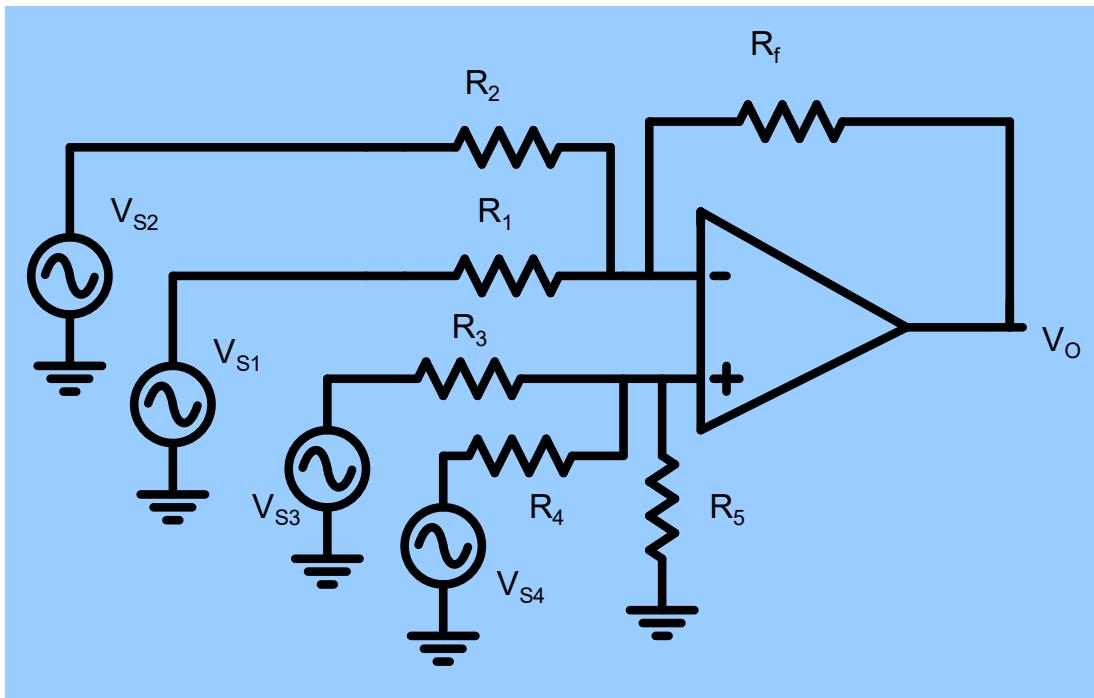


$$v_o = -\left(\frac{R_f}{R_1}\right)v_{s1} + \left(-\frac{R_f}{R_2}\right)v_{s2} + v_{s3} \frac{R_5 \| R_4}{R_5 \| R_4 + R_3} \times \left(1 + \frac{R_f}{R_1 \| R_2}\right)$$
$$+ v_{s4} \frac{R_5 \| R_3}{R_5 \| R_3 + R_4} \times \left(1 + \frac{R_f}{R_1 \| R_2}\right)$$

Adder/Subtractor

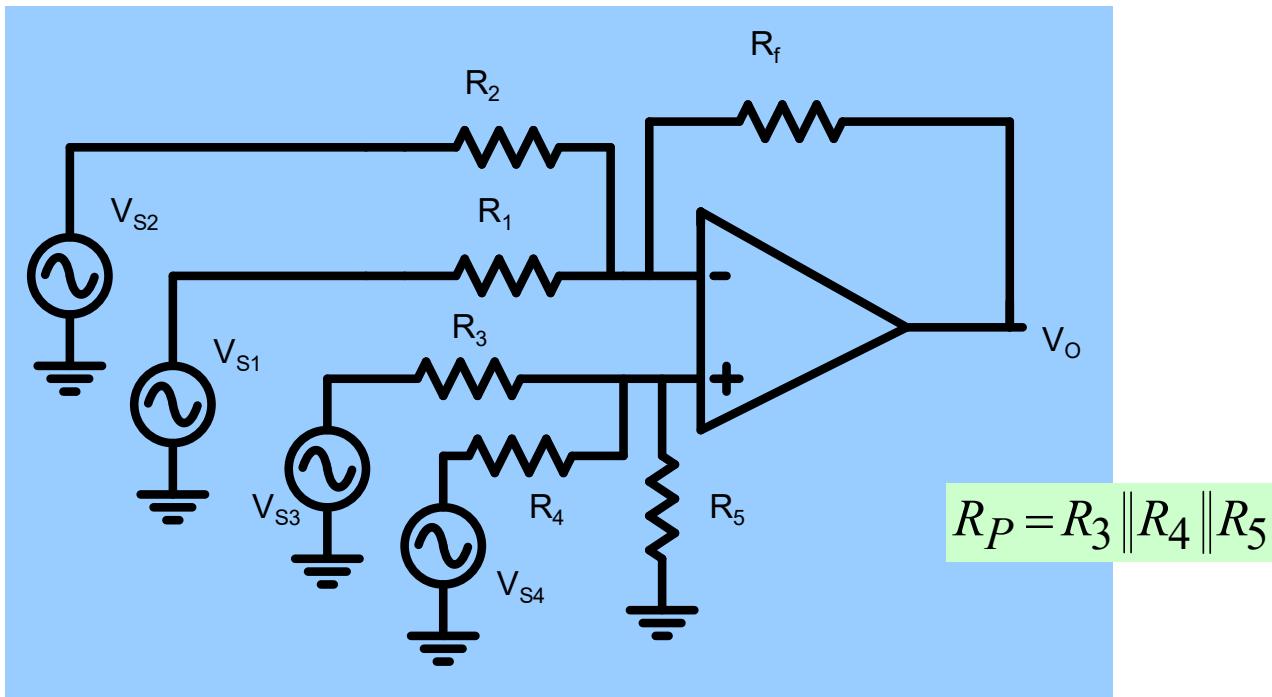

$$\begin{aligned} v_o = & -\left(\frac{R_f}{R_1}\right)v_{s1} + -\left(\frac{R_f}{R_2}\right)v_{s2} + v_{s3} \frac{R_P}{R_3} \times \left(1 + \frac{R_f}{R_1 \parallel R_2}\right) \\ & + v_{s4} \frac{R_P}{R_4} \times \left(1 + \frac{R_f}{R_1 \parallel R_2}\right) \end{aligned}$$

Example

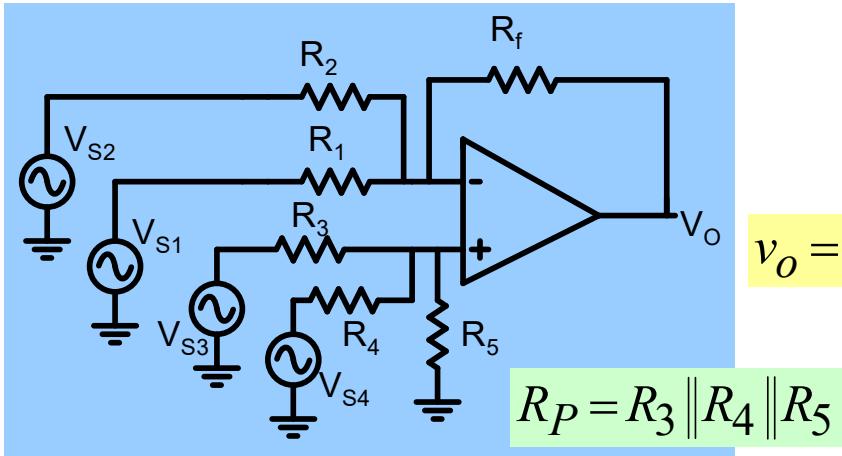

$$v_o = -10v_{s1} - 4v_{s2} + 5v_{s3} + 2v_{s4}$$

$$R_P = R_3 \parallel R_4 \parallel R_5$$

$$v_o = -\left(\frac{R_f}{R_1}\right)v_{s1} - \left(\frac{R_f}{R_2}\right)v_{s2} + \left(1 + \frac{R_f}{R_1 \parallel R_2}\right) \times \frac{R_P}{R_3} v_{s3} + \left(1 + \frac{R_f}{R_1 \parallel R_2}\right) \times \frac{R_P}{R_4} v_{s4}$$

Choose : $R_f = 10K$ $\Rightarrow R_1 = 1K$ $\Rightarrow R_2 = 2.5K$

$$\Rightarrow \frac{R_P}{R_3} = 0.33$$

$$\Rightarrow \frac{R_P}{R_4} = 0.133$$

$$\Rightarrow \frac{R_4}{R_3} = 2.5$$



Choose : $R_3 = 1K$ $\Rightarrow R_4 = 2.5K$ $\Rightarrow R_P = 0.33K$ $\Rightarrow R_5 = 0.625K$

ESC201T : Introduction to Electronics

Lecture 30: Operational Amplifier Circuits-2

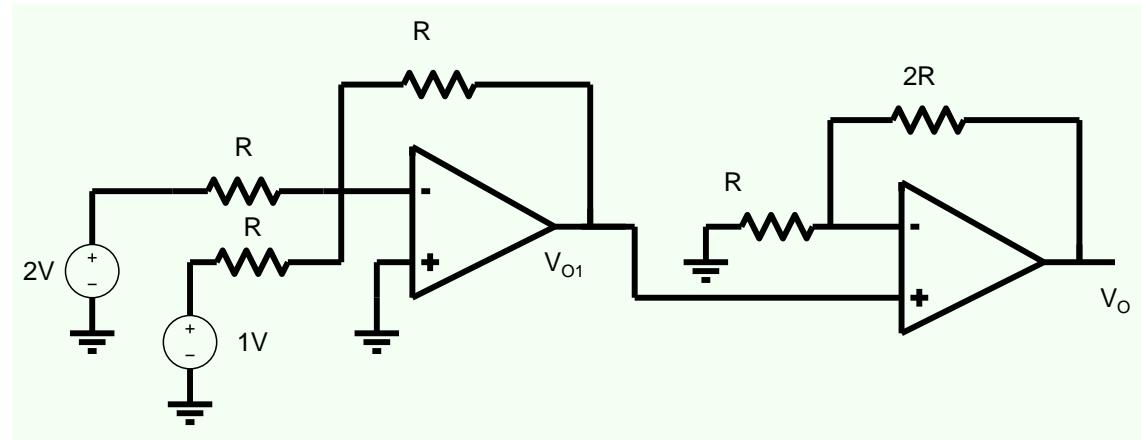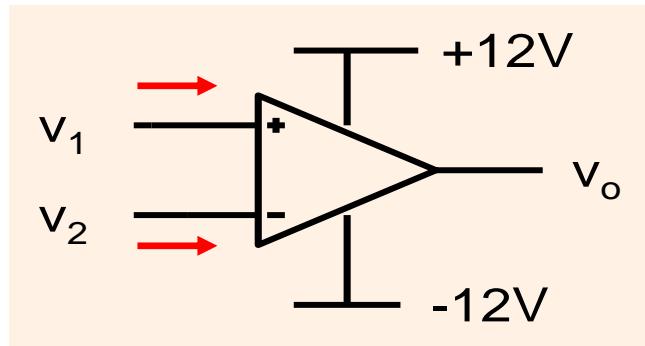B. Mazhari
Dept. of EE, IIT Kanpur

Important properties for analyzing ideal opamp circuits under negative feedback




$$1. \quad v_1 = v_2$$

$$2. \quad i_1 = i_2 = 0$$

One stage does not load the preceding stage due to very small output impedance of the opamp


Adder/Subtractor

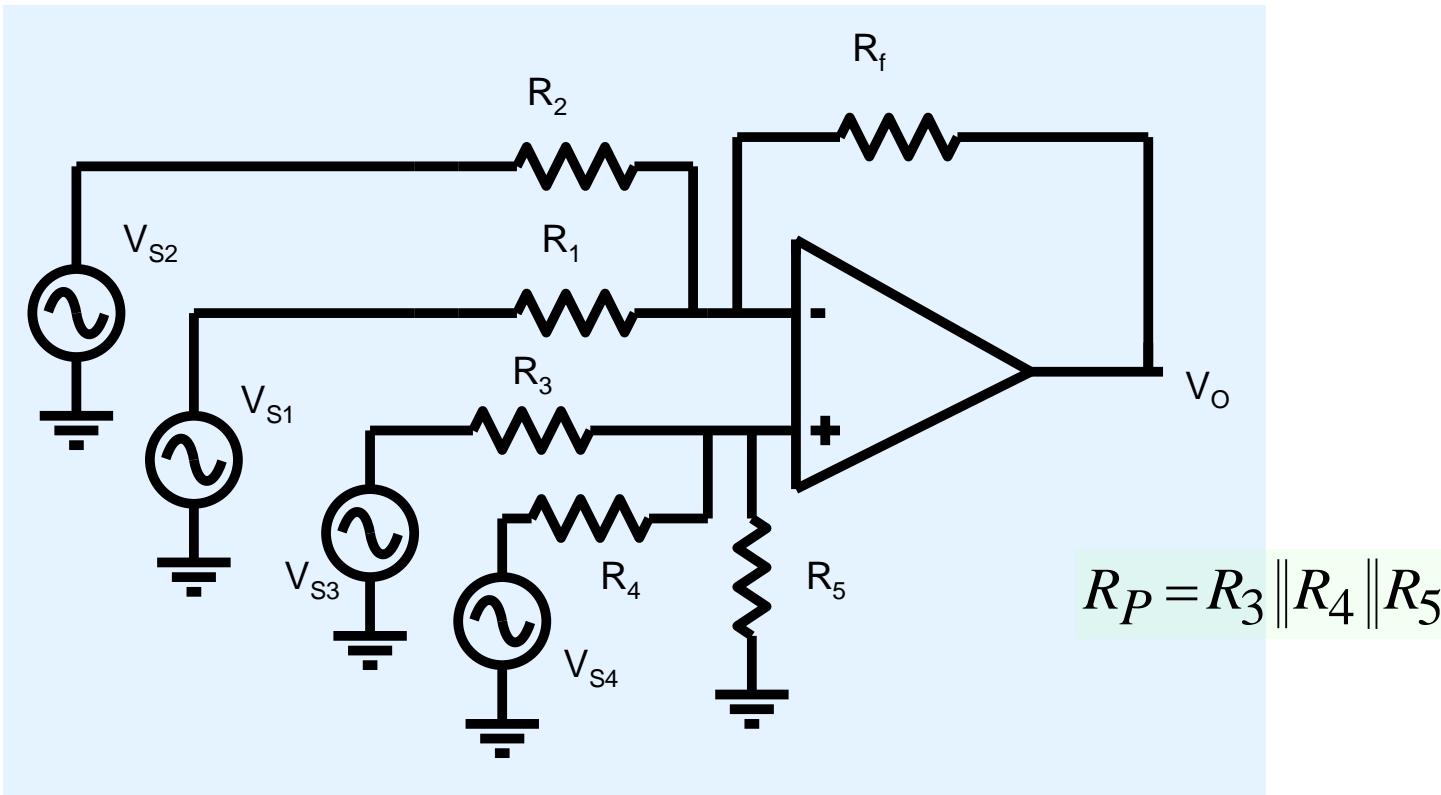

$$v_o = -\left(\frac{R_f}{R_1}\right)v_{s1} + -\left(\frac{R_f}{R_2}\right)v_{s2} + v_{s3} \frac{R_P}{R_3} \times \left(1 + \frac{R_f}{R_1 \parallel R_2}\right)$$


$$+ v_{s4} \frac{R_P}{R_4} \times \left(1 + \frac{R_f}{R_1 \parallel R_2}\right)$$

Integrator

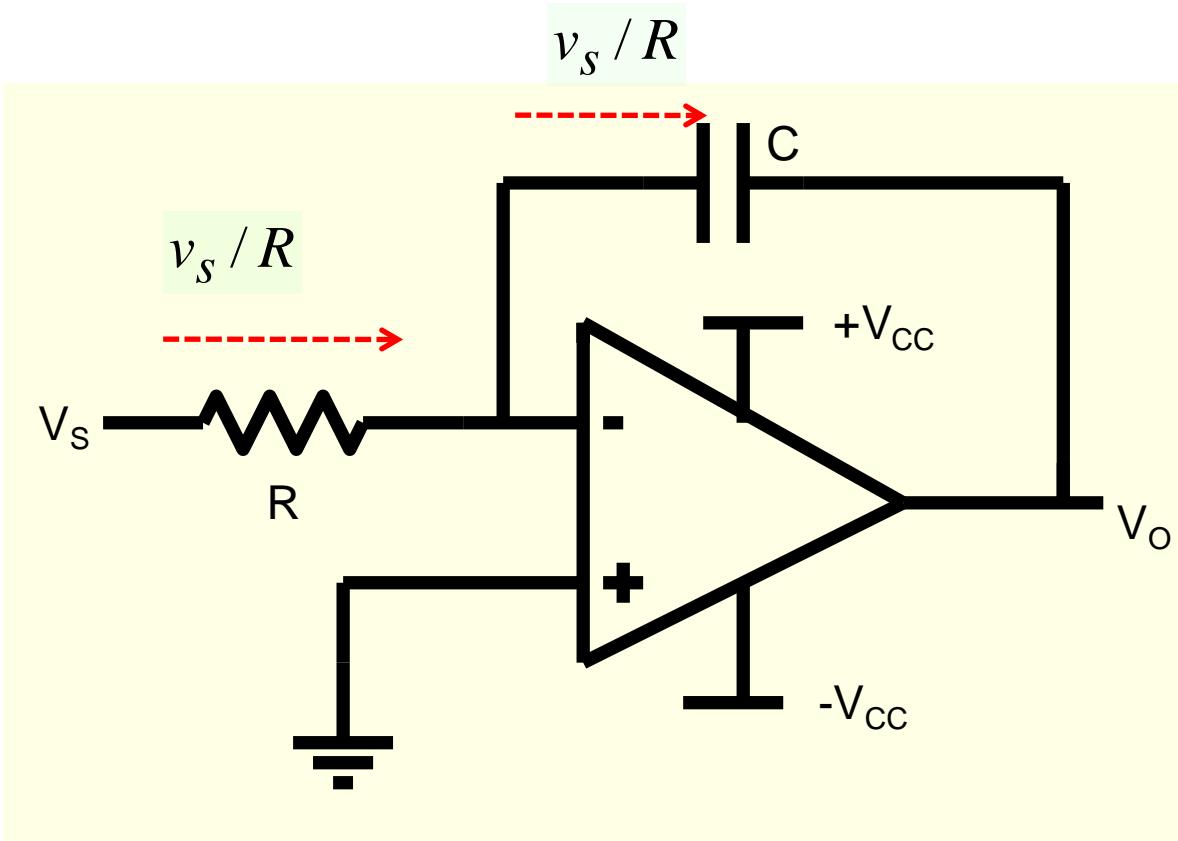


$$\frac{V_S}{R} = -C \frac{dV_O}{dt} \Rightarrow V_O(t) = -\frac{1}{RC} \int V_S dt$$

Differentiator

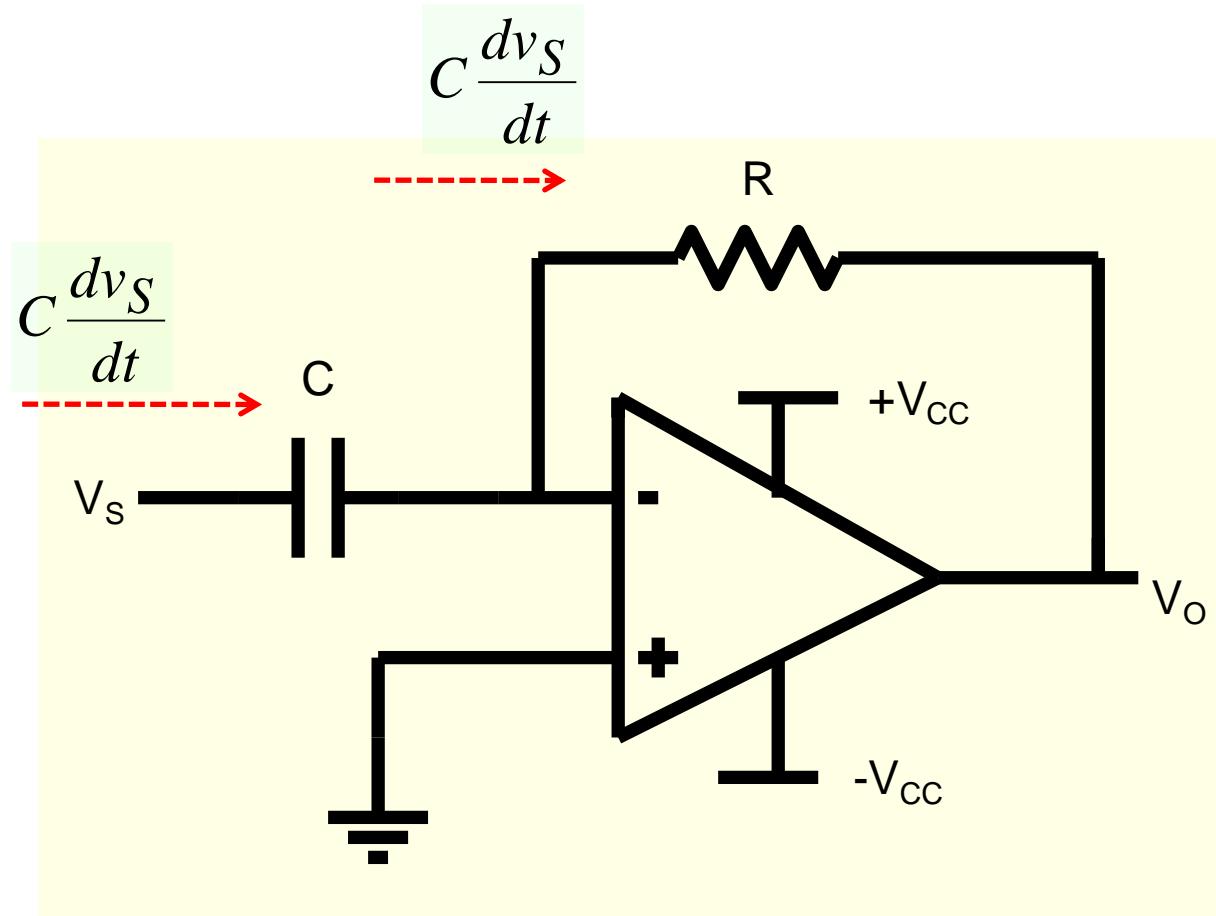


$$-\frac{V_o}{R} = C \frac{dV_s}{dt} \Rightarrow V_o(t) = -RC \frac{dV_s}{dt}$$

Log Amplifier

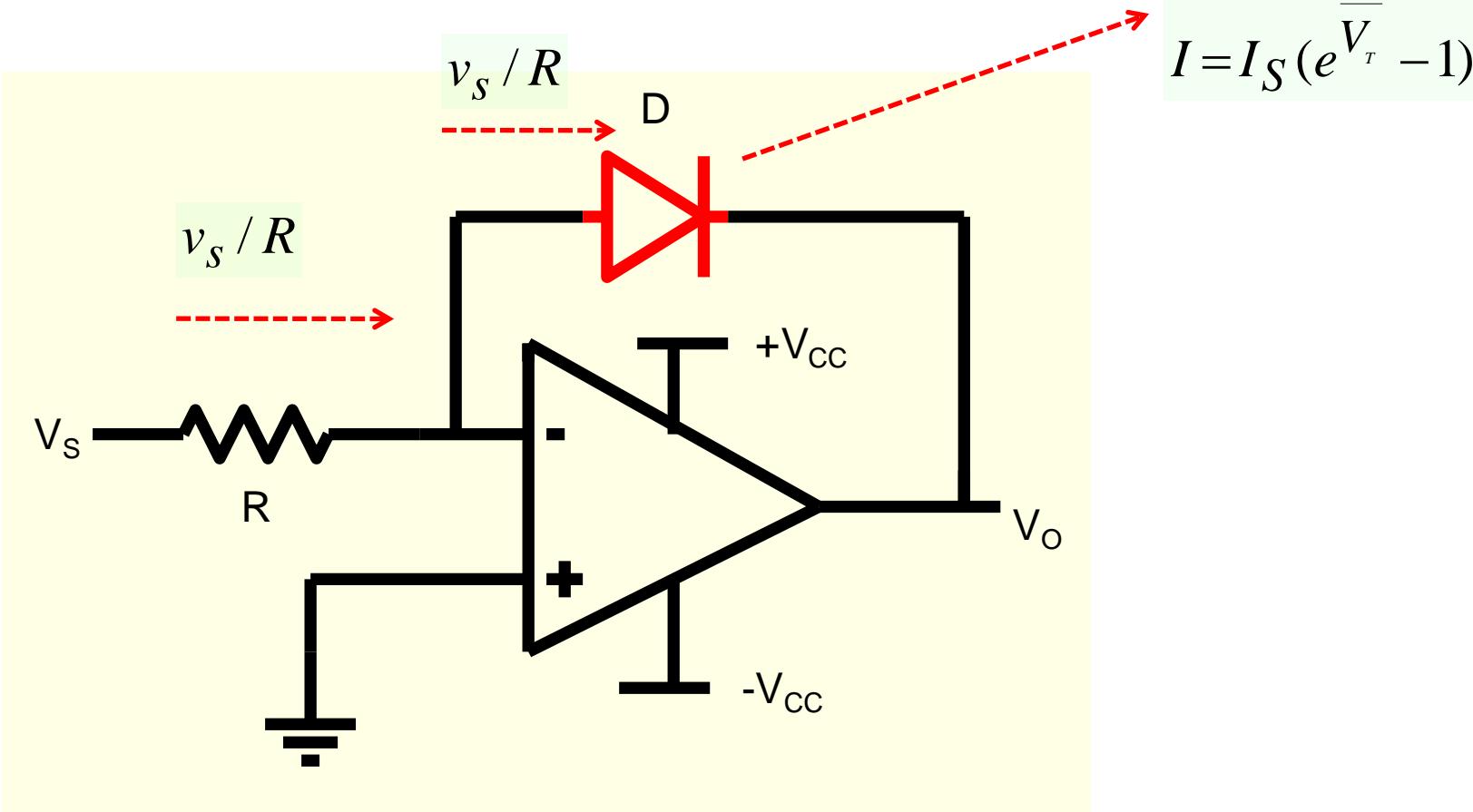


$$\frac{V_S}{R} = I_S \left(e^{-\frac{V_O}{V_T}} - 1 \right) \Rightarrow -V_O = V_T \times \ln \left(1 + \frac{V_S}{R I_S} \right) \cong V_T \times \ln \left(\frac{V_S}{R I_S} \right)$$

Temperature Sensor ?

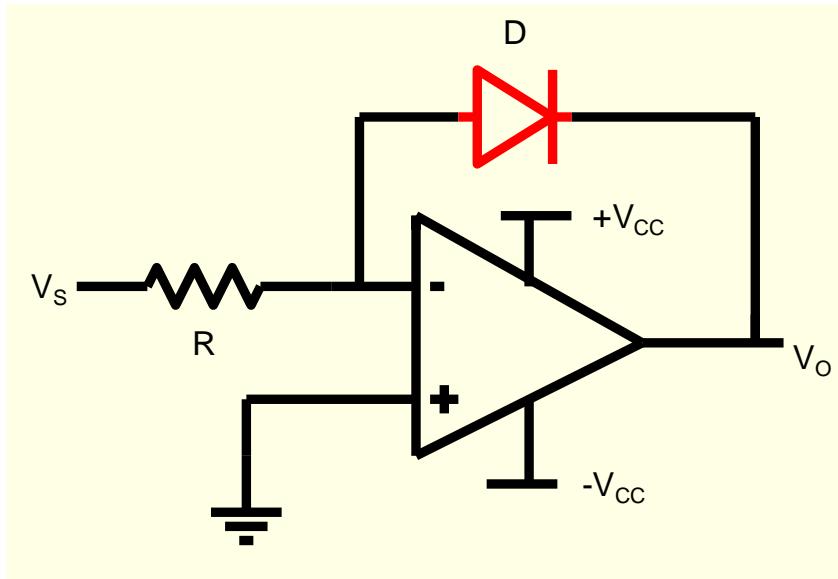


$$V_O = -V_T \times \ln\left(\frac{V_S}{R I_S}\right); V_T = \frac{k_B T}{q}$$

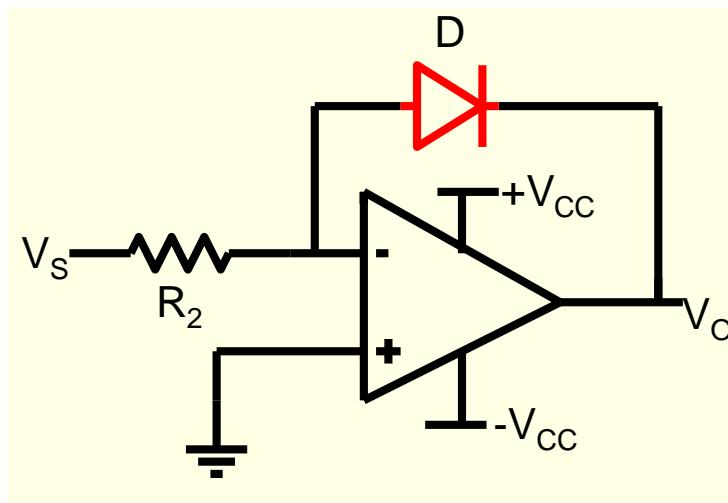
But I_S is a function of temperature as well.



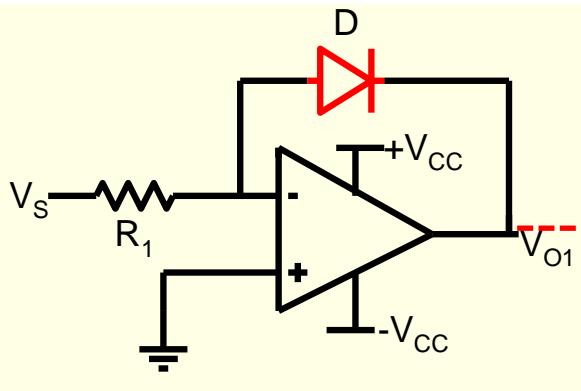
$$V_O = -V_T \times \ln\left(\frac{V_S}{R_2 I_S}\right)$$


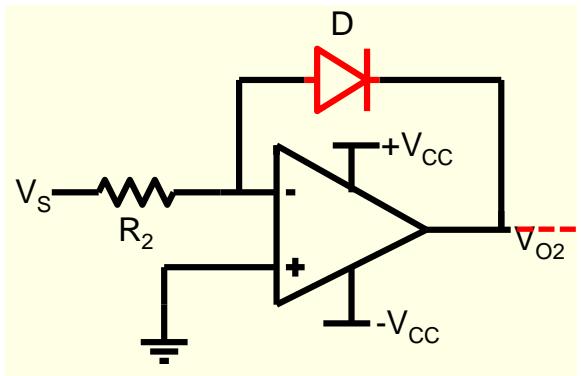
$$V_{O1} = -V_T \times \ln\left(\frac{V_s}{R_1 I_s}\right)$$



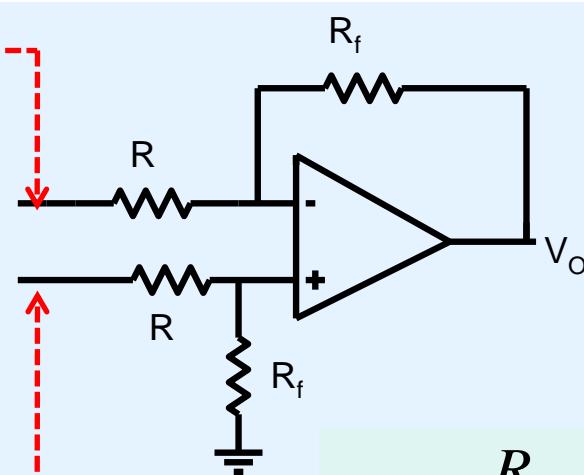
$$V_{O2} = -V_T \times \ln\left(\frac{V_s}{R_2 I_s}\right)$$



$$V_O = \frac{R_f}{R} V_T \times \ln\left(\frac{R_2}{R_1}\right)$$


Output voltage is directly proportional to temperature

AntiLog Amplifier

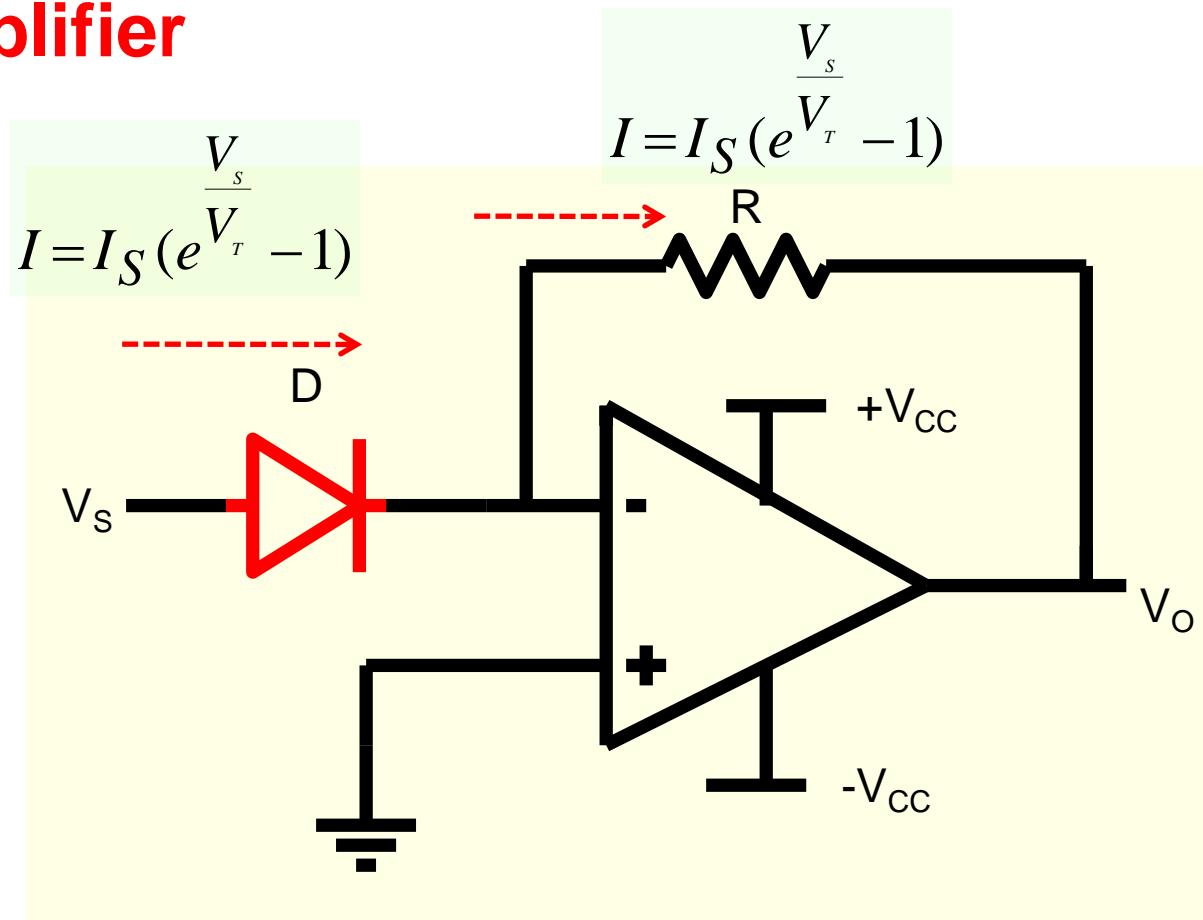


$$-\frac{V_o}{R} = I_S (e^{\frac{V_s}{T}} - 1) \Rightarrow V_o = -RI_S (e^{\frac{V_s}{T}} - 1) \cong -RI_S \times e^{\frac{V_s}{T}}$$

Multiplier

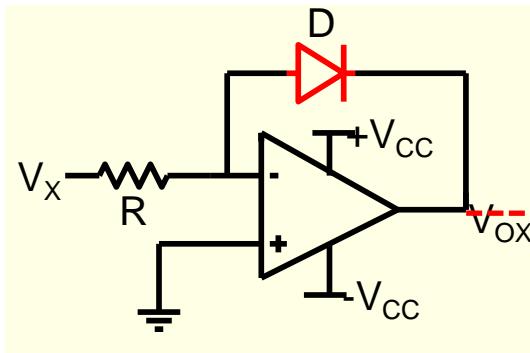


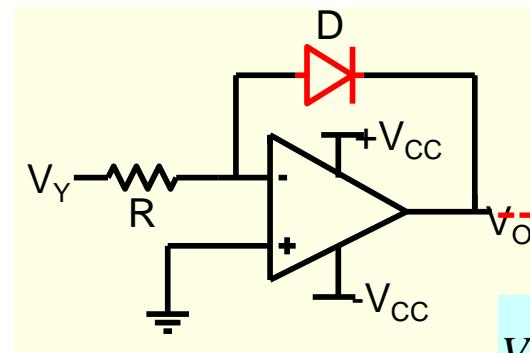
$$V_{OX} = -V_T \times \ln\left(\frac{V_X}{RI_S}\right)$$



$$V_{OY} = -V_T \times \ln\left(\frac{V_Y}{RI_S}\right)$$

$$V_{O1} = V_T \times \left(\ln\left(\frac{V_X}{RI_S}\right) + \ln\left(\frac{V_Y}{RI_S}\right) \right)$$
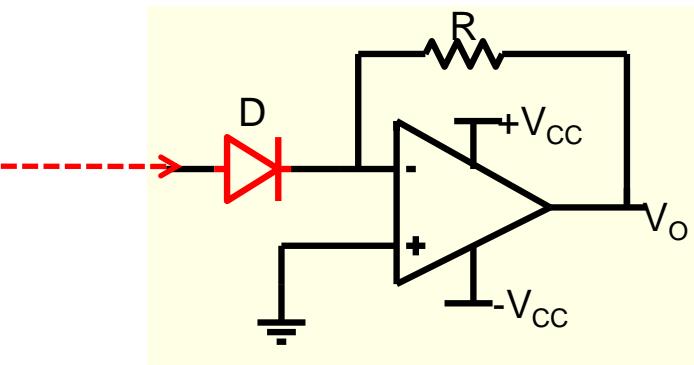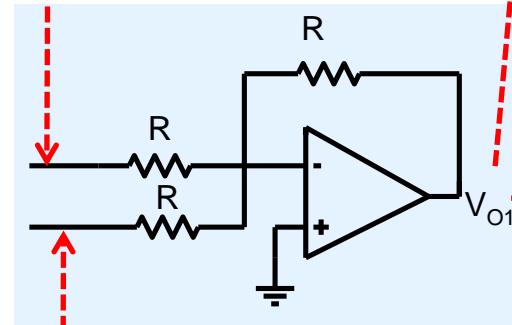
$$V_{O1} = V_T \times \ln\left(\frac{V_X V_Y}{R^2 I_S^2}\right)$$




$$V_O \cong -RI_S \times e^{\frac{V_{O1}}{V_T}} = -\frac{V_X V_Y}{RI_S}$$

Solving Differential Equations?

$$\frac{dy}{dt} + y = f(t)$$

$$y = f(t) - \frac{dy}{dt}$$

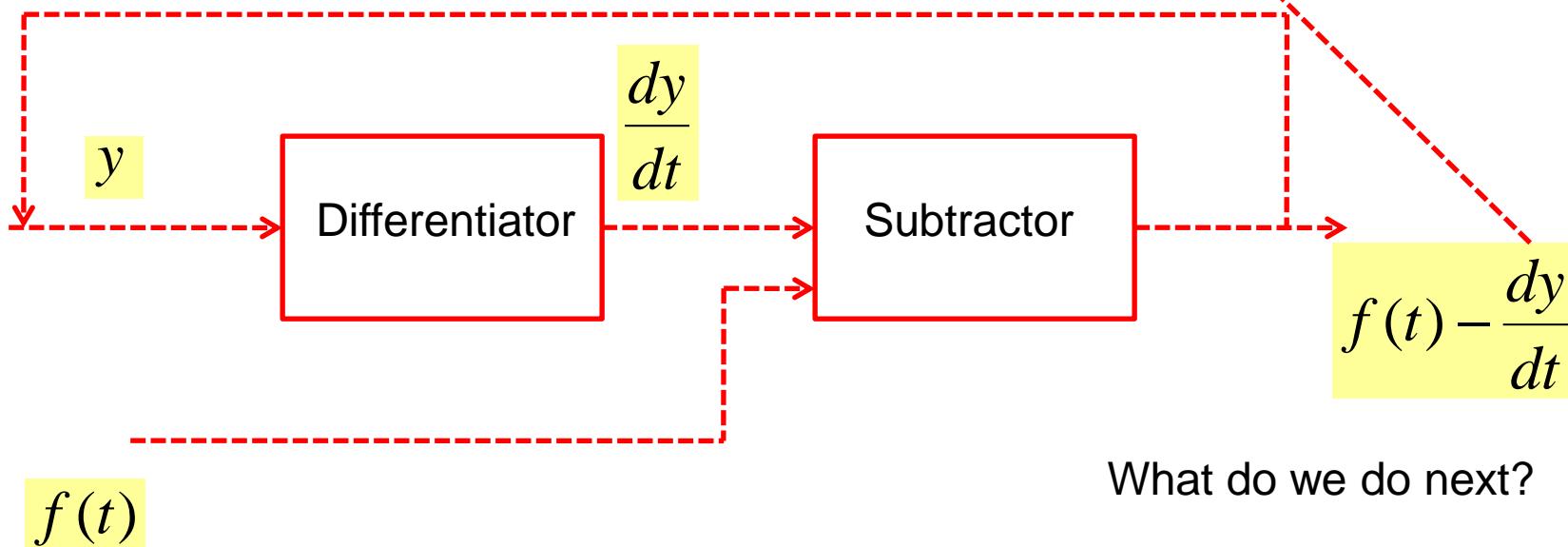

What do we do next?


Where do we get y from?

Integrators are preferred over Differentiators because they are less sensitive to noise




$$\frac{dy}{dt} + y = f(t)$$


$$\frac{dy}{dt} = f(t) - y \Rightarrow$$

$$y = \int f(t) - y dt$$

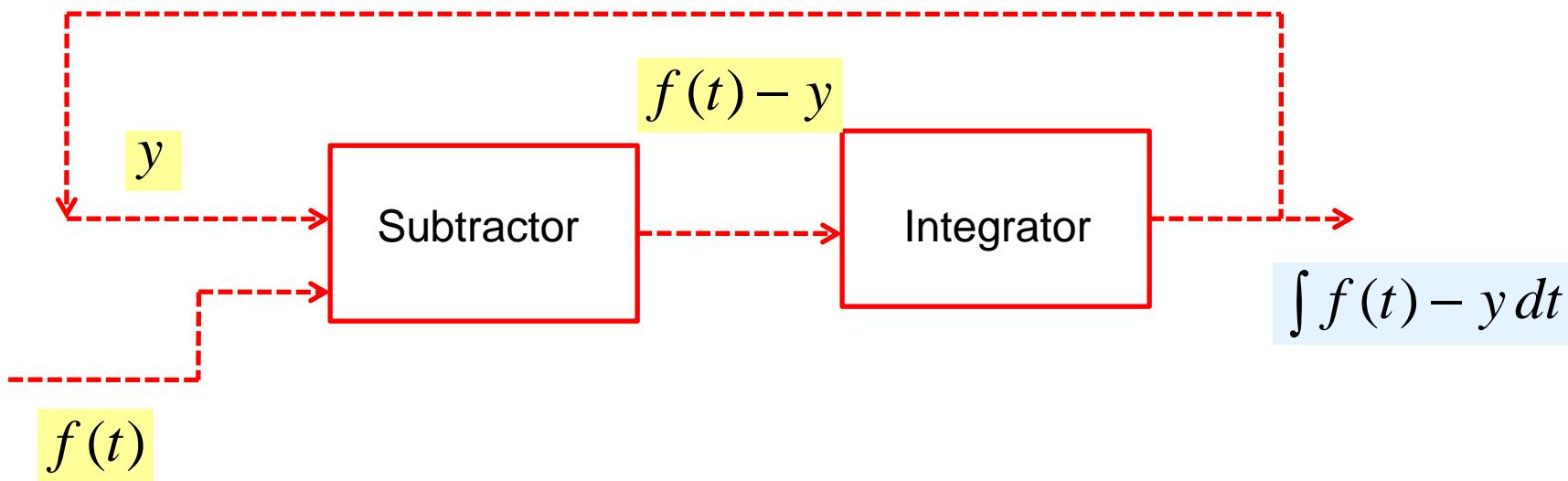


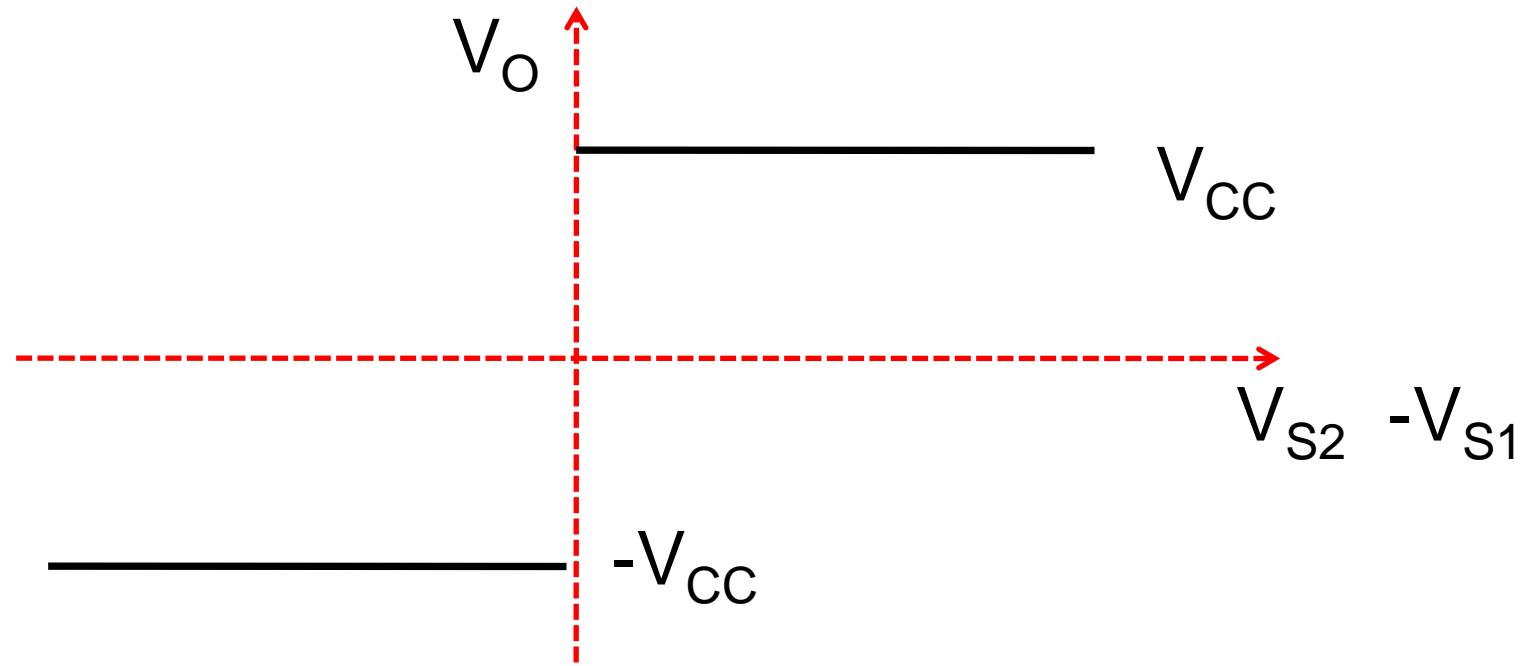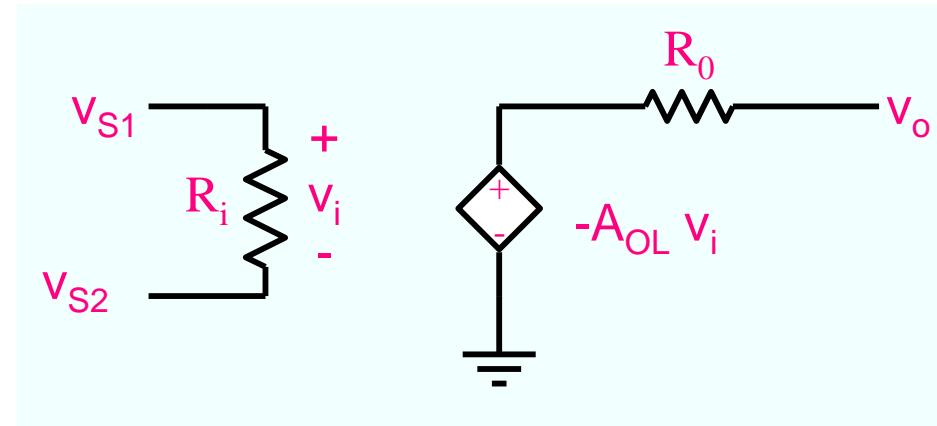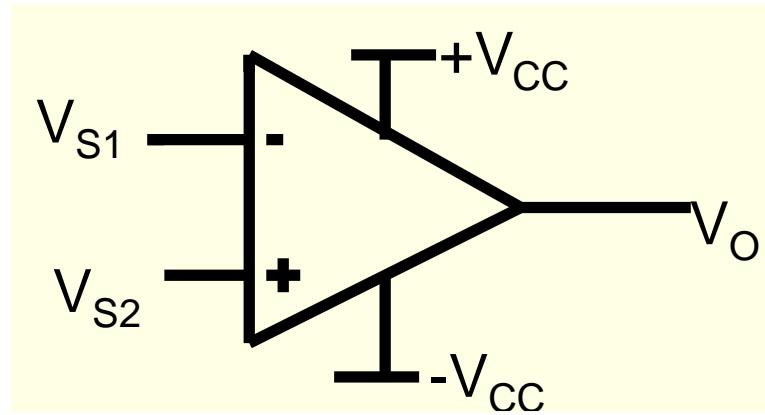Comparator: Opamp under open Loop condition





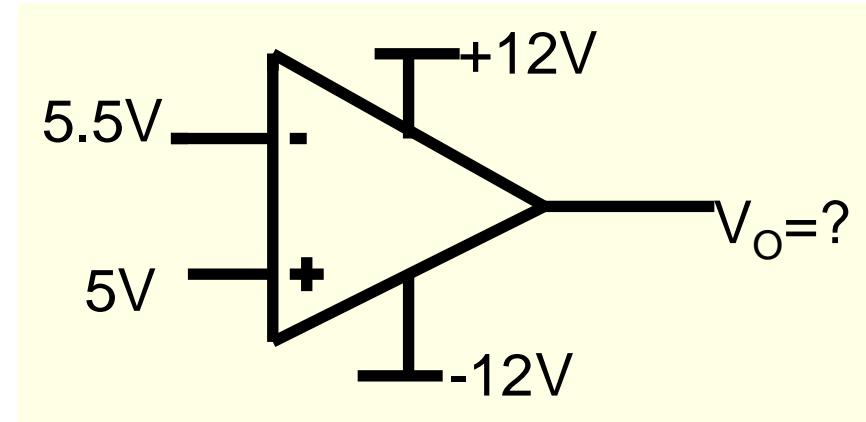


$\sim -12V$



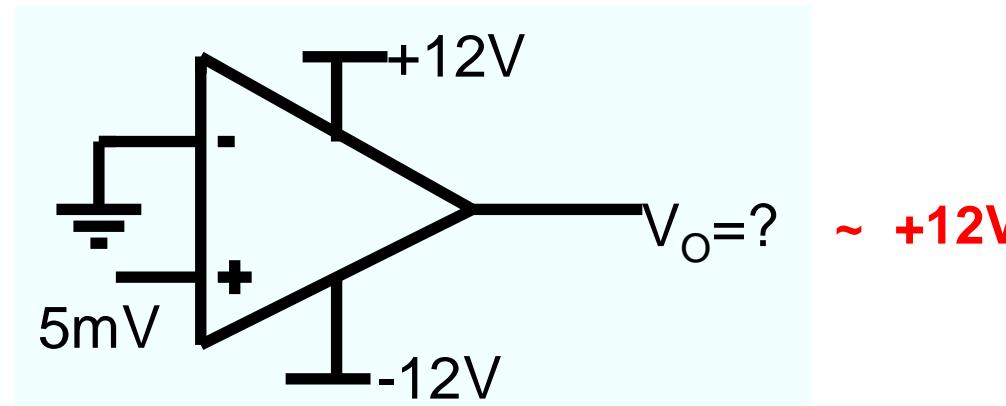


$\sim +12V$

Example

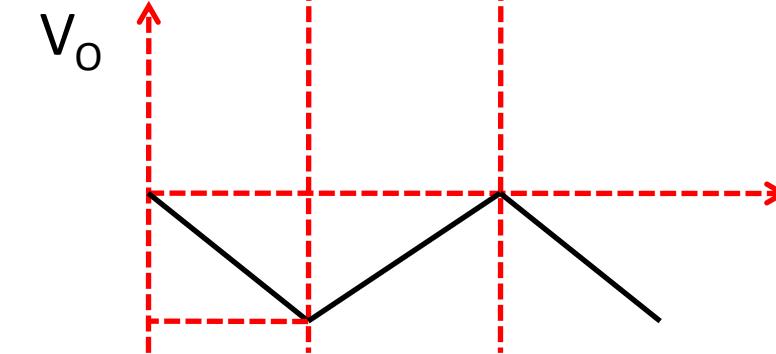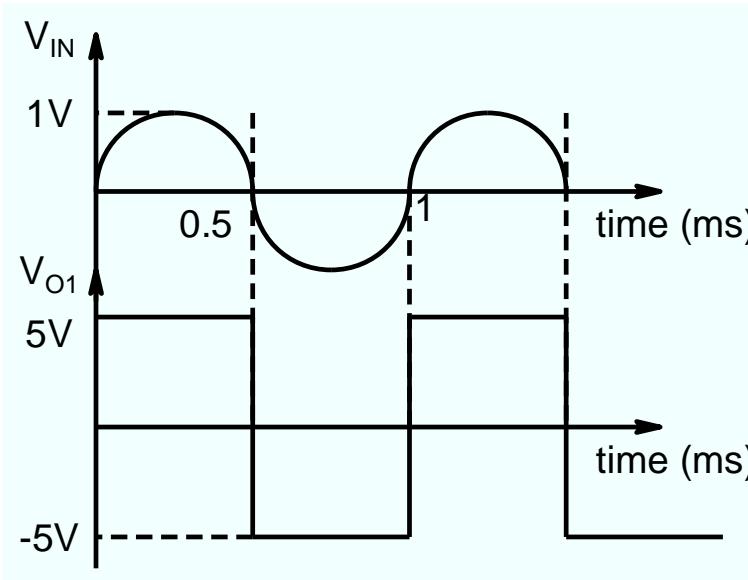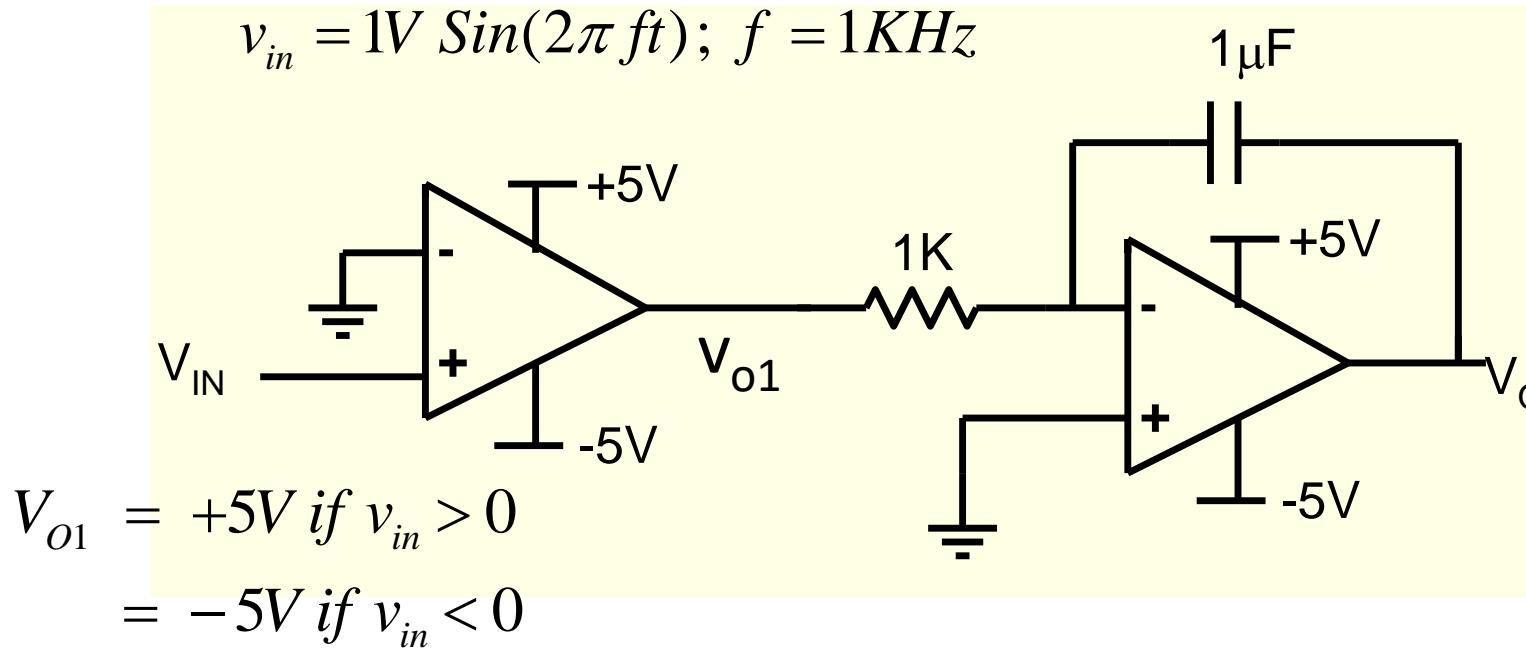


Example

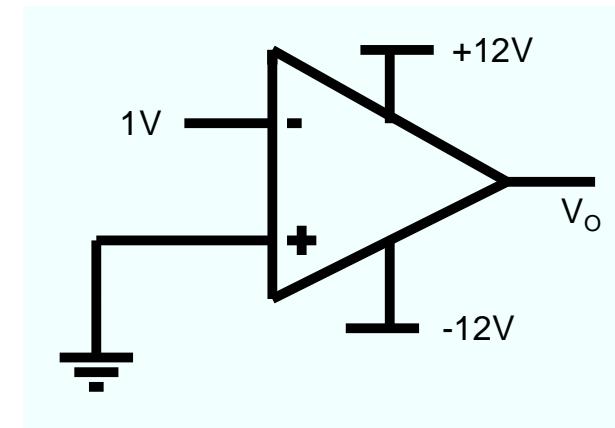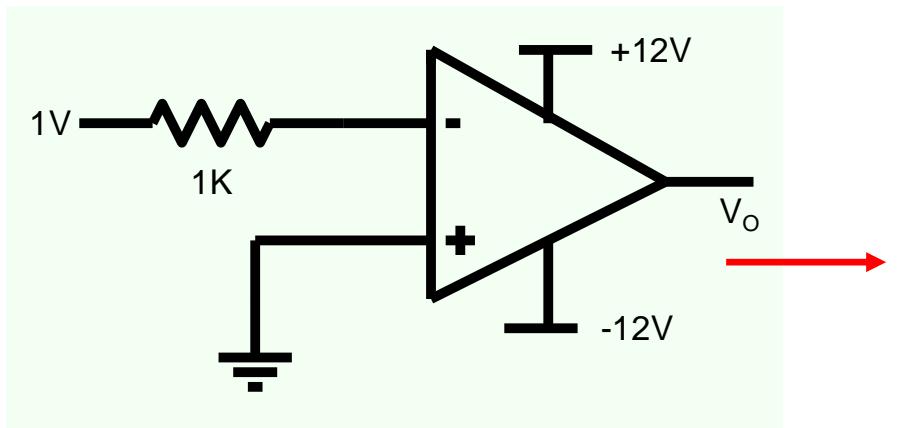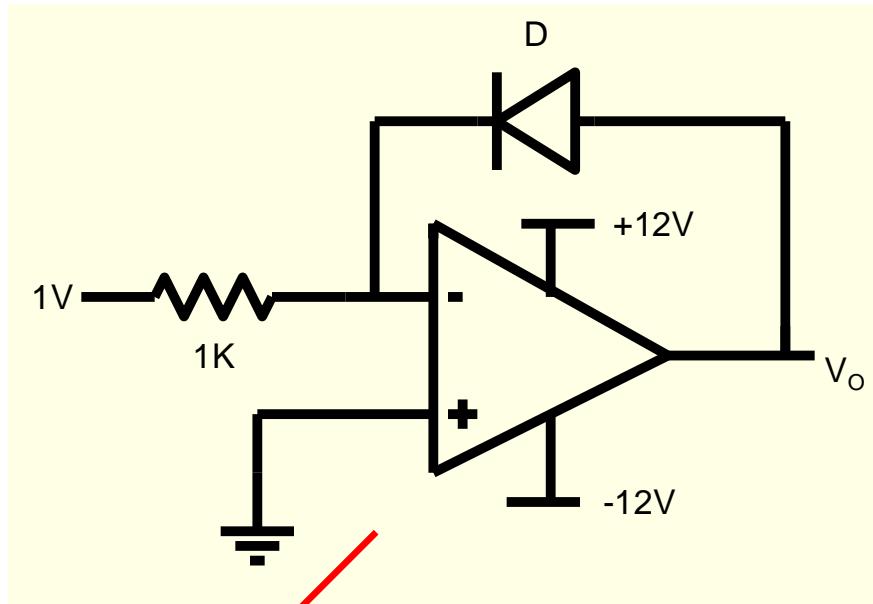

$\sim -12V$

Difference Amplifier

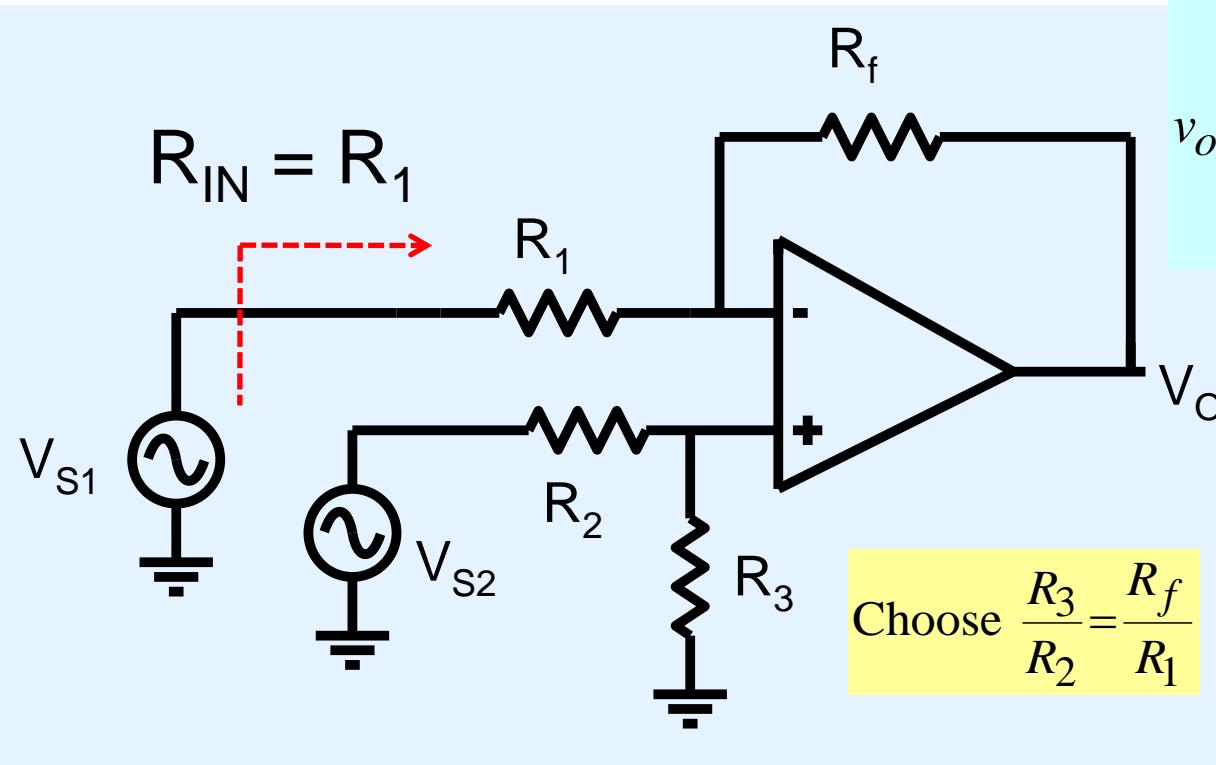

$$v_o = v_{s2} \frac{\frac{R_3}{R_2} (1 + \frac{R_f}{R_1}) - (\frac{R_f}{R_1}) v_{s1}}{(1 + \frac{R_3}{R_2})}$$

$$v_o = \frac{R_f}{R_1} (v_{s2} - v_{s1})$$


A drawback is that input resistance is relatively Lower

To change gain, we have to change two resistors and a slight mismatch can drastically reduce common mode rejection ratio

Solving Differential Equations?

$$\frac{dy}{dt} + y = f(t)$$

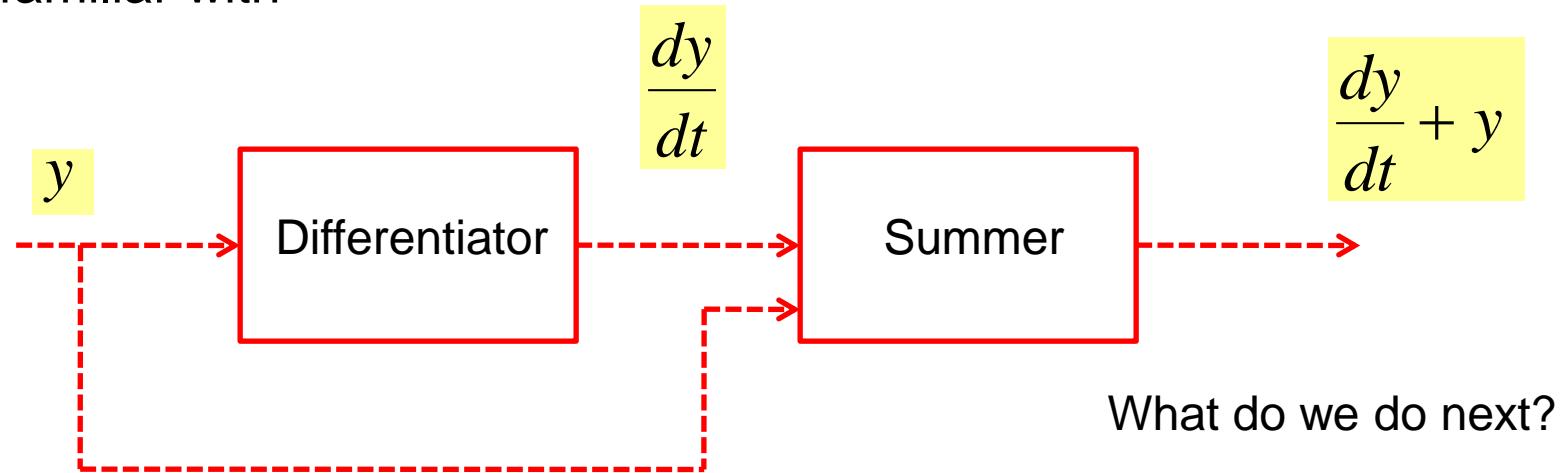Let us try and solve this equation using opamp circuit blocks that we are familiar with




Where do we get y from?

Solving Differential Equations?

$$\frac{dy}{dt} + y = f(t)$$

$$y = f(t) - \frac{dy}{dt}$$

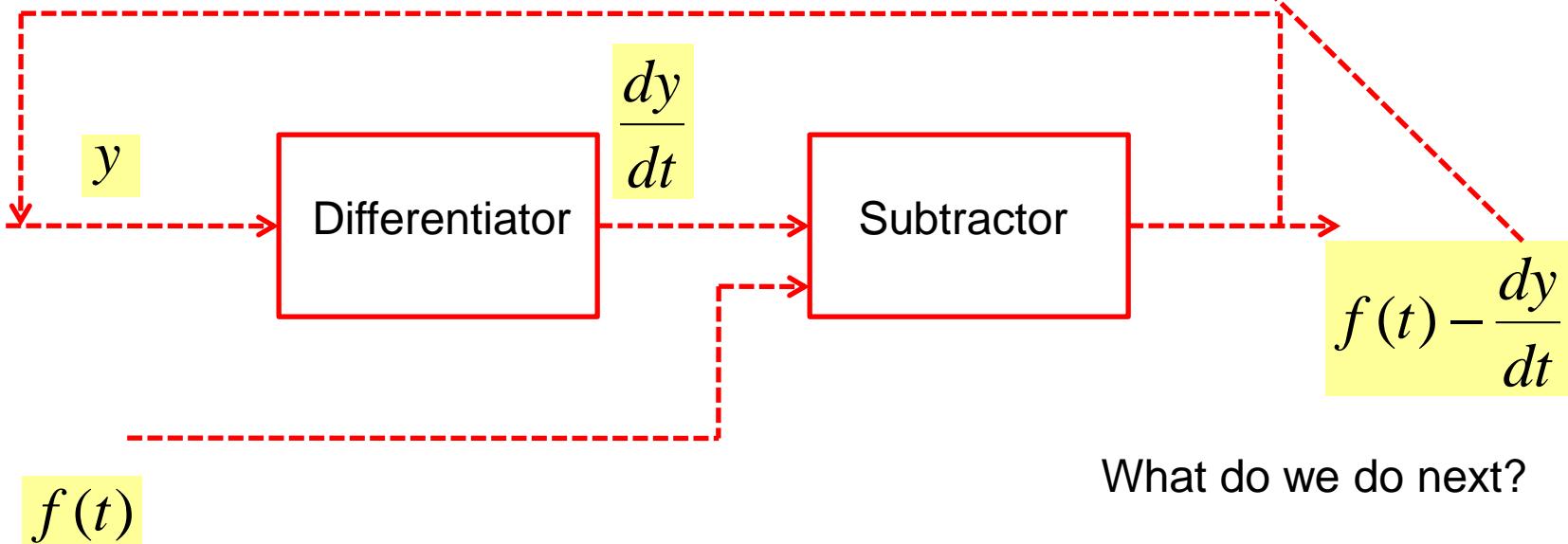

What do we do next?


Where do we get y from?

Integrators are preferred over Differentiators because they are less sensitive to noise


$$\frac{dy}{dt} + y = f(t)$$

$$\frac{dy}{dt} = f(t) - y \Rightarrow$$

$$y = \int f(t) - y dt$$

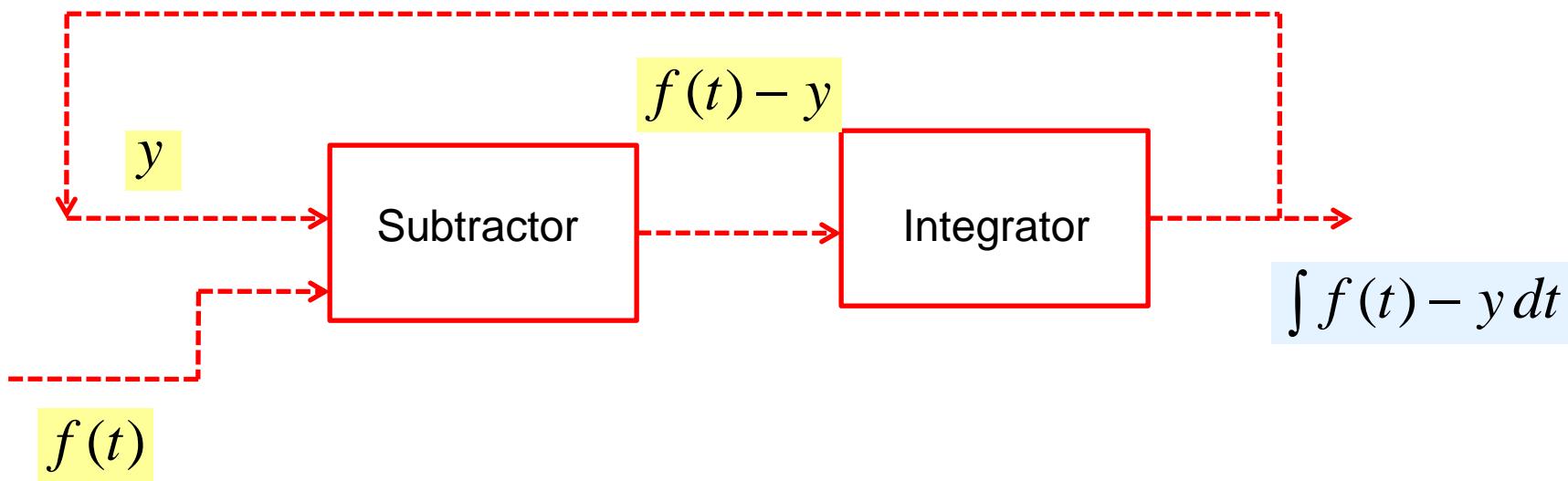

Effect Of Mismatches

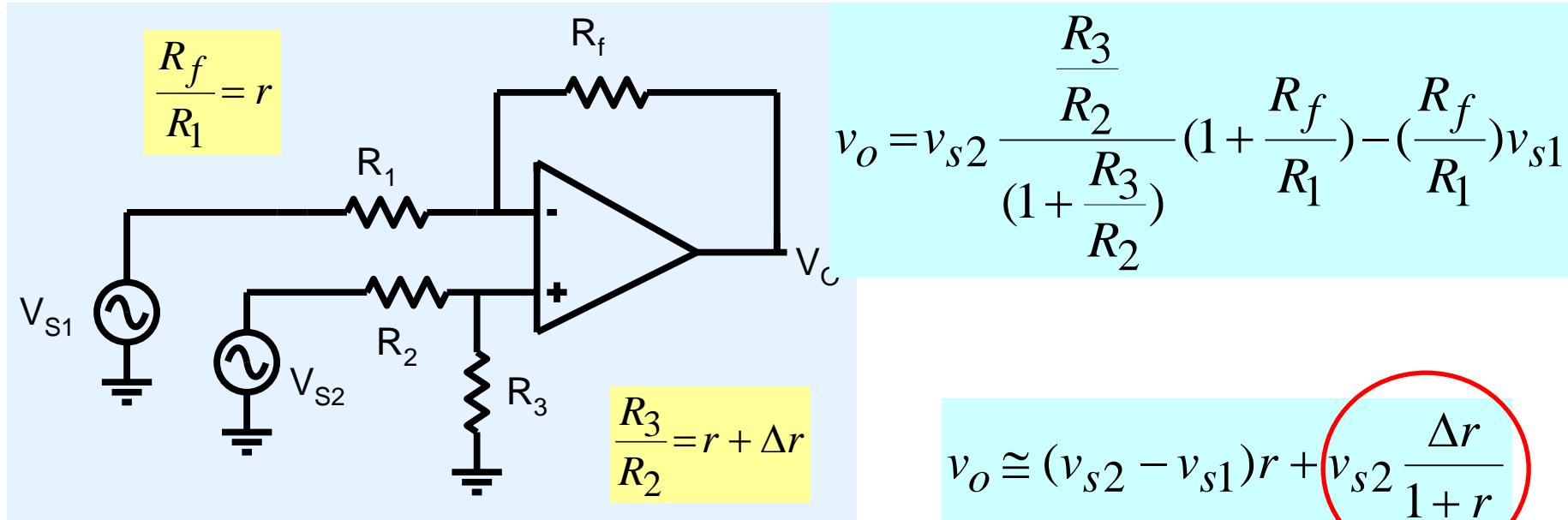

$$v_{id} = v_{S2} - v_{S1}$$

$$v_{ic} = \frac{v_{S1} + v_{S2}}{2}$$

$$v_{S2} = 0.5v_{id} + v_{ic}$$

$$v_o = A_d v_{id} + A_{cm} v_{ic}$$


$$A_{dm} = r$$

$$A_{cm} = \frac{\Delta r}{1+r}$$

Error term

Common mode gain and CMRR depend on mismatches

Instrumentation Amplifier

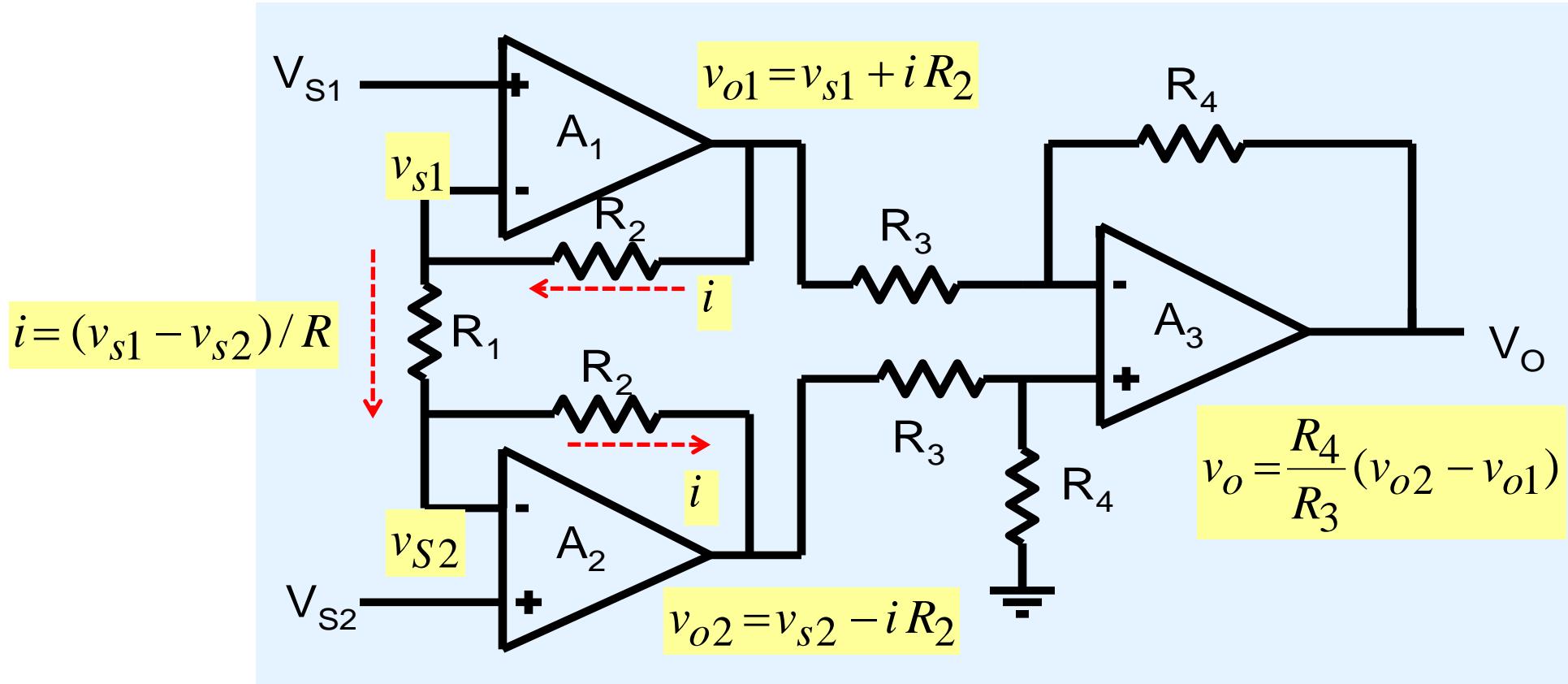

$$v_o = \frac{R_4}{R_3} \times \left(1 + \frac{2R_2}{R_1}\right) \times (v_{S2} - v_{S1})$$

Very high input Resistance


Can change one resistor R_1 and change gain

ESC102 : Introduction to Electronics


HW10: Solution

B. Mazhari
Dept. of EE, IIT Kanpur

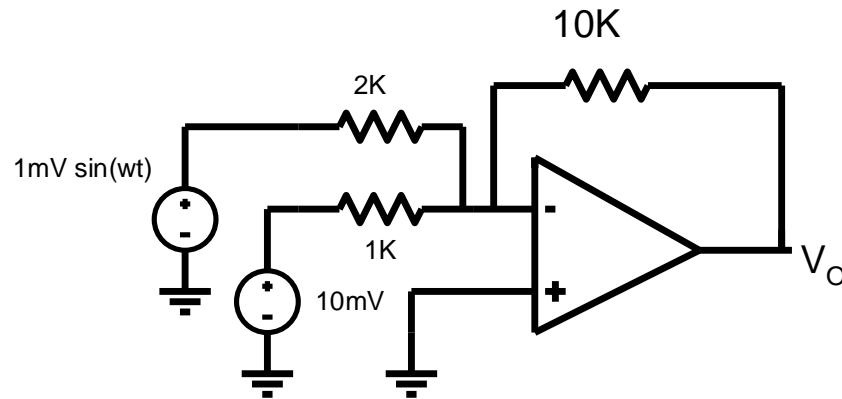Q.1 Determine the output of the ideal opamp circuits shown below




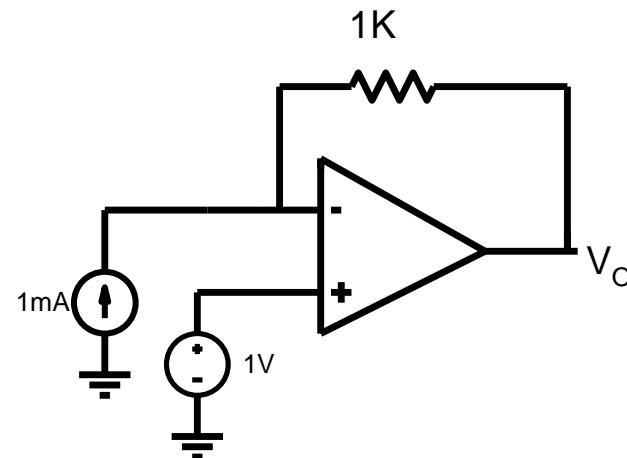
$$v_o = -\left\{ \frac{10K}{1K} \times 10mV + \frac{10K}{2K} \times 1mV \sin(\omega t) \right\}$$
$$= -\{0.1 + 5 \times 10^{-3} \sin(\omega t)\}$$




$$v_+ = v_- = 1V$$
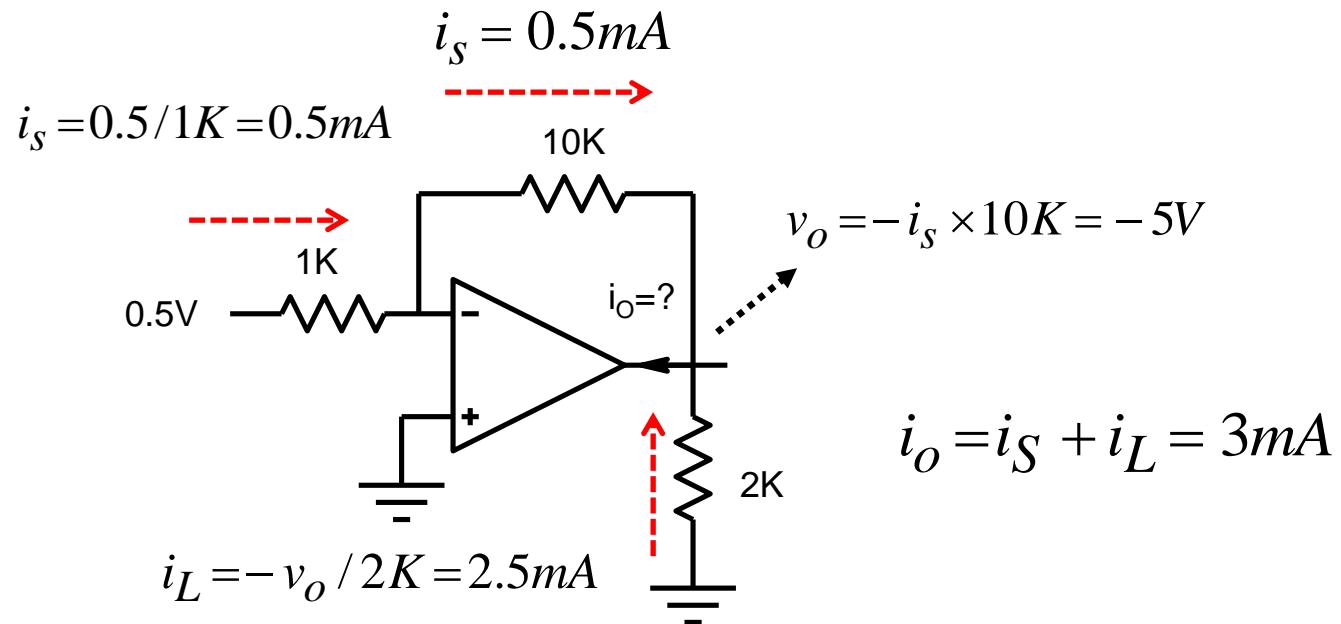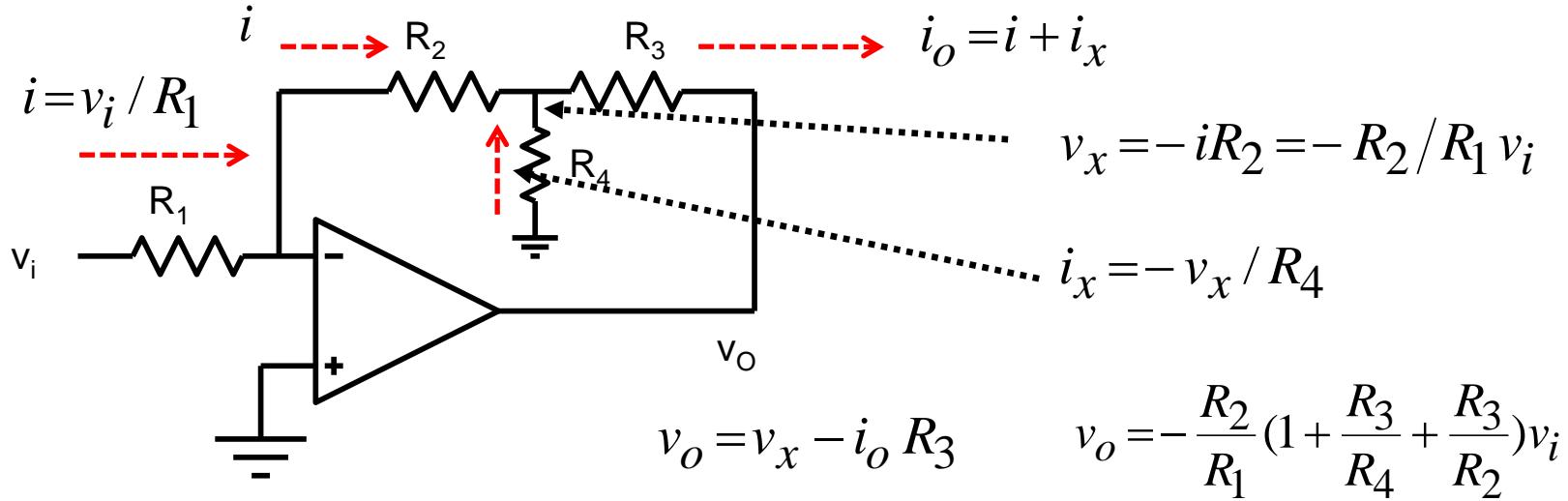
$$\frac{1 - v_o}{1K} = 1mA \quad v_o = 0V$$



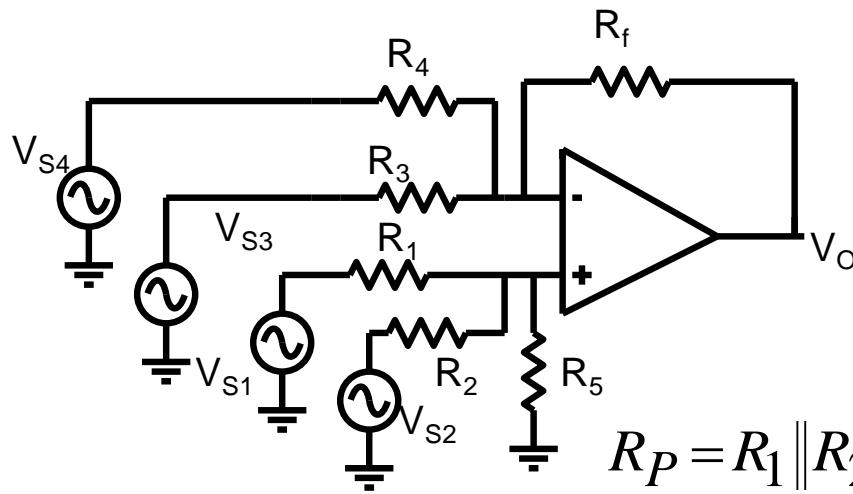Q.2 Design an opamp circuit that would generate the following output voltage where V_{s1} , V_{s2} , V_{s3} and V_{s4} are input voltages

$$V_O = 2v_{s1} + 4v_{s2} - 8v_{s3} - 10v_{s4}$$



$$R_P = R_1 \parallel R_2 \parallel R_5$$

$$v_o = -\left(\frac{R_f}{R_3}\right)v_{s3} - \left(\frac{R_f}{R_4}\right)v_{s4} + \left(1 + \frac{R_f}{R_3 \parallel R_4}\right) \times \frac{R_P}{R_1} v_{s1} + \left(1 + \frac{R_f}{R_3 \parallel R_4}\right) \times \frac{R_P}{R_2} v_{s2}$$

Choose : $R_f = 10K \Rightarrow R_3 = 1.25K \Rightarrow R_4 = 1K$


$$\Rightarrow \frac{R_P}{R_1} = 0.105$$

$$\Rightarrow \frac{R_P}{R_2} = 0.211$$

$$\Rightarrow \frac{R_1}{R_2} = 2$$

Choose : $R_2 = 1K \Rightarrow R_1 = 2K \Rightarrow R_P = 0.211K \Rightarrow R_5 = 0.308K$

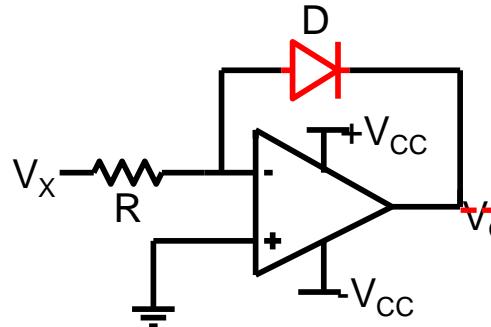
Q.3 Design an opamp circuit that can produce $V_O = K \times V_{IN}^2$ where Vin is the input voltage.



$$V_{O_X} = -V_T \times \ln\left(\frac{V_X}{R I_S}\right)$$


$$V_{O_1} = V_T \times \left(\ln\left(\frac{V_X}{R I_S}\right) + \ln\left(\frac{V_X}{R I_S}\right) \right)$$

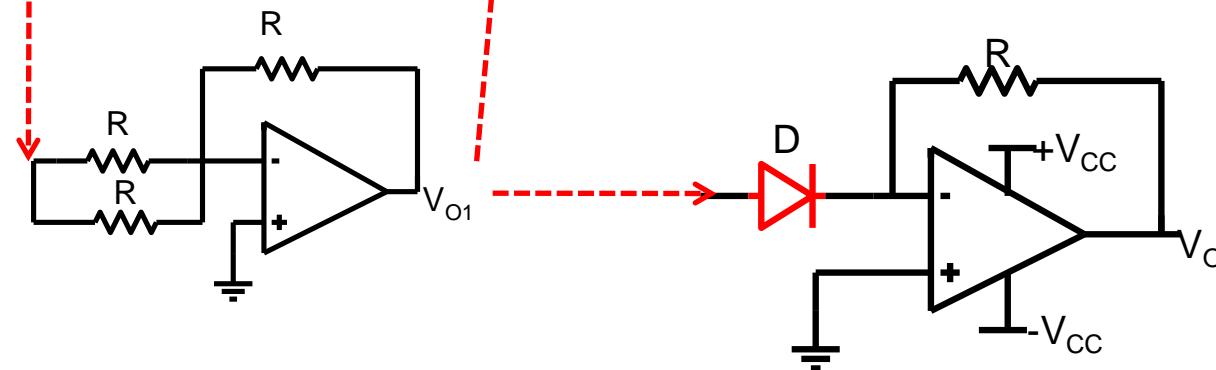
$$V_{O_1} = V_T \times \ln\left(\frac{V_X^2}{R^2 I_S^2}\right)$$



$$V_O \approx -R I_S \times e^{\frac{V_{O_1}}{V_T}} = -\frac{V_X^2}{R I_S}$$

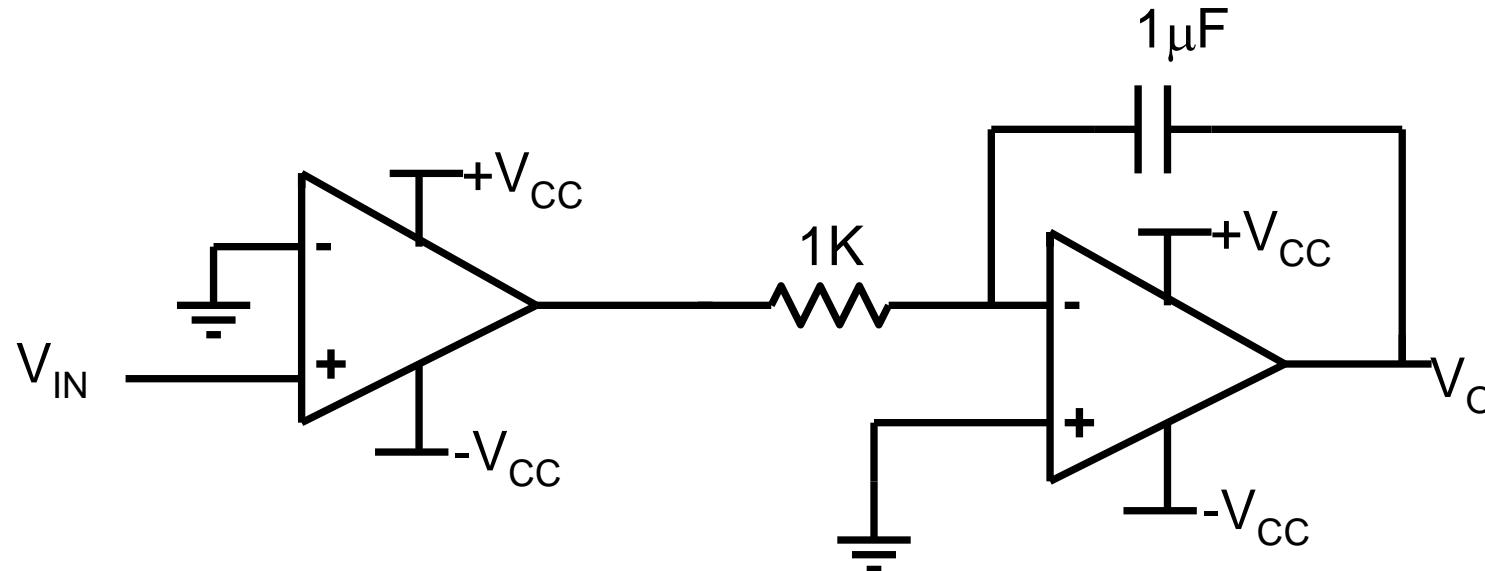
Q.4 Sketch the output voltage of the circuit shown below for
 $V_{in} = 1V \ Sin(2\pi ft)$; $f = 1KHz$ and supply voltages of $\pm 5V$




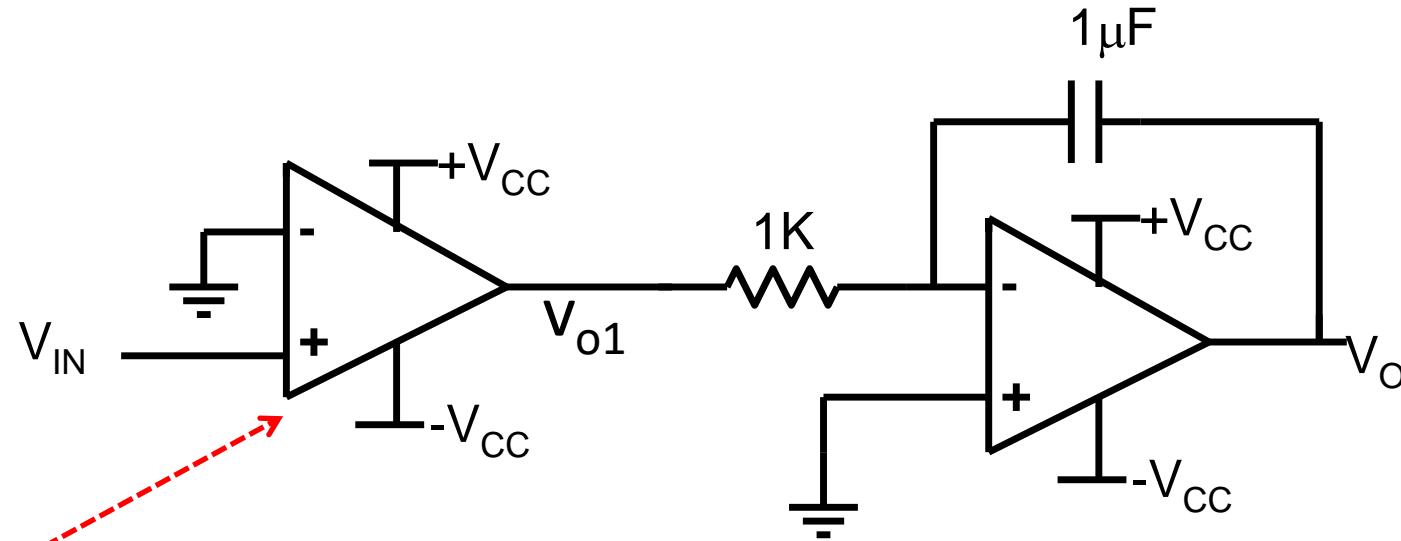

comparator

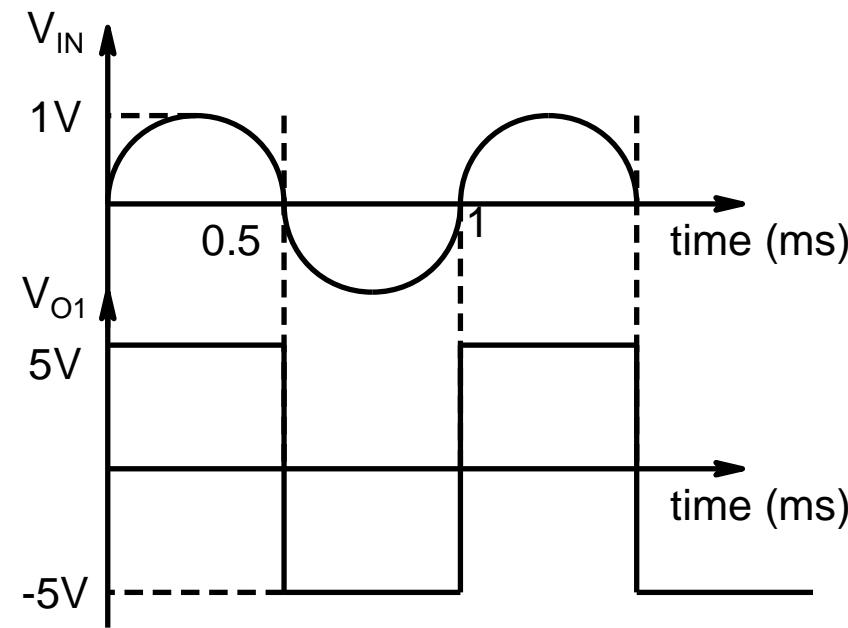
$$V_{O1} = +5V \text{ if } v_{in} > 0 \\ = -5V \text{ if } v_{in} < 0$$



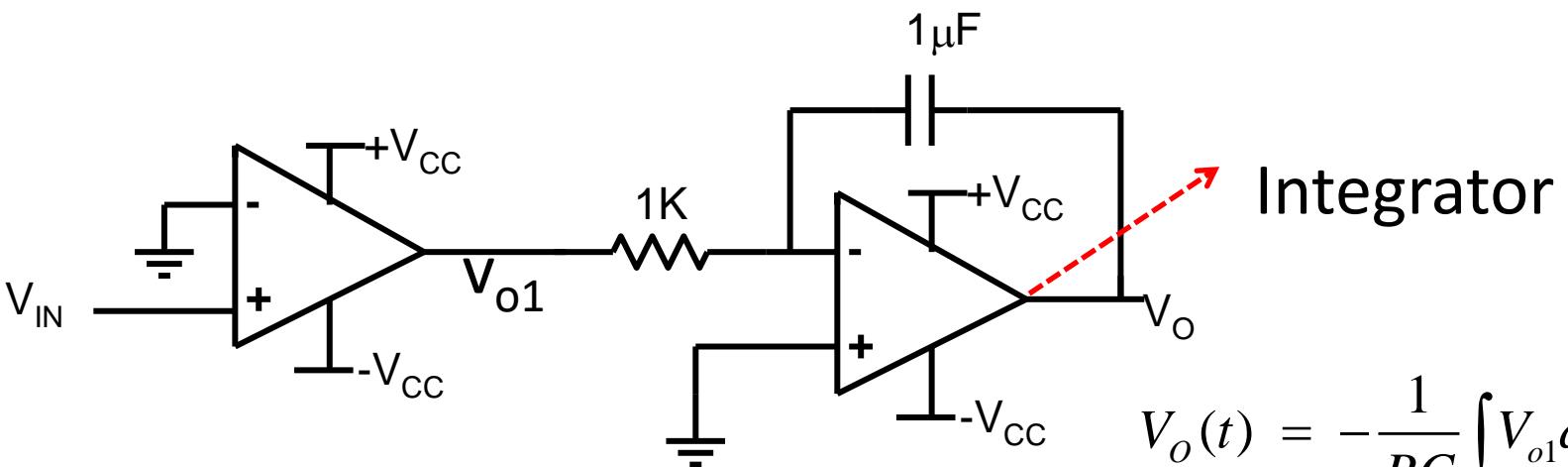

Integrator



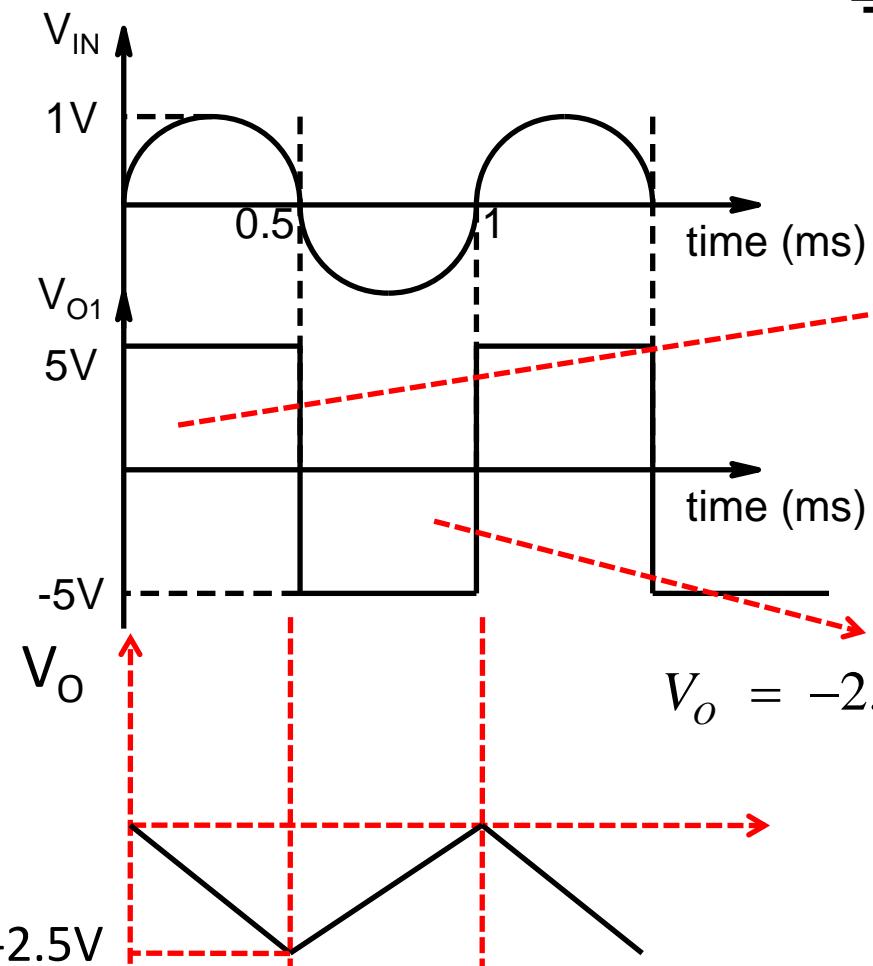
$$V_o(t) = -\frac{1}{RC} \int V_{o1} dt \\ = -10^3 \int V_{o1} dt$$




$$V_O = -5 \times 10^3 \times t \text{ for } 0 \leq t \leq 0.5ms$$

$$V_O = -2.5 + 5 \times 10^3 \times (t - 0.5ms) \text{ for } 0.5ms \leq t \leq 1ms$$

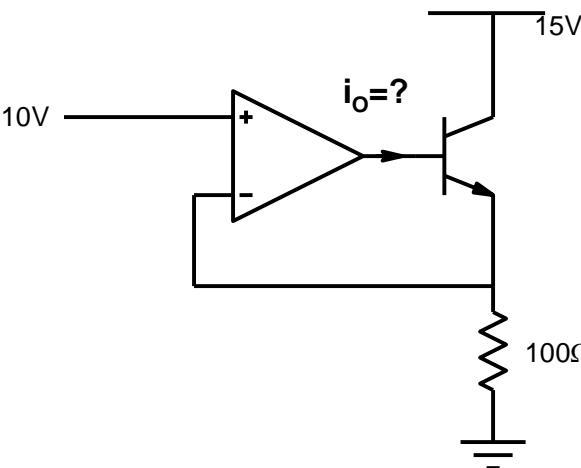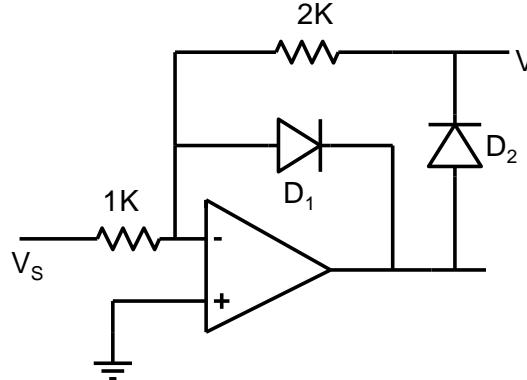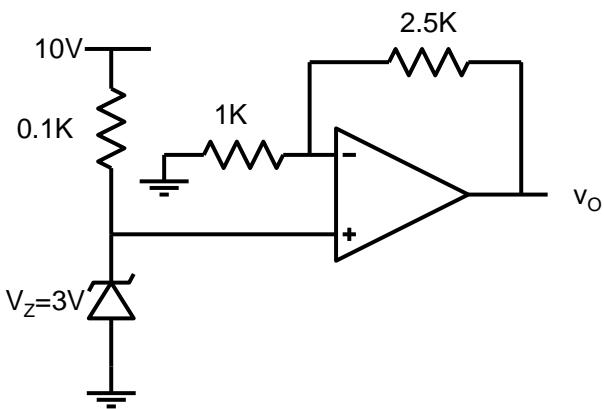
Q.5 Determine the output for the ideal opamp circuits shown below. For the circuit on the right assume that diodes have cut-in voltage of 0.7V. Analyze the circuit for $V_s = 1V$ and $V_s = -1V$. For the transistor assume a current gain of 100. What is the usefulness of each of the circuits?



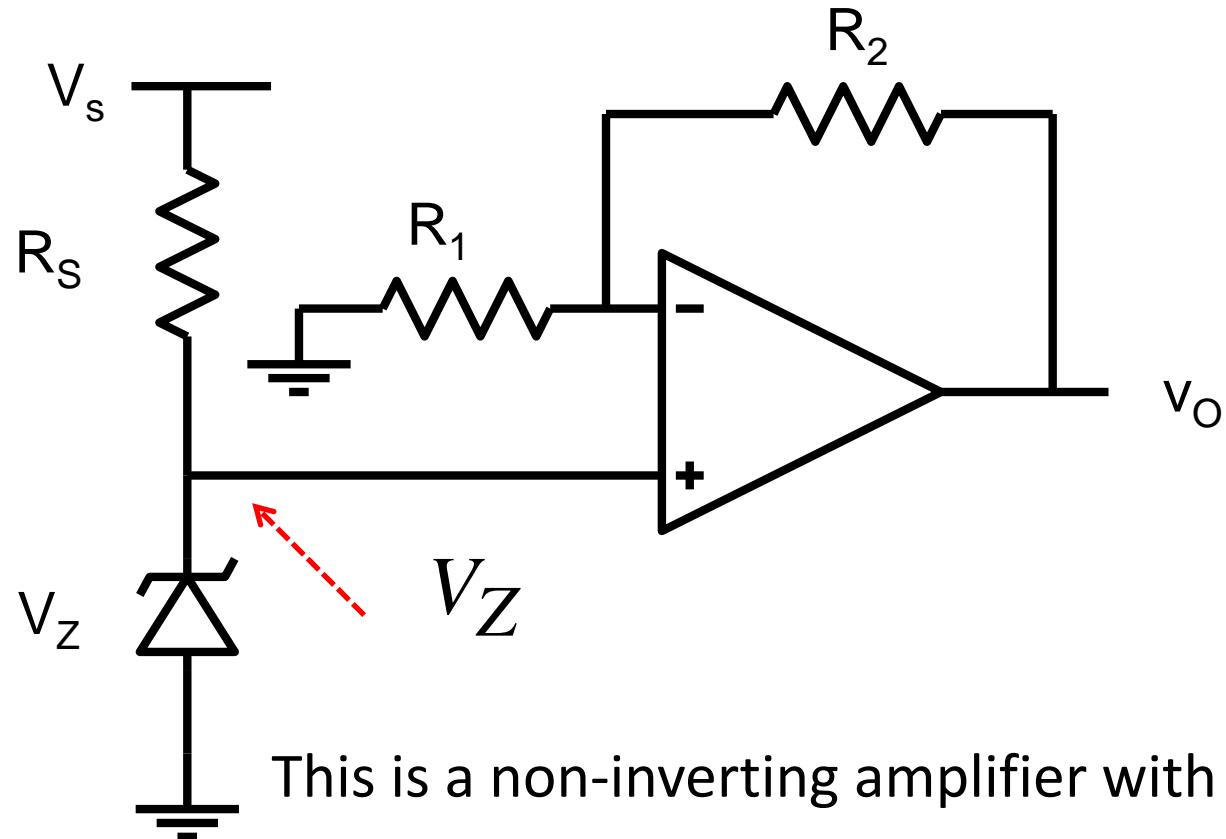

$$v_o = V_Z \left(1 + \frac{R_2}{R_1}\right)$$


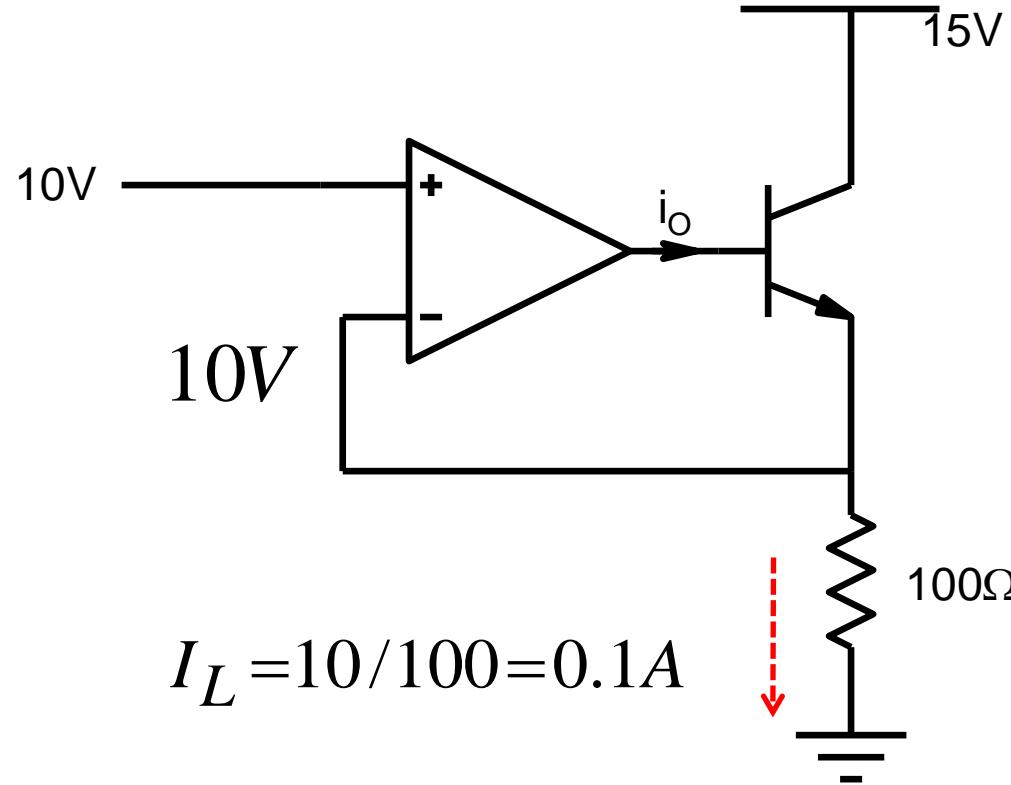
The circuit produces a constant output voltage v_o even though supply voltage may vary and thus acts like a voltage regulator.



$$I_L = 10/100 = 0.1A$$

$$I_o = I_B = \frac{I_E}{\beta + 1} = 0.99mA$$

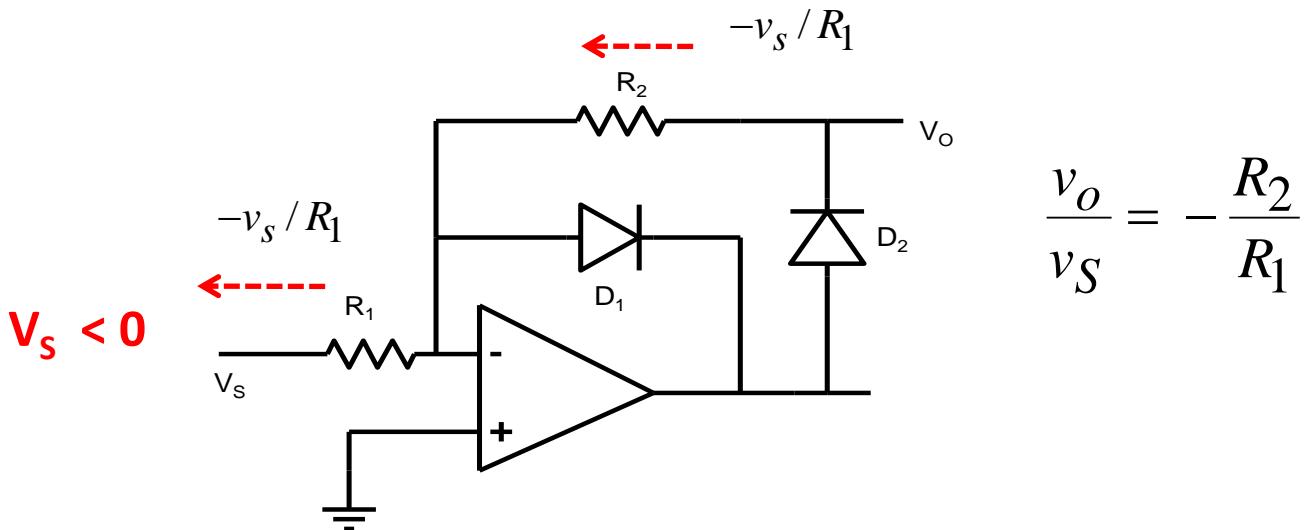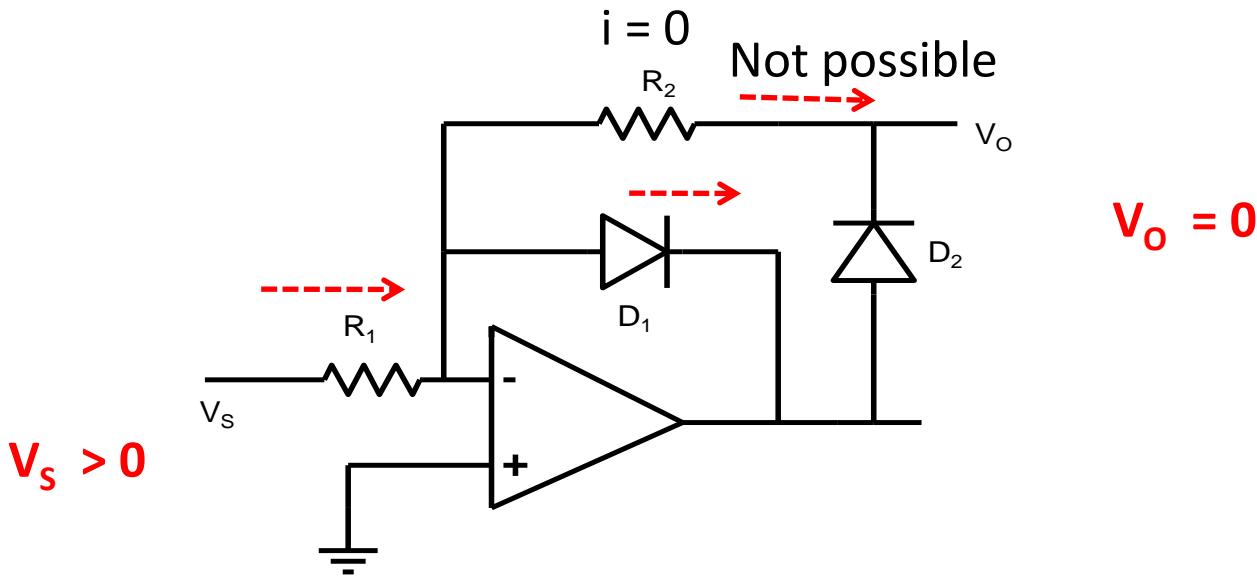The circuit can supply load current that is much larger than opamp output current



The circuit acts like a rectifier