


ESC201T : Introduction to Electronics

Lecture 21: Diode Model For Circuit Analysis

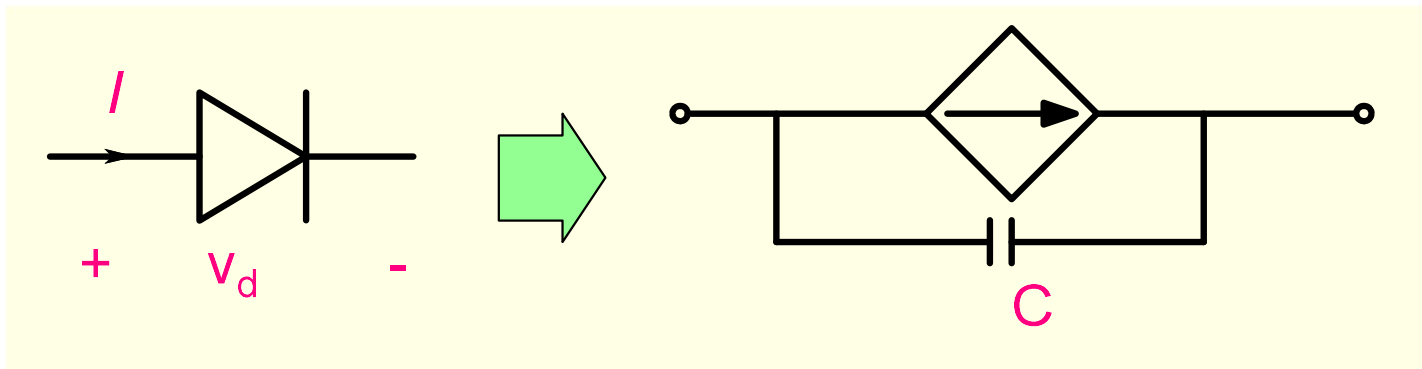B. Mazhari
Dept. of EE, IIT Kanpur


Diode Model: Forward Bias

$$I = I_s \times \left\{ \exp\left(\frac{V_d}{n V_T}\right) - 1 \right\}$$





For dc and low frequency ac circuits, the effect of diode capacitance can be neglected



Diode Model: Reverse Bias

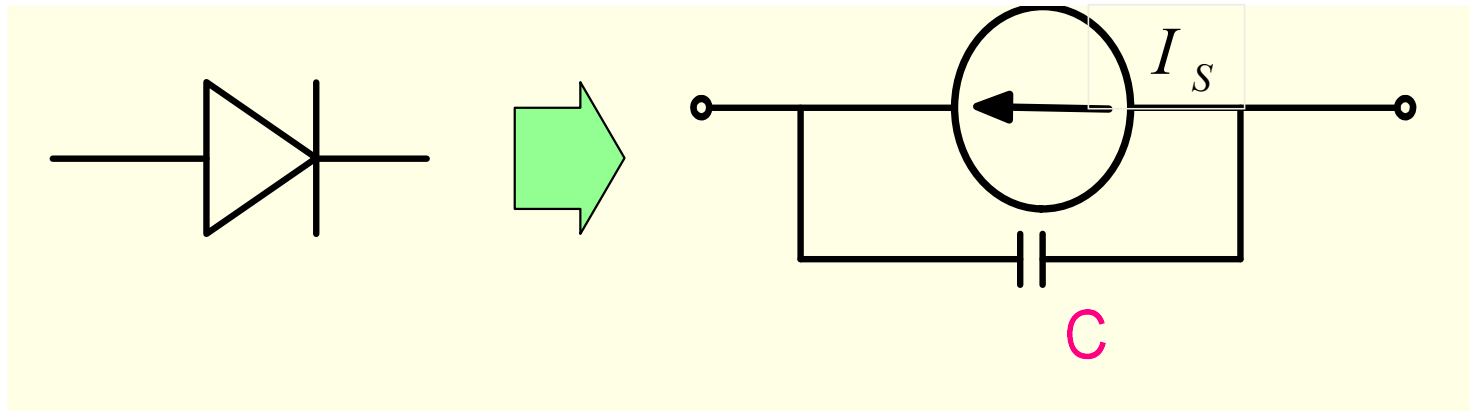

Because of capacitance, a diode even though reverse biased, can carry significant current **momentarily**


Example

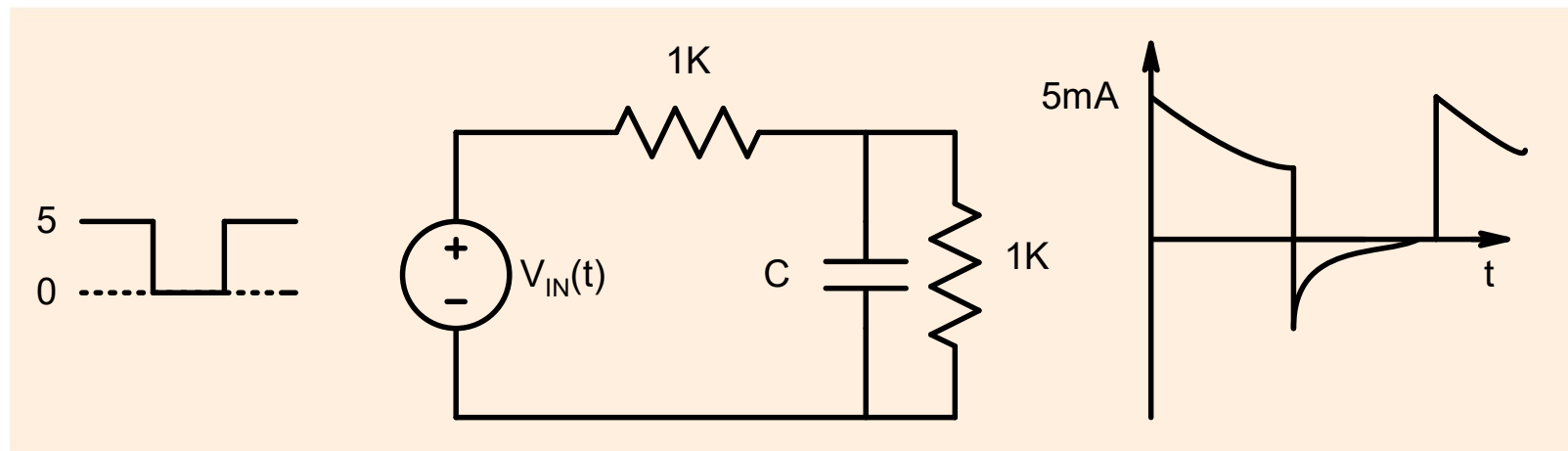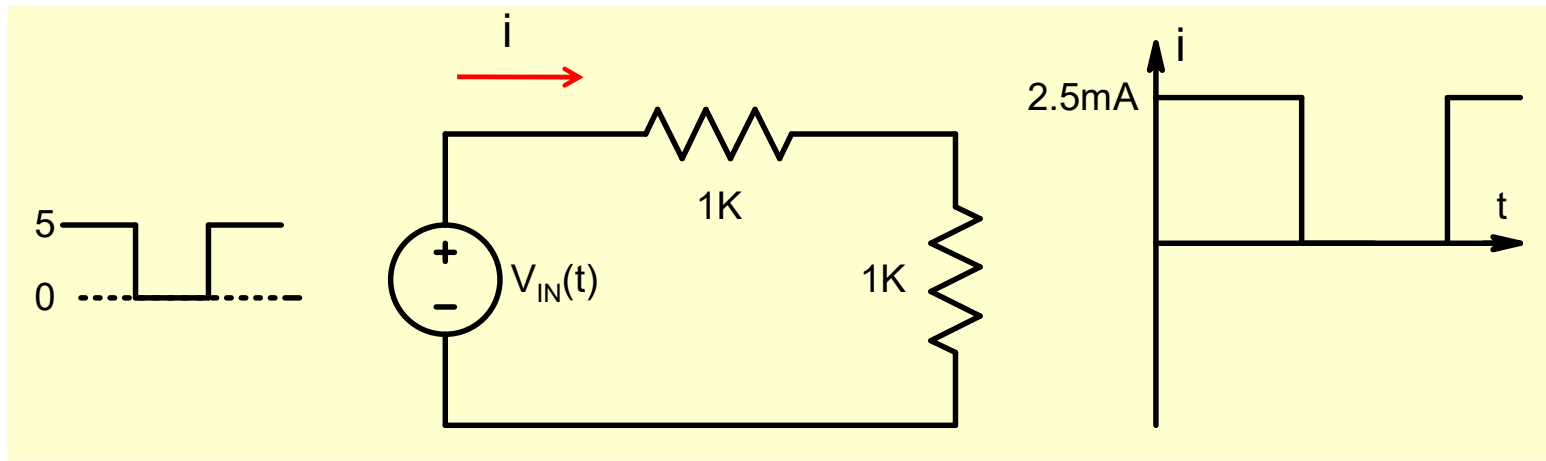

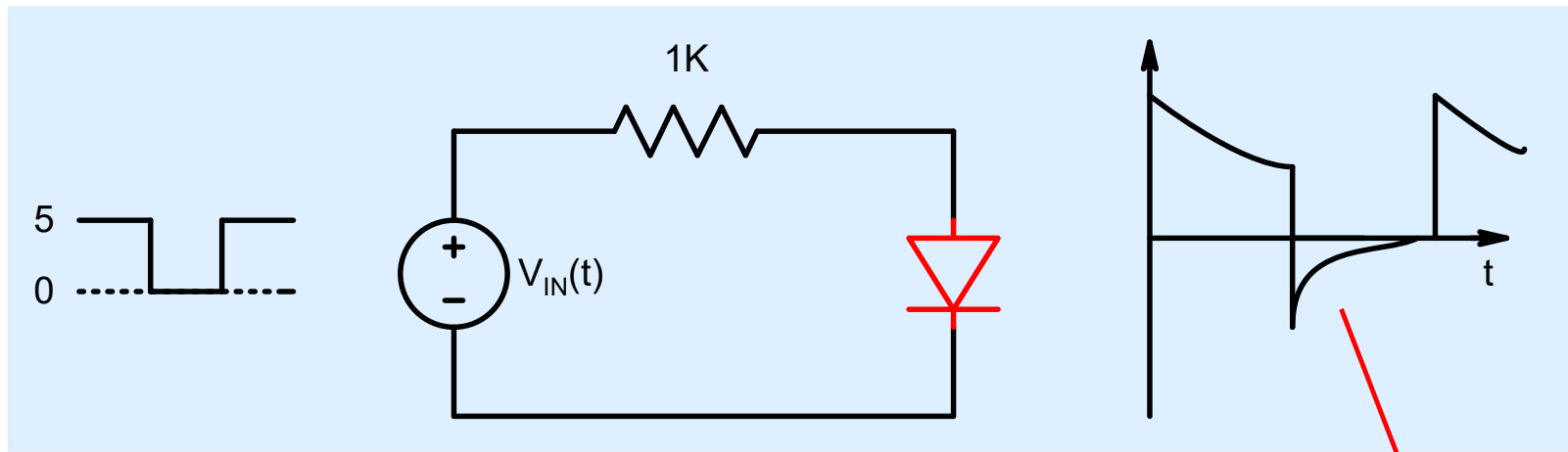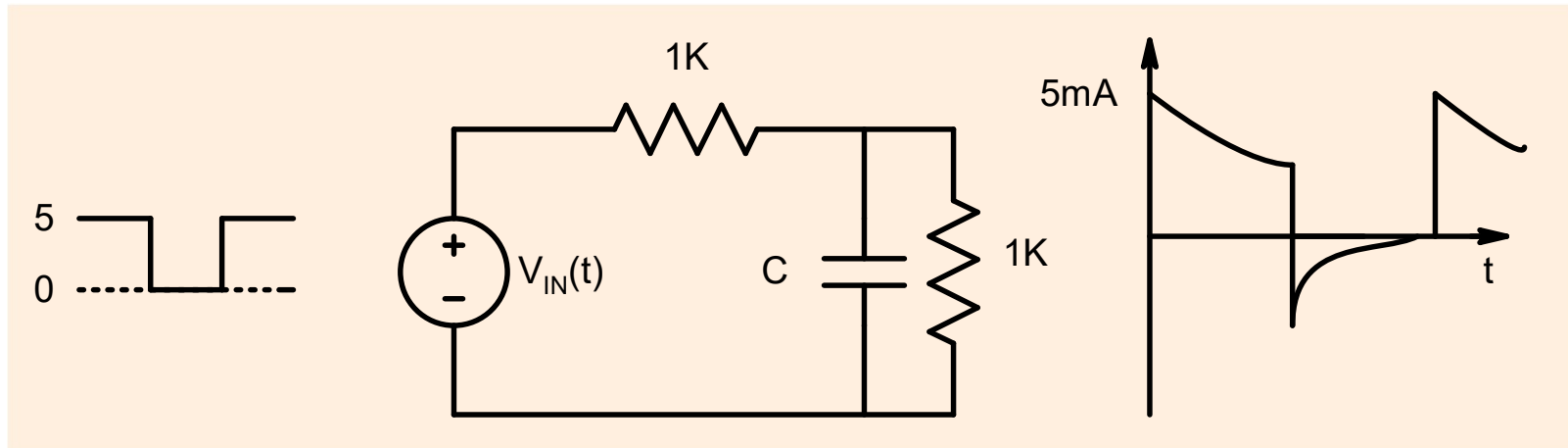


Current in reverse direction

Transient Response

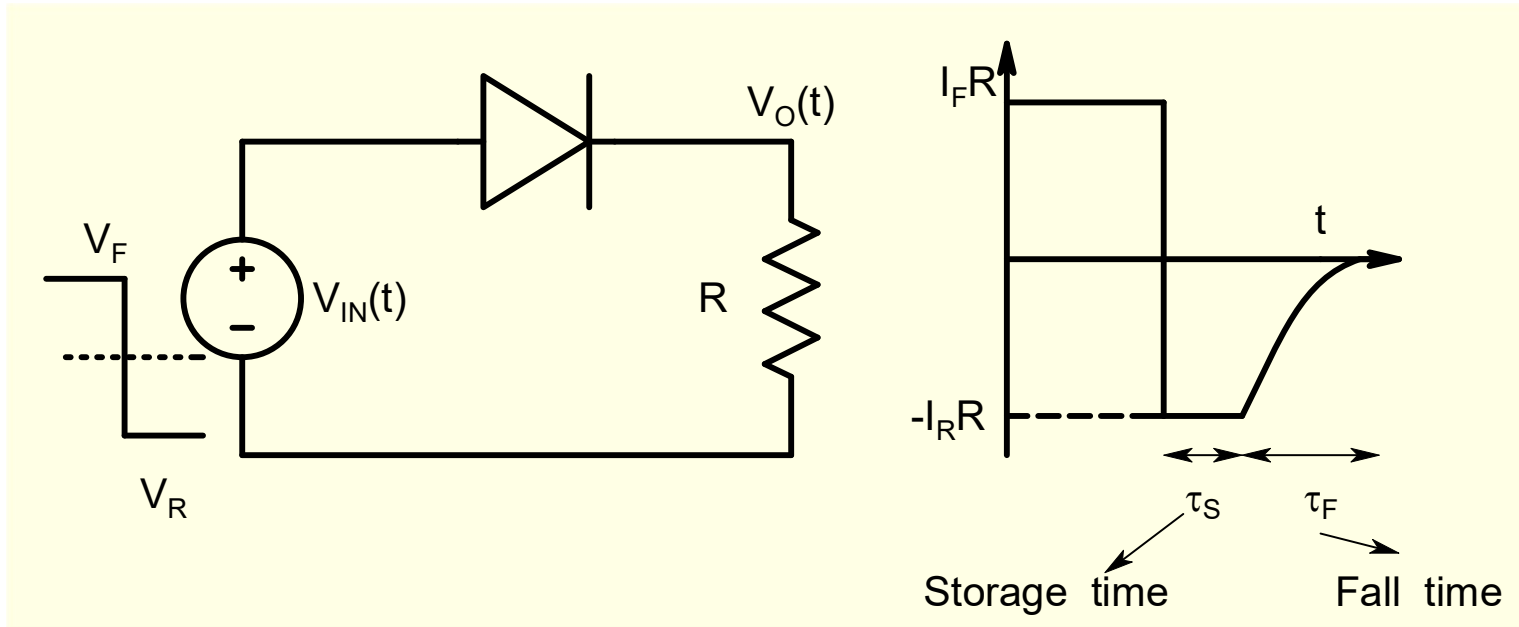

Diode does not switch off instantly but remains conducting for a period called reverse recovery time which is sum of storage and fall delay times..

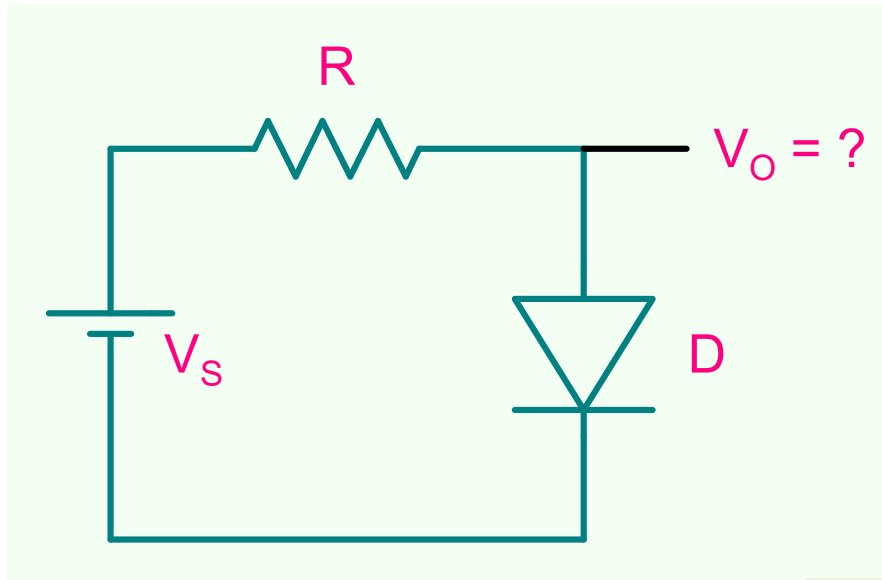Analysis using non-linear diode model is not easy



$$V_S = IR + V_O \quad (1)$$

$$I = I_S \times \left\{ \exp\left(\frac{V_O}{nV_T}\right) - 1 \right\} \quad (2)$$

$$\Rightarrow V_O = nV_T \times \ln\left(\frac{I}{I_S} + 1\right) \quad (3)$$

$$\Rightarrow V_S = IR + nV_T \times \ln\left(\frac{I}{I_S} + 1\right) \quad (4)$$

Iterative Method:

$$V_S = IR + V_O \quad (1)$$

$$I = I_S \times \left\{ \exp\left(\frac{V_O}{nV_T}\right) - 1 \right\} \quad (2)$$

Assume

$$V_O = 0.6\text{V}$$

Calculate


$$I = \frac{V_S - V_O}{R}$$


Re-calculate

$$V_O = nV_T \times \ln(I/I_S + 1)$$

Convergence:

$$\frac{\Delta I}{I} \leq \varepsilon$$

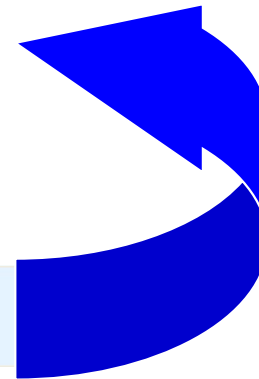

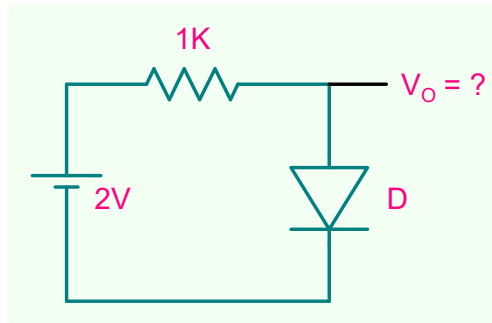

$$I = I_S \times \left\{ \exp\left(\frac{V}{V_T}\right) - 1 \right\}$$

$$I_S = 2 \times 10^{-15} \text{ A}$$

$$V_T = kT / q \cong 26 \text{ mV at } T = 300\text{K}$$

Assume V_O

$$V_O = 0.5$$

$$V_O = 0.711$$

$$V_O = 0.707$$

$$I = \frac{V_S - V_O}{R}$$

$$I = 1.5 \times 10^{-3}$$

$$I = 1.289 \times 10^{-3}$$

$$I = 1.293 \times 10^{-3}$$


$$V_O = nV_T \times \ln(I/I_S + 1)$$

$$V_O = 0.711$$

$$V_O = 0.707$$

$$V_O = 0.707$$

CONVERGENCE

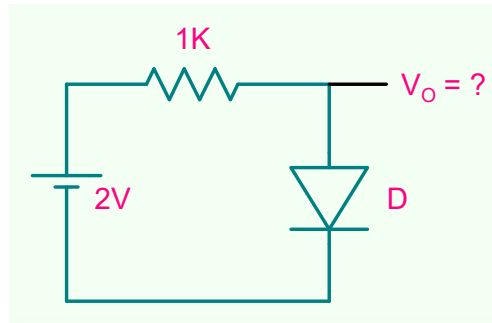

$$I = I_S \times \left\{ \exp\left(\frac{V}{V_T}\right) - 1 \right\}$$

$$I_S = 2 \times 10^{-15} \text{ A}$$

$$V_T = kT / q \cong 26 \text{ mV at } T = 300\text{K}$$

Assume V_O

$$V_O = 1.0$$

$$V_O = 0.7$$

$$V_O = 0.707$$

$$I = \frac{V_S - V_O}{R}$$

$$I = 1.0 \times 10^{-3}$$

$$I = 1.3 \times 10^{-3}$$

$$I = 1.293 \times 10^{-3}$$

$$V_O = nV_T \times \ln(I/I_S + 1)$$


$$V_O = 0.7$$

$$V_O = 0.707$$

$$V_O = 0.707$$

CONVERGENCE to the same Result


Graphical Method: Method of Load Line

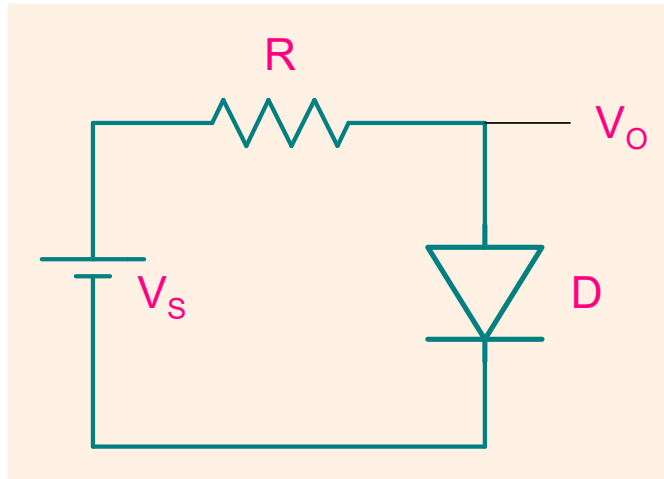


$$V_S = I \times R + V_O$$

$$I = \frac{V_S - V_O}{R}$$
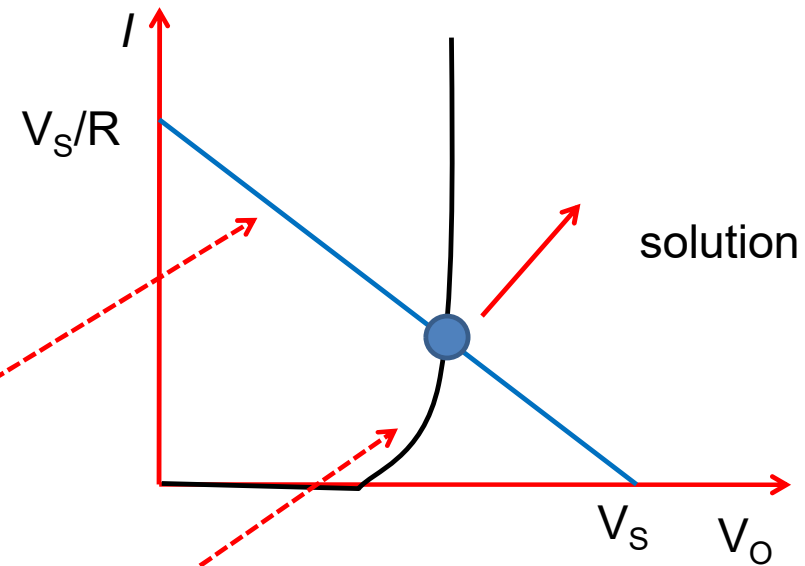
$$I = I_S \times \left\{ \exp\left(\frac{V_O}{n V_T}\right) - 1 \right\}$$



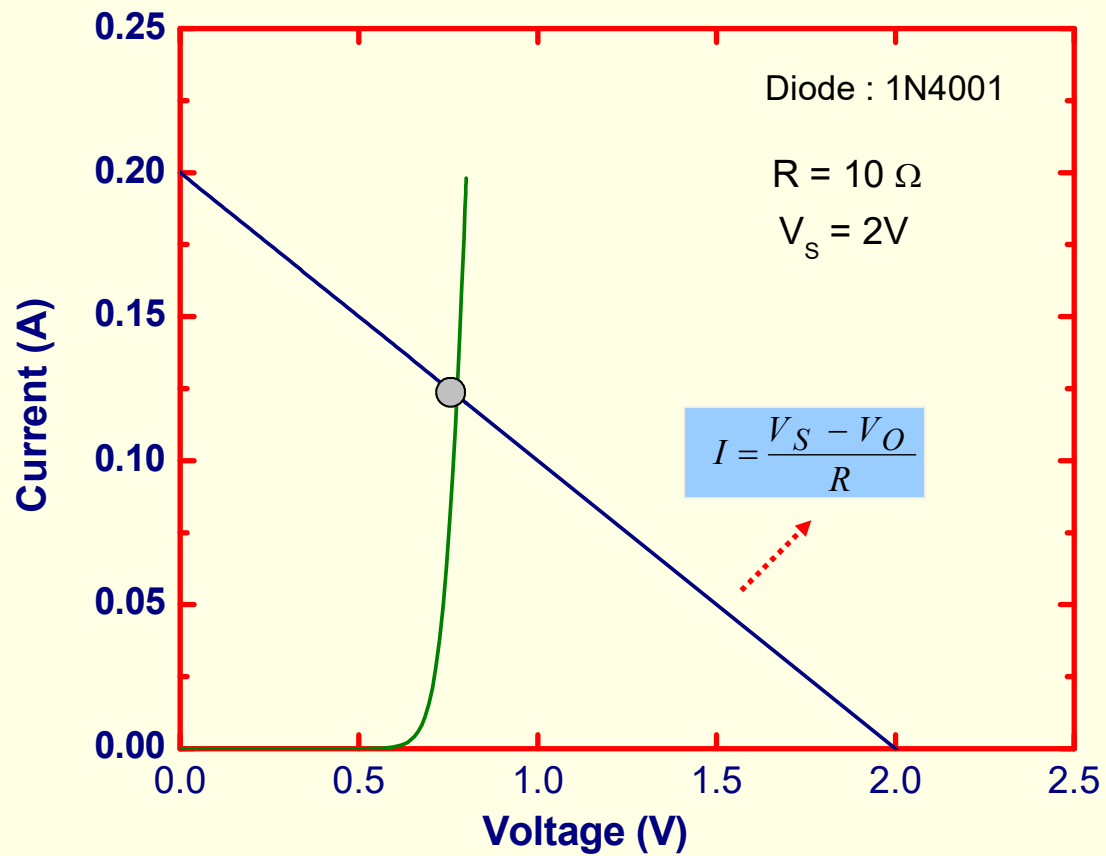


$$V_O = 0.77V; I = 0.12A$$

**For hand analysis of circuits, we need
simpler models!**


What is a model?

“A model is a representation for a **PURPOSE**”



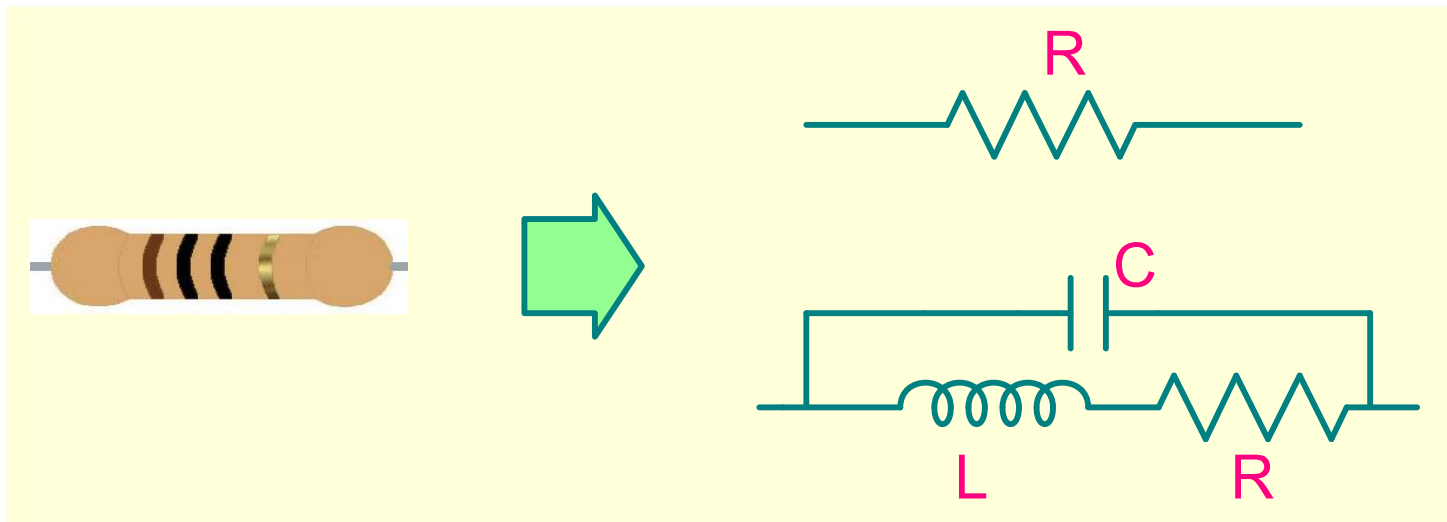
Depending on the purpose, an element can have several different models



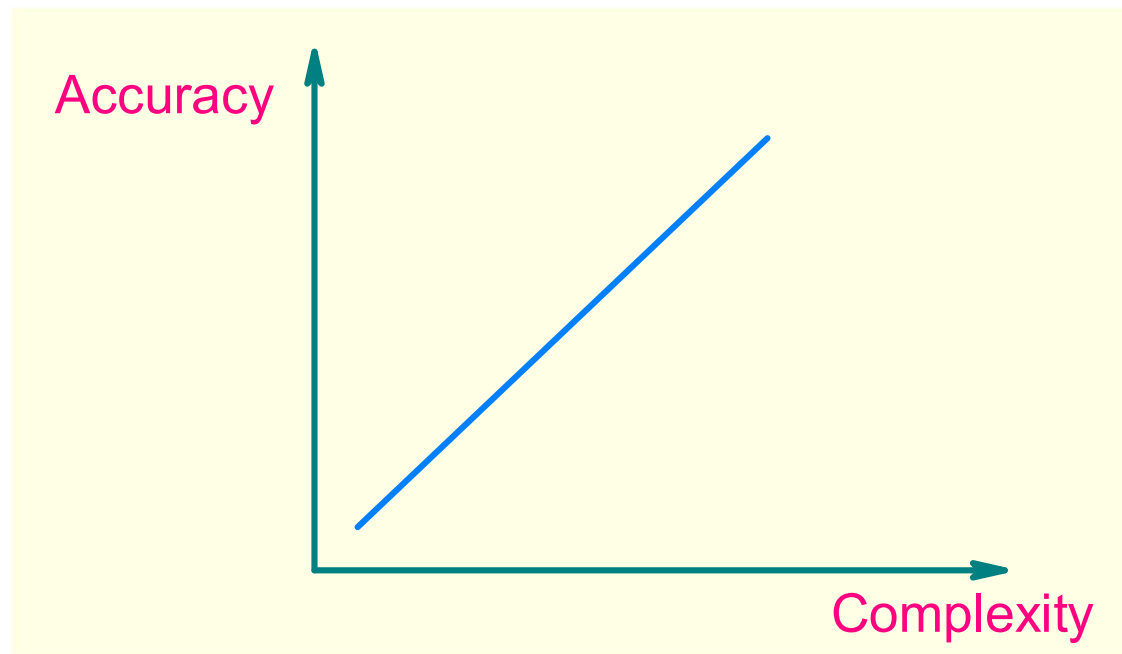In general, there is a tradeoff between Accuracy and Complexity of model



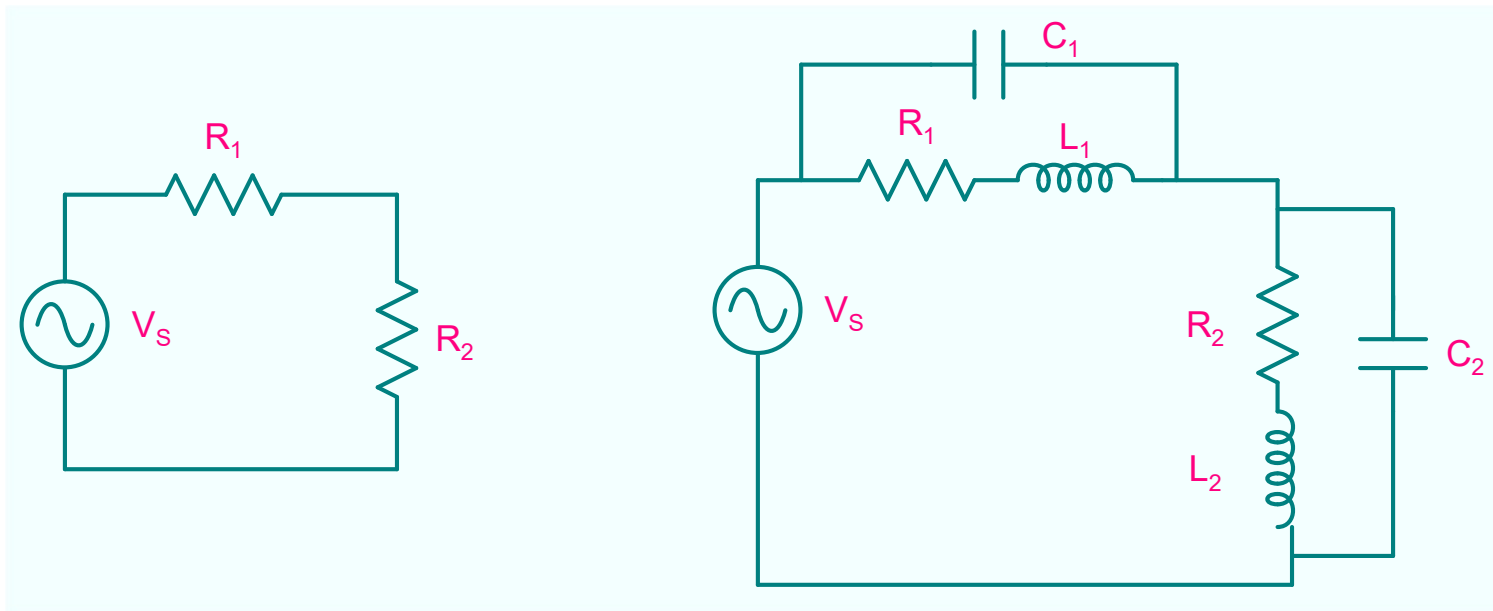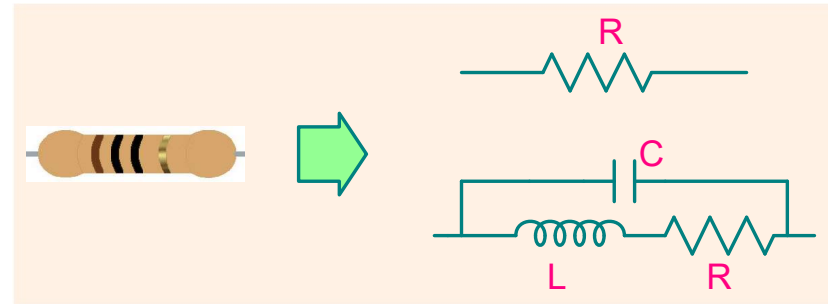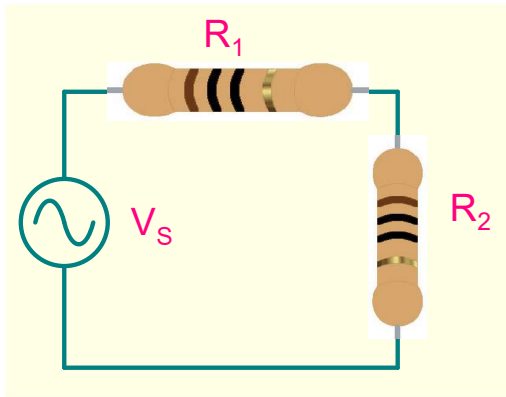
What is the use of a less accurate model?



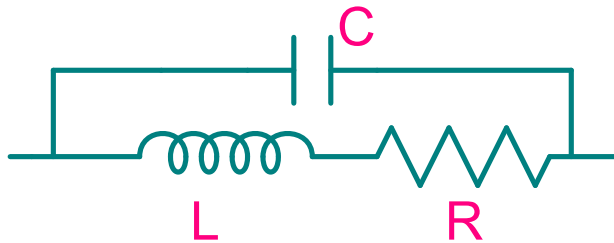1. A simpler model makes analysis easier



$$\frac{V_2}{V_S} = \frac{R_2}{R_1 + R_2}$$



$$\frac{V_2}{V_S} = \frac{R_2 + j\omega L_2}{R_2 + j\omega L_2 + (R_1 + j\omega L_1) \frac{j\omega C_2 R_2 - \omega^2 L_2 C_2 + 1}{j\omega C_1 R_1 - \omega^2 L_1 C_1 + 1}}$$


The results of analysis are easier to understand

3. The results of analysis can be used easily to carry out the design

Design the circuit such that :

$$\frac{V_2}{V_s} = 0.2 \quad \text{at 1kHz frequency}$$

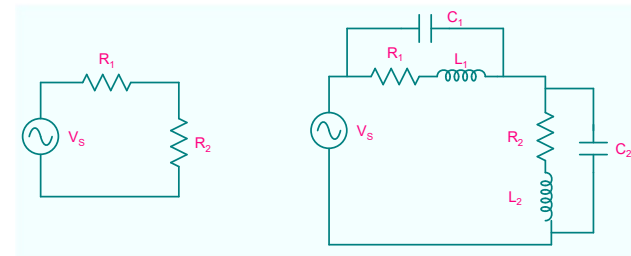
$$\frac{R_2}{R_1 + R_2} = 0.2 \quad \Rightarrow \quad \frac{R_1}{R_2} = 4$$



Try doing the design with this expression:


$$\frac{V_2}{V_s} = \frac{R_2 + j\omega L_2}{R_2 + j\omega L_2 + (R_1 + j\omega L_1) \frac{j\omega C_2 R_2 - \omega^2 L_2 C_2 + 1}{j\omega C_1 R_1 - \omega^2 L_1 C_1 + 1}}$$

Role of simple model in design cycle

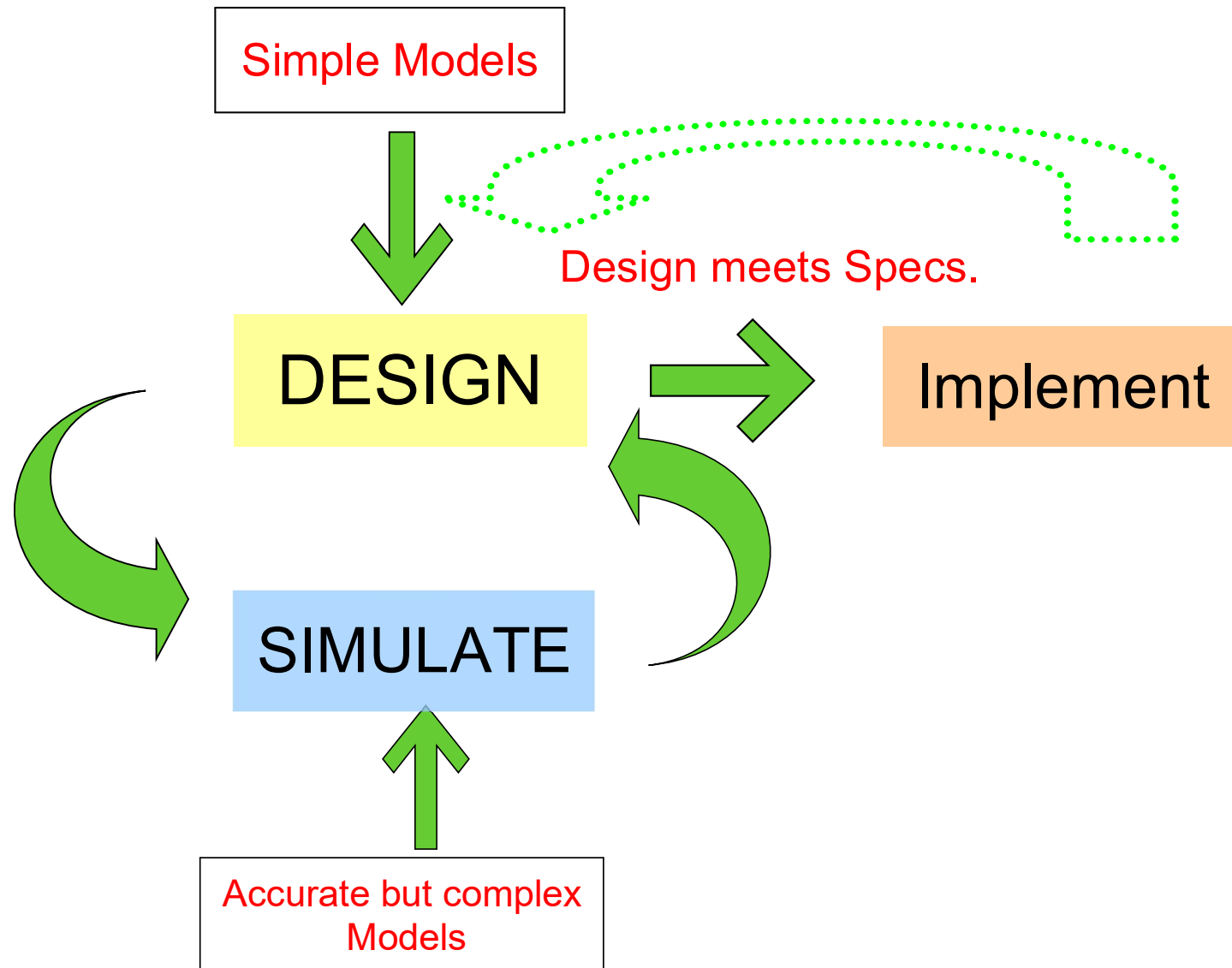


- Analysis using a **non-linear** diode model is relatively difficult and time consuming.
- It also does not give a symbolic expression that can provide insight and help in the design of the circuit.

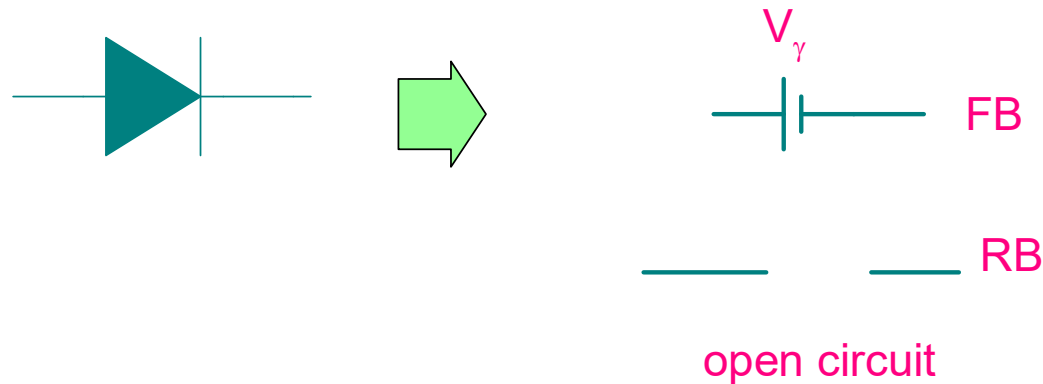Need **Simpler** and **Linear** Device Models



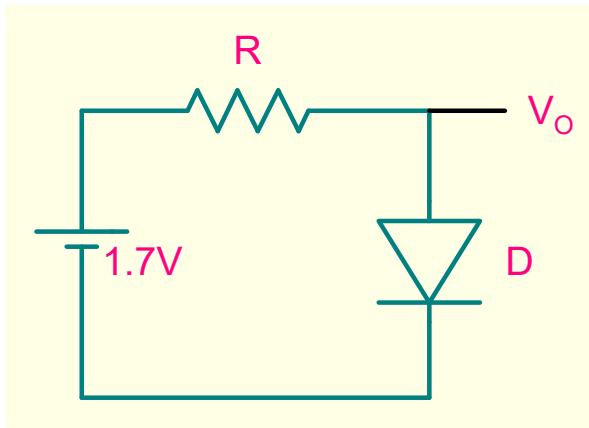What should we take as diode drop?.....0.7V?



$$I = I_S \times \left\{ \exp\left(\frac{V}{V_T} \right) - 1 \right\}$$



$$I_S = 2 \times 10^{-15} \text{ A}$$


$$V_T = kT / q \cong 26 \text{ mV} \text{ at } T = 300\text{K}$$

$$R : 10\Omega \rightarrow 1M\Omega$$

Simple 0.7V model would predict:


$$I = \frac{1}{R}$$

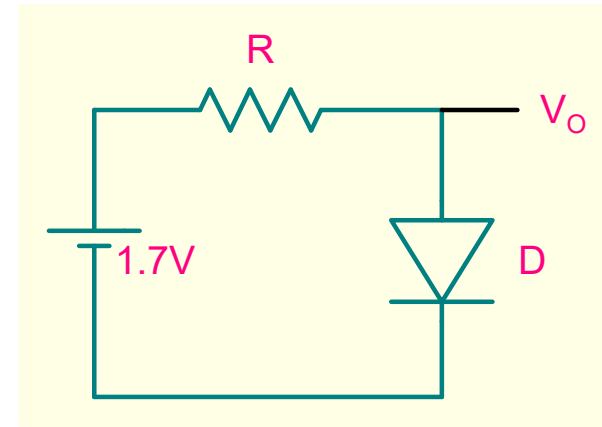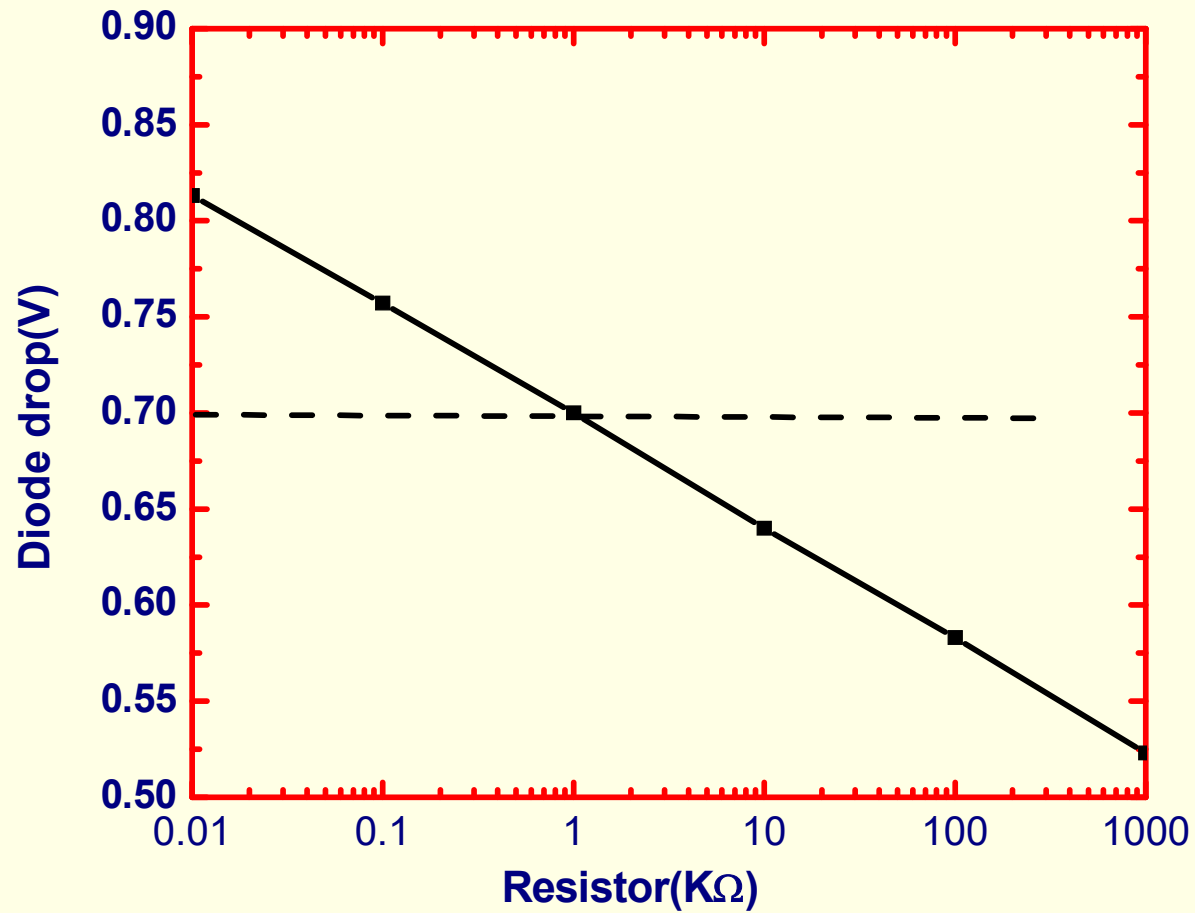

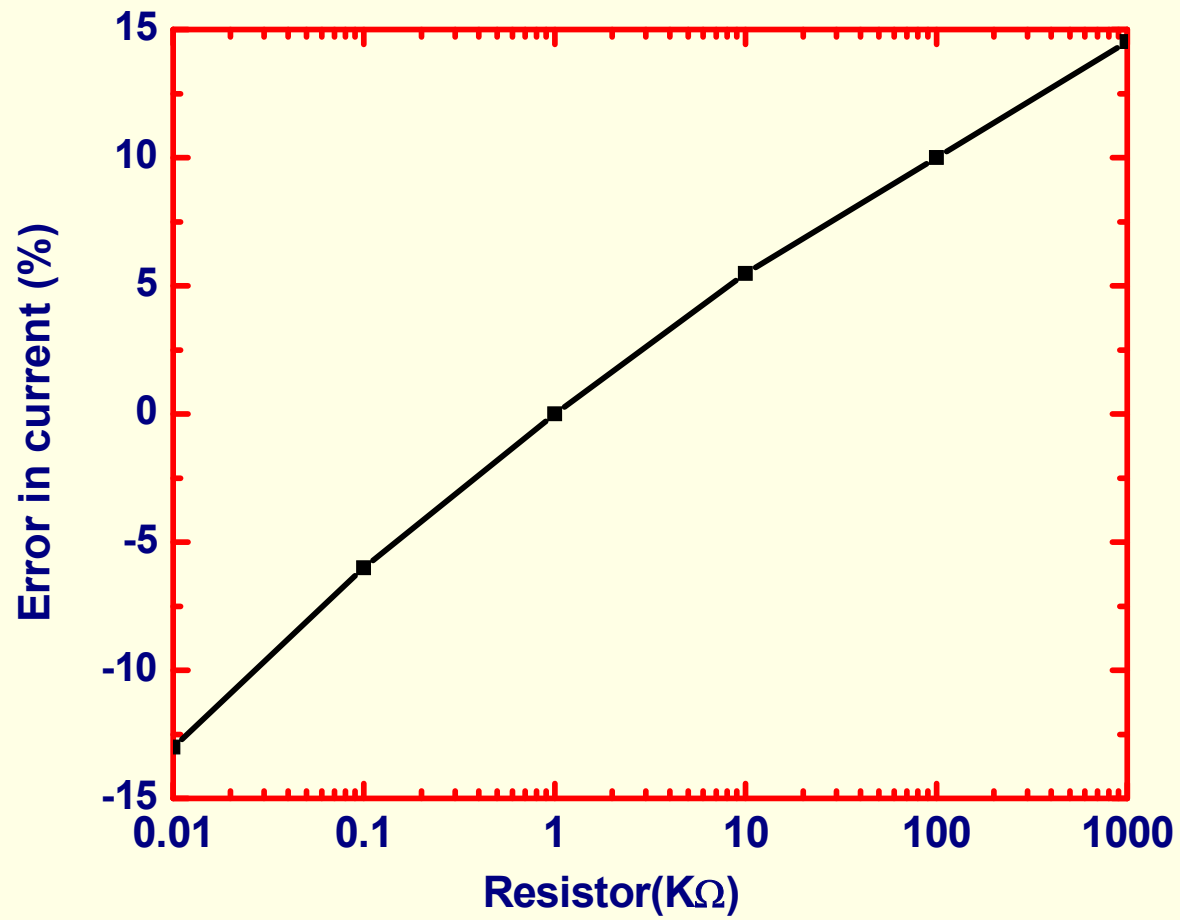


(100mA - 1 μ A)


Different Diode: ~1N4148

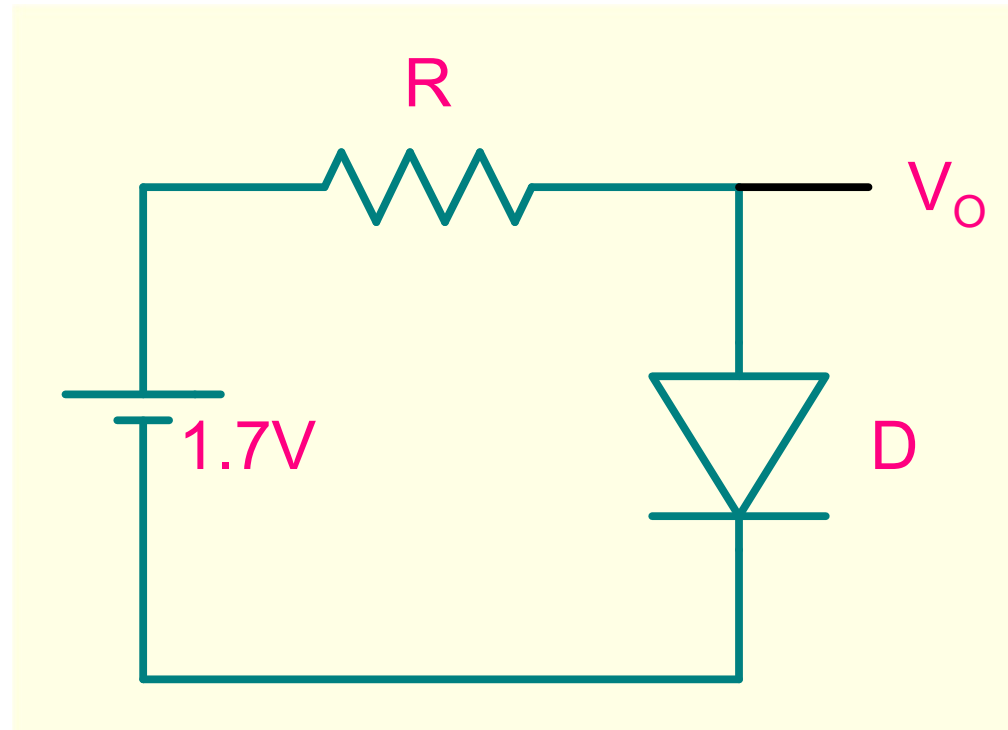


$$I = I_S \times \left\{ \exp\left(\frac{V}{nV_T} \right) - 1 \right\}$$
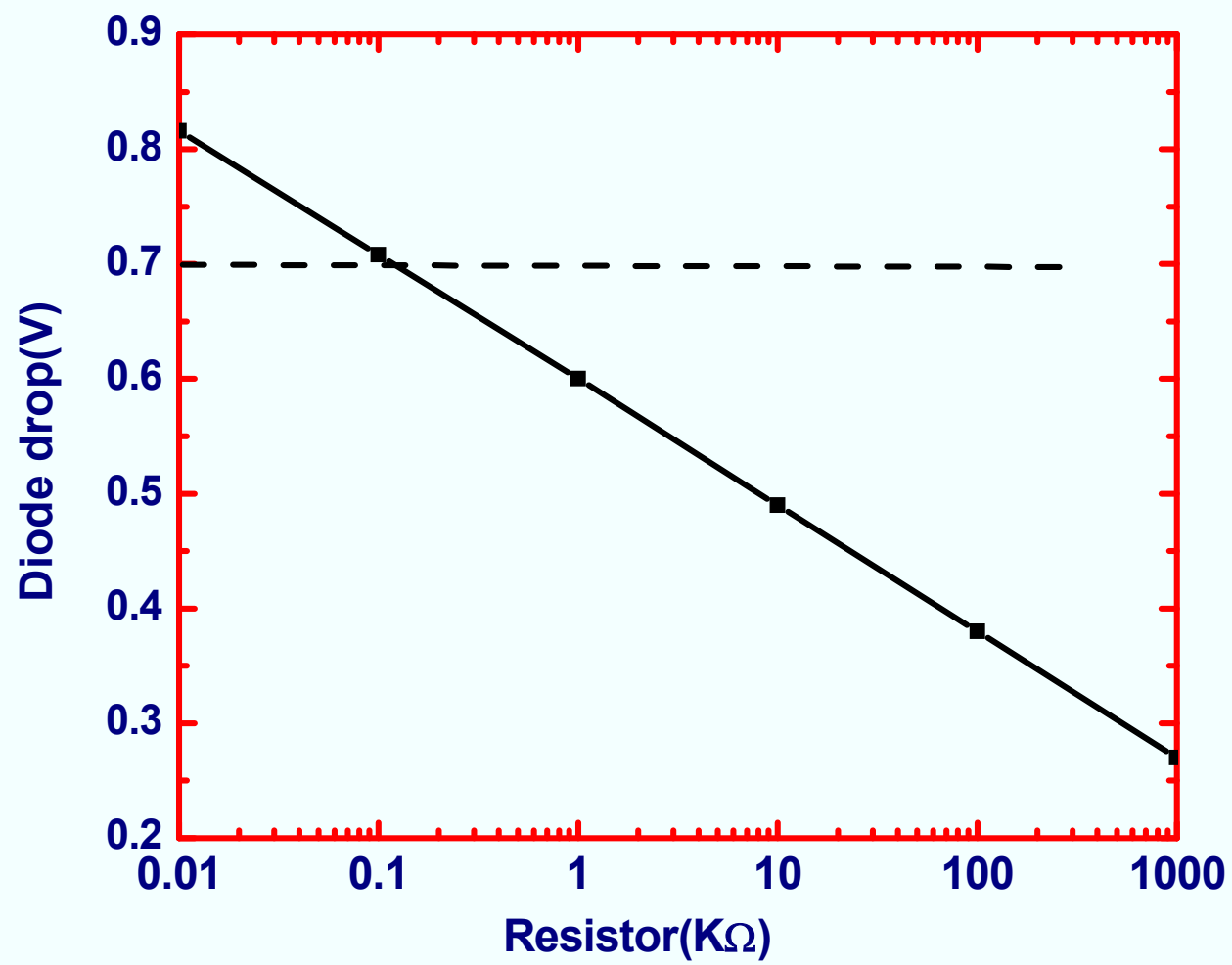
$$I_S = 5.9 \times 10^{-9} \text{ A} ; n = 1.91$$



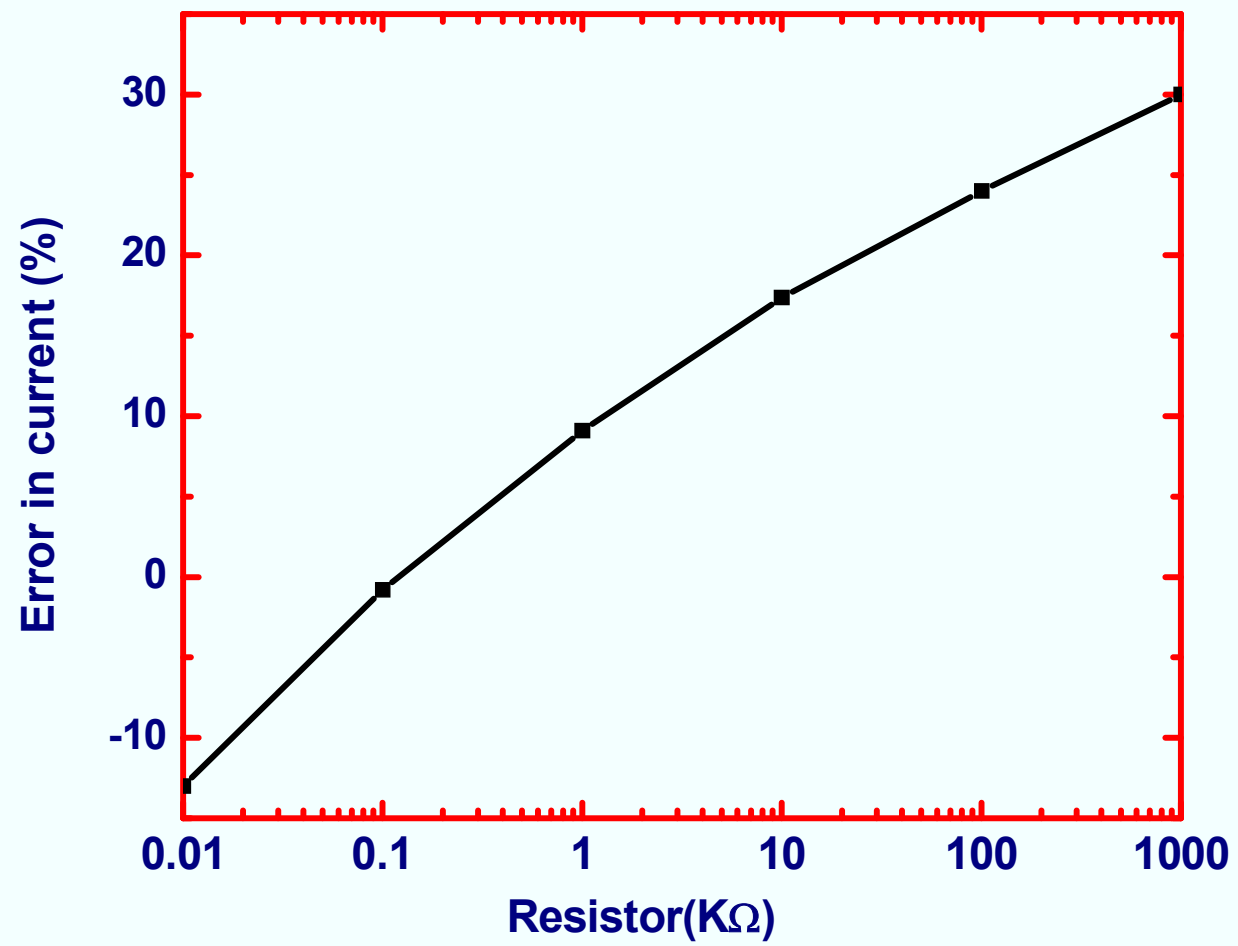

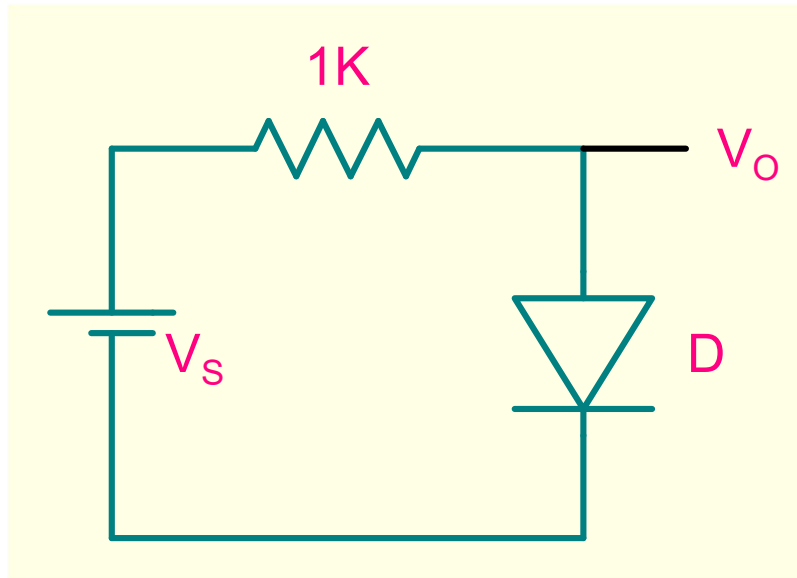Constant diode voltage approximation becomes worse as applied voltage approaches the diode drop !





$$I = \frac{V_S - V_D}{R}$$
$$\Delta I = -\frac{\Delta V_D}{R}$$
$$\frac{\Delta I}{I} = -\left(\frac{\Delta V_D}{V_S - V_D}\right)$$



As V_S approaches $V_D \rightarrow \left(\frac{\Delta I}{I}\right)$ increases

Error was ~9% with 1.7 V but 63% with 0.8V supply

A better Diode Model

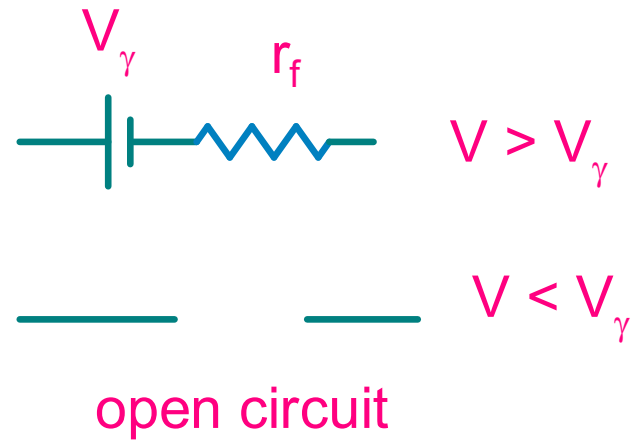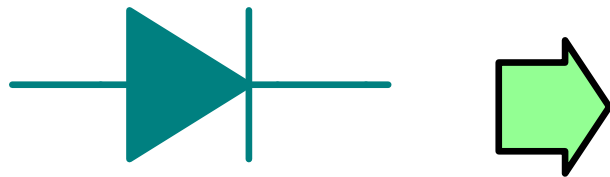

Piece-Wise Linear Model

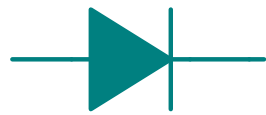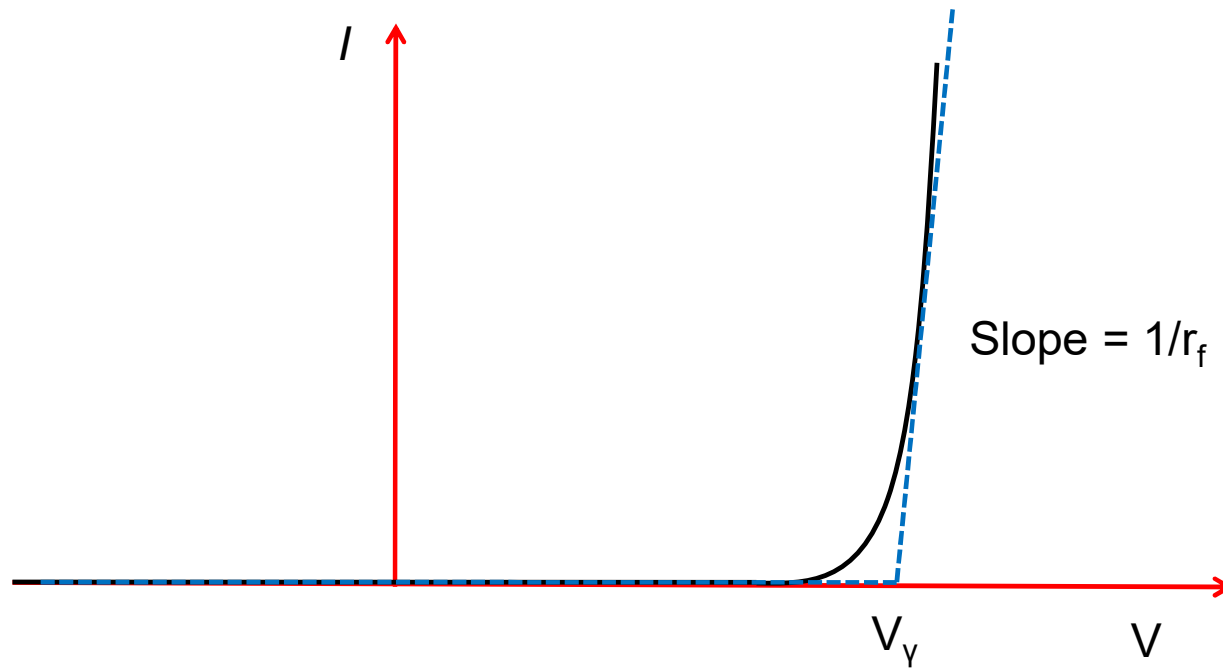

$$V > V_\gamma$$





$$V < V_\gamma$$

open circuit

V_γ is called cut-in or turn-on voltage and depends on nature of diode and range of current considered

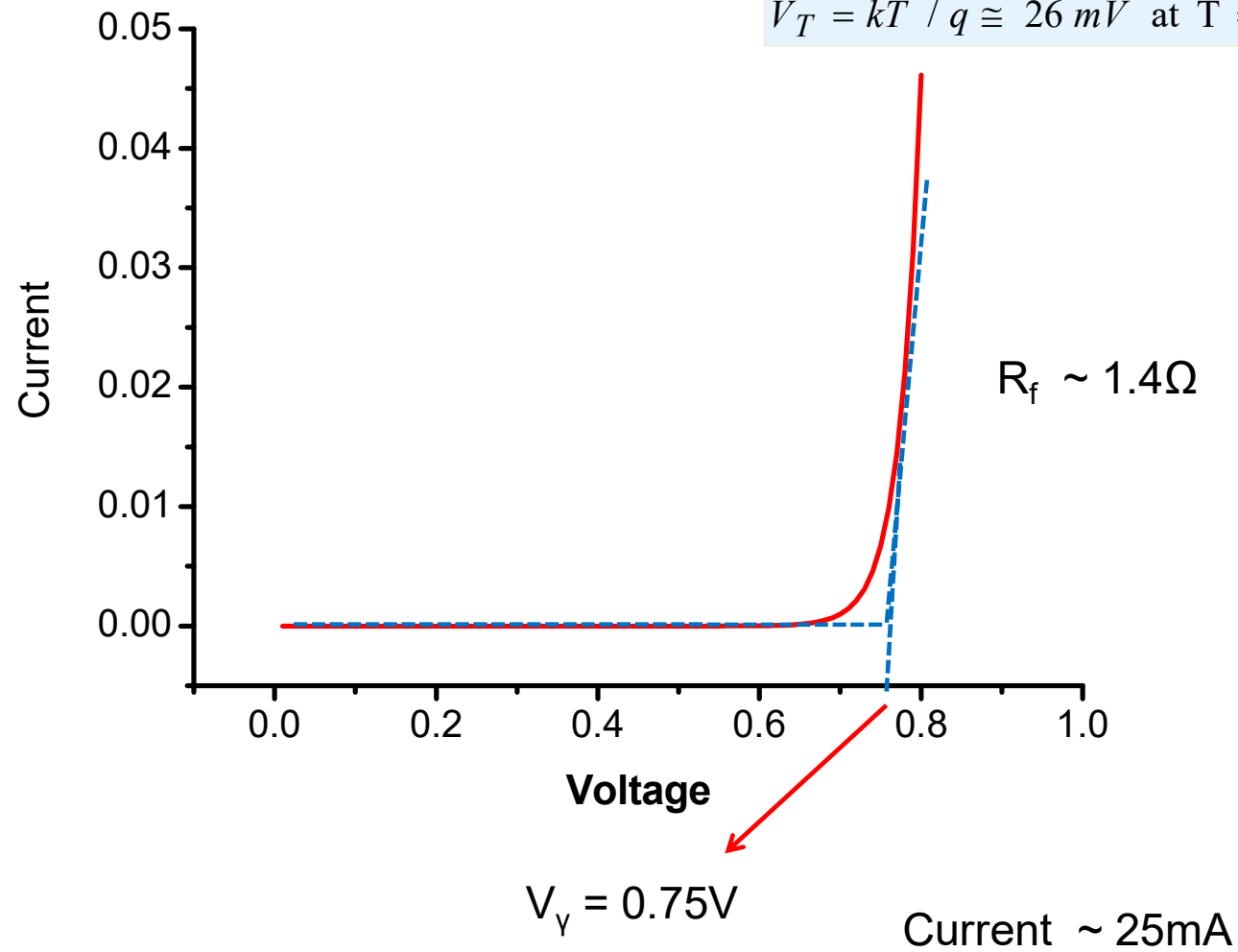
$$I = I_S \times \left\{ \exp\left(\frac{V}{V_T} \right) - 1 \right\}$$
$$I_S = 2 \times 10^{-15} \text{ A}$$
$$V_T = kT / q \cong 26 \text{ mV at } T = 300\text{K}$$



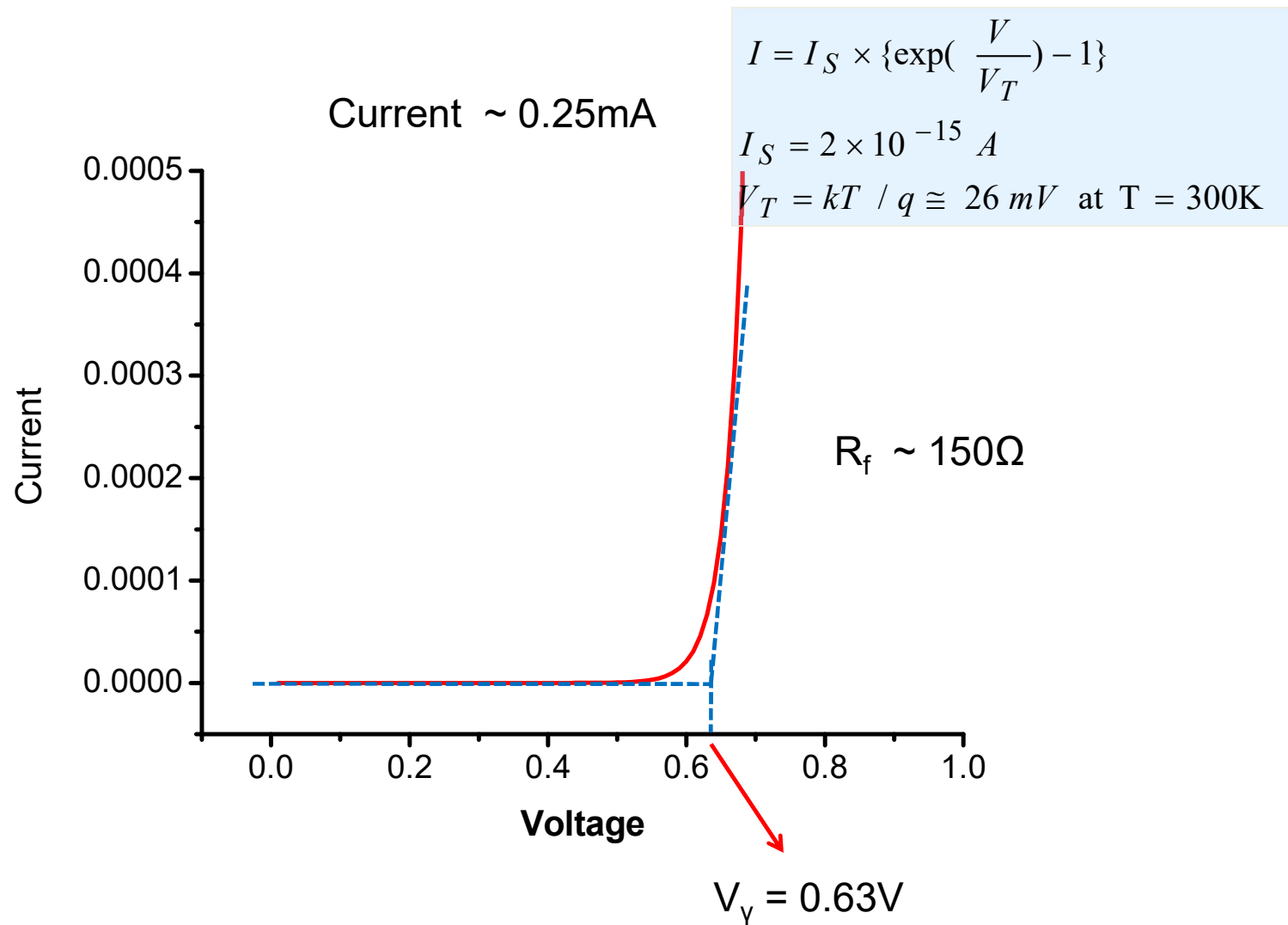


For most of our analysis, we will take $V_Y = 0.7\text{V}$ and $r_f \sim 10\Omega$

Even Simpler Diode Models

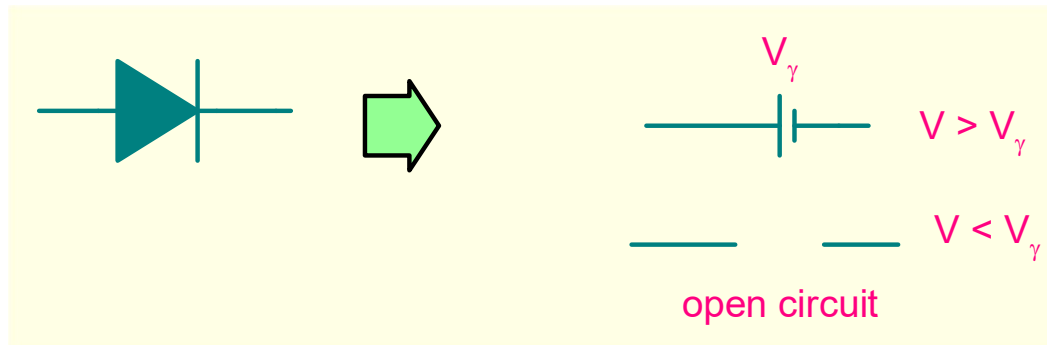

Ideal diode model

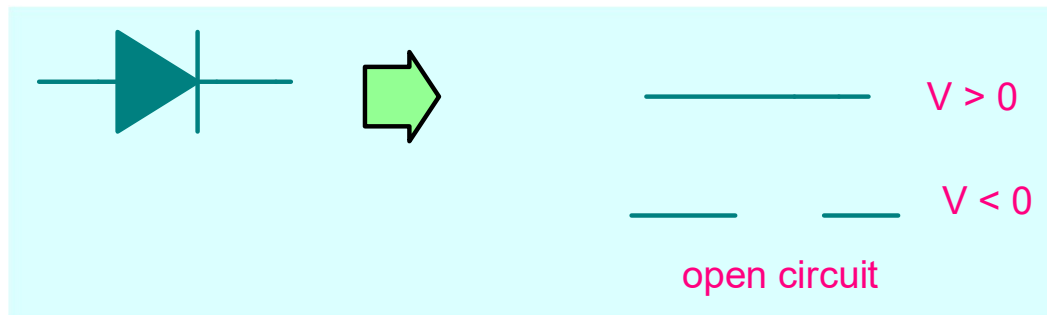


Diode Models



$$I = I_s \times \left\{ \exp\left(\frac{V_d}{V_T}\right) - 1 \right\}$$

Simplicity


Accuracy

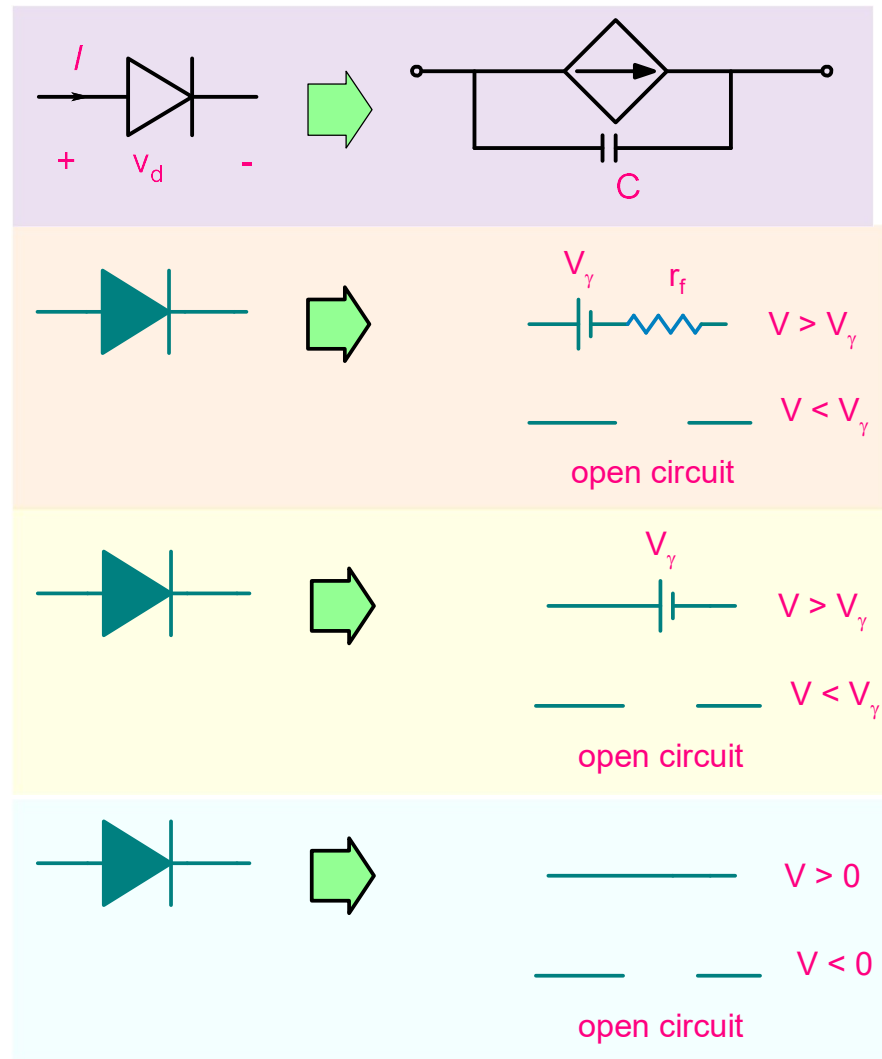

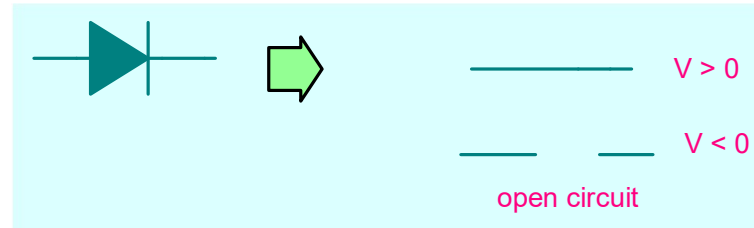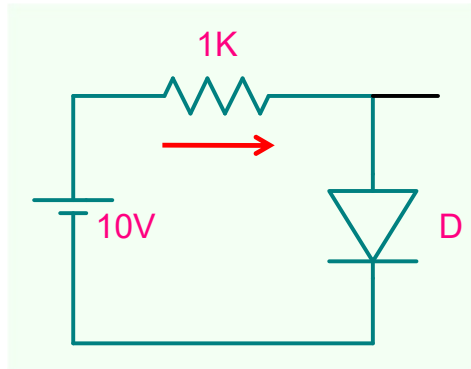Use the simplest model that will yield results with desired accuracy



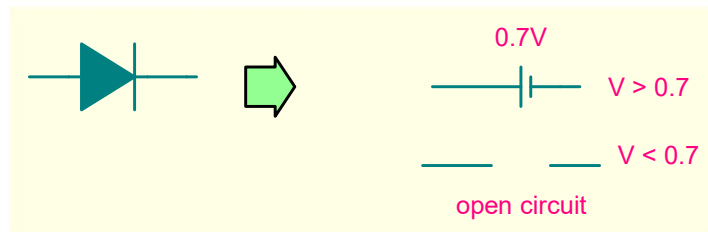
$$I = 10 / 10^3 = 10 \text{ mA} \quad 8.2\%$$




$$I = (10 - 0.7) / 10^3 = 9.3 \text{ mA}$$

0.65%

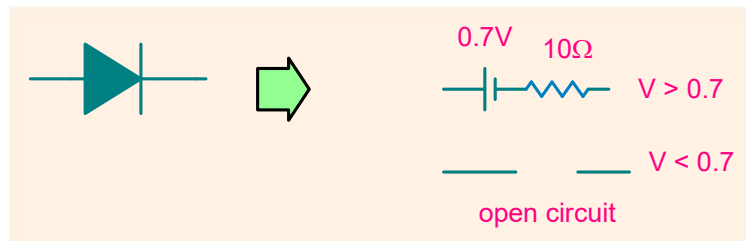



$$I = (10 - 0.7) / (10^3 + 10) = 9.208 \text{ mA}$$

-0.34%

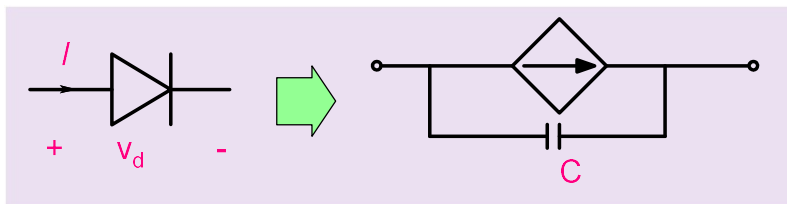


$$I = 9.24 \text{ mA}$$

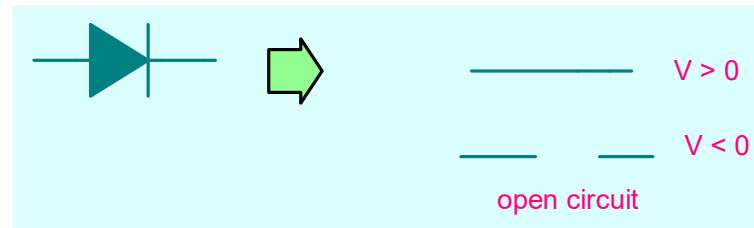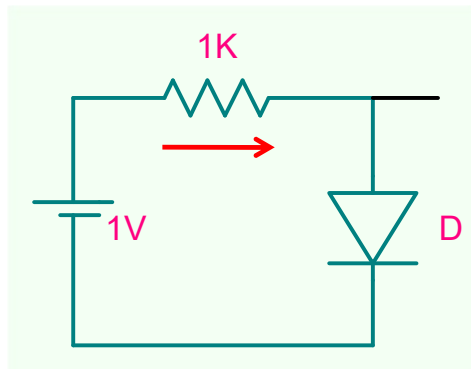
Use the simplest model that will yield results with desired accuracy



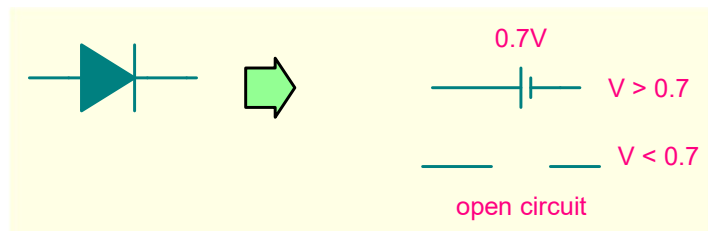
$$I = 1 / 10^3 = 1 \text{ mA} \quad \sim 200\%$$


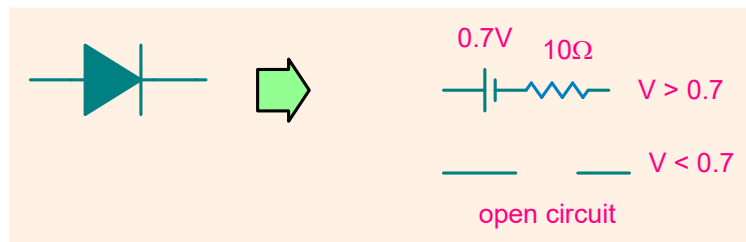
$$I = (1 - 0.7) / 10^3 = 0.3 \text{ mA} \quad -8.8\%$$



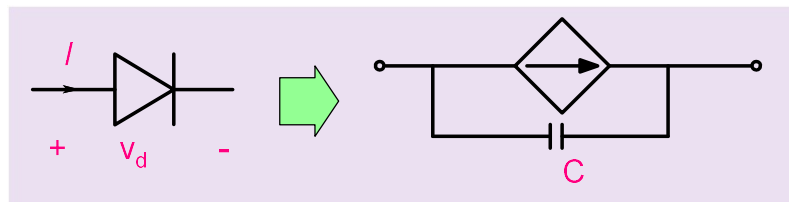
$$I = (1 - 0.7) / (10^3 + 10) = 0.297 \text{ mA} \quad -9.7\%$$



$$I = 0.329 \text{ mA}$$

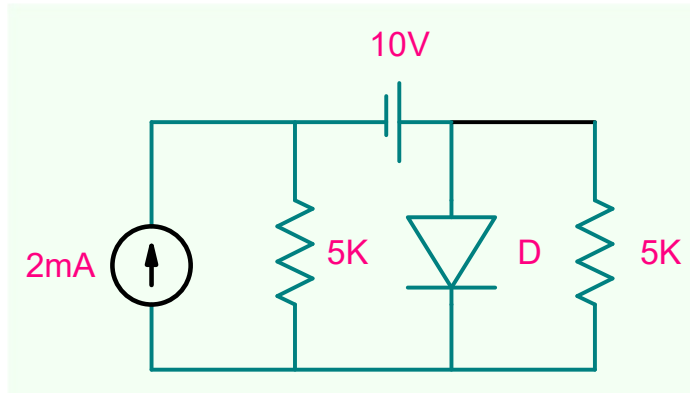Example

Find the current through the diode using ideal diode model





If it is not evident whether diode is forward or reverse biased then we can assume that it is forward biased, carry out analysis and then check if current through the diode is in **appropriate** direction. If not, diode is reverse biased and we carry out analysis again.

$$-2 \text{ mA} + \frac{-10}{5 \text{ K}} + i_D = 0$$

↓ Assume forward bias


$$i_D = 4 \text{ mA}$$

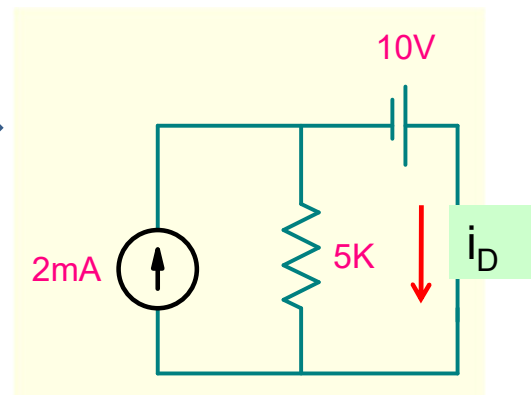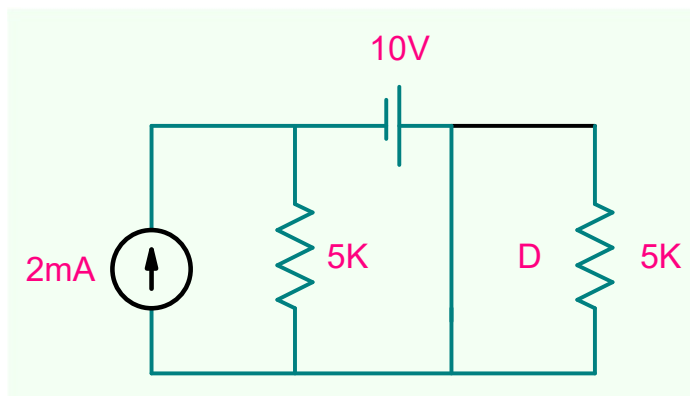Current is positive, so our assumption is correct




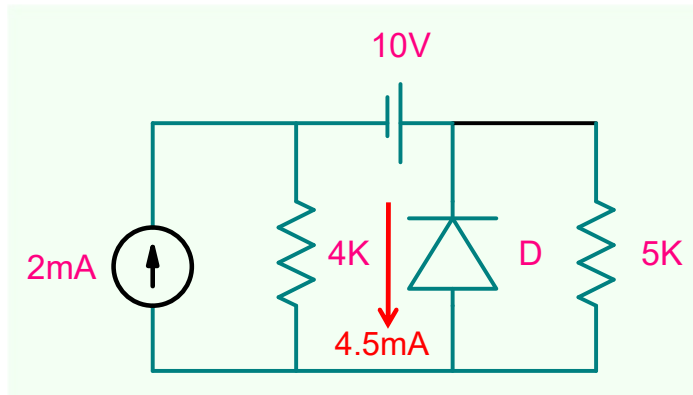Example

Find the current through the 5K resistor using ideal diode model




Assume forward bias

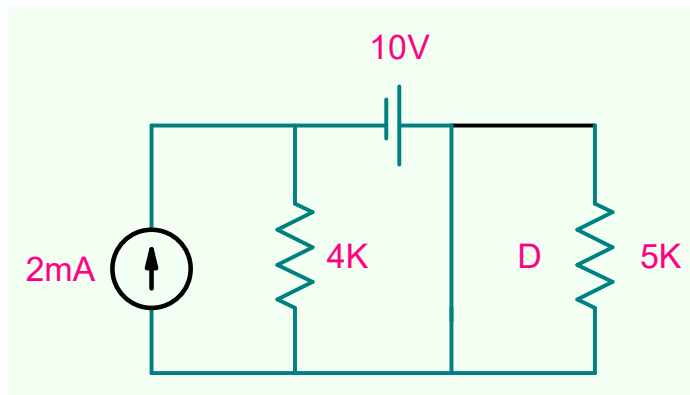


$$-2 \text{ mA} + \frac{-10}{4 \text{ K}} + i_D = 0$$


$$i_D = 4.5 \text{ mA}$$

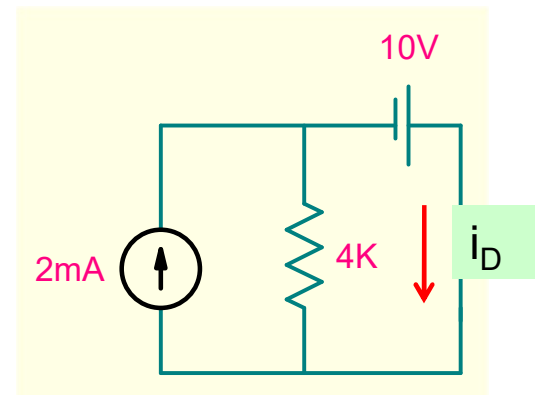But this cannot be, so our assumption is incorrect




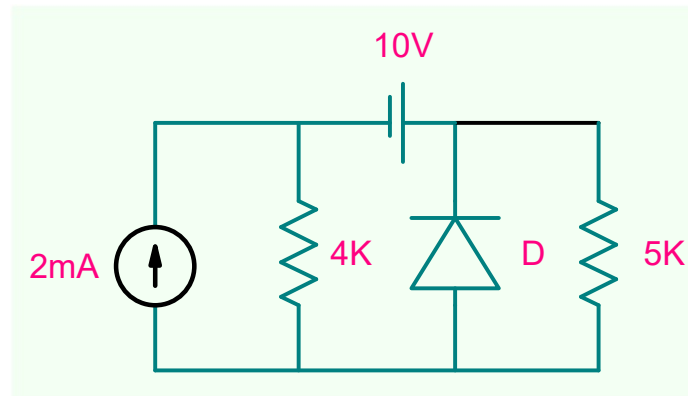


Assume reverse bias

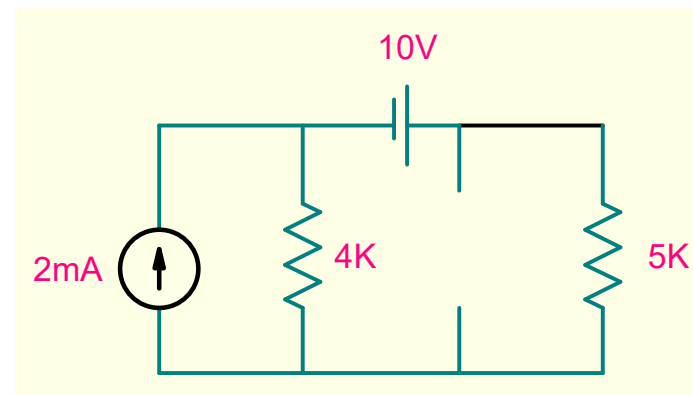


Design Cycle

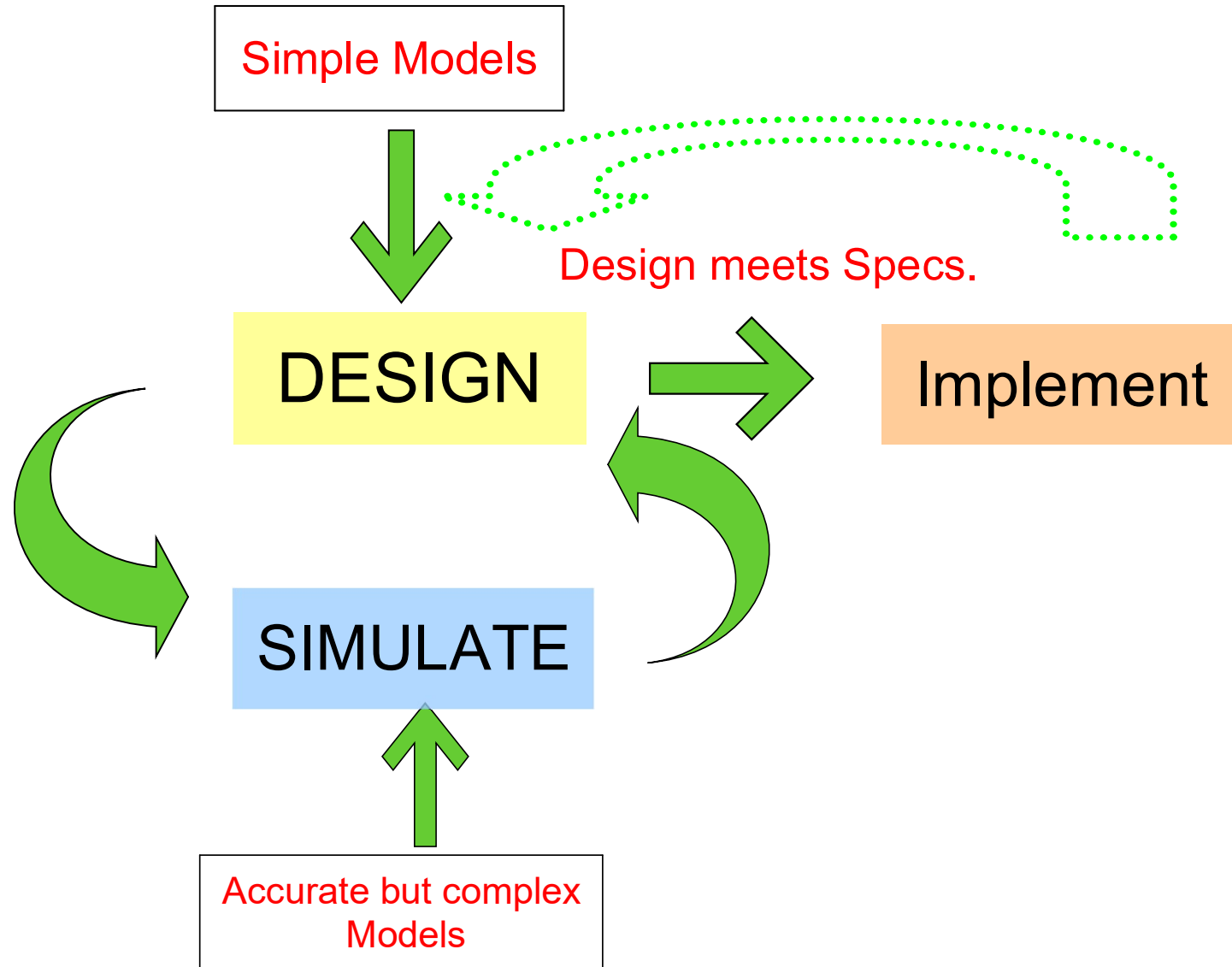

Design the following circuit

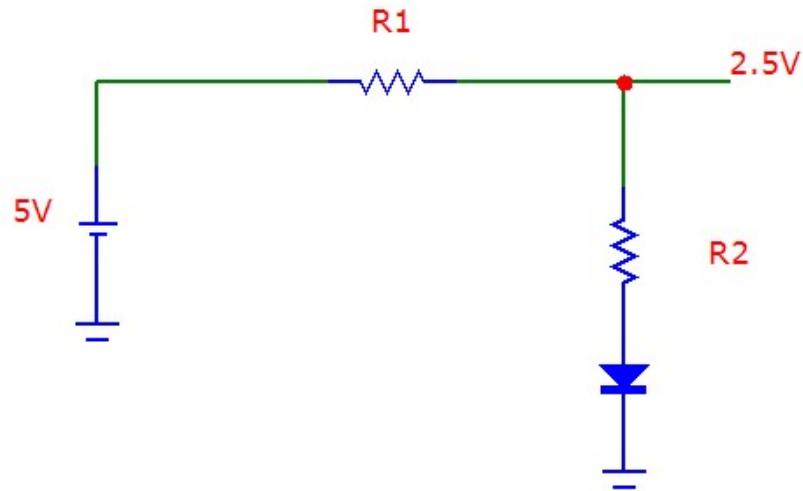


Assuming ideal diode model

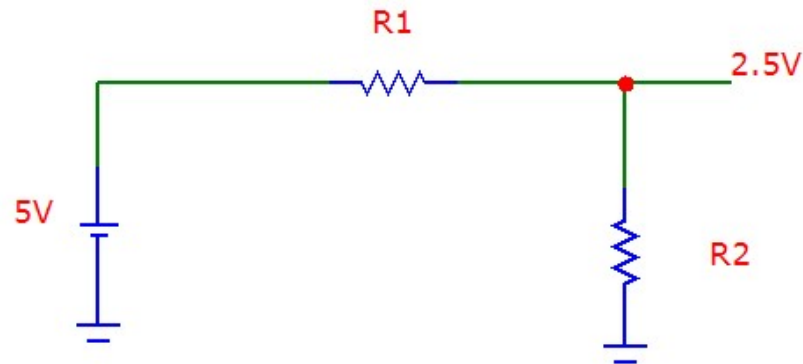


$$R_1 = R_2 = 1K$$

Carry out simulations to fine tune the design

Design Cycle

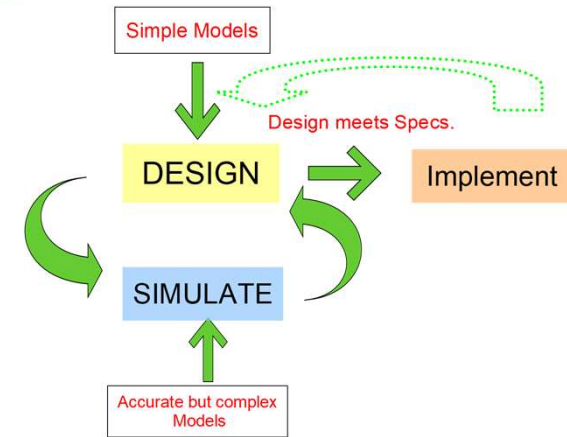

Initial design

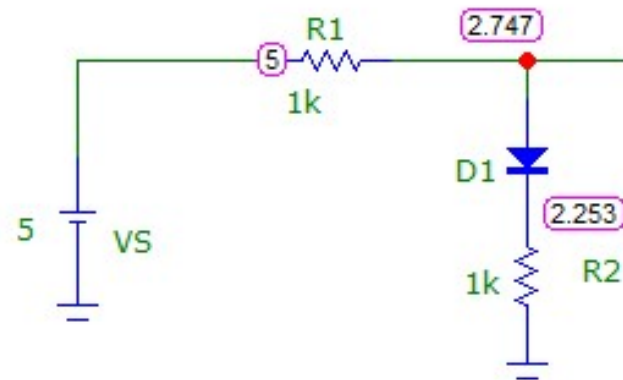

Final Design

