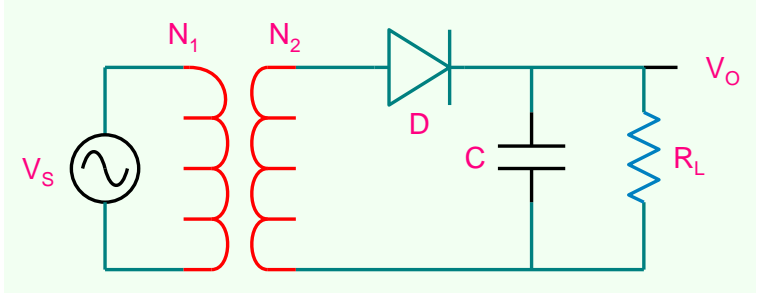


ESC201T : Introduction to Electronics



Lecture 24: Power Supply (part-2)



B. Mazhari
Dept. of EE, IIT Kanpur




Full wave Rectifier



$$V_r \cong \frac{V_M}{fR_L C}$$

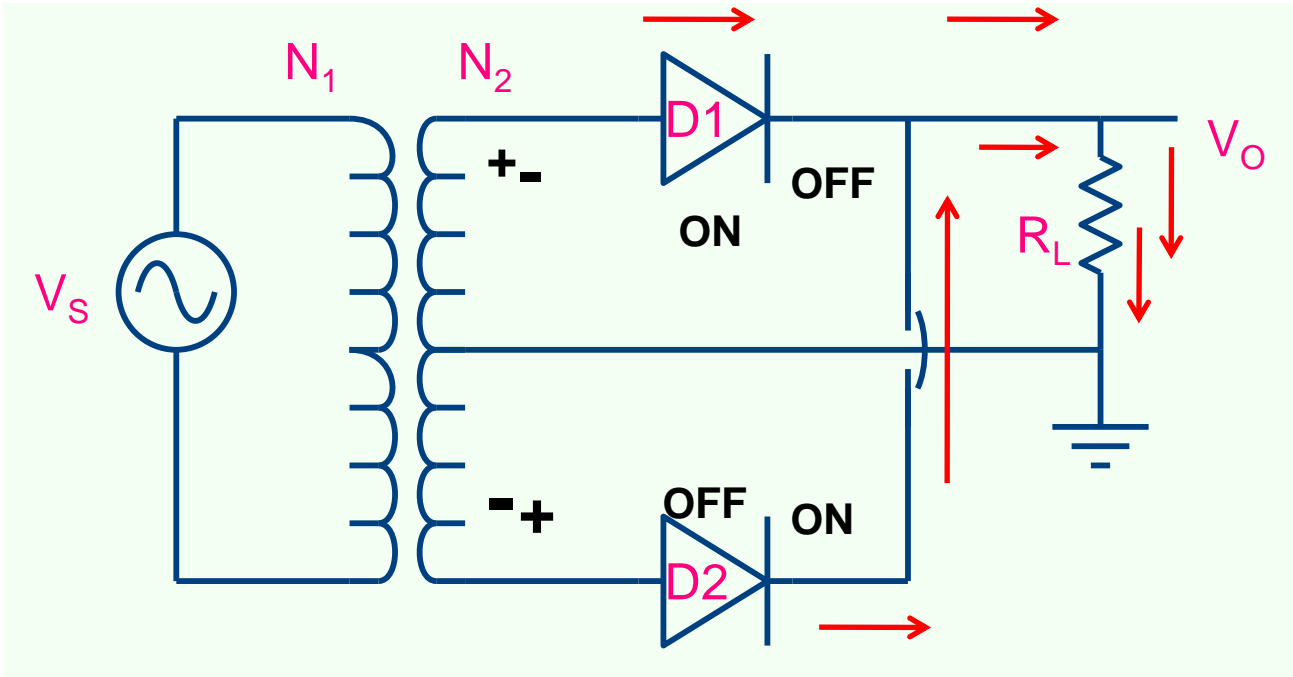
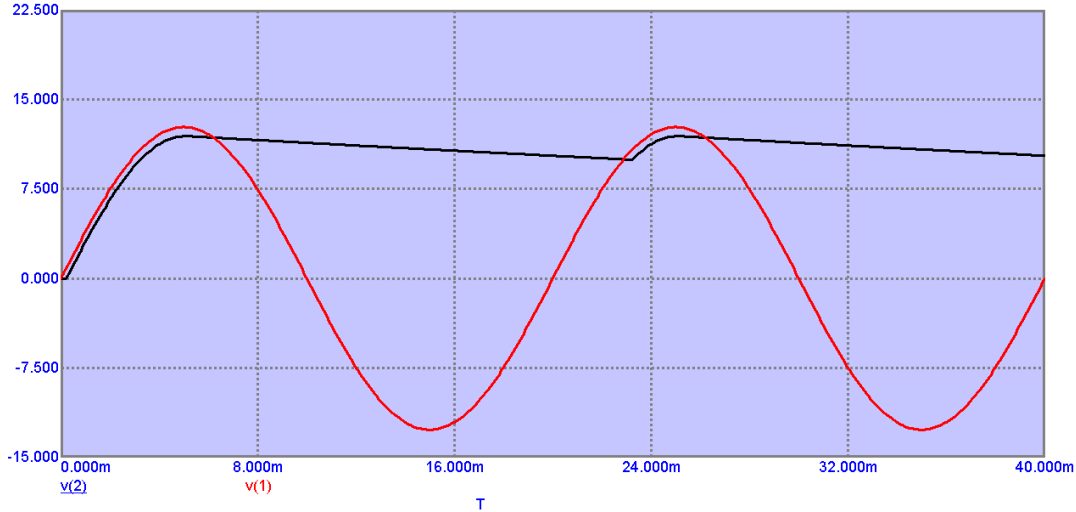


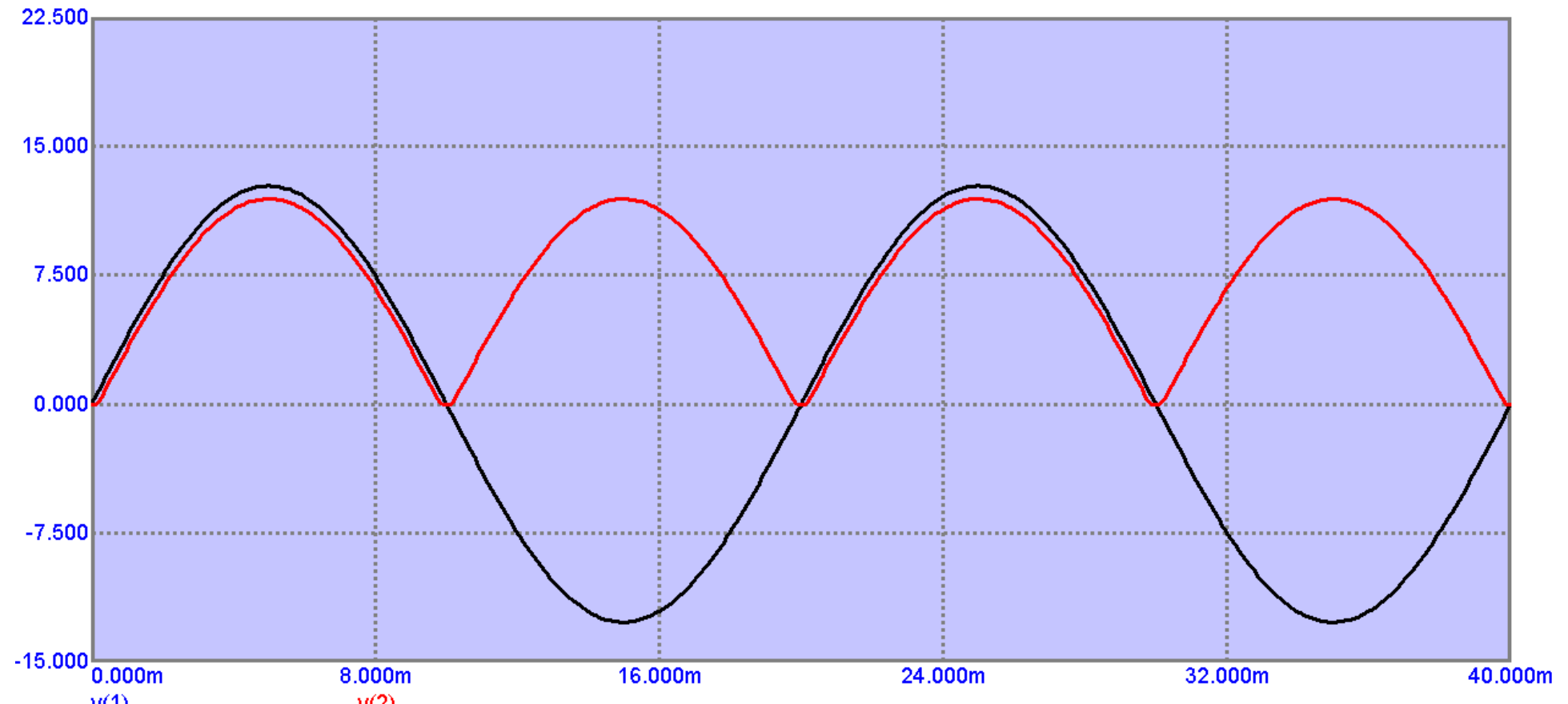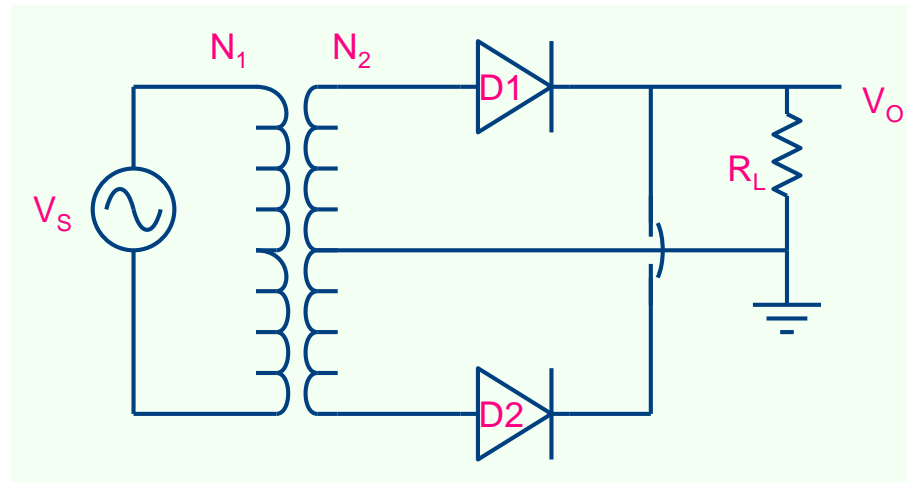

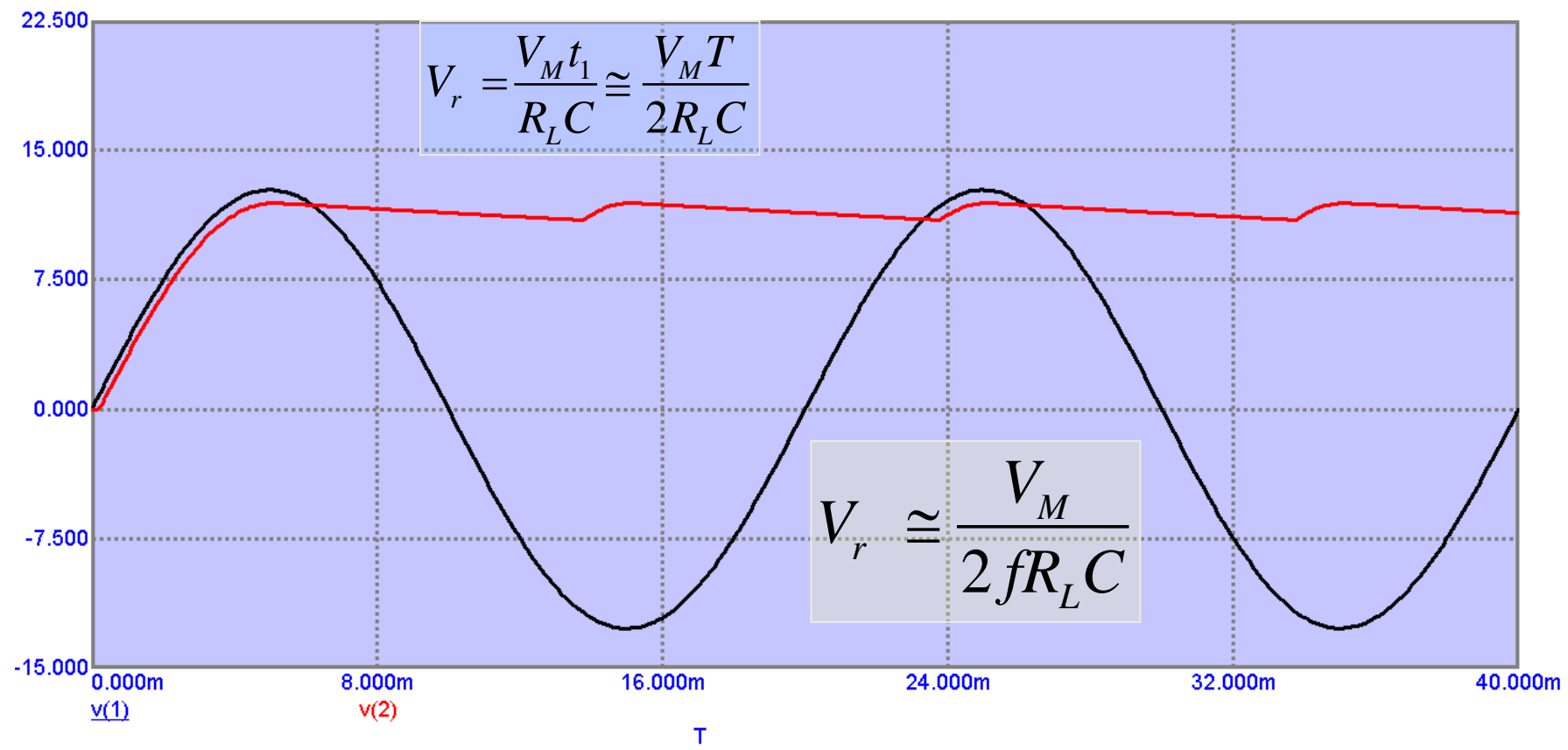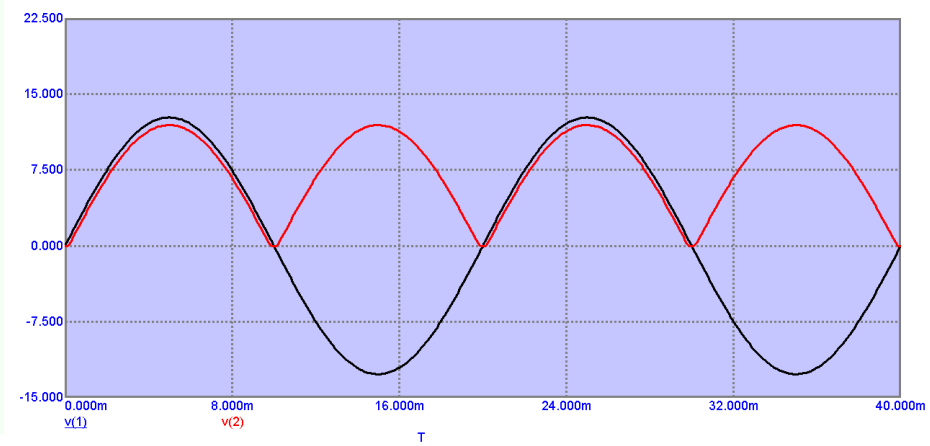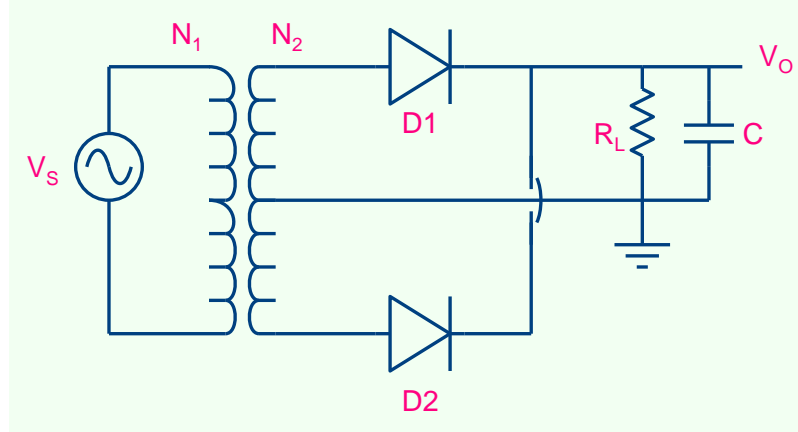


Comparison of full and half Wave Rectifier




$$V_r \cong \frac{V_M}{fR_L C}$$

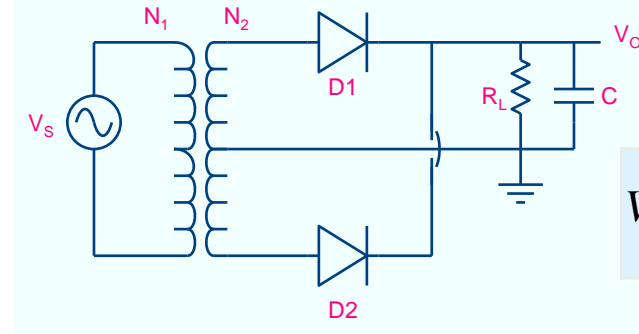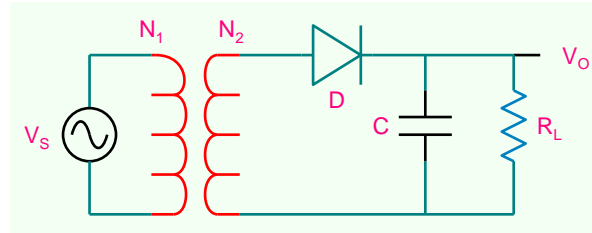


$$V_r \cong \frac{V_M}{2fR_L C}$$

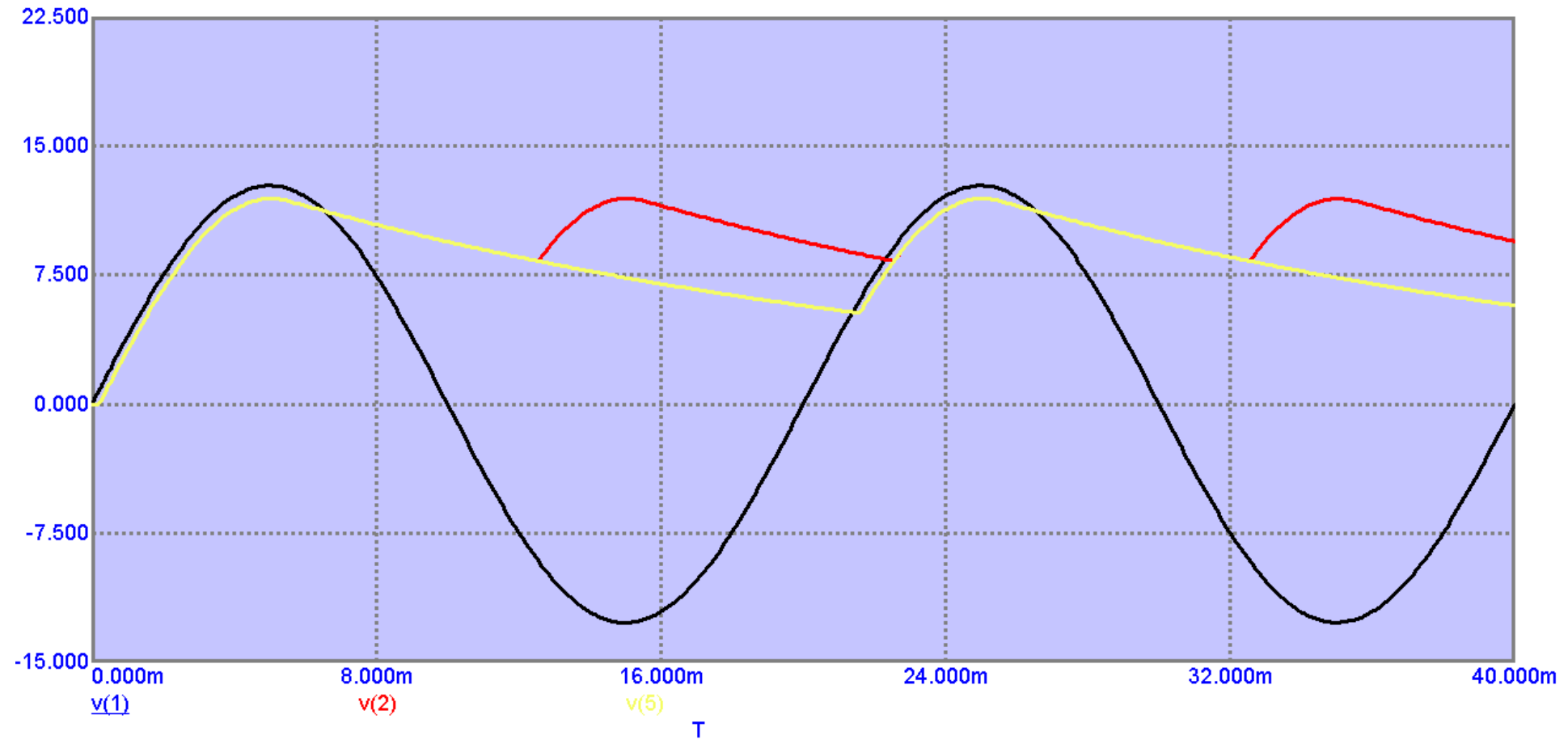


Diode Currents in Full wave Rectifier


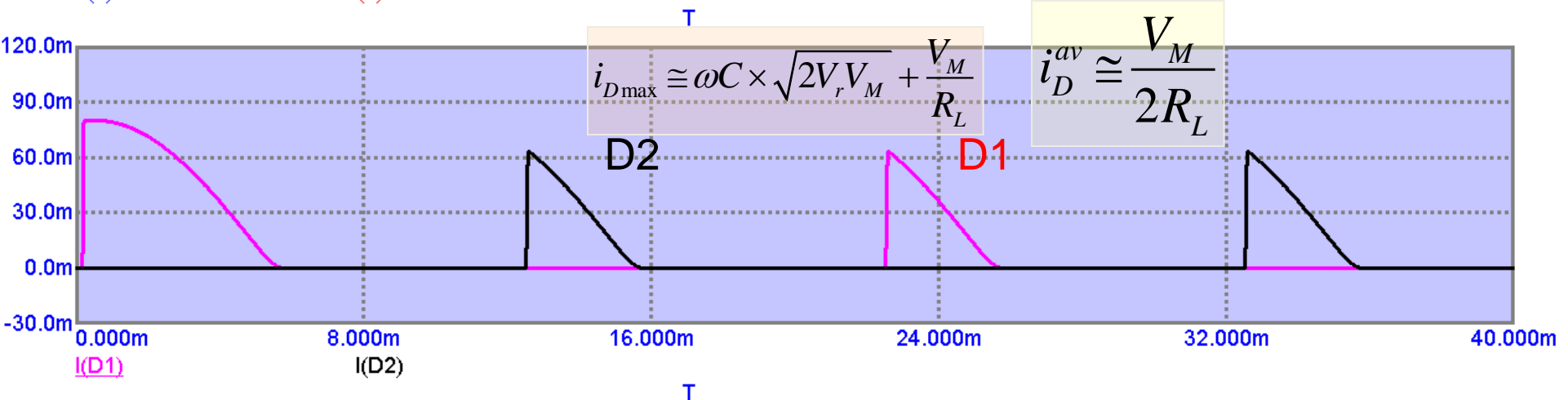
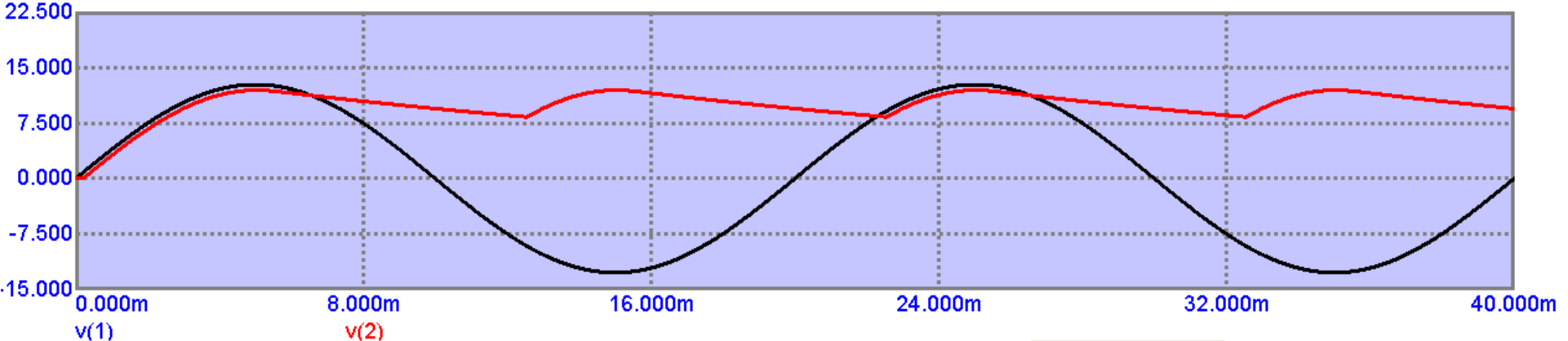
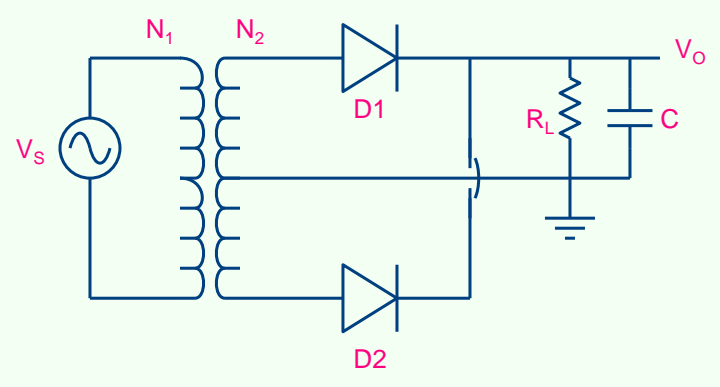


Bridge Rectifier

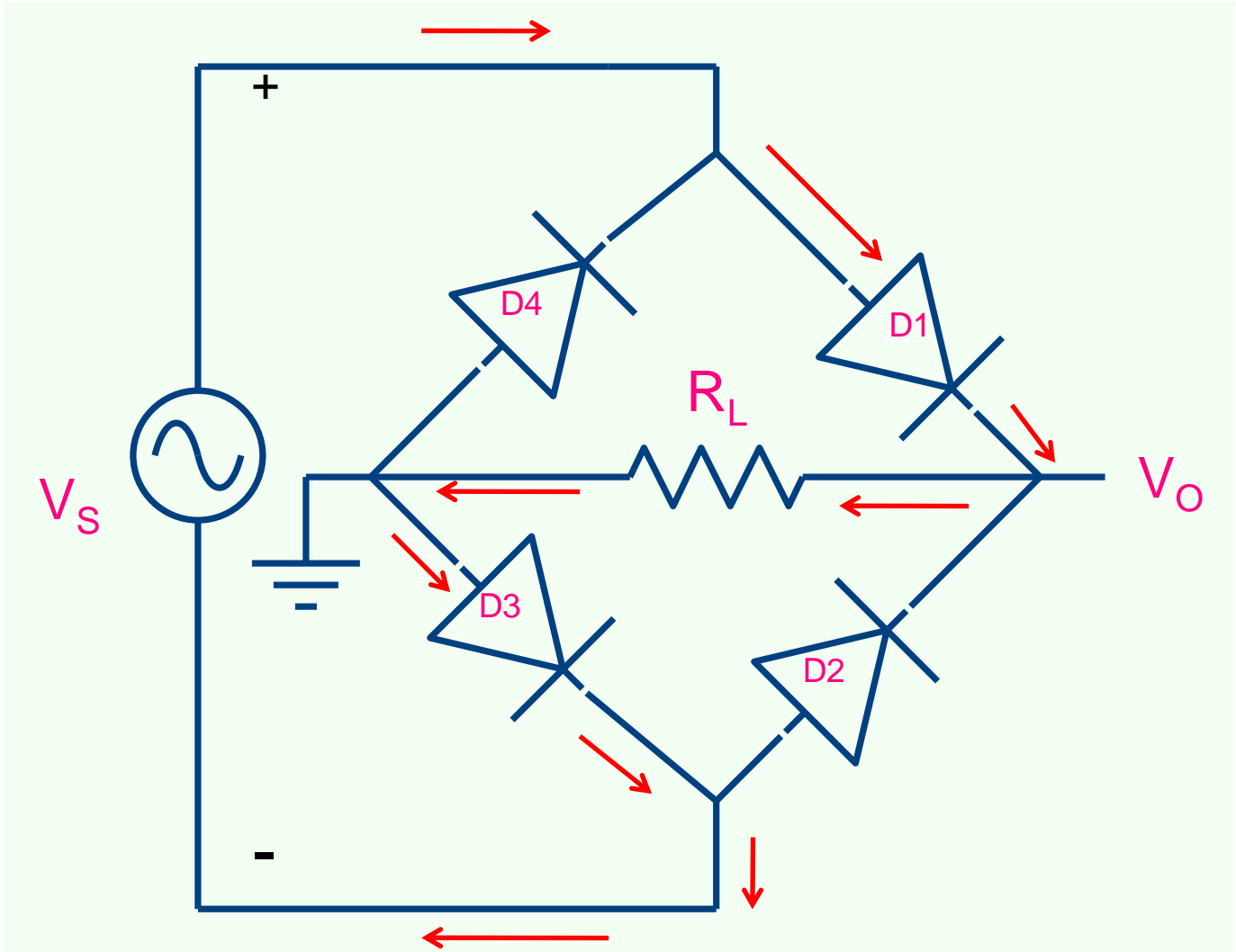

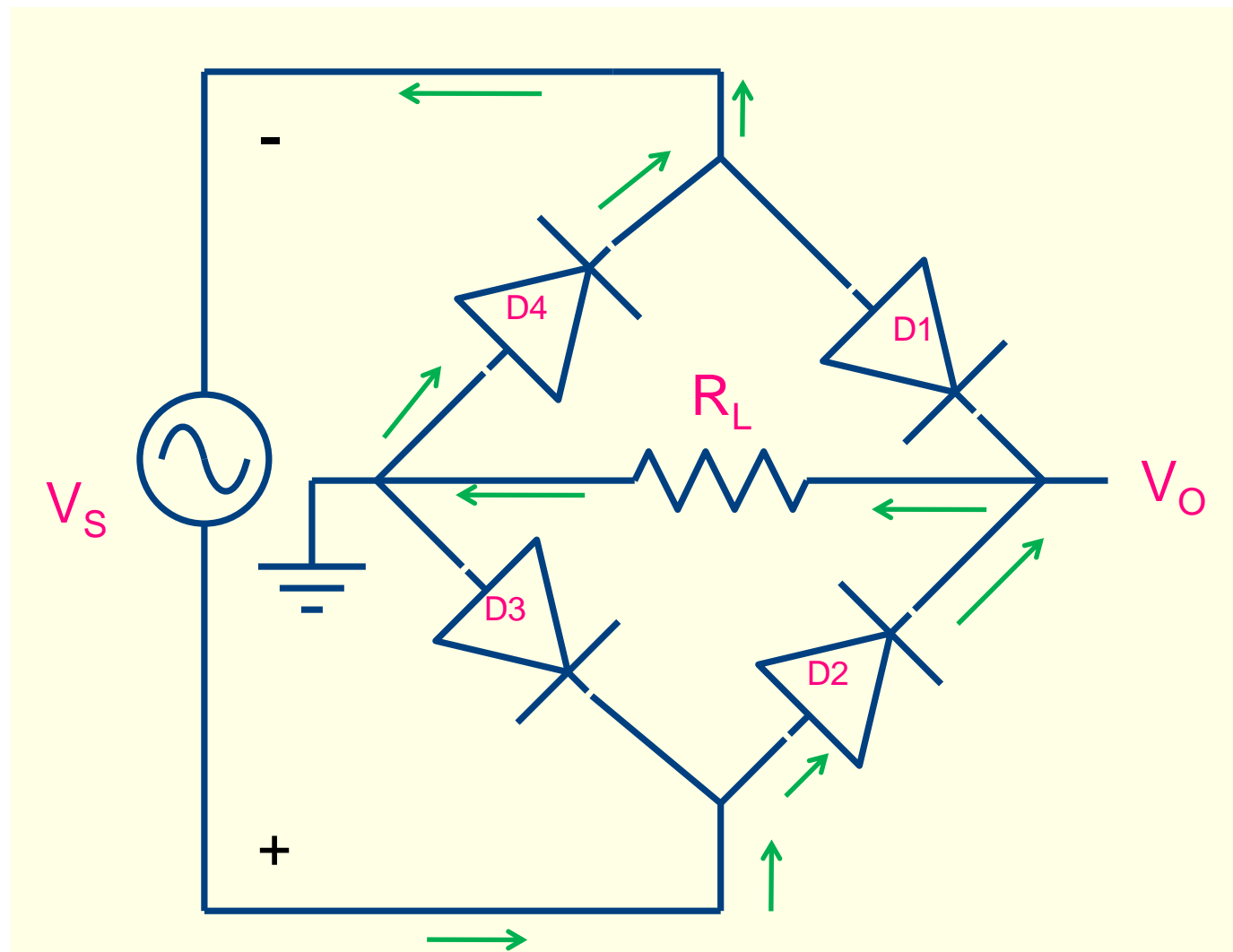

Power supply using full wave Rectifier

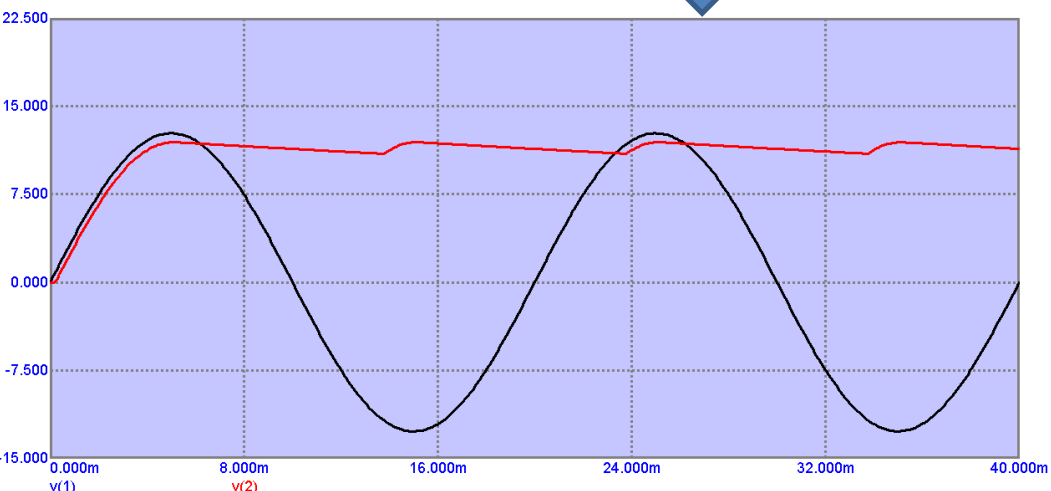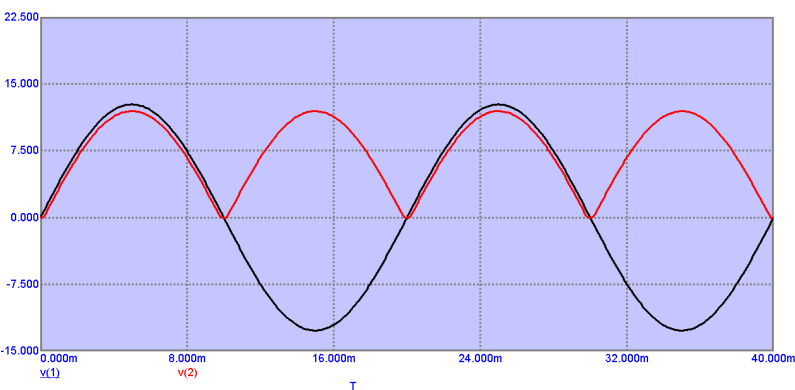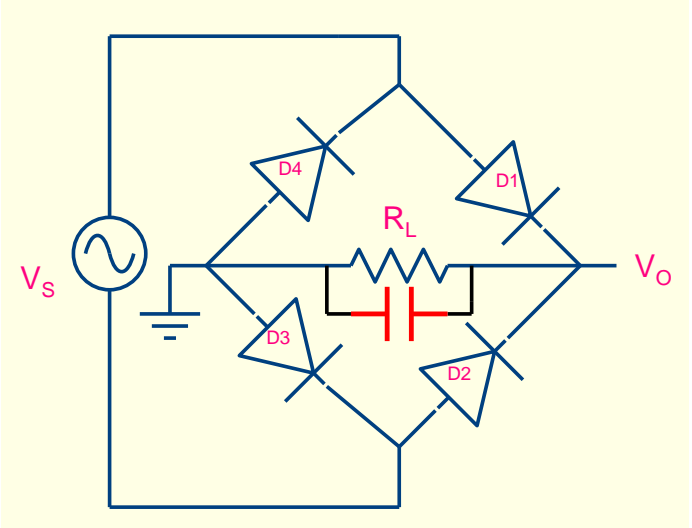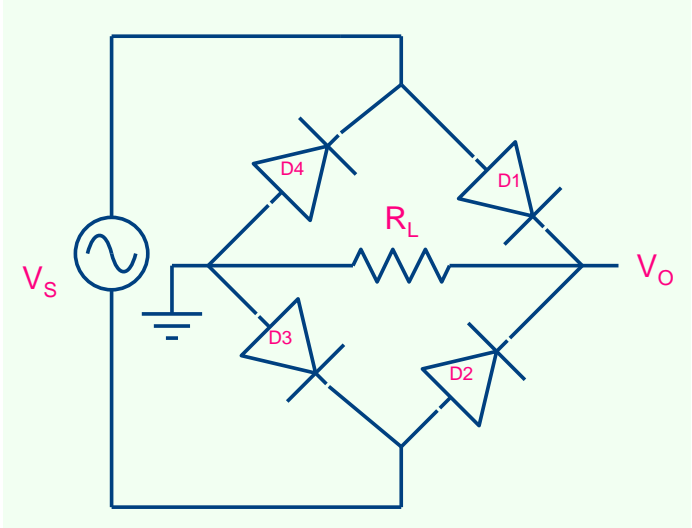


Ripple is smaller in full wave rectifier based power supply




$$V_r \cong \frac{V_M}{2fR_L C}$$

Peak Inverse Voltage

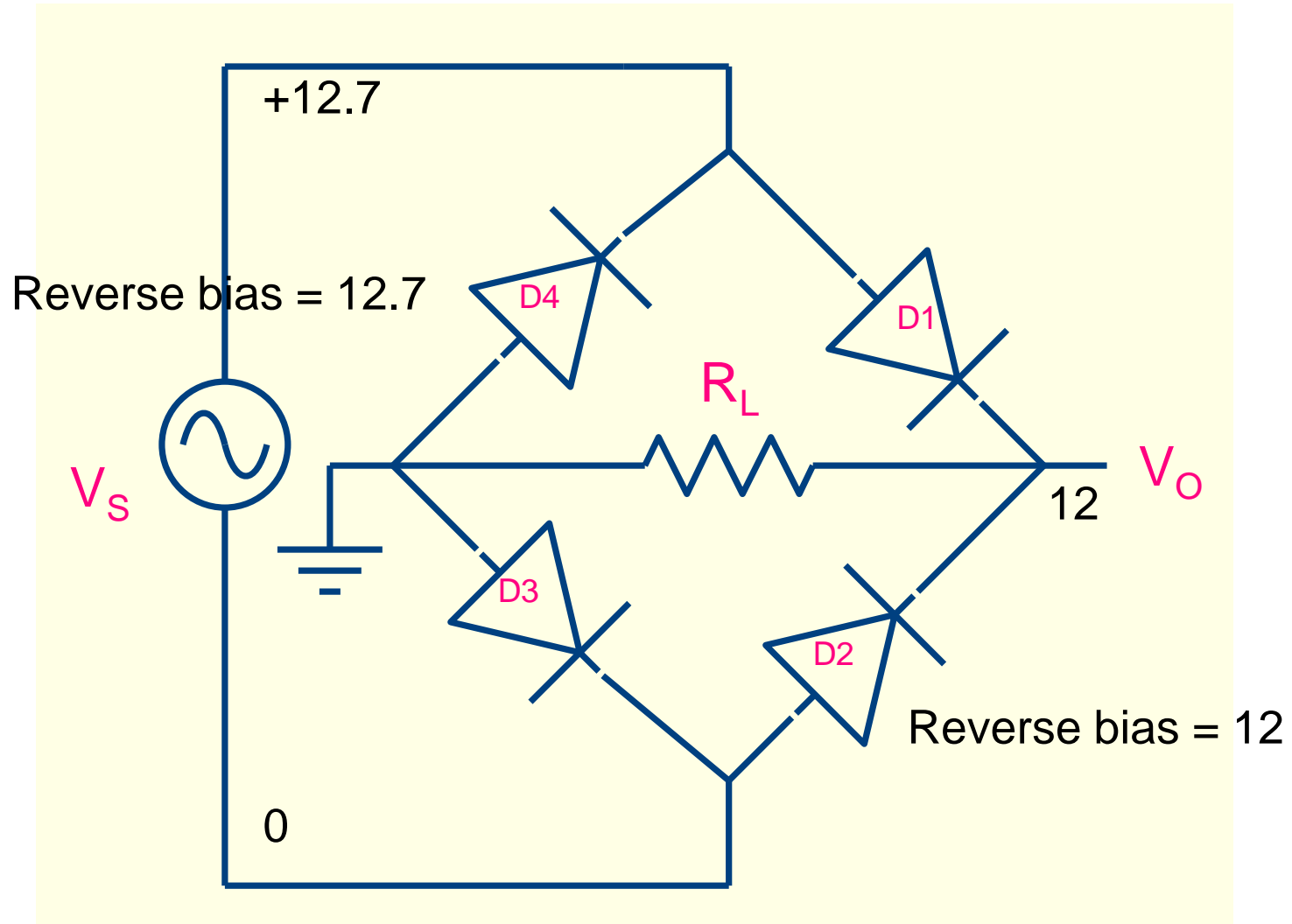


$$PIV \cong v_o + 0.7$$

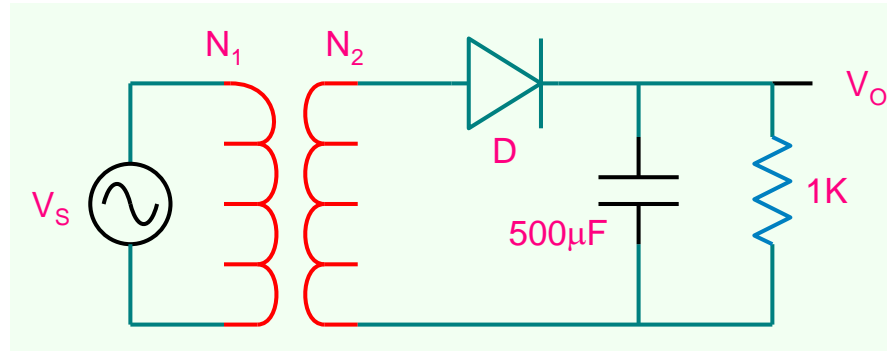Reducing Ripple to a very small value is not easy !





$$V_r = 0.438\text{V}$$

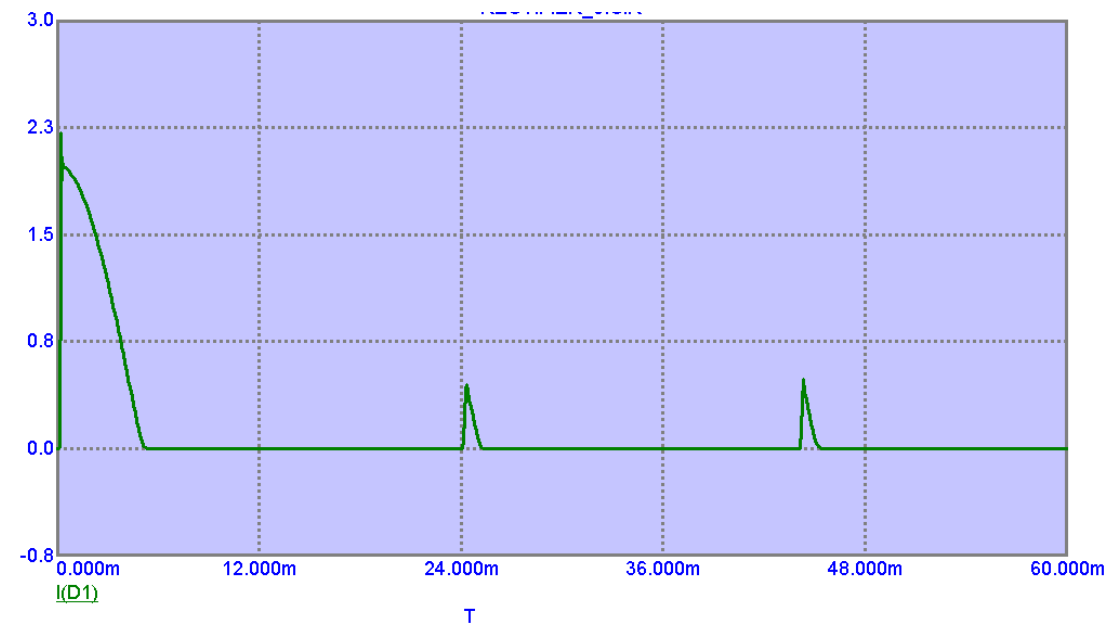



Zener Diode

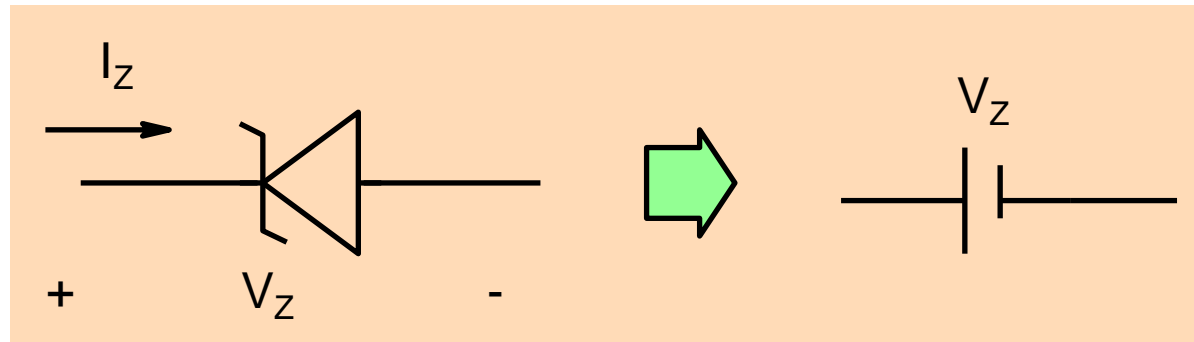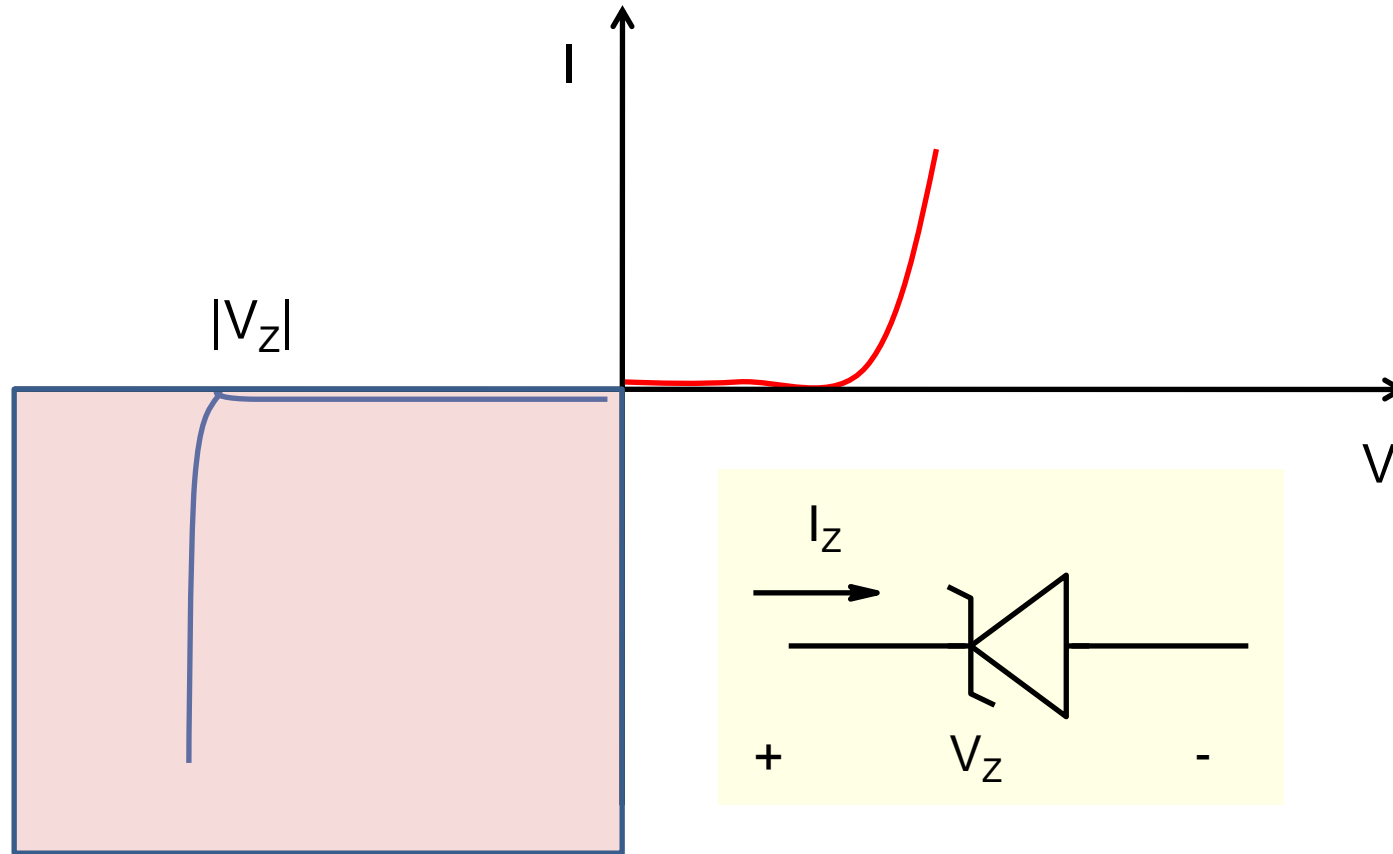A diode specially designed to operate in reverse bias in 'breakdown' region






Zener diode: Important Characteristics




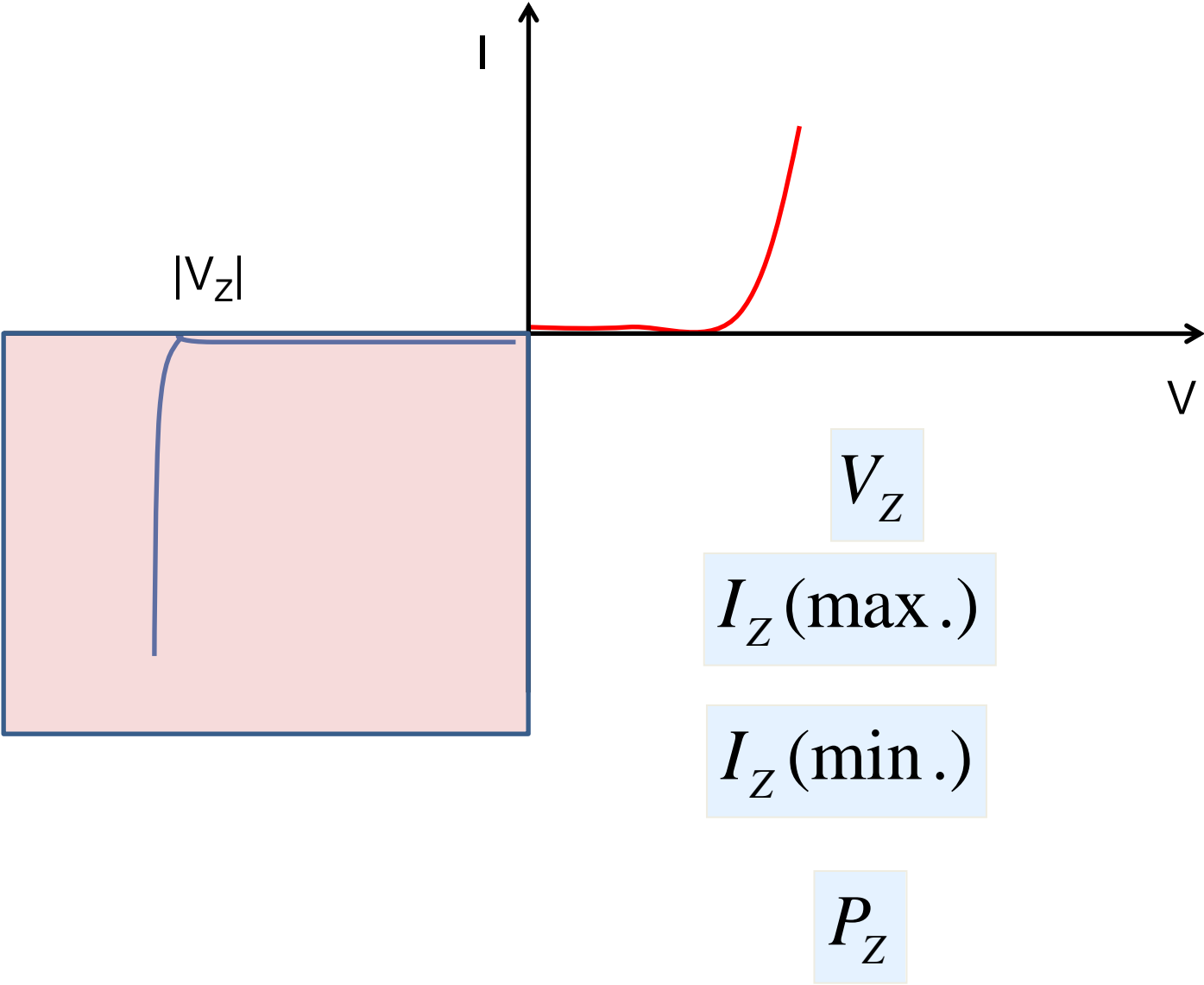


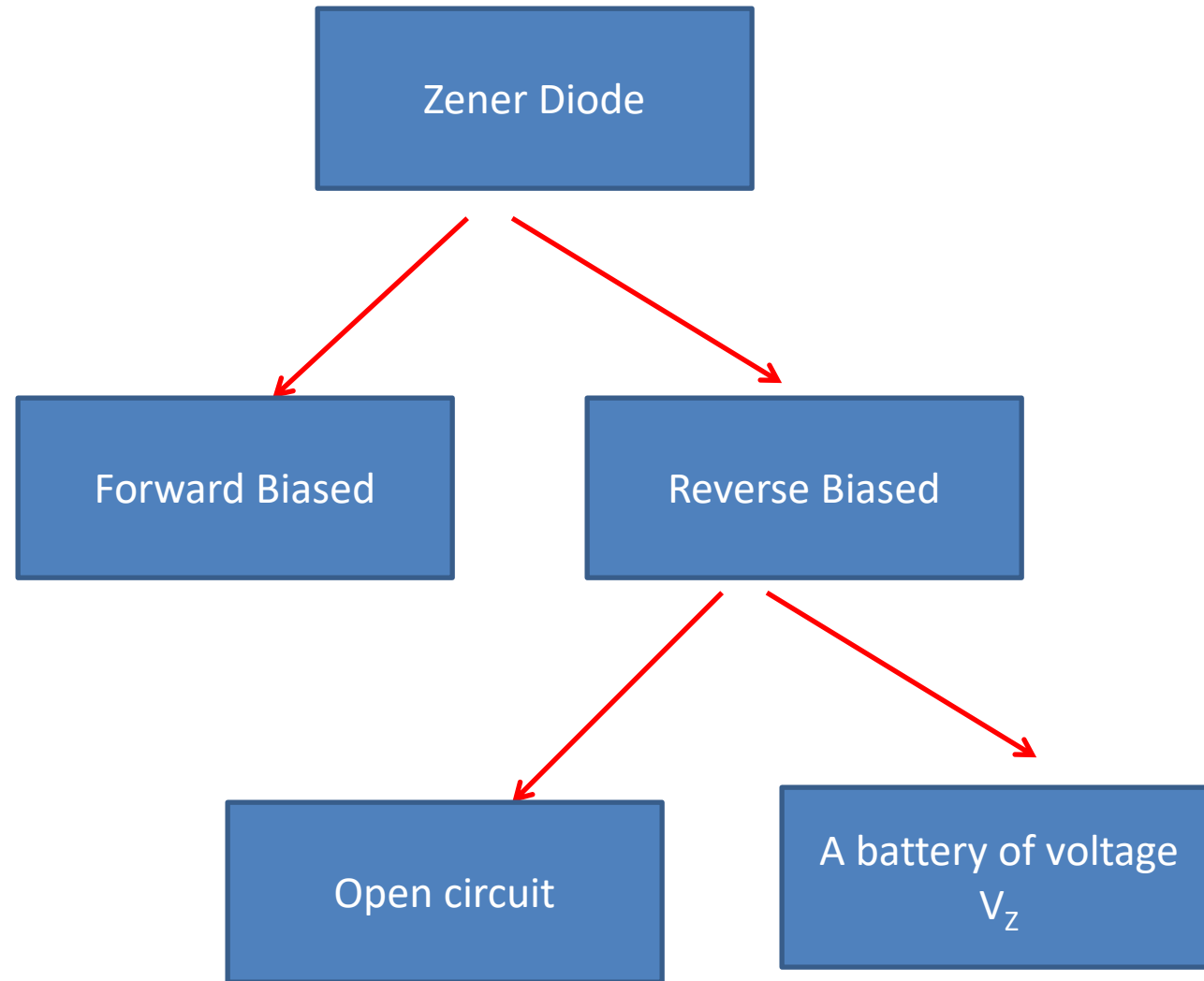



Voltage Reference Circuit

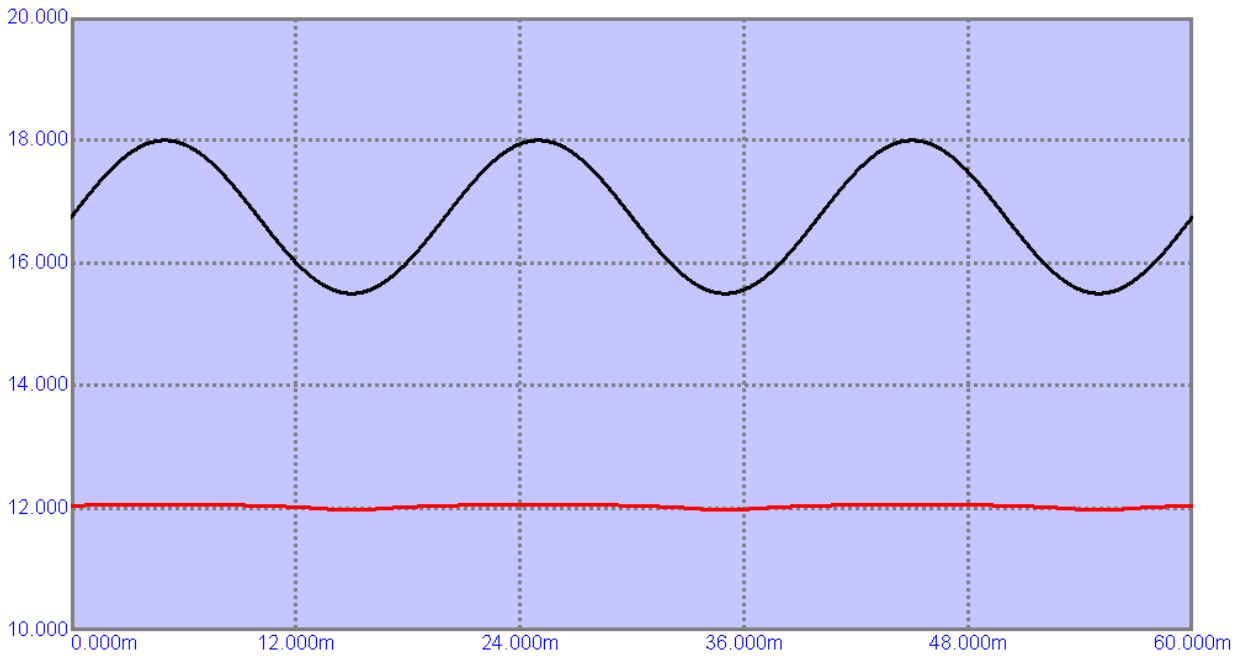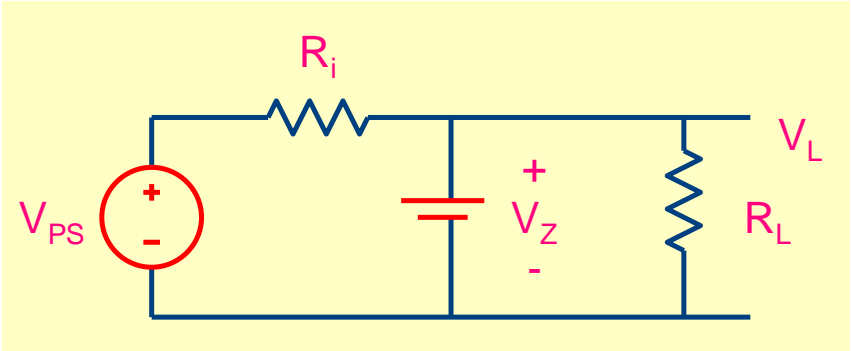
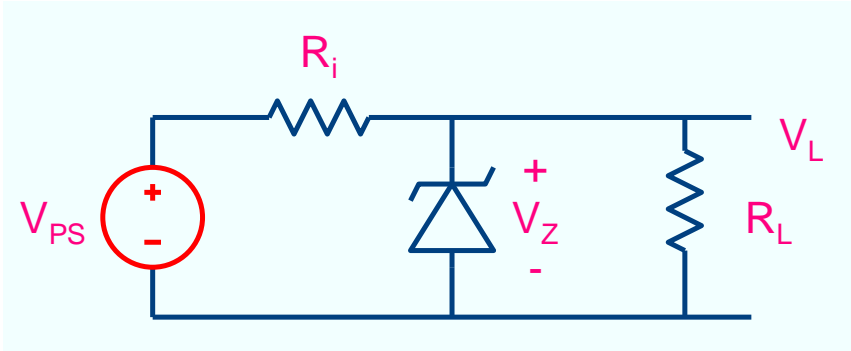


Power supply with regulator

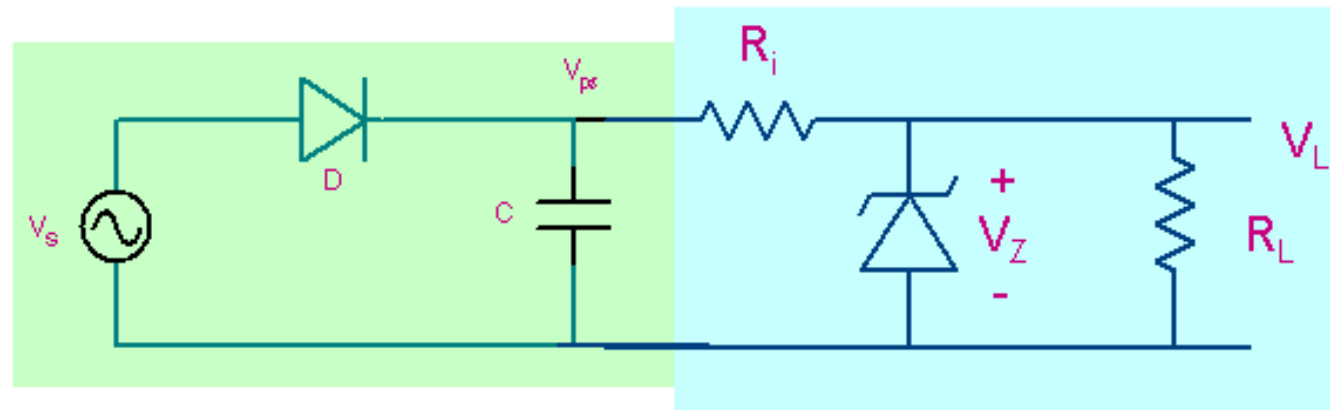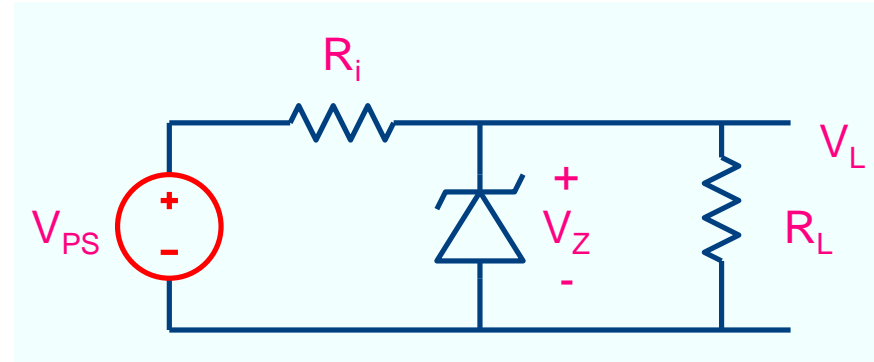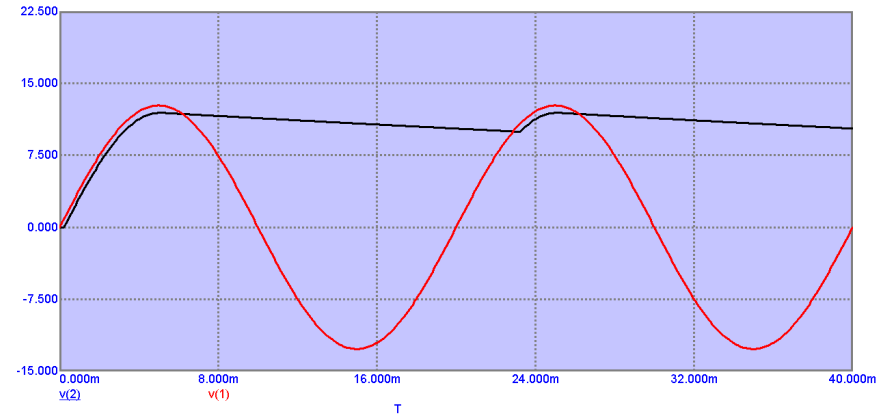
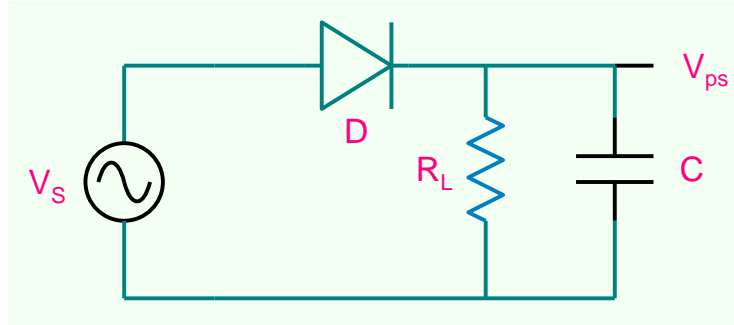


Zener diode as Voltage Regulator

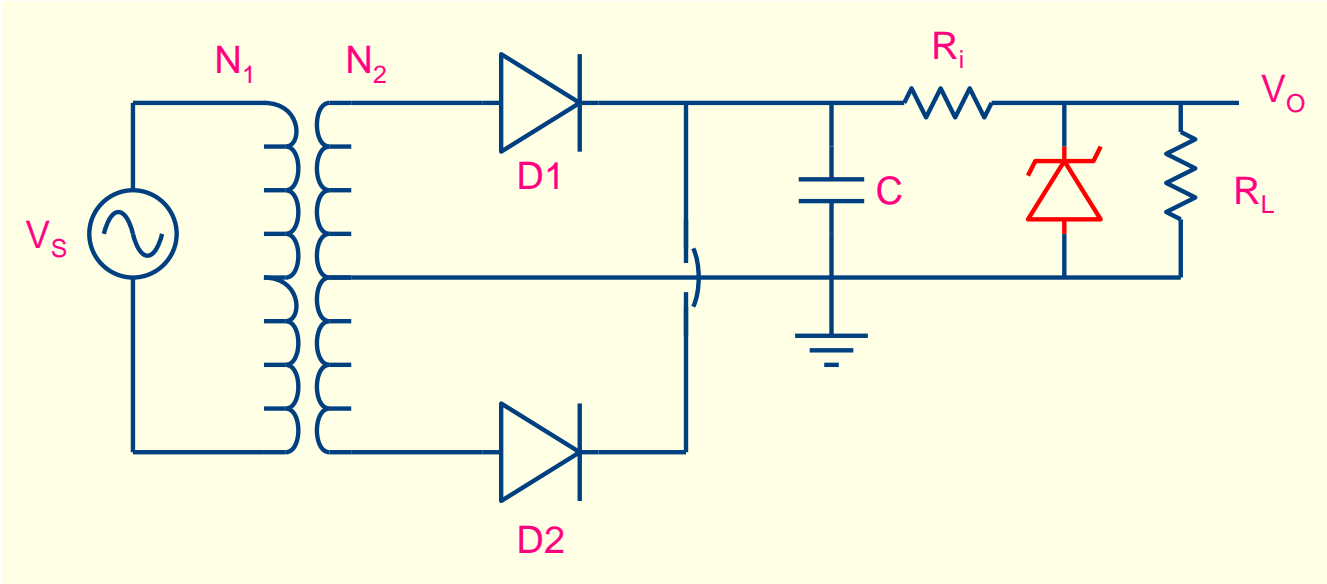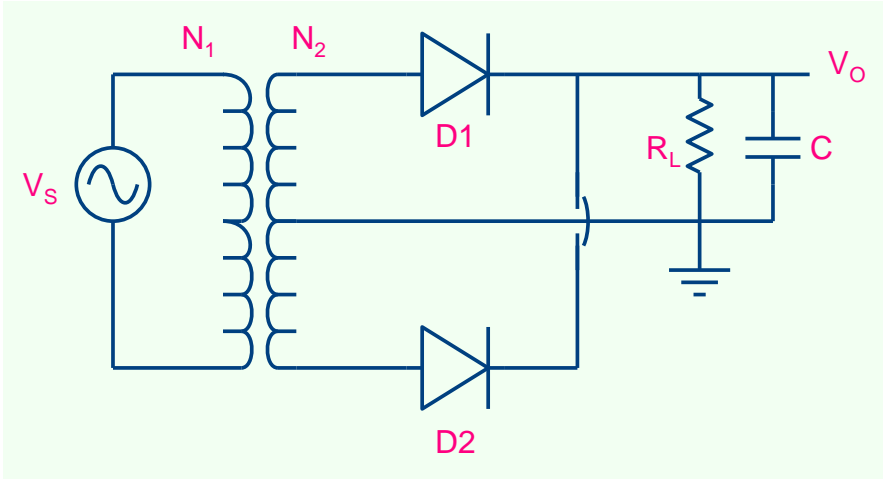

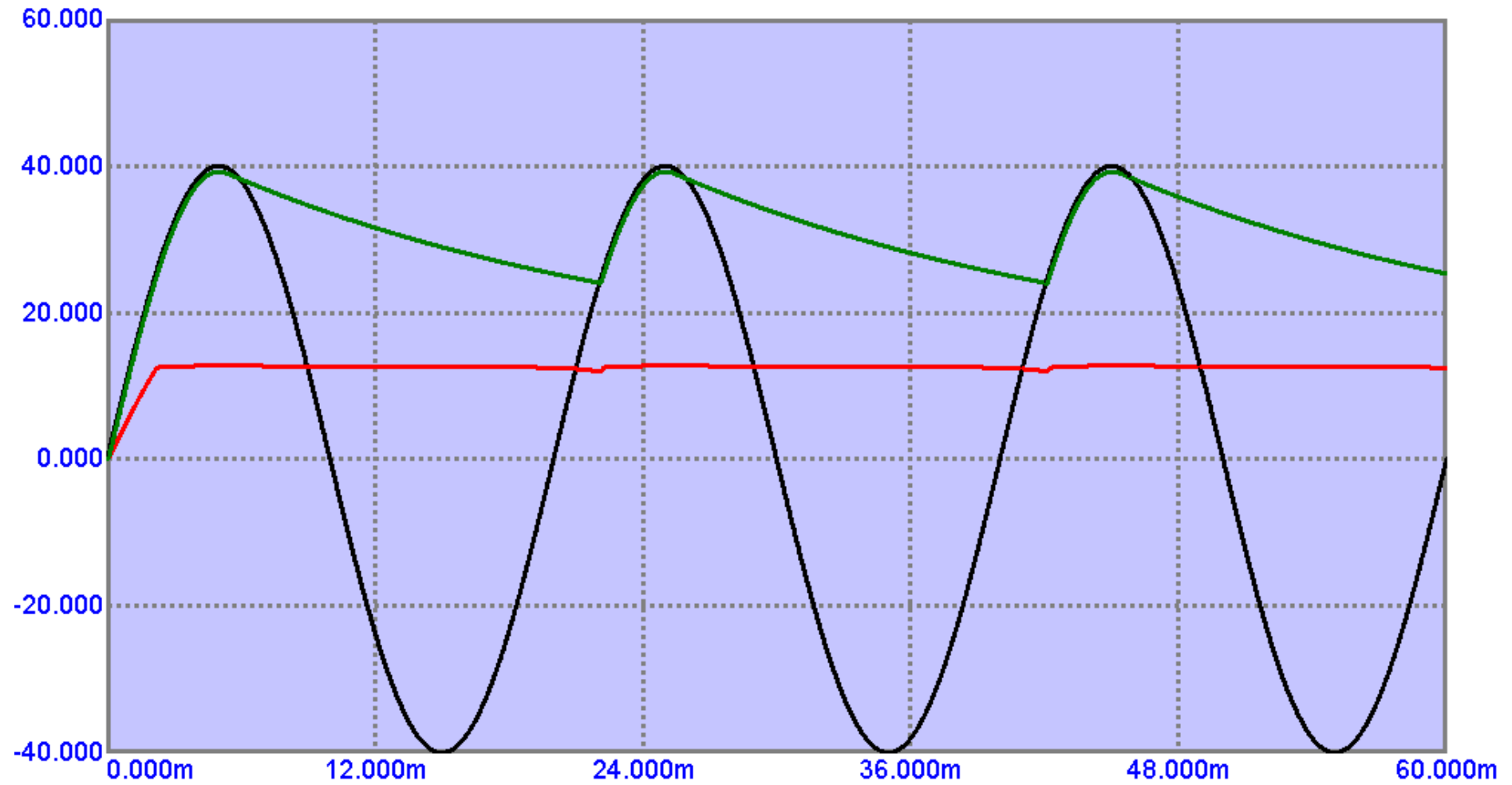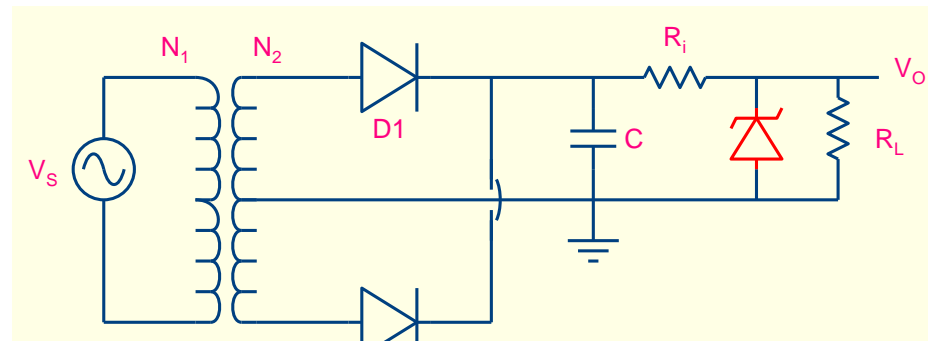


Voltage Reference Circuit

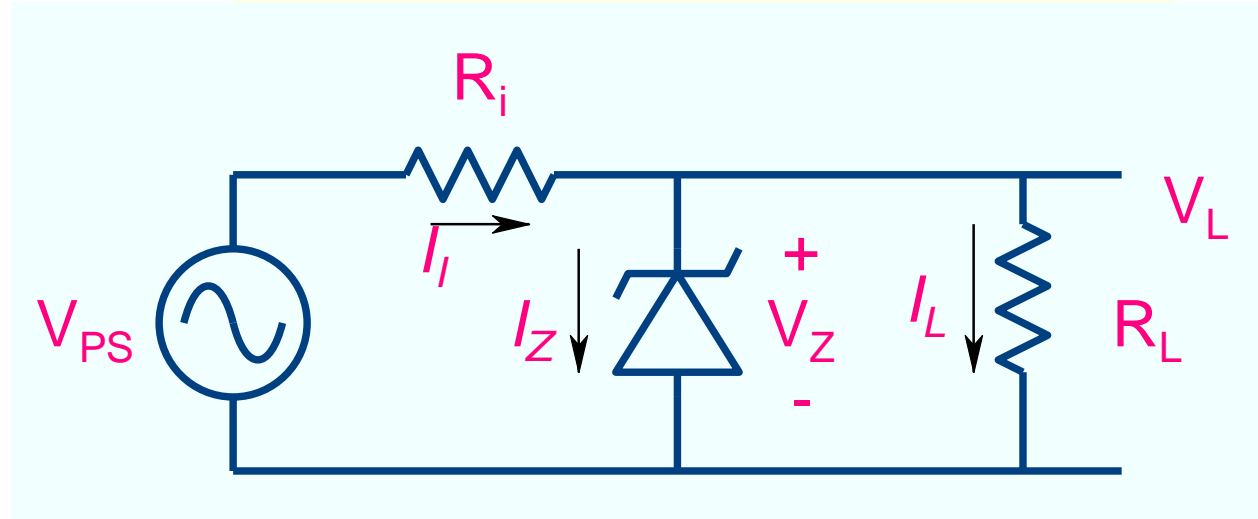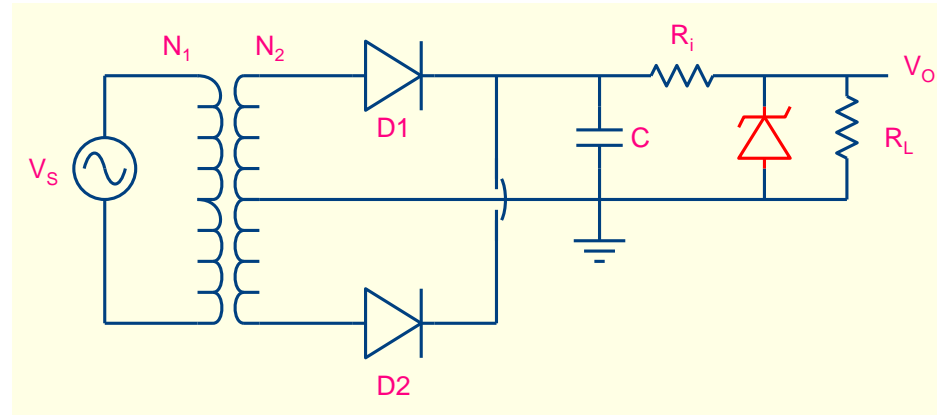

Design Problem: Determine R_i and zener diode specifications such that output voltage is +12V, load current can vary between 0 to 0.1A. The input voltage may vary between 18 to 15.5V.

Voltage Reference Equations

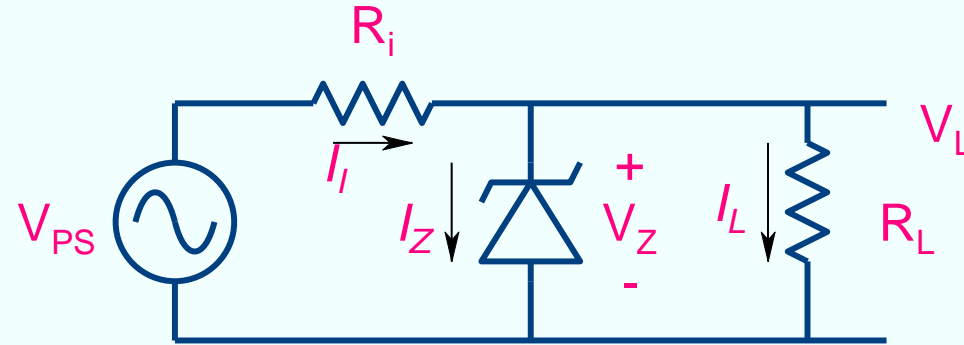

$$I_i = \frac{V_{PS} - V_Z}{R_i} = I_Z + I_L$$

$$I_Z = \frac{V_{PS} - V_Z}{R_i} - I_L$$


$$I_{Z \max} = \frac{V_{PS \max} - V_Z}{R_i} - I_{L \min}$$

$$I_{Z \min} = \frac{V_{PS \min} - V_Z}{R_i} - I_{L \max}$$

$$P_{Z \max} = V_Z I_{Z \max}$$

Check correctness of design by checking compliance with Zener diode ratings

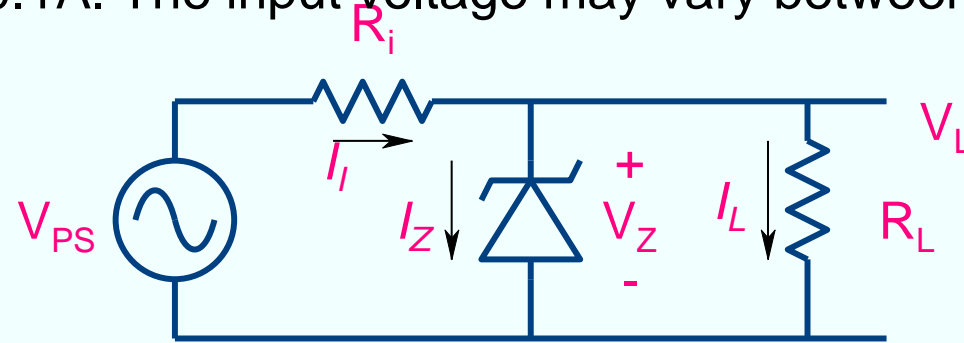Design Problem: Determine R_i and zener diode specifications such that output voltage is +12V, load current can vary between 0 to 0.1A. The input voltage may vary between 18 to 15.5V.




$$I_i = \frac{V_{PS} - V_Z}{R_i} = I_Z + I_L$$

$$I_Z = \frac{V_{PS} - V_Z}{R_i} - I_L$$

$$I_{Z\max} = \frac{V_{PS\max} - V_Z}{R_i} - I_{L\min}$$

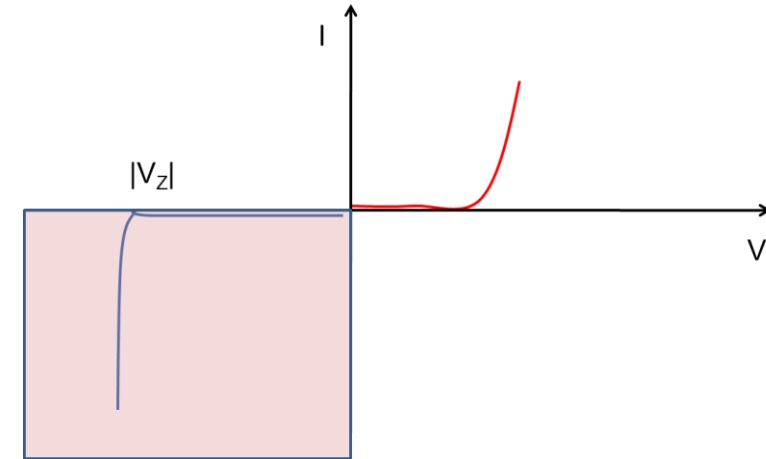
$$I_{Z\min} = \frac{V_{PS\min} - V_Z}{R_i} - I_{L\max}$$



$$R_i = 40\Omega \Rightarrow I_{Z\max} = 0.15A; I_{Z\min} = -0.013A$$

$$R_i = 10\Omega \Rightarrow I_{Z\max} = 0.6A; I_{Z\min} = 0.25A$$

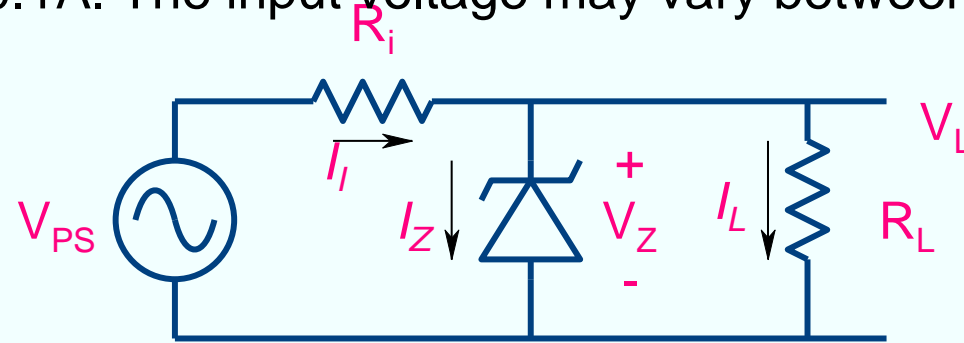Design Problem: Determine R_i and zener diode specifications such that output voltage is +12V, load current can vary between 0 to 0.1A. The input voltage may vary between 18 to 15.5V.




$$I_i = \frac{V_{PS} - V_Z}{R_i} = I_Z + I_L$$

$$I_Z = \frac{V_{PS} - V_Z}{R_i} - I_L$$

$$I_{Z \max} = \frac{V_{PS \max} - V_Z}{R_i} - I_{L \min}$$
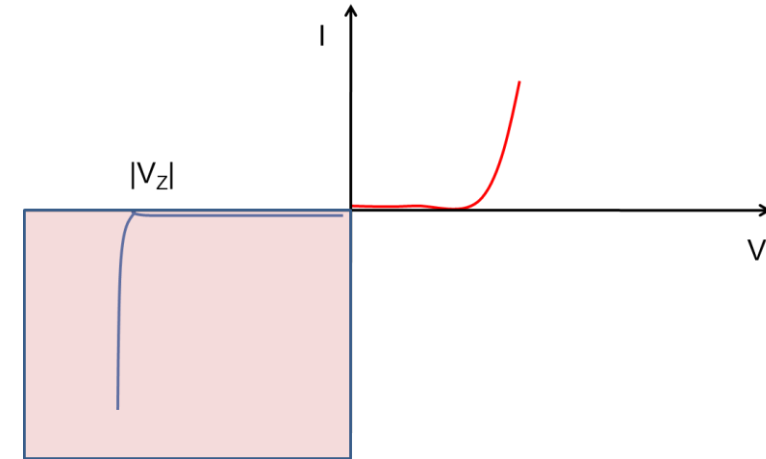
$$I_{Z \min} = \frac{V_{PS \min} - V_Z}{R_i} - I_{L \max}$$



$$\frac{I_{Z \max}}{I_{Z \min}} \cong 10$$

$$R_i = \frac{V_{PS \min} - 0.1V_{PS \max} - 0.9V_Z}{I_{L \max}}$$

$$P_{Z \max} = V_Z I_{Z \max}$$

Design Problem: Determine R_i and zener diode specifications such that output voltage is +12V, load current can vary between 0 to 0.1A. The input voltage may vary between 18 to 15.5V.


$$R_i = \frac{V_{PS \min} - 0.1V_{PS \max} - 0.9V_Z}{I_{L \max}} = 29\Omega$$


$$I_{Z \max} = \frac{V_{PS \max} - V_Z}{R_i} - I_{L \min} = 0.207 A$$

$$I_{Z \min} = \frac{V_{PS \min} - V_Z}{R_i} - I_{L \max} = 0.0207$$

$$P_{Z \max} = V_Z I_{Z \max} = 2.48 W$$

Check the design through simulations

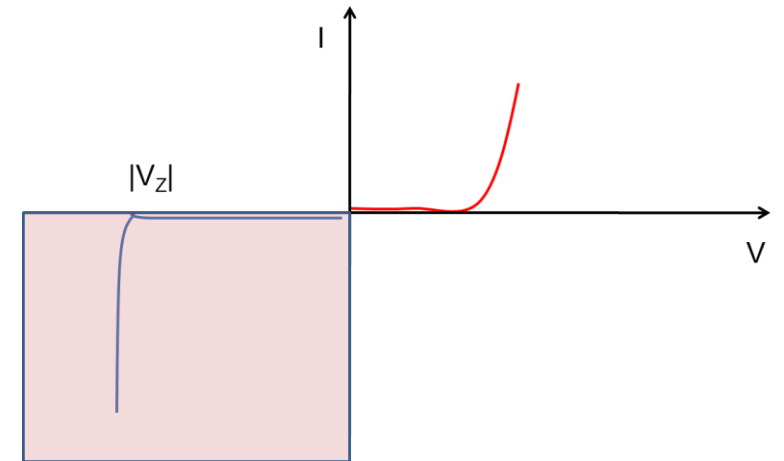

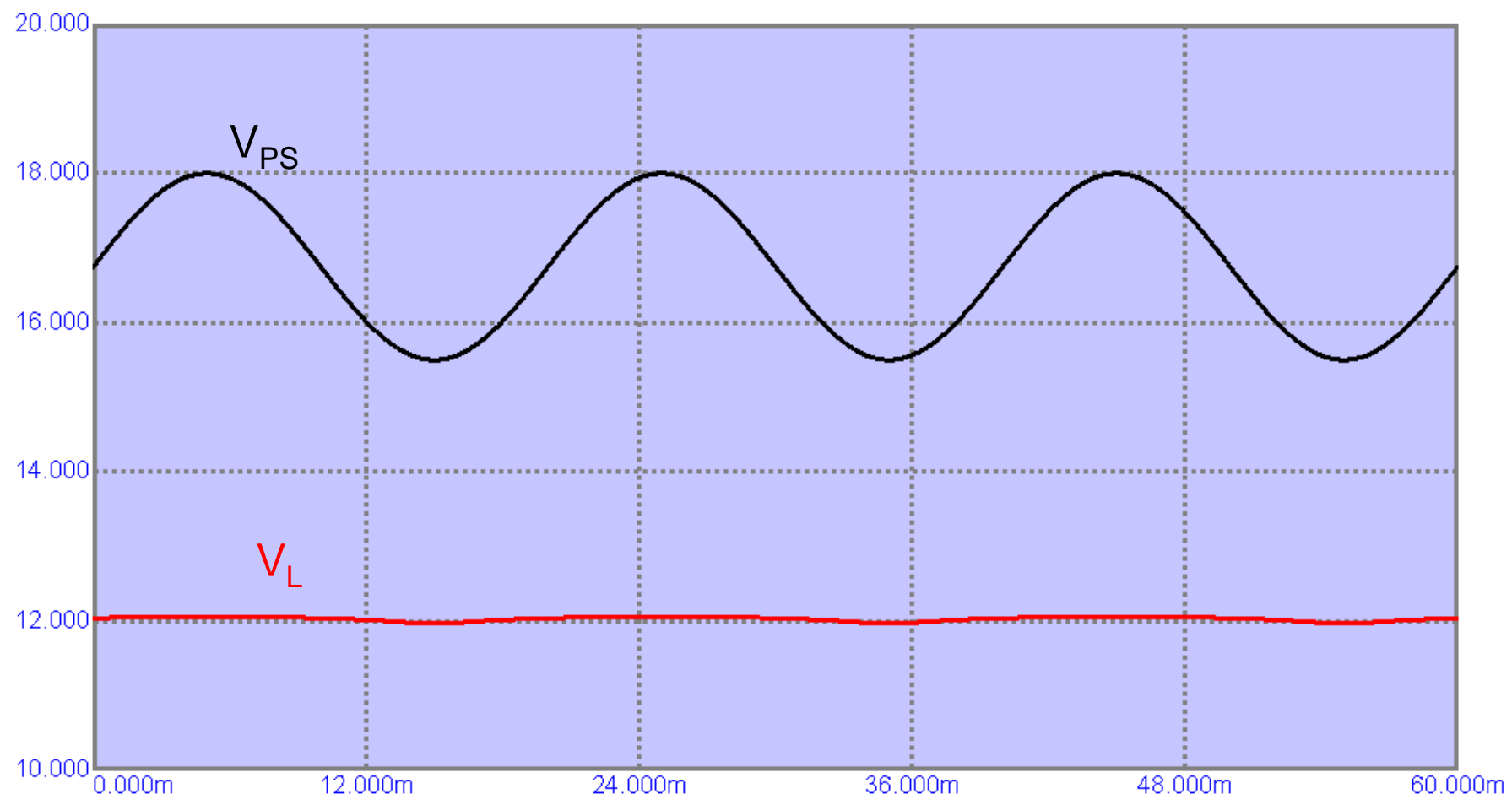

Design Problem-2: Determine R_i and zener diode specifications such that output voltage is +12V, load current can vary between 0 to 0.1A. The input voltage may vary between 15 to 12.915V.

$$R_i = \frac{V_{PS \min} - 0.1V_{PS \max} - 0.9V_Z}{I_{L \max}} = 6.1\Omega$$

$$I_{Z \max} = \frac{V_{PS \max} - V_Z}{R_i} - I_{L \min} = 0.488A$$

$$I_{Z \min} = \frac{V_{PS \min} - V_Z}{R_i} - I_{L \max} = 0.049$$

$$P_{Z \max} = V_Z I_{Z \max} = 5.85W$$