

ESC201T : Introduction to Electronics

Discussion-7 : 04/11/20



B. Mazhari
Professor, Dept. of EE
IIT Kanpur

Announcements

Discussion Quiz from 6.45-6.55 pm
Topic : Diode Circuit


Major Quiz-3 on 11/11/2020 during Discussion hour.
Topic : 2 port parameters, semiconductors, diode circuits till Lecture 23
Non-Objective Type

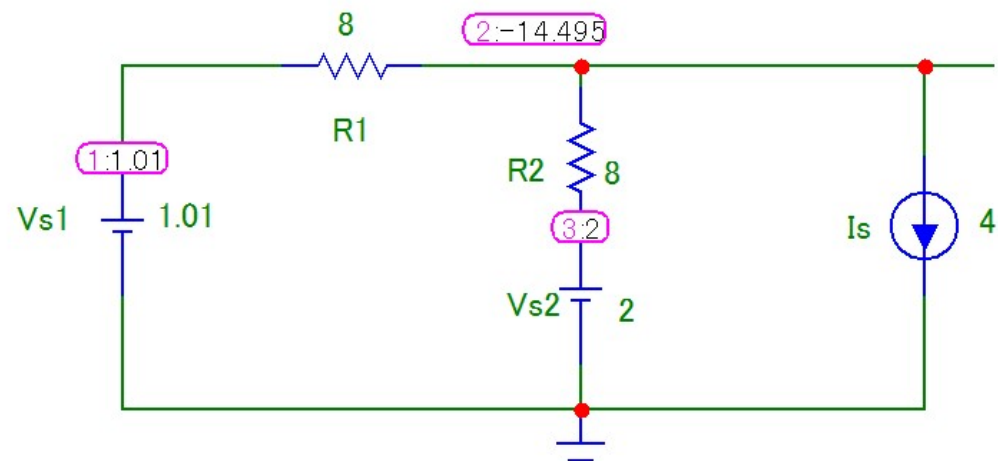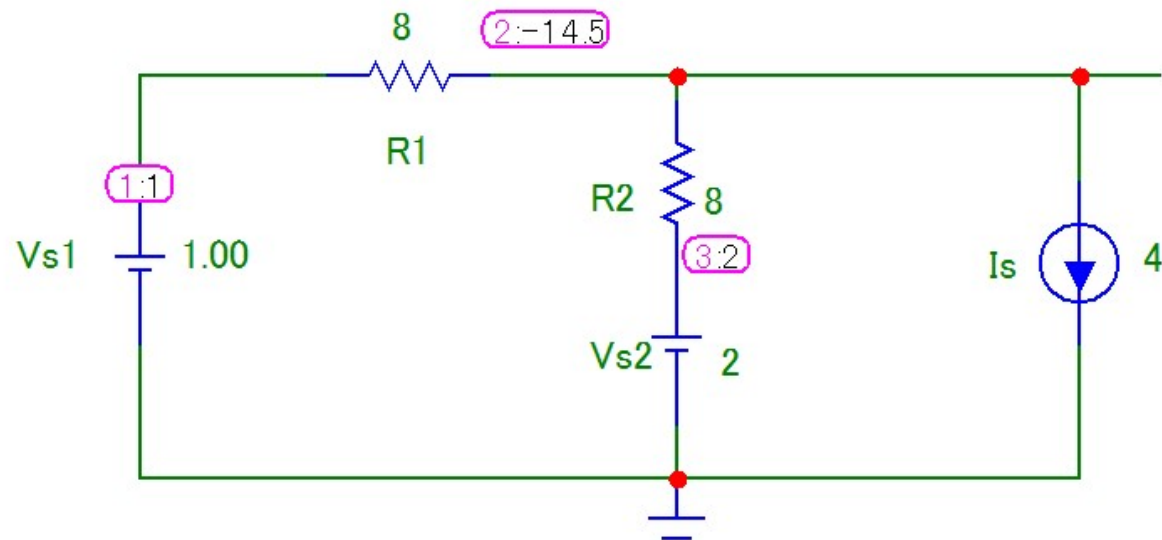Major Quiz-4 on 27/11/2020 during Tutorial hour.
Topic : Amplifiers and Digital Circuits
Objective type




$$\Delta V_0 = 5\text{mV}$$

Incremental (ac) Circuit Analysis

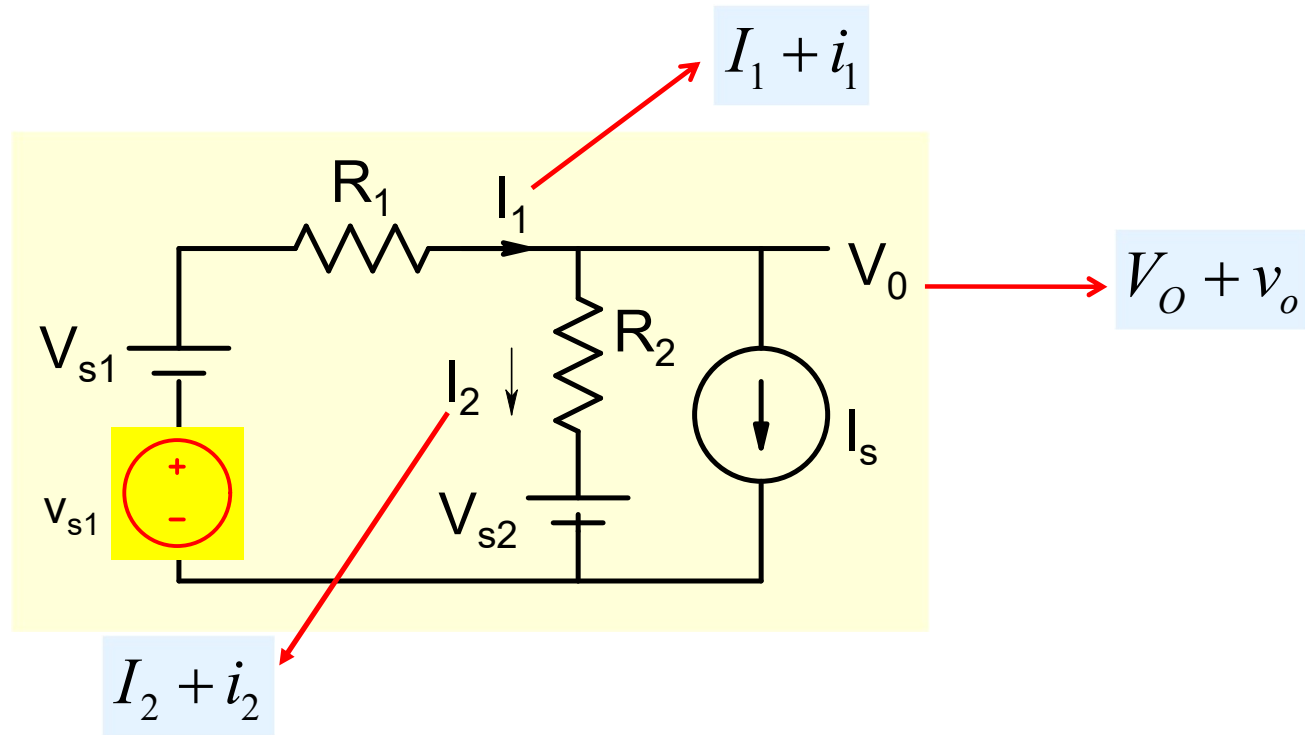

Incremental circuit analysis attempts to find the relationships between incremental voltages and currents v_{s1} , i_1 , v_o

Incremental (ac) Circuit Analysis

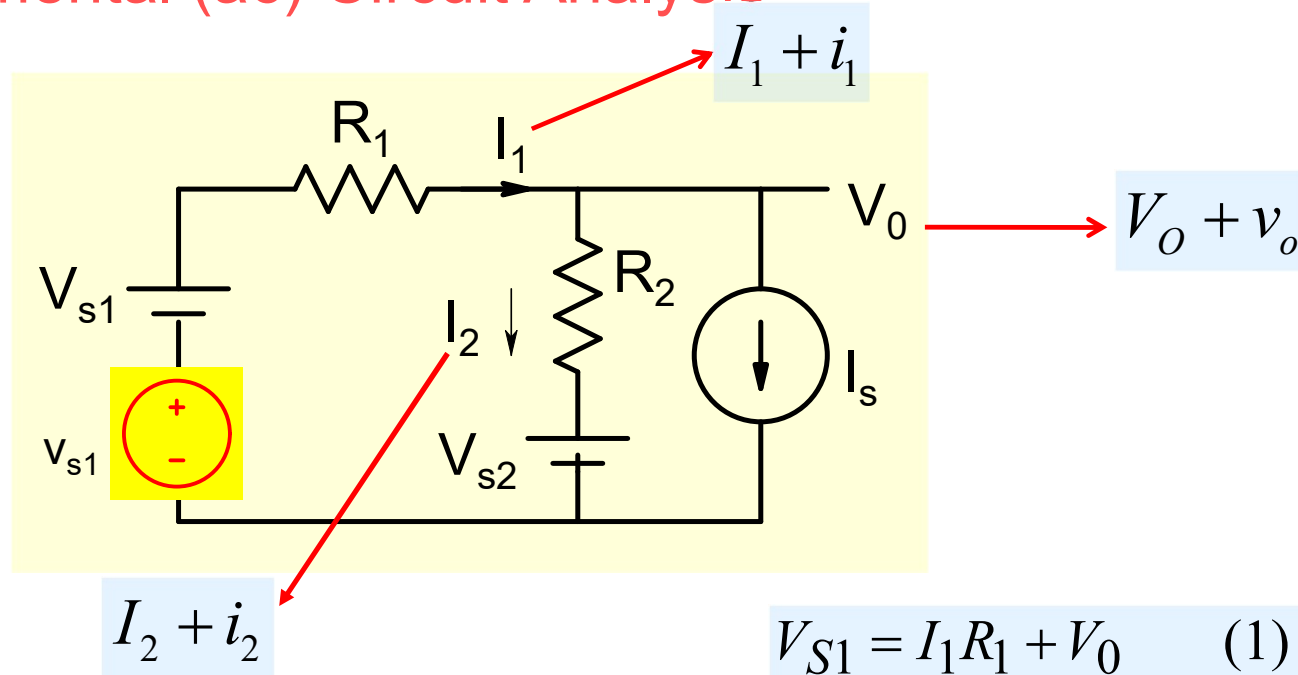

$$V_{S1} = I_1 R_1 + V_0 \quad (1)$$

$$I_1 = I_S + (V_0 - V_{S2})/R_2 \quad (2)$$


$$V_{S1} + v_{s1} = (I_1 + i_1) \times R_1 + V_0 + v_o \quad (3)$$

$$I_1 + i_1 = I_S + (V_0 + v_o - V_{S2})/R_2 \quad (4)$$


$$(3)-(1): v_{s1} = i_1 R_1 + v_o$$

$$(4)-(2): i_1 = v_o/R_2$$

$$v_{s1} = i_1 R_1 + i_1 R_2$$

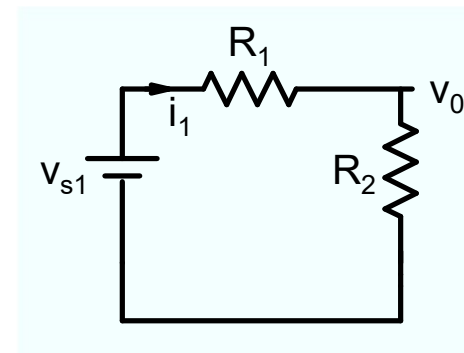

Method: Incremental equivalent circuit

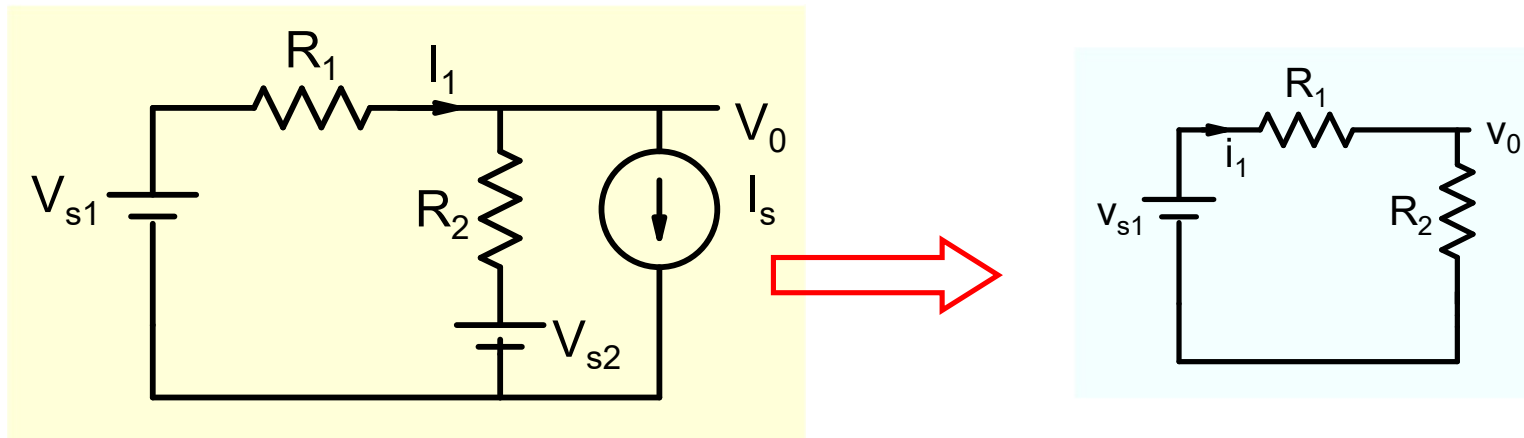

Analyze incremental equivalent circuit obtained by replacing each circuit element by its increment circuit model (sometimes called ac model).

Incremental model




$$I = f(V)$$

$$I + i = f(V + v)$$

Relation between i and v

Incremental (ac) Models: Resistor

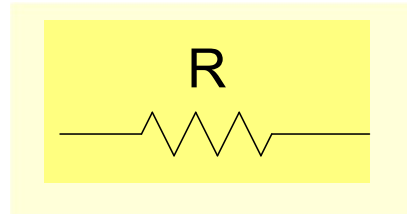


$$V = I \times R$$

$$V + v = (I + i) \times R$$

$$\Rightarrow v = i \times R$$

Incremental model of a resistor is a resistor of the same magnitude

Incremental (ac) Models: Capacitor

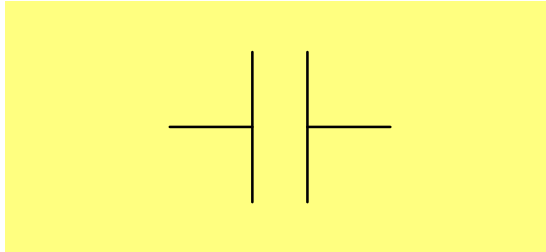


$$I = C \frac{dV}{dt}$$

$$I + i = C \frac{d(V + v)}{dt}$$

$$i = C \times \frac{dv}{dt}$$

Incremental model of a capacitor is a capacitor of the same magnitude. The same holds for an inductor as well.


Incremental (ac) Models

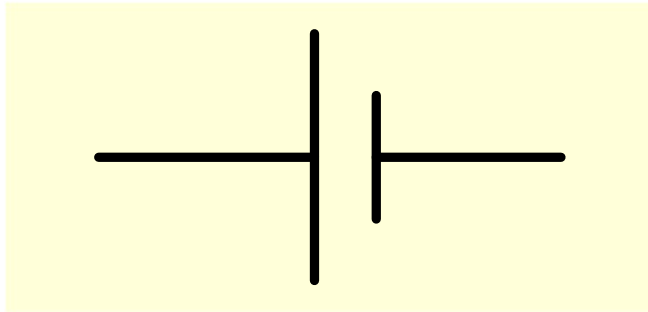

$$V = \text{const} \tan t$$

$$V + v = \text{const} \tan t$$

$$\Rightarrow v = 0$$

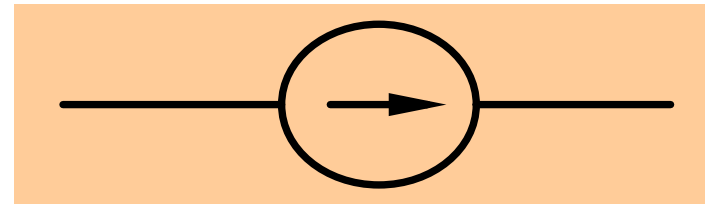



$$I = \text{const} \tan t$$

$$\Rightarrow i = 0$$




Incremental model of a constant Voltage Source is a short circuit

Incremental model of a constant current Source is an open circuit


Incremental (ac) circuit Analysis

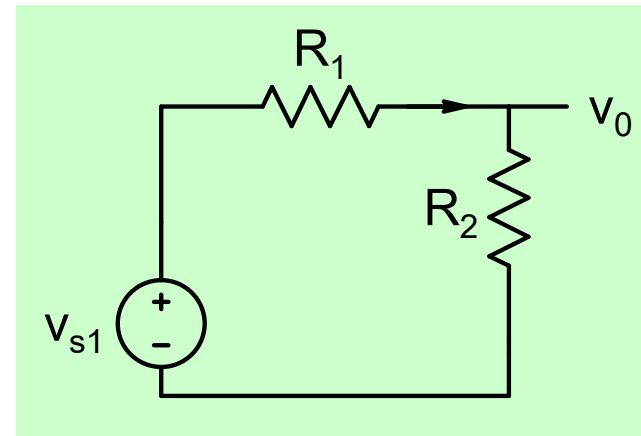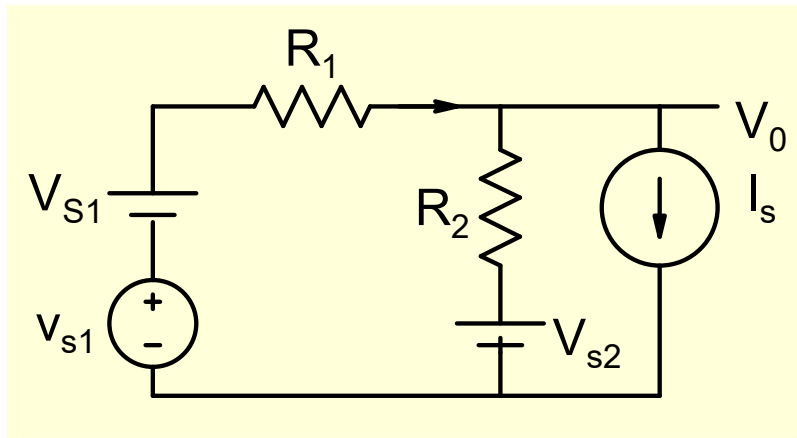
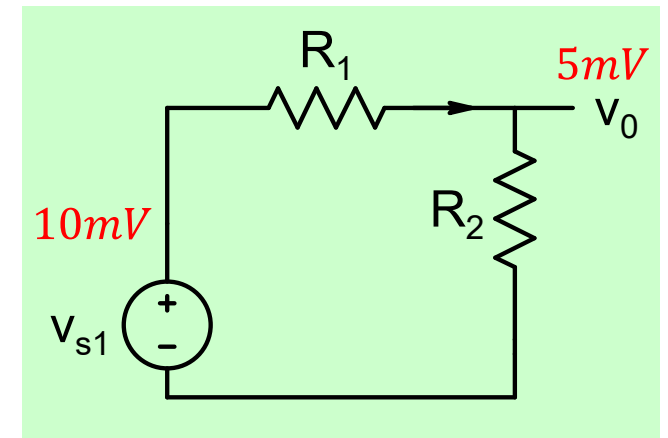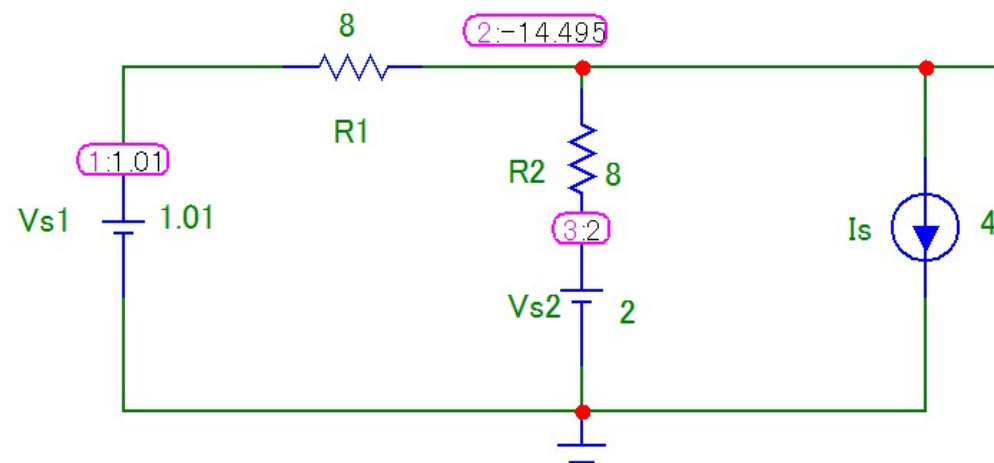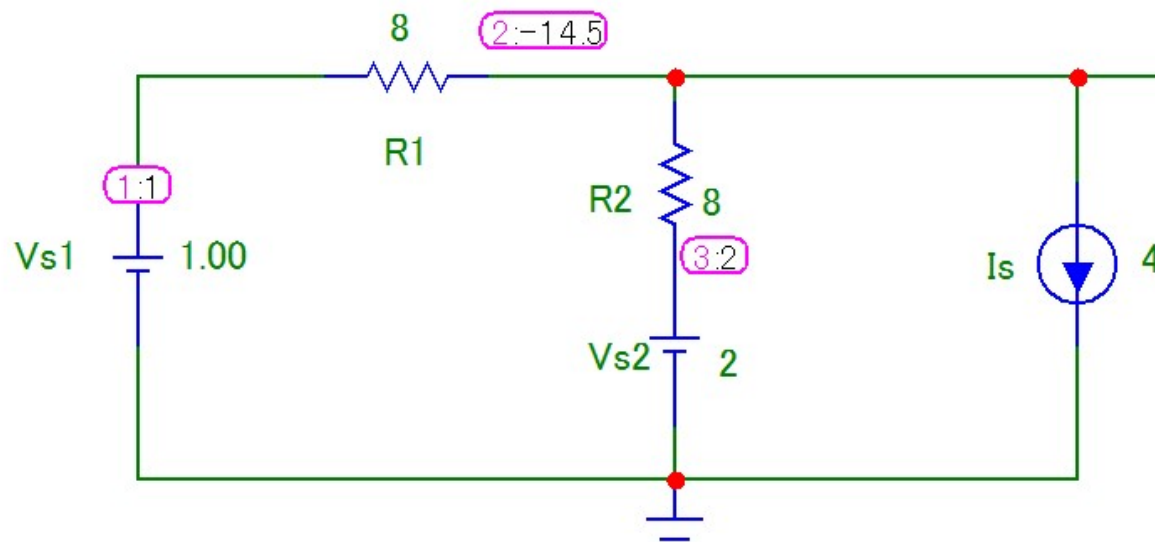
$$v_o = v_{s1} \times \frac{R_2}{R_1 + R_2}$$




$$\Delta V_0 = 5\text{mV}$$

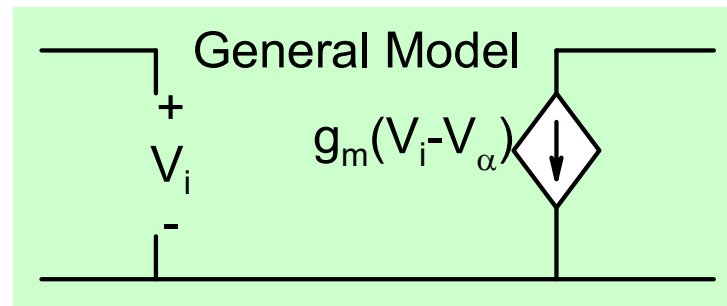


$$I_o = g_m (V_i - V_\alpha)$$

$$I_O + i_o = g_m (V_I + v_i - V_\alpha)$$


$$i_o = g_m v_i$$

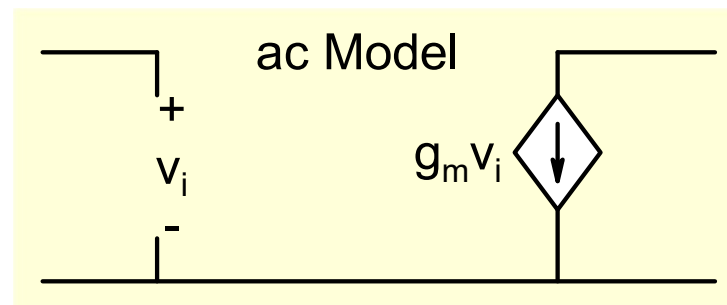

Nonlinear element

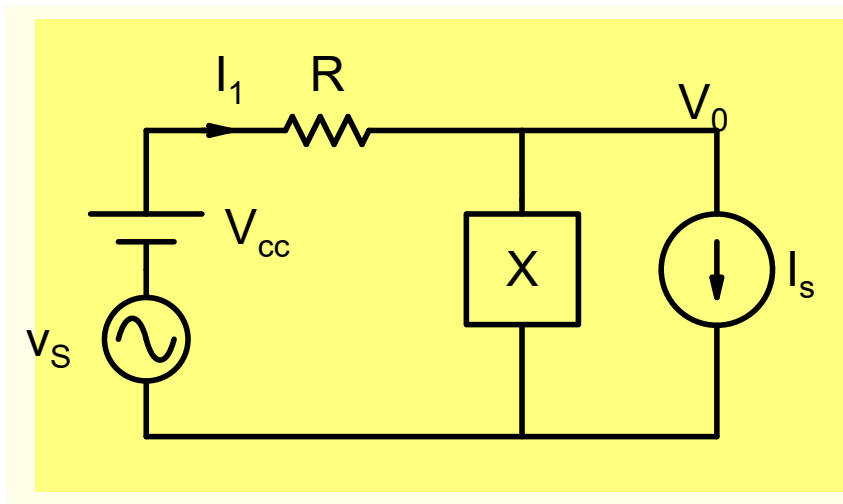

$$I_x = k \times V_x^2$$

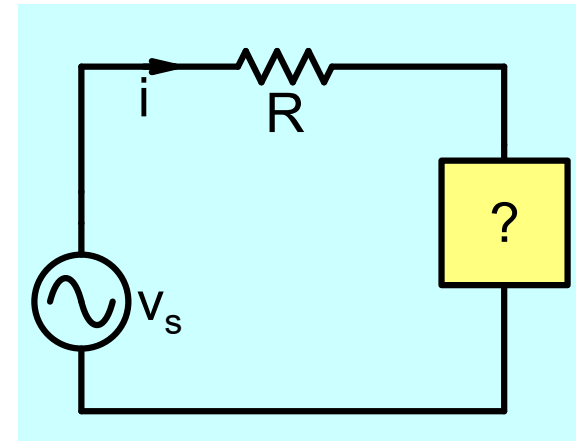

$$I_x + i_x = k \times (V_x + v_x)^2$$

Incremental Model

$$I_x + i_x = k \times (V_x + v_x)^2$$

$$i_x = k \{ (V_x + v_x)^2 - V_x^2 \}$$
$$i_x = k V_x^2 \{ (1 + v_x/V_x)^2 - 1 \}$$

Problem: model is **NONLINEAR**

Small signal approximation:


$$v_x \ll V_x$$

$$\left(1 + \frac{v_x}{V_x}\right)^2 \cong 1 + 2 \frac{v_x}{V_x}$$


$$i_x \cong 2 k V_x \times v_x$$

$$i_x = v_x / r_x \quad ; \quad r_x = \frac{1}{2 k V_x}$$

Nonlinear element

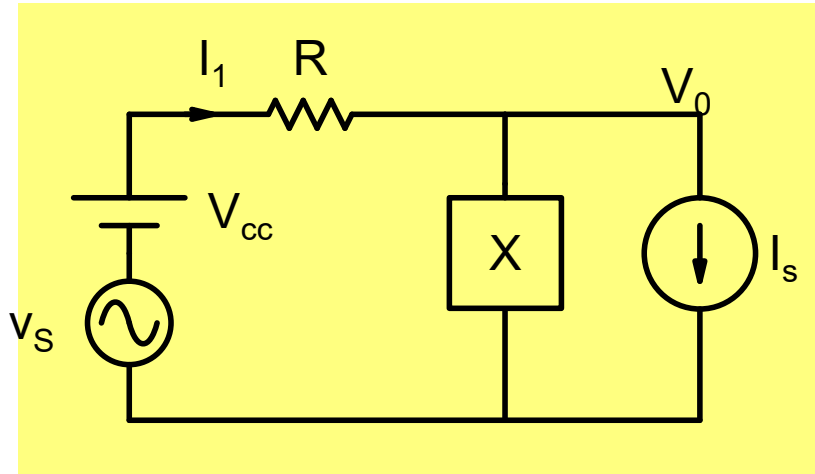

$$I_x = k \times V_x^2$$

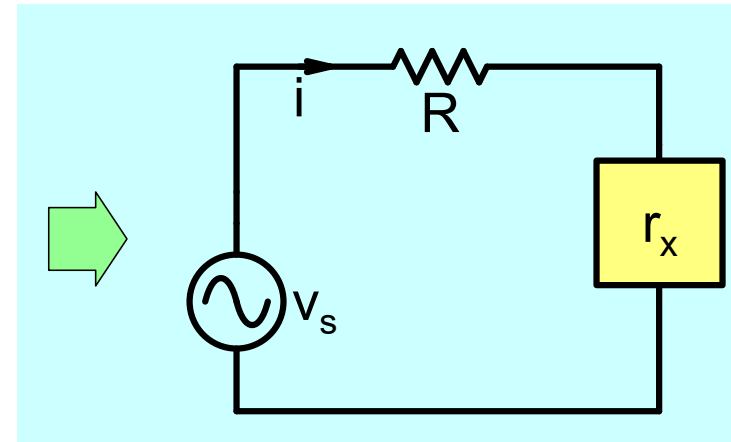

$$r_x = \frac{1}{2kV_o}$$

$$v_o = v_s \times \frac{r_x}{R + r_x}$$

How small is small?

Depends on how much error we can tolerate!

$$i_x = kV_X^2 \{(1 + v_x / V_X)^2 - 1\}$$

$$i'_x \cong 2k \times V_X \times v_x$$

$$V_X = 1V$$

v_x (V)	Error (%)
0.02	1
0.22	10
0.5	20
1.0	33.3

$$I_x = k \times V_x^4$$

$$V_X = 1V$$

v_x (V)	Error (%)
0.007	1
0.071	10
0.5	50.77
1.0	73.3

Stronger nonlinearity implies smaller voltage for same error

One of the strongest non-linearity is exponential

$$I_x = k \times \exp\left(\frac{V_x}{.026}\right) \quad I_X + i_x = k \times \exp\left(\frac{V_X + v_x}{.026}\right)$$



$$i_x = k \times \exp\left(\frac{V_X}{.026}\right) \times \left\{ \exp\left(\frac{v_x}{.026}\right) - 1 \right\} \quad i_x \cong k \times \exp\left(\frac{V_X}{.026}\right) \times \left(\frac{v_x}{.026}\right)$$

$$V_X = 0.7V$$

v_x (mV)	Error (%)
0.53	1
5.4	10
10	18
26	41.8


Small Signal Models

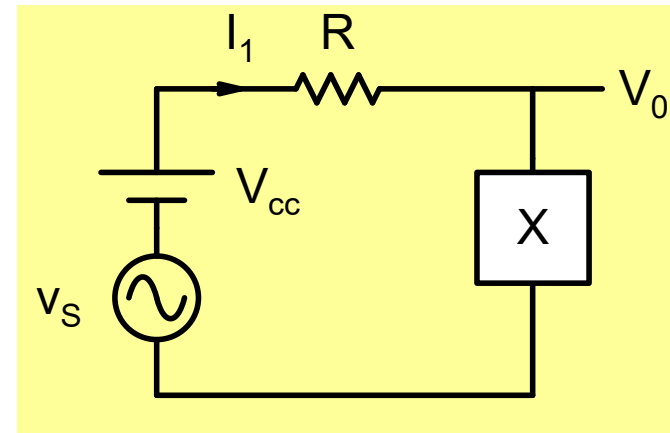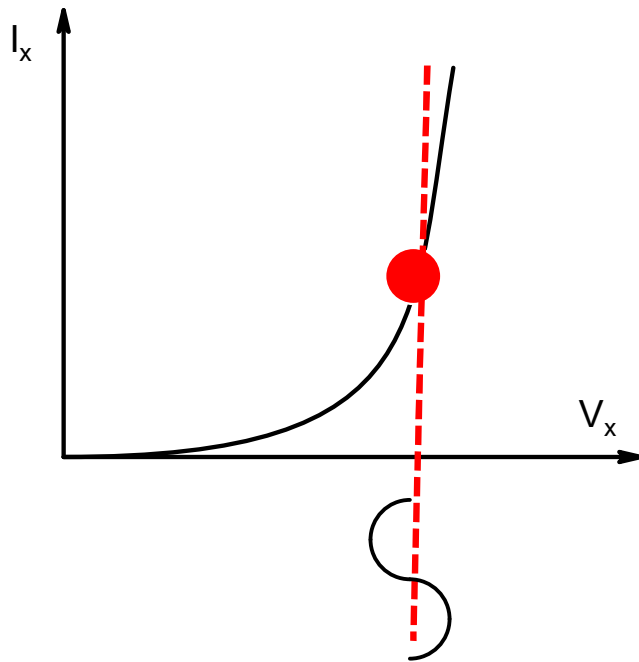Narrowing the magnitude of applied voltage to very small values allows development of model which are linear



A SS model is a linear model which is valid for small changes around a nominal value

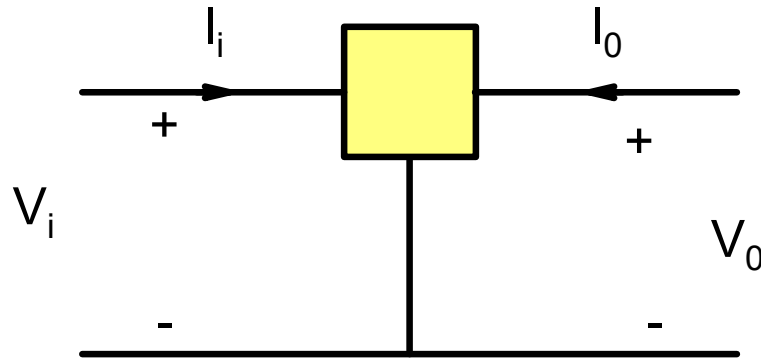General approach for obtaining small **signal model** for a 3-terminal device



$$I_i = f_i(V_i)$$


$$I_I + i_i = f_i(V_I + v_i)$$

Assumption: unilateral
(Output does not affect the input)

$$\Rightarrow i_i = v_i \left. \frac{\delta f_i}{\delta V_i} \right|_{V_I} = \frac{v_i}{r_i}$$

$$r_i = \frac{1}{\left. \frac{\delta f_i}{\delta V_i} \right|_{V_I}}$$

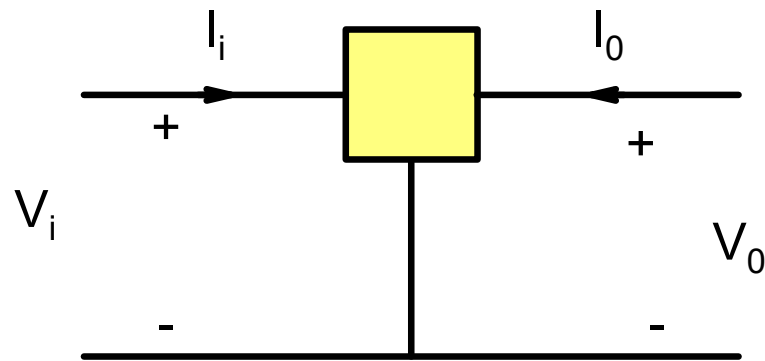From the input port, the device appears as a resistance



Output port:

$$I_O = f_O(V_i, V_O)$$


$$I_O + i_o = f_O(V_i + v_i, V_O + v_o)$$

$$I_O + i_o = f_O(V_i, V_O) + v_i \frac{\partial f_O}{\partial V_i} \Big|_{V_O} + v_o \frac{\partial f_O}{\partial V_O} \Big|_{V_i} + \dots$$

$$i_o \cong v_i \frac{\partial f_O}{\partial V_i} \Big|_{V_O} + v_o \frac{\partial f_O}{\partial V_O} \Big|_{V_i}$$

$$i_o = g_m v_i + \frac{v_o}{r_o}$$

$$g_m = \frac{\partial f_O}{\partial V_i} \Big|_{V_O} \quad r_o = \frac{1}{\frac{\partial f_O}{\partial V_O} \Big|_{V_i}}$$

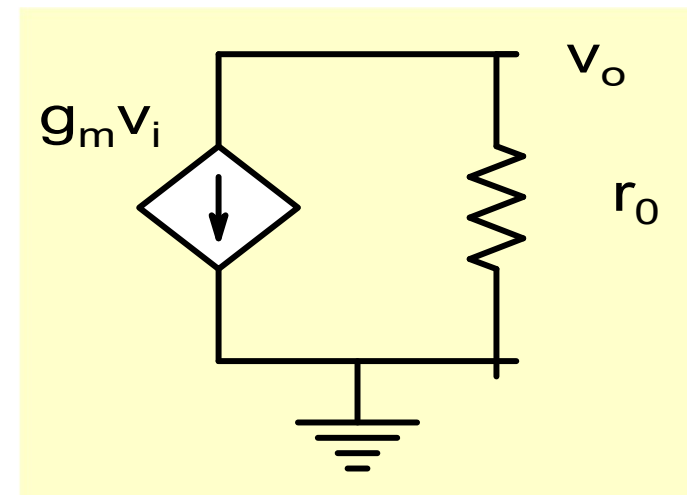

Complete **small signal model** (dc) for a 3-terminal unilateral device.

